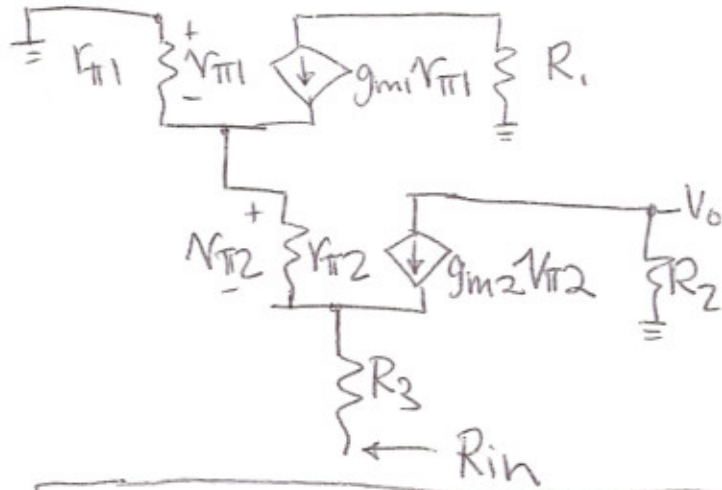



HW #5 sol'n

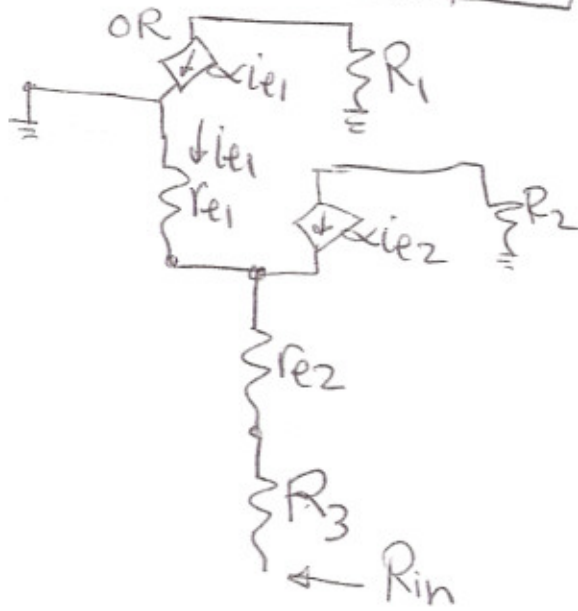1.



$$r_e(\beta+1) = r_{\pi}$$

$$R_{in} = R_3 + \frac{r_{\pi 2}}{(\beta+1)} + \frac{r_{\pi 1}}{(\beta+1)^2}$$



$$R_{in} = R_3 + r_{e2} + \frac{r_{e1}}{(\beta+1)}$$

2.



$$H(s) = \frac{10s \left(\frac{s}{10} + 1\right) \left(\frac{s}{100} + 1\right) \left(\frac{s}{10000} + 1\right)}{\left(\frac{s}{20} + 1\right) \left(\frac{s}{200} + 1\right) \left(\frac{s}{400} + 1\right) \left(\frac{s}{1000} + 1\right) \left(\frac{s}{2000} + 1\right)}$$

pole frequencies = 20, 200, 400, 1,000, 2,000 rad/sec.

zero frequencies = 1 at origin, 10, 100, 10,000 rad/sec.

$$H(s) = \frac{10 \cdot s \cdot \frac{s}{10} \left(1 + \frac{10}{s}\right) \cdot \frac{s}{100} \left(1 + \frac{100}{s}\right) \left(\frac{s}{10000} + 1\right)}{\frac{s}{20} \left(1 + \frac{20}{s}\right) \cdot \frac{s}{200} \left(1 + \frac{200}{s}\right) \cdot \frac{s}{400} \left(1 + \frac{400}{s}\right) \left(\frac{s}{1000} + 1\right) \left(\frac{s}{2000} + 1\right)}$$

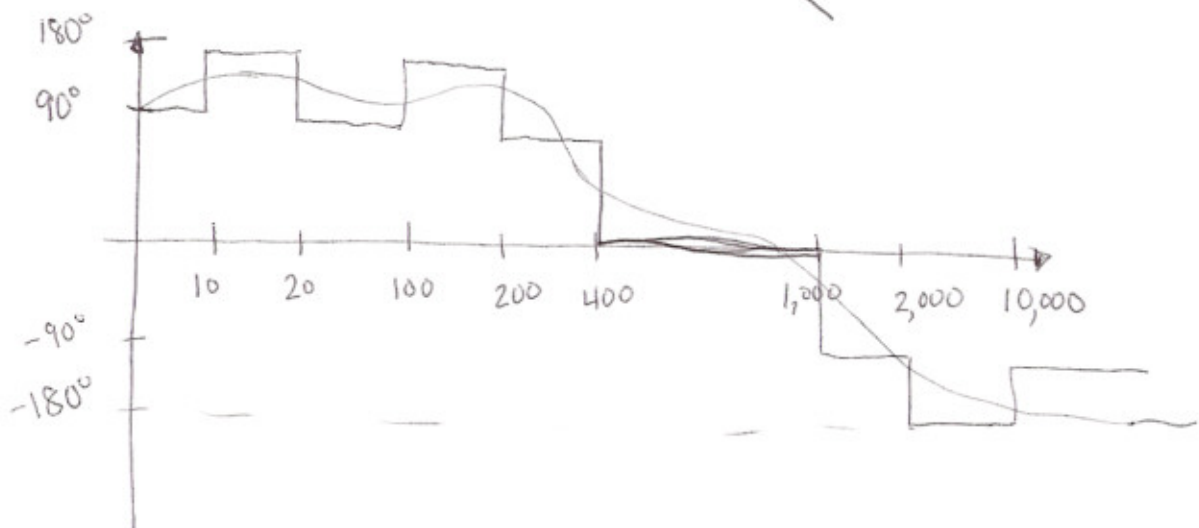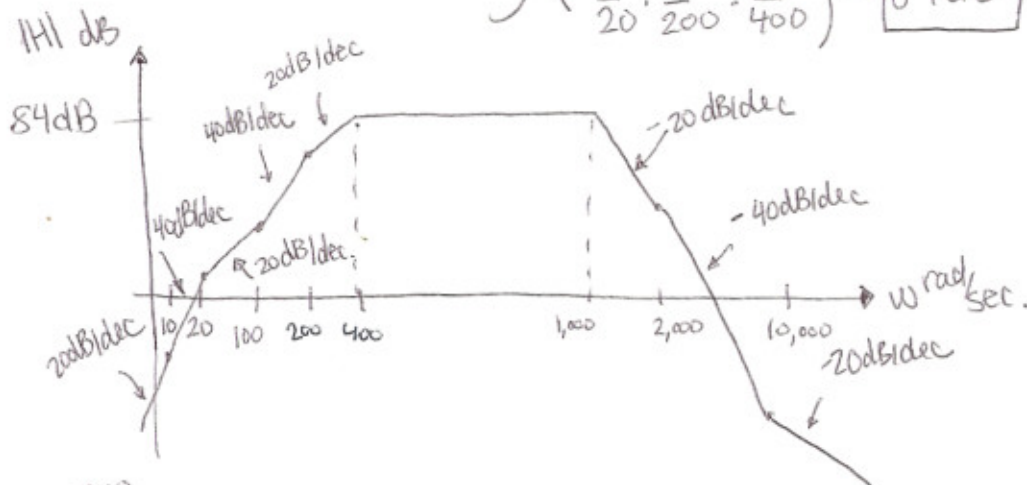
midband gain = $20 \log \left(\frac{10 \cdot \frac{1}{10} \cdot \frac{1}{100}}{\frac{1}{20} \cdot \frac{1}{200} \cdot \frac{1}{400}} \right) \approx \boxed{84 \text{ dB}}$



3. C_1 and C_2 affect the low frequency:

Using short-circuit time constants \Rightarrow

①

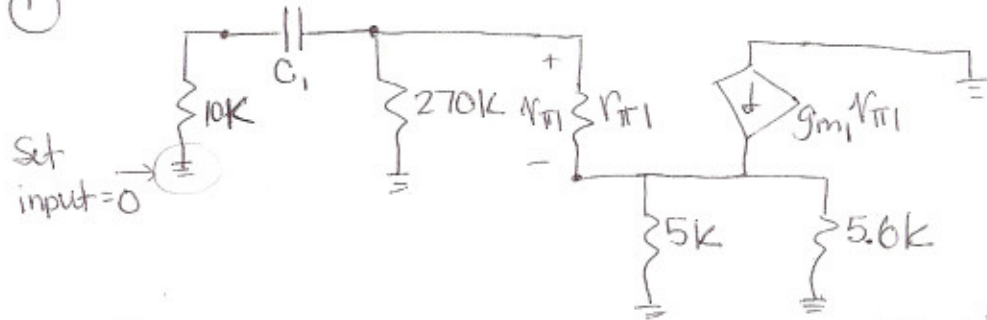

Resistance seen by $C_1 \Rightarrow$ {Using Resistance reflection rule}

$$10k + [270k \parallel \{ (5k \parallel 5.6k)(\beta+1) + r_{\pi 1} \}]$$

$$r_{\pi 1} = \frac{V_{T1}\beta}{I_C} = \frac{V_T}{I_B}$$

$$I_B \Rightarrow -5 + 270k(I_B) + 0.7 + 5k(I_E) = 0$$

$$I_B(\beta+1) = I_E$$


$$+4.3 = [270k + 5k(\beta+1)] I_B$$

$$\therefore I_B = 4.9 \mu$$

$$r_{\pi 1} = \frac{25m}{4.9 \mu} = 5102$$

$$R_{c1} = 10k + [270k \parallel 324,725] = 157,422$$

②

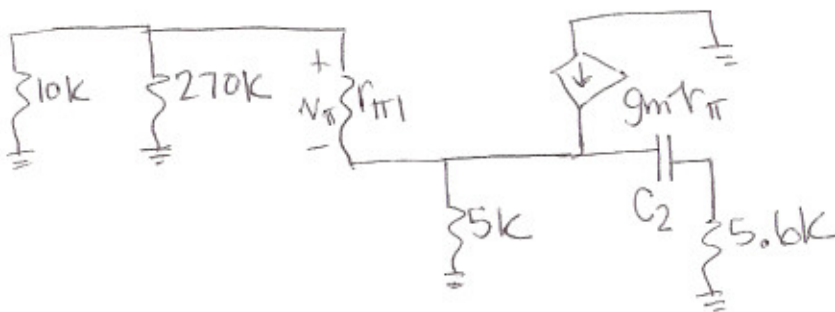

$$R_{c2} = 5.6k + [5k \parallel \frac{270k \parallel 10k + r_{\pi 1}}{\beta+1}]$$

$$R_{c2} = 5,719$$


$$3. \quad \omega = 2\pi \cdot (100) = \frac{1}{C_1 \cdot R_{c1}} + \frac{1}{C_2 \cdot R_{c2}}$$

$$\left[628 = \frac{1}{10 C_2 \cdot 157,422} + \frac{1}{C_2 \cdot 5,719} \right] C_2$$

$$C_2 = \frac{\left[\frac{1}{10(157,422)} + \frac{1}{5,719} \right]}{628} \cong \underline{\underline{279 \text{ nF}}}$$

$$\therefore C_1 = \underline{\underline{2.79 \mu\text{F}}}$$

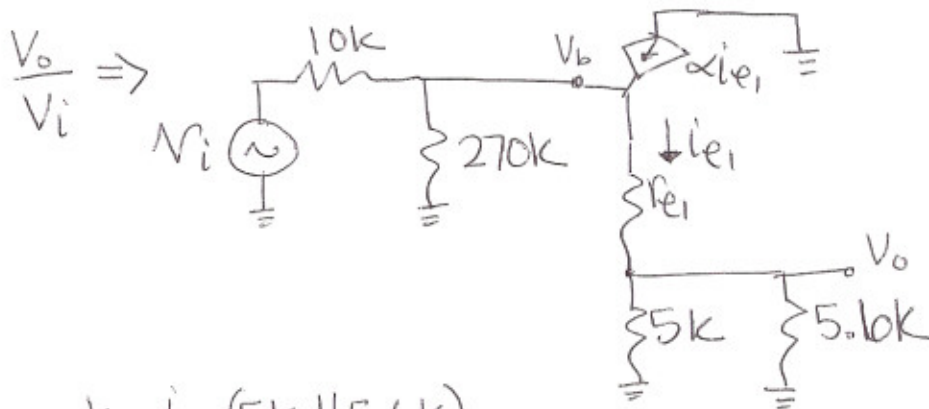midband gain, $A_m \Rightarrow$ same as overall gain (short caps)



$$V_o = i_{e1} (5\text{k} \parallel 5.6\text{k})$$

$$i_{e1} = \frac{V_b}{r_{e1} + (5\text{k} \parallel 5.6\text{k})}$$

$$V_b = \frac{V_i (270\text{k})}{270\text{k} + 10\text{k}}$$

$$r_{e1} = \frac{r_{\pi}}{(\beta+1)} = \frac{5,102}{121} \cong 42.2$$

$$\frac{V_o}{V_i} = \frac{(270\text{k})}{(280\text{k})} \cdot \frac{1}{(42.2 + 2642)} (2642) = 0.95$$


$$A_m \text{ in dB} = \boxed{-0.45 \text{ dB or } 0.95 \text{ V/V}}$$

3. $\omega_L = \boxed{628 \text{ rad/sec or } 100 \text{ Hz}}$

high-frequency \Rightarrow use open-circuit time constants

$$\omega_H \approx \frac{1}{C_{\mu} R_{\mu} + C_{\pi} R_{\pi}}$$

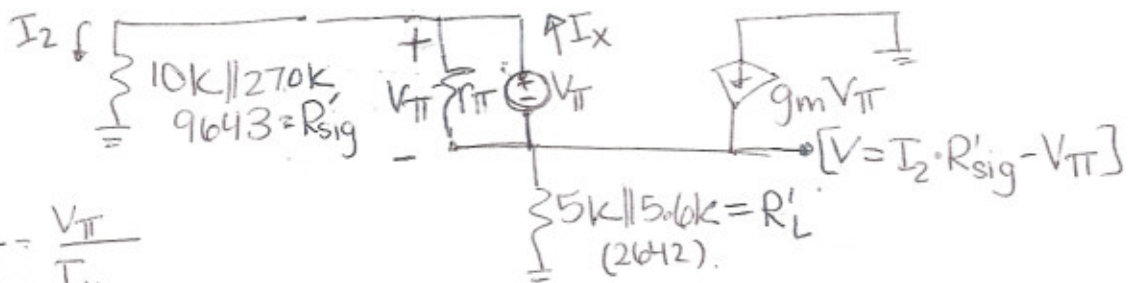C_{π} : (short bypass/coupling caps, set input = 0)



$$R_{\pi} = \frac{V_{\pi}}{I_x}$$


$$I_x - \frac{V_{\pi}}{r_{\pi}} - I_2 = 0 \Rightarrow I_2 = I_x - \frac{V_{\pi}}{r_{\pi}}$$

$$g_m V_{\pi} - I_x + \frac{V_{\pi}}{r_{\pi}} - \frac{V}{R'_L} = 0 \Rightarrow (g_m + \frac{1}{r_{\pi}}) V_{\pi} - I_x - \frac{[(I_x - \frac{V_{\pi}}{r_{\pi}}) R'_{sig} - V_{\pi}]}{R'_L} = 0$$

$$g_m = \frac{\beta}{r_{\pi}}, \text{ so } (g_m + \frac{1}{r_{\pi}}) = (\frac{\beta+1}{r_{\pi}}) = \frac{1}{r_e}$$

$$\frac{V_{\pi}}{I_x} \left(\frac{1}{r_e} + \frac{1}{r_{\pi} R'_L} + \frac{1}{R'_L} \right) = I_x \left(1 + \frac{R'_{sig}}{R'_L} \right)$$
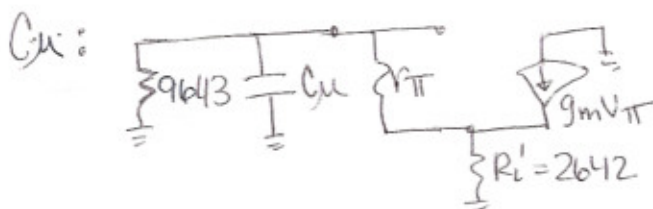
$$R_{\pi} = \frac{V_{\pi}}{I_x} = \frac{\left(1 + \frac{R'_{sig}}{R'_L} \right) \cdot R'_L}{\left(\frac{1}{r_e} + \frac{\beta R'_{sig}}{r_{\pi} R'_L} + \frac{1}{R'_L} \right) R'_L} = \frac{(R'_L + R'_{sig})}{\left(\frac{R'_L}{r_e} + \frac{\beta R'_{sig}}{r_{\pi}} + 1 \right)} = \frac{2642 + 9643}{\frac{2642}{42.2} + \frac{9643}{5102} + 1} \approx 188$$



$$R_{\mu} = 9643 \parallel \left[\frac{2642(\beta+1) + r_{\pi}}{324784} \right] = 9365$$


$$\omega_H \approx \frac{1}{(0.5p)(9365) + (0.2p)(188)} \approx \boxed{219 \text{ Mrad/sec.}} \\ \text{or } \underline{33.7 \text{ MHz}}$$

$$4. \text{ NPN} \Rightarrow g_m = 2\text{m} = \frac{I_{c_n}}{25\text{m}} \Rightarrow I_{c_n} = 50\mu\text{A}$$

$$\therefore I_1 = 2 \cdot I_{c_n} = \underline{100\mu\text{A}}$$


$$\text{PNP} \Rightarrow g_m = 60\text{mA/V} = \frac{I_{c_p}}{25\text{m}} = 1.5\text{mA}$$
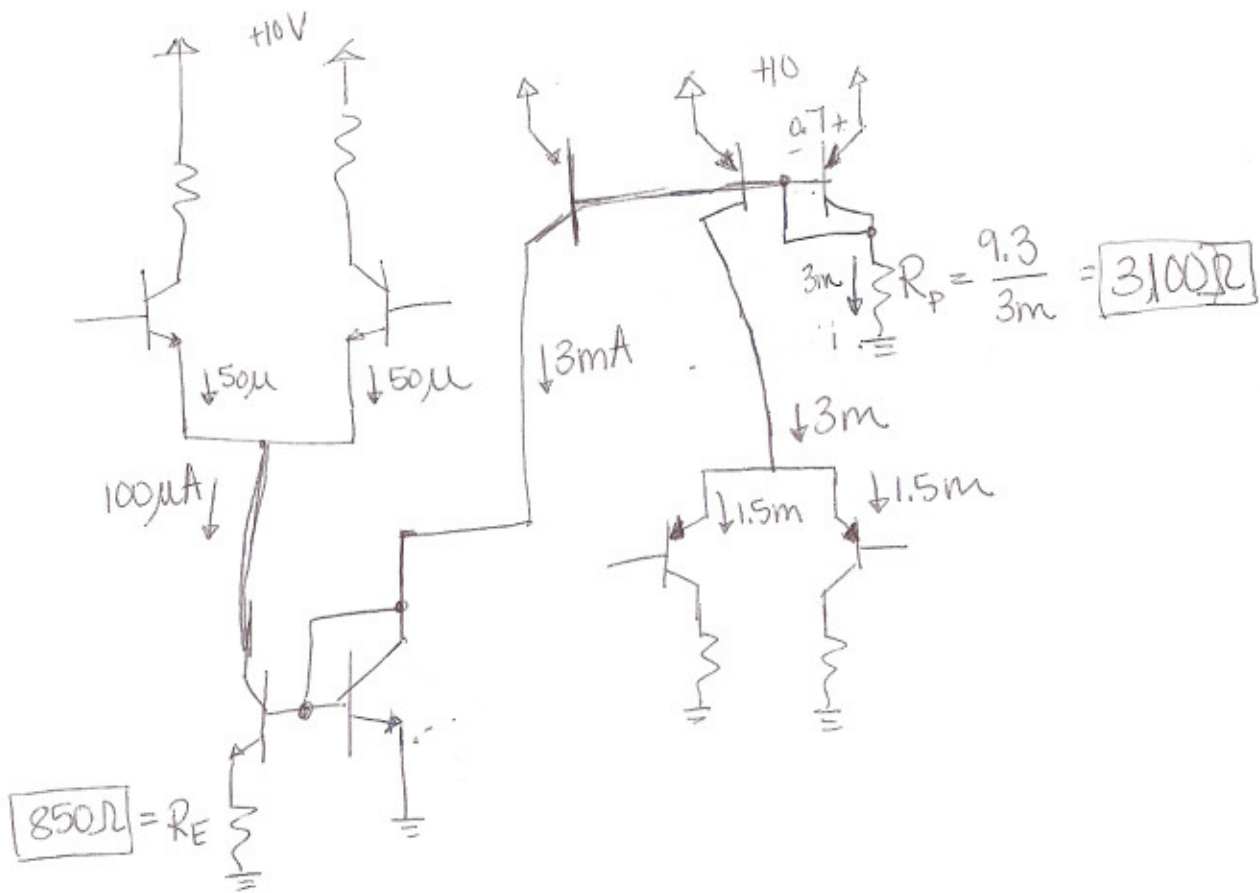
$$\therefore I_2 = 2 \cdot I_{c_p} = \underline{3\text{mA}}$$



$$R_E = \frac{V_T}{100\mu} \ln\left(\frac{3\text{m}}{100\mu}\right) = 850\Omega$$

5.

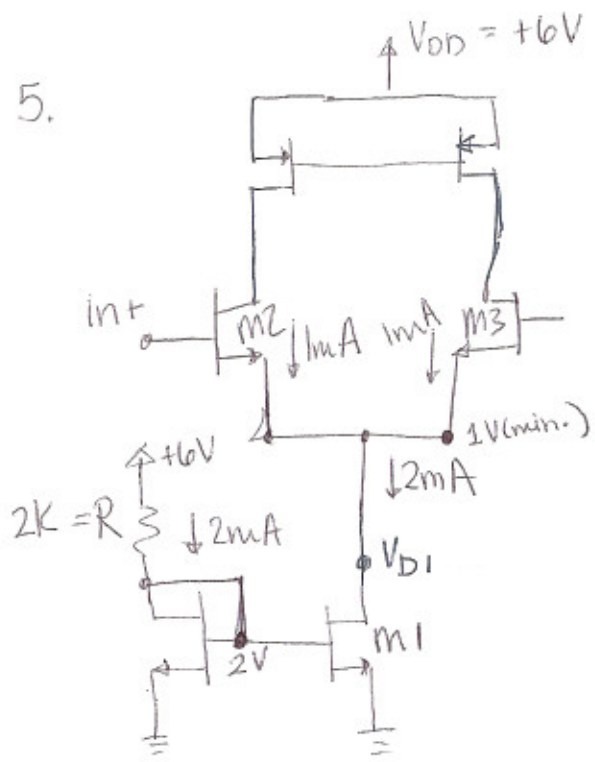

$$A_d = g_m R_o \Rightarrow$$

$$g_m = \frac{2I_D}{V_{ov}}$$

$$\therefore A_d = 50 = \frac{2I_D}{V_{ov}} \cdot \frac{V_A}{2I_D} = \frac{20}{V_{ov}}$$

$$V_{ov} = 0.4$$

$$V_{GS} - V_t = 0.4$$

$$\therefore V_{GS} = \boxed{1.4V}$$

Needs to have this voltage bias on the gate to operate

Current mirror \Rightarrow

$$2m = \frac{1}{2} (4m) (V_{GS} - V_t)^2$$

$$1 = V_{GS} - V_t$$

$$\therefore V_{GS} = 1 + 1 = 2V$$

$$R = \frac{6 - 2}{2m} = \boxed{2K}$$

minimum drain voltage for M1 to be saturated \Rightarrow

$$V_{DS1} = V_{GS1} - V_{t1}$$

$$\therefore V_{D1} = V_{G1} - V_t = 2 - 1 = 1V.$$

Since M2 & M3 need $V_{GS} = 1.4V$ to operate

$$\therefore V_G - V_S = 1.4V$$

$$(\text{min.}) V_G = 1.4 + 1V = \boxed{2.4V}$$