

(Due Friday, Oct. 14 by 6pm in homework locker)

1. A negative-feedback amplifier has a closed-loop gain $A_f = 200$ and an open-loop gain $A = 10,000$. What is the feedback factor β ? Assuming that the feedback factor remains the same and a manufacturing error causes a reduction of A to 1,000, what closed-loop gain results?
2. Do Exercise 8.1 (a) through (e) for $A=200$.
3. Consider the noninverting op-amp circuit analyzed in (2). Let the open-loop gain A have a low-frequency value of 10,000 and a uniform -6-dB/octave rolloff at high frequencies with a 3-dB frequency of 200Hz. Find the low-frequency gain and the upper 3dB frequency of a closed-loop amplifier with $R_1 = 1\text{k}\Omega$ and $R_2=19\text{k}\Omega$.
3. In a feedback amplifier for which $A=100,000$ and $A_f= 100$, what is the gain-desensitivity factor?
4. An amplifier has a dc gain of 1,000 V/V, a single high-frequency pole at 10kHz, and a single low-frequency pole at 150Hz. Negative feedback results in reducing the midband gain to 100V/V. What are the upper and lower 3-dB frequencies (in Hz) of the closed-loop gain?
5. A series-shunt feedback amplifier seen in Fig. 8.4(a) and using an ideal basic voltage amplifier operates with $V_s= 200\text{mV}$, $V_f=95\text{mV}$, and $V_o=9\text{V}$. What are the corresponding values of A and β ? Include the correct units for each.
6. A shunt-series feedback amplifier seen in Fig. 8.4(b) and using an ideal basic current amplifier operates with $I_s= 150\mu\text{A}$, $I_f=95\mu\text{A}$, and $I_o=9\text{mA}$. What are the corresponding values of A and β ? Include the correct units for each.
7. A series-series feedback amplifier seen in Fig. 8.4(c) and using an ideal transconductance amplifier operates with $V_s= 200\text{mV}$, $V_f=95\text{mV}$, and $I_o=9\text{mA}$. What are the corresponding values of A and β ? Include the correct units for each.