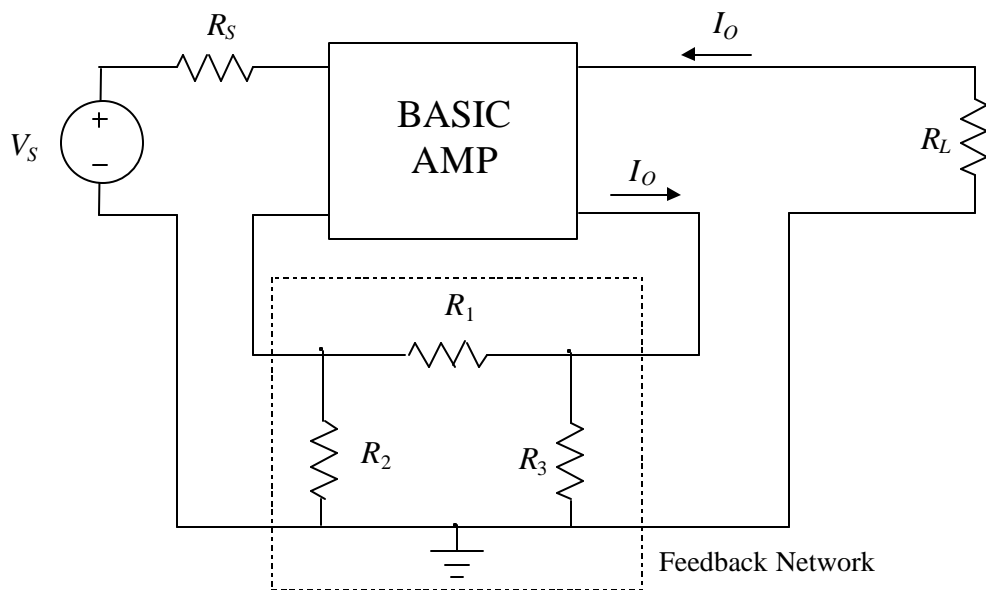


(Due Oct. 19 by 6pm in homework locker)

1. What type of feedback topology is shown below (e.g., series-series, shunt-series,...)?

Draw three pictures showing the circuit configurations used for measuring \mathbf{b} , R_{11} , and R_{22} for the feedback network shown, and derive expressions for \mathbf{b} , R_{11} , and R_{22} as a function of circuit parameters.



2. A voltage amplifier (voltage input, voltage output) having an open-circuit gain of 500, an input resistance of 50 k Ω , and an output resistance of 200 Ω is connected in a negative-feedback loop.

(a) Which feedback topology (e.g., series-shunt, series-series, etc.) would be used in this situation?


The feedback network has an R_{11} and R_{22} of 10 k Ω and provides a feedback factor $\mathbf{b} = 0.1$. The amplifier is fed by a voltage source having $R_S = 100 \Omega$, and a load resistance $R_L = 10 \text{ k}\Omega$ is connected at the output.

(b) What is A ? (Hint: It is *not* 500!)

(c) What is the closed-loop gain A_f of the feedback amplifier?

(d) What is the feedback amplifier's input resistance R_{in} ?

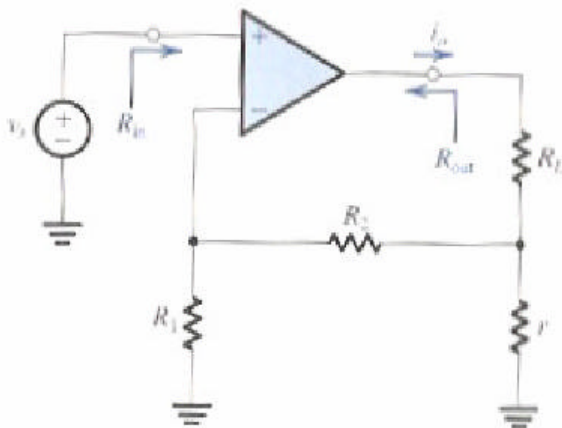3. Use the series-series feedback amplifier shown below. The op amp is characterized by an open-loop gain of $10,000\text{V/V}$, an input differential resistance of $10\text{k}\Omega$, and an output resistance $r_o = 1\text{k}\Omega$. The feedback network consists of R_1 , R_2 , and r . Let $R_L = 5\text{k}\Omega$, $R_1 = 200\Omega$, $R_2 = 5\text{k}\Omega$, and $r = 200\Omega$. Find the closed-loop gain $A_f = i_o/v_s$, the input resistance R_{in} , and the output resistance R_{out} .



4. Negative feedback is to be used to modify the characteristics of a particular amplifier for various purposes. Identify the feedback topology to be used if:

- (a) Input resistance is to be increased and output resistance lowered.
- (b) Input resistance is to be lowered and output resistance is to be increased.
- (c) Input and output resistance is to be lowered.

5. Use Figure P8.42 from the book. The shunt-shunt feedback amplifier shown has $I = 2\text{mA}$ and $V_{GS} = 0.5\text{V}$. The MOSFET has $V_t = 1\text{V}$, $V_A = 50\text{V}$, $R_s = 1\text{k}\Omega$, $R_1 = 100\text{k}\Omega$, and $R_2 = 500\text{k}\Omega$, find the voltage gain, the input resistance R_{in} , and the output resistance R_{out} .

6. Reconsider Exercise 8.14 for the case of the op amp wired as a unity-gain buffer. At what frequency is $|A\beta| = 1$? What is the corresponding phase margin?

7. Reconsider Exercise 8.14 for the case when a manufacturing error introduces a second pole at $100,000$. What is now the frequency for which $|A\beta| = 1$? What is the corresponding phase margin? For what values of β is the phase margin 45° or more?

8. For the amplifier described by Fig. 8.47 and with independent frequency-independent feedback, what is the minimum closed-loop voltage gain that can be obtained for phase margins of 60° and 90° ?

9. Exercises 14.1, 14.2, 14.3, 14.4