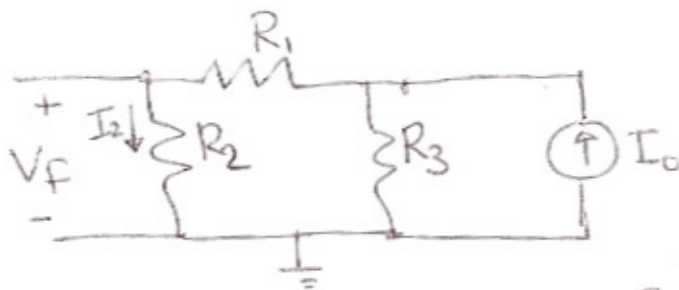


HW #7 Sol'n

I. Series-series topology


a.



$$\beta = \frac{V_f}{I_o} \Rightarrow V_f = I_2 \cdot R_2 = \frac{R_3 R_2 I_o}{R_1 + R_2 + R_3}$$


$$\therefore \beta = \boxed{\frac{R_3 R_2}{R_1 + R_2 + R_3}}$$

b. $R_{11} \Rightarrow$

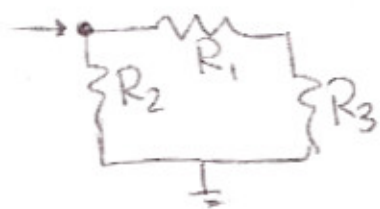

$$R_{11} = \boxed{R_2 \parallel (R_1 + R_3)}$$


c. R_{22}

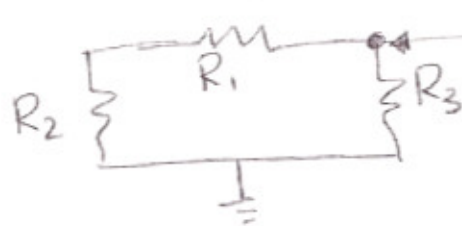

$$R_{22} = \boxed{R_3 \parallel (R_1 + R_2)}$$

2. a. Series-Shunt topology (just from voltage amp.)

b. circuit:

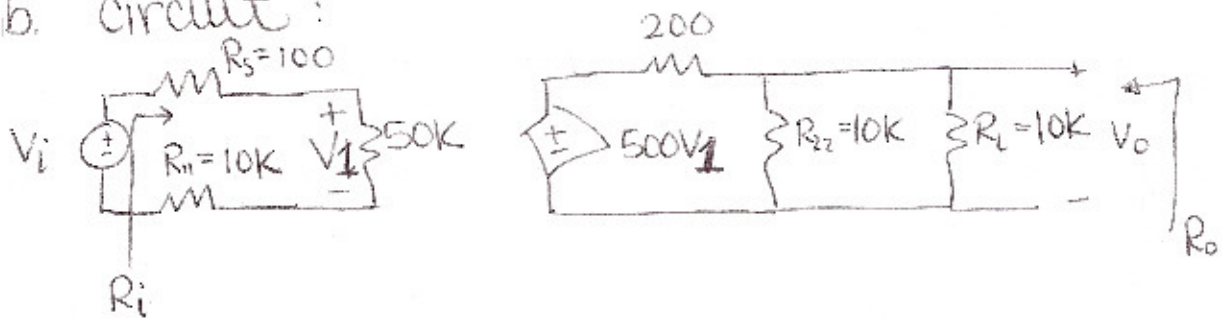

$$A \Rightarrow \frac{500 \cdot V_1 (R_{22} \parallel R_L)}{(R_{22} \parallel R_L + 200)} = \frac{500 (5k) V_1}{5.2k} = V_o$$

$$V_1 = \frac{V_i \cdot 50k}{R_s + 50k + 10k} = \frac{50k V_i}{60.1k}$$

$$\frac{V_o}{V_i} \equiv A = \frac{500 (5k) 50k}{(5.2k) (60.1k)} \approx \boxed{400 V/V}$$


$$c. A_f = \frac{A}{1 + A\beta} = \frac{400}{1 + (400)(1)} \approx \boxed{9.8 V/V}$$

$$d. R_i = R_s + 50k + R_{11} = 60.1k \Omega$$

$$R_{if} = R_i (1 + A\beta) = 2.464 \times 10^6 \Omega$$


$$R_{in} = R_{if} - R_s \approx \boxed{2.5M \Omega}$$

3. Feedback network:

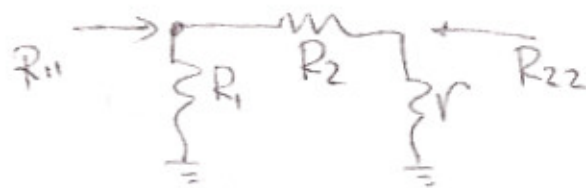


$$R_{11} = R_1 \parallel (R_2 + r) = 200 \parallel (5k + 200) \approx 193$$
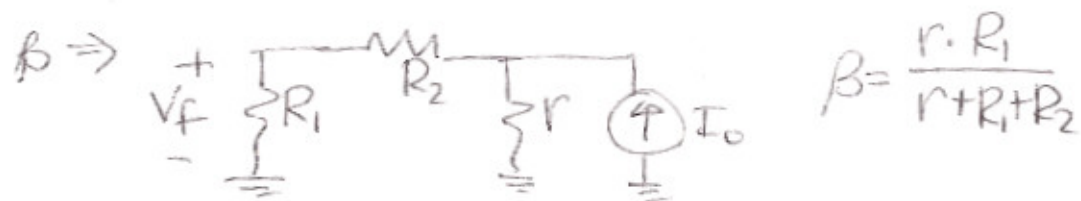
$$R_{22} = r \parallel (R_1 + R_2) = 200 \parallel (5k + 200) \approx 193$$



$$\therefore \beta = \frac{(200)(200)}{5k + 400} = 74 \times 10^{-3}$$

A-circuit:

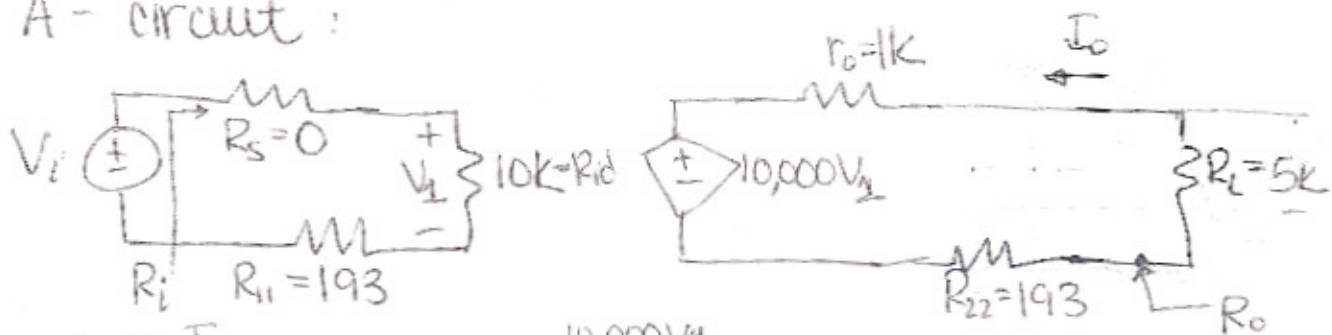

$$A \equiv \frac{I_o}{V_i} : I_o = -\frac{10,000V_1}{1k + 5k + 193} \Rightarrow A = \frac{-10,000(10k)}{(6,193)(10,193)}$$

$$V_1 = \frac{V_i \cdot 10k}{10k + 193} \quad A \approx -1.6$$

$$\therefore A_f = \frac{A}{1 + A\beta} \approx \boxed{-1.8k}$$

$$R_i = 10,193$$

$$R_{if} = 10,193(1 + A\beta) \approx 8,986\Omega$$

$$R_{in} = R_{if} - R_s = \boxed{8,986\Omega}$$


$$R_o = R_L + r_o + R_{22} = 6,193$$

$$R_{of} = R_o(1 + A\beta) \approx 5,460\Omega$$

$$R_{out} = R_{of} - R_L \approx \boxed{5,460\Omega}$$


4. a. series-shunt
 b. shunt-series
 c. shunt-shunt

5. Shunt-shunt topology:
 Feedback topology \Rightarrow

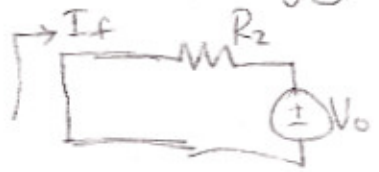$\frac{I_f}{V_o} \equiv \beta \Rightarrow$  $\therefore I_f = \frac{-V_o}{R_2} \Rightarrow \beta = -\frac{1}{R_2}$

$R_{11} = R_{22} = R_2$

A-circuit:

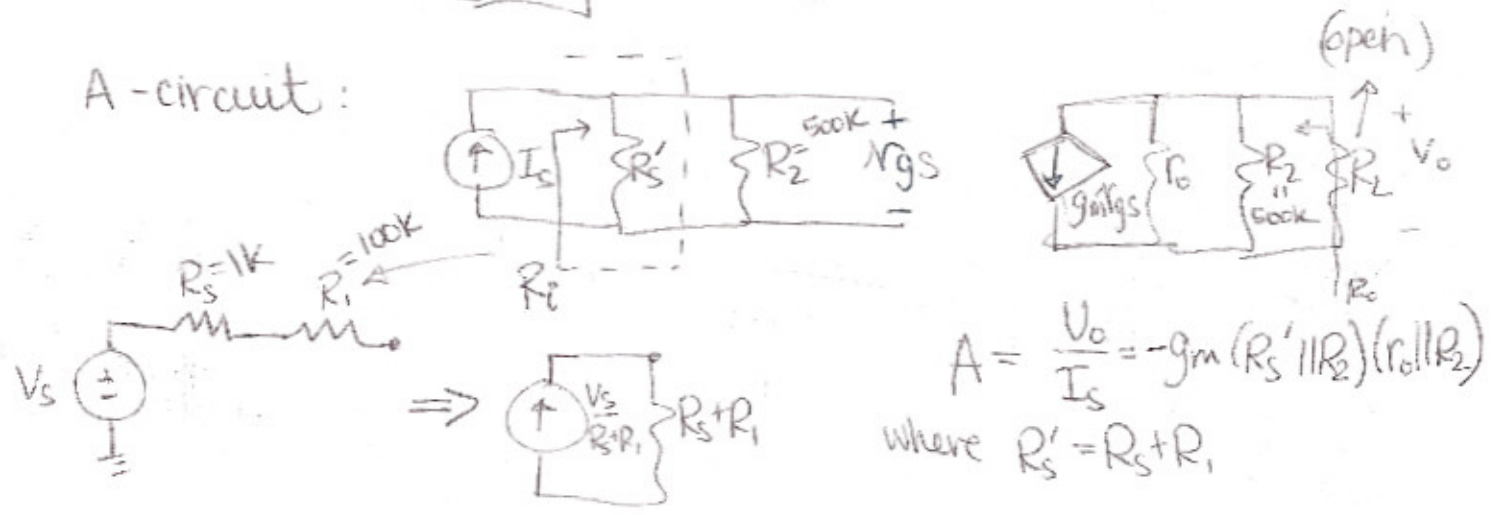

$g_m = \frac{2I_D}{V_{ov}} = \frac{2(2m)}{1.5-1} = 8m A/V$; $r_o = \frac{V_A}{I} = \frac{50}{2m} = 25k\Omega$

$\therefore A = -8m (101k \parallel 500k) (25k \parallel 500k) \approx -16.1 M V/V$

$A_f = \frac{A}{1+A\beta} = \frac{-16.1M}{[1 + (-16.1M)(-\frac{1}{500k})]} \approx -485 k V/V$

$\frac{V_o}{V_s} = \frac{V_{of}}{I_s(R_s+R_i)} = \frac{-485k}{(101k)} \approx \boxed{-4.8 V/V}$

$R_o = R_2 \parallel r_o \approx 24k\Omega \Rightarrow R_{of} = \frac{R_o}{(1+A\beta)} = \frac{24k}{33.2} = \boxed{723\Omega} = R_{out}$

$R_i = (R_s + R_i) \parallel R_2 = 84k$

$R_{if} = 84k / (1+A\beta) \approx 2,531\Omega \Rightarrow R_{in} = R_{if} - R_s \approx \boxed{1,531\Omega}$

6. $|A\beta| = 1$ unity-gain buffer $\Rightarrow \beta = 1$ $A = \frac{A_0}{1 + j(\frac{f}{10})}$

$$\therefore |A\beta| = \frac{10^5 (1)}{\sqrt{1 + \frac{f^2}{100}}} = 1$$

$$\therefore \boxed{f \approx 1 \text{ MHz}}$$

$$\phi = -\tan^{-1}\left(\frac{1 \text{ M}}{10}\right) \approx -90^\circ$$

$$\therefore \text{phase margin} = \boxed{90^\circ}$$

7. $A(f) = \frac{A_0}{(1 + j\frac{f}{100\text{k}})(1 + j\frac{f}{10})}$, $\beta = 1$

$$|A\beta| = \frac{10^5 \cdot (1)}{\sqrt{1 + \frac{f^2}{(100\text{k})^2}} \cdot \sqrt{1 + \frac{f^2}{10^2}}} = 1 \Rightarrow f \approx \boxed{308 \text{ kHz}}$$

$$\phi = -\left[\tan^{-1}\left(\frac{f}{100\text{k}}\right) + \tan^{-1}\left(\frac{f}{10}\right)\right] = -162^\circ$$

$$\therefore \text{phase margin} = 180 - 162^\circ \approx \boxed{18^\circ}$$

For phase margin $\geq 45^\circ$

$$\tan^{-1}\left(\frac{f_1}{100\text{k}}\right) \leq 45^\circ \Rightarrow f_1 \leq 100\text{k}$$

$$|A\beta| = \frac{10^5 \cdot \beta}{\sqrt{2} \cdot \sqrt{1 + 1,000}} = 1 \therefore \boxed{\beta \approx 447 \mu}$$

8. For 60° phase margin: (Use eq. 8.79)

$$\tan^{-1}\left(\frac{f_1}{10^5}\right) + \tan^{-1}\left(\frac{f_1}{10^6}\right) + \tan^{-1}\left(\frac{f_1}{10^7}\right) = 120^\circ$$

from graph $\Rightarrow f_1 \approx 8 \times 10^5 \text{ Hz}$

check $\Rightarrow \tan^{-1}\left(\frac{8 \times 10^5}{10^5}\right) + \tan^{-1}\left(\frac{8 \times 10^5}{10^6}\right) + \tan^{-1}\left(\frac{8 \times 10^5}{10^7}\right) \approx$

$83 + 39 + 5 = 127$ (close) $\rightarrow f_1 = 7 \times 10^5 \text{ Hz}$ gives $\phi \approx 120.9$

$$|A(f_1)| = \frac{10^5}{\sqrt{1 + \left(\frac{7 \times 10^5}{10^5}\right)^2} \sqrt{1 + \left(\frac{7 \times 10^5}{10^6}\right)^2} \sqrt{1 + \left(\frac{7 \times 10^5}{10^7}\right)^2}} \approx 11,905$$

$\approx 7 \quad \approx 1.2 \quad \approx 1$

$$|A\beta| = 1$$

$$\beta \approx 84 \mu$$

$$A_f = \frac{10^5}{1 + (10^5 \cdot 84 \mu)} = 10,638 \text{ V/V}$$

For 90° pm: From graph $\Rightarrow f_2 \approx 3 \times 10^5 \text{ Hz}$

$$\tan^{-1}\left(\frac{3 \times 10^5}{10^5}\right) + \tan^{-1}\left(\frac{3 \times 10^5}{10^6}\right) + \tan^{-1}\left(\frac{3 \times 10^5}{10^7}\right) \approx 89.9^\circ \text{ (ok)}$$

$$|A(f_2)| = \frac{10^5}{\sqrt{1 + \left(\frac{3 \times 10^5}{10^5}\right)^2} \sqrt{1 + \left(\frac{3 \times 10^5}{10^6}\right)^2} \sqrt{1 + \left(\frac{3 \times 10^5}{10^7}\right)^2}} \approx 30.3 \times 10^3 \text{ V/V}$$

$$|A\beta| = 1 \Rightarrow \beta \approx 33 \mu$$

$$A_f = \frac{10^5}{1 + (10^5 \cdot 33 \mu)} = 23,300 \text{ V/V}$$

Chapter 14 - Exercises

$$I = \frac{-V_{CC} + V_{CE(sat)}}{R_L}$$

14.1 $= \frac{-15 + 0.2}{1} = 14.8 \text{ mA}$

$$R = \frac{V_{CC} - V_0}{I}$$

$$= \frac{15 - 0.7}{14.8} = 0.976 \Omega$$

Output voltage swing = -14.8 V to $+14.8 \text{ V}$

Min. emitter current = 0 mA

Max. emitter current = $2I$

$$= 2 \times 14.8 = 29.6 \text{ mA}$$

At $V_0 = -10 \text{ V}$, the load current is -10 mA and the emitter current of Q_2

is $14.8 - 10 = 4.8 \text{ mA}$. Thus

$$V_{BE1} = 0.6 + 0.025 \ln\left(\frac{4.8}{1}\right) = 0.64 \text{ V}$$

Thus, $V_{I1} = -10 + 0.64 = -9.36 \text{ V}$

At $V_0 = 0 \text{ V}$, $i_L = 0$ and $i_{E1} = 14.8 \text{ mA}$

Thus, $V_{BE1} = 0.6 + 0.025 \ln\left(\frac{14.8}{1}\right) = 0.67 \text{ V}$

$$V_{I1} = +0.67 \text{ V}$$

At $V_0 = +10 \text{ V}$, $i_L = 10 \text{ mA}$ and $i_{E1} = 24.8 \text{ mA}$

Thus, $V_{BE1} = 0.6 + 0.025 \ln(24.8) = 0.68 \text{ V}$

$$V_{I1} = 10.68 \text{ V}$$

To calculate the incremental voltage gain

we use $\frac{v_o}{v_i} = \frac{R_L}{R_L + r_{E1}}$

At $V_0 = -10 \text{ V}$, $i_{E1} = 4.8 \text{ mA}$ and $r_{E1} = \frac{25}{4.8} = 5.2 \Omega$

Thus, $\frac{v_o}{v_i} = \frac{1}{1 + 0.0052} = 0.995 \text{ V/V}$

Similarly, at $V_0 = 0 \text{ V}$, $r_{E1} = \frac{25}{14.8} = 1.7 \Omega$

and, $\frac{v_o}{v_i} = \frac{1}{1 + 0.0017} = 0.998 \text{ V/V}$

At $V_0 = +10 \text{ V}$, $i_{E1} = 24.8 \text{ mA}$ and $r_{E1} = 1 \Omega$

Thus, $\frac{v_o}{v_i} = \frac{1}{1 + 0.001} = 0.999 \text{ V/V}$

14.3 For $v_0 = 0 \text{ V}$, 100

$$P_{D1} = V_{CC} I = 10 \times 0.1 = 1 \text{ W}$$

$$P_{D2} = V_{CC} I = 10 \times 0.1 = 1 \text{ W}$$

For a 10-V amplitude output signal, the waveforms shown in Fig. 9.4 apply and the average power dissipation in Q_1 is seen to be $\frac{1}{2} V_{CC} I = \frac{1}{2} \times 10 \times 0.1 = 0.5 \text{ W}$. Transistor Q_2 carries a constant current I and has an average V_{CE} of 15 V, thus the average power dissipated in Q_2 remains unchanged at 1 W. The load power is

$$P_L = \frac{(\hat{V}/\sqrt{2})^2}{R_L} = \frac{1}{2} \times \frac{100}{100} = 0.5 \text{ W}$$

14.4 $R = \frac{(8/\sqrt{2})^2}{100} = 0.32 \Omega$

$$P_1 = 10 \times 0.1 = 1 \text{ W}$$

$$P_2 = 10 \times 0.1 = 1 \text{ W}$$

$$P_{\text{supply}} = 2 \text{ W}$$

$$\eta = \frac{P_L}{P_S} \times 100$$

$$= \frac{0.32}{2} \times 100 = 16 \%$$

14.5 (a) $P_L = \frac{1}{2} \frac{V_0^2}{R_L}$

$$= \frac{1}{2} \frac{(4.5)^2}{4} = 2.53 \text{ W}$$

(b) $P_+ = P_- = V_{CC} I = \frac{1}{\pi} \frac{V_0}{R_L}$

$$= 6 \times \frac{1}{\pi} \times \frac{4.5}{4} = 2.15 \text{ W}$$

(c) $\eta = \frac{P_L}{P_S} = \frac{2.53}{2 \times 2.15} \times 100$

$$= 59 \%$$

(d) Peak input currents = $\frac{1}{\beta+1} \frac{V_0}{R_L}$

$$= \frac{1}{51} \times \frac{4.5}{4}$$

$$= 22.1 \text{ mA}$$

(e) Using Eq. (9.22)

$$P_{D1(\text{max})} = P_{D2(\text{max})} = \frac{V_{CC}^2}{\pi^2 R_L}$$

$$= \frac{6^2}{\pi^2 \times 4} = 0.91 \text{ W}$$