

HW #8 Sol'n

1. $V_{BB} = 2V_T \ln\left(\frac{I_Q}{I_S}\right) = 2(25\text{mV}) \ln\left(\frac{1\text{m}}{1 \times 10^{-14}}\right) = 1.27\text{V}$

Let I_{C_1} also = 2mA

If $I_{Bias} = 3\text{mA}$

then $I_R = 1\text{mA}$

$\therefore R_1 + R_2 = \frac{V_{BB}}{I_R} = \frac{1.27}{1\text{mA}} = 1.27\text{KR}$

For Q_1 : $V_{BE1} = V_T \ln\left(\frac{2\text{mA}}{1 \times 10^{-14}}\right) = 0.65\text{V}$

$R_1 = \frac{0.65}{1\text{mA}} \approx \boxed{651\Omega}$

$R_2 = 1.27\text{K} - 651 = \boxed{619\Omega}$

2. $P_D = 60\text{W}$ at 40°C , $T_{J\text{MAX}} = 120^\circ\text{C}$

(a.) $\theta_{JC} = \frac{T_J - T_C}{P_D} = \frac{120 - 40}{60} = +1.33^\circ\text{C/W}$

$\theta_{CS} = 0.5^\circ\text{C/W} \Rightarrow T_J - T_S = (\theta_{JC} + \theta_{CS})P_D$

(b.) $T_S - T_A = \theta_{SA} P_D$ $\therefore T_S = 120 - (1.33 + 0.5)30 = \boxed{65.1^\circ\text{C}}$

$65.1 - 30 = \theta_{SA} \cdot 30 \Rightarrow \theta_{SA} = \boxed{+1.17^\circ\text{C/W}}$

c. $\frac{4.5^\circ\text{C/W/cm}}{1.17^\circ\text{C/W}} \approx \boxed{3.9\text{cm}}$

$$3. \text{ (9.1)} \quad V_{Icm}(\max) \leq V_{DD} - |V_{tp}| - |V_{ov1}| - |V_{ov5}|$$

$$\leq 2.5 - 0.7 - 0.3 - 0.3 = \boxed{+1.2V}$$

$$V_{Icm}(\min) \geq -V_{SS} + V_{ov3} + V_{tn} - |V_{tp}|$$

$$\geq -2.5 + 0.3 + 0.7 - 0.7 = \boxed{-2.2V}$$

$$-V_{SS} + V_{ov6} \leq V_o \leq V_{DD} - |V_{ov7}|$$

$$-2.5 + 0.3 \leq V_o \leq 2.5 - 0.3$$

$$\boxed{-2.2 \leq V_o \leq 2.2V}$$

$$(9.2) \quad A = A_1 \cdot A_2 = G_{m1} (r_{o2} \parallel r_{o4}) G_{m2} (r_{o6} \parallel r_{o7})$$

$$r_{o7} = \frac{V_{AP} = 20V/\mu m \cdot 0.8\mu m}{I_o = 0.4mA} = 40K, \quad r_{o6} = \frac{25V/\mu m \cdot 0.8\mu m}{I_o = 0.4mA} = 50K\Omega$$

$$r_{o7} \parallel r_{o6} = 22.2K\Omega$$

$g_{m1} = G_{m1}$ ← has $0.4mA/2$ current through it so

$$\frac{2I_o}{V_{ov}} = g_{m1} = \frac{2(0.4mA)}{V_{ov} = 0.25V} = 1.6mA/V$$

$$G_{m2} = g_{m6} = \frac{2(0.4mA)}{0.25V} = 3.2mA/V$$

$$\therefore A_v = 1.6mA \left[\underbrace{\frac{(20V/\mu m \cdot 0.8\mu m)}{(0.4mA/2)}}_{80K} \parallel \underbrace{\frac{(25V/\mu m \cdot 0.8\mu m)}{(0.4mA/2)}}_{100K} \right] (3.2mA) (22.2K)$$

$$A_1 = 1.6mA (44.4K) = 71.04V/V$$

$$A_2 = 3.2mA (22.2K) = 71.04V/V$$

$$A_v = (71.04)(71.04) = \boxed{5047V/V}$$

#3. (cont.)

9.2

$$R_o = r_{o7} \parallel r_{o6} = \boxed{22.2 \text{ k}\Omega}$$

For a unity gain amplifier $\Rightarrow \beta = 1$

$$\therefore R_{of} = \frac{R_o}{(1+A\beta)} = \frac{22.2 \text{ k}}{(1+5047)} \approx \boxed{4.4 \Omega}$$

4. Exercise 9.3

$$(a) f_t = \frac{G_{m1}}{2\pi C_c} \Rightarrow 100 \mu = \frac{1 \text{ m}}{2\pi C_c}$$

$$\therefore C_c = \boxed{1.4 \text{ pF}}$$

$$A_1 = -G_{m1} \cdot (r_{o2} \parallel r_{o4}) = -1 \text{ m} \left(\frac{100 \text{ k}}{2} \right) = -50$$

$$A_2 = -G_{m2} (r_{o6} \parallel r_{o7}) = -2 \text{ m} \left(\frac{40 \text{ k}}{2} \right) = -40$$

$$A_v = -50(-40) = +2,000 \text{ V/V}$$

$$f_t = |A_v| \cdot f_{p3dB} \Rightarrow f_{3dB} = \frac{100 \text{ M}}{2,000} = \boxed{50 \text{ kHz}}$$

$$(b) R = \frac{1}{G_{m2}} = \frac{1}{2 \text{ m}} = \boxed{500 \Omega}$$

$$(c) f_{p2} \approx \frac{G_{m2}}{2\pi C_2} = \frac{2 \text{ m}}{2\pi \cdot 1 \text{ p}} \approx \boxed{318 \text{ MHz}}$$

$$\theta = \tan^{-1} \frac{f_t}{f_p} = \tan^{-1} \left(\frac{100 \text{ M}}{318 \text{ M}} \right) \approx \boxed{17.5^\circ}$$

$$\text{pm} = 90 - \theta = \boxed{72.6^\circ}$$