

UNIVERSITY OF UTAH  
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 3110  
Electronics II

Midterm 2



November 22, 2004

NAME: \_\_\_\_\_

(Please print)

- Do not open the exam until instructed.
- Draw a circle or box around your final answers.
- All answers should include units (e.g., V, mA, k $\Omega$ ) where appropriate. **For frequencies, use Hz (or kHz, or MHz), *not* radians/second.**
- If you want partial credit on incorrect answers, *show your work on the pages you turn in!* If you choose to turn in any sheets of scratch paper, *write your name on those sheets!*
- Don't spend all of your time on one difficult problem. Don't be afraid to skip ahead if you get stuck. You don't have to work the problems in order.
- The use of wireless devices is prohibited during the exam.

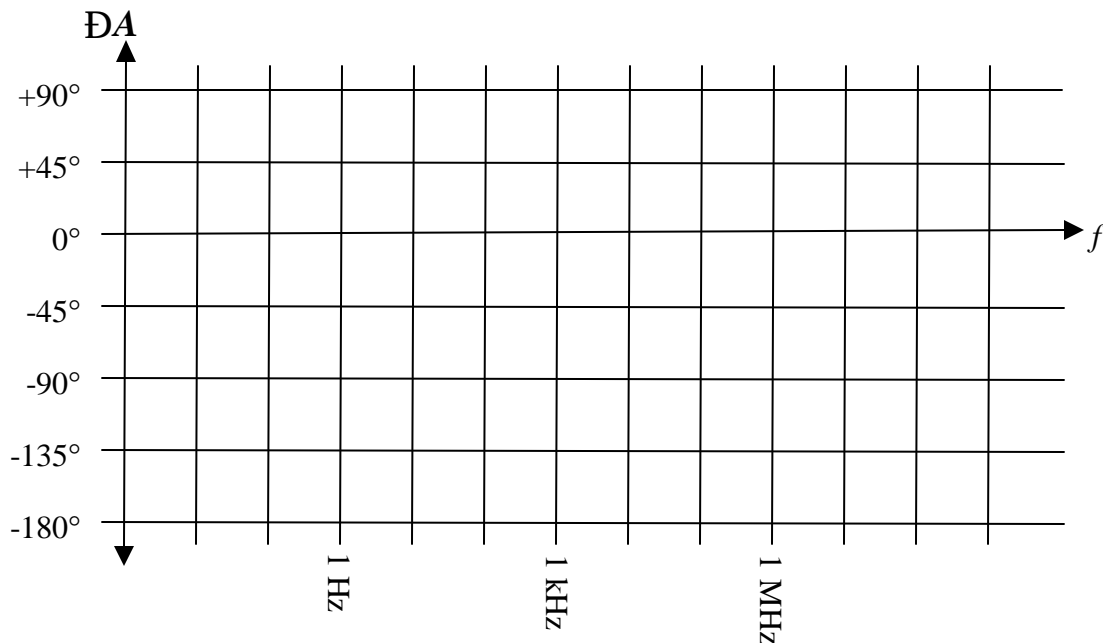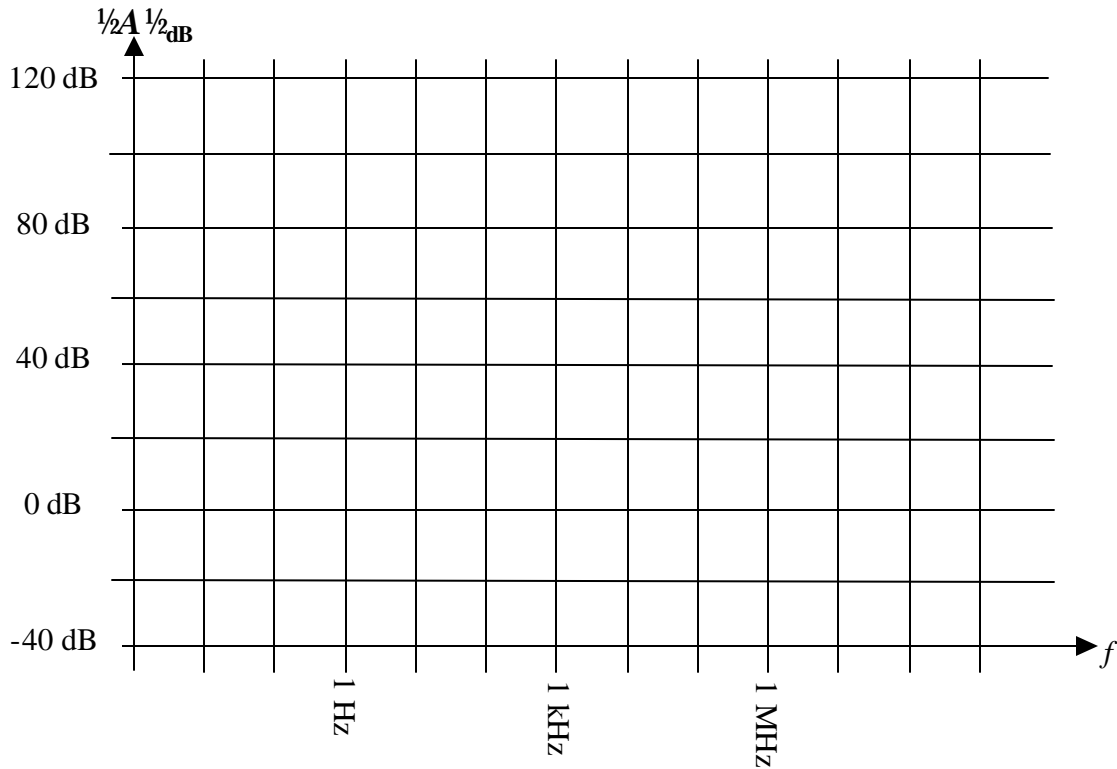1. (20 points) (a) We have an amplifier with a dc gain of 100 dB and (normal) poles at 100 Hz and 1 MHz. Draw the Bode magnitude and phase plots of this amplifier below.




(b) What is the phase margin for  $b = 0.001$ ? \_\_\_\_\_

(c) What is the *lowest* closed-loop gain  $A_f$  for which this amplifier has acceptable stability (having a phase margin of at least  $45^\circ$ )?  $A_f =$  \_\_\_\_\_

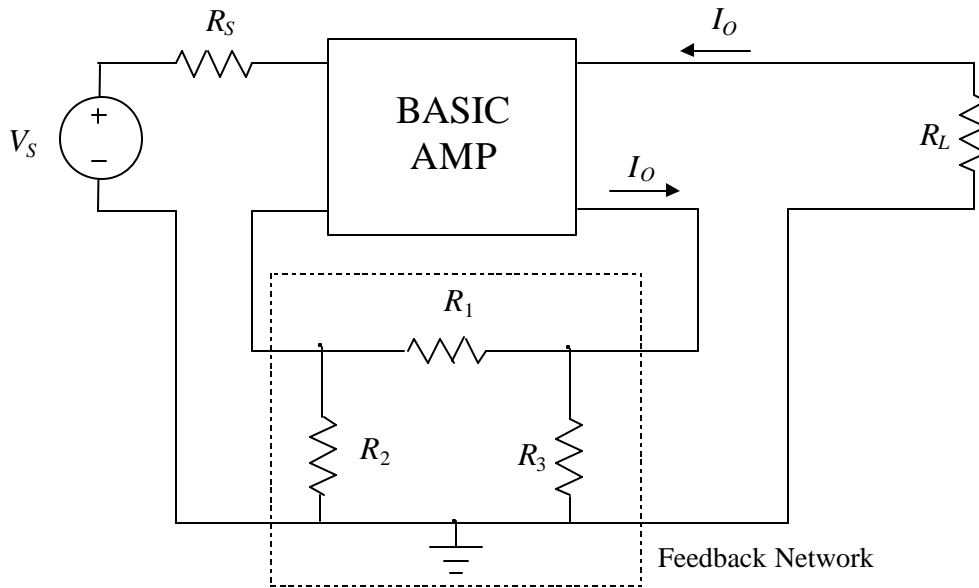2. (22 points) What type of feedback topology is shown below (e.g., series-series, shunt-series,...)?

\_\_\_\_\_

Draw three pictures showing the circuit configurations used for measuring  $\mathbf{b}$ ,  $R_{11}$ , and  $R_{22}$  for the feedback network shown, and derive expressions for  $\mathbf{b}$ ,  $R_{11}$ , and  $R_{22}$  as a function of circuit parameters.



3. (22 points) A voltage amplifier (voltage input, voltage output) having an open-circuit gain of 200, an input resistance of  $10\text{ k}\Omega$ , and an output resistance of  $100\ \Omega$  is connected in a negative-feedback loop.

(a) Which feedback topology (e.g., series-shunt, series-series, etc.) would be used in this situation?

---

The feedback network has an  $R_{11}$  and  $R_{22}$  of  $5\text{ k}\Omega$  and provides a feedback factor  $\mathbf{b} = 0.15$ . The amplifier is fed by a voltage source having  $R_S = 1\text{ k}\Omega$ , and a load resistance  $R_L = 1\text{ k}\Omega$  is connected at the output.

(b) What is  $A$ ? (Hint: It is *not* 200!)

(c) What is the closed-loop gain  $A_f$  of the feedback amplifier?

(d) What is the feedback amplifier's input resistance  $R_{in}$ ?

4. (20 points) The datasheet of the PN2222A bipolar transistor contains the following information:

Maximum allowable junction temperature  $T_{Jmax} = 150^{\circ}\text{C}$

Maximum power dissipation  $P_{Dmax} = 625 \text{ mW}$  at ambient temperature  $T_A = 25^{\circ}\text{C}$

Junction-to-case thermal resistance  $\theta_{JC} = 80^{\circ}\text{C/W}$

(a) Draw an equivalent electrical circuit for this thermal system. Label all components as well as the junction temperature  $T_J$ , the case temperature  $T_C$ , and the ambient temperature  $T_A$ . (Note that we are not using a heat sink in this problem.)

(b) Find the case-to-ambient thermal resistance  $\theta_{CA}$ .

(c) Assuming an ambient temperature of  $25^{\circ}\text{C}$ , what is the case temperature  $T_C$  when the transistor dissipates 500 mW?

5. (16 points) Circuit concepts.

(a) We discussed three types of power amplifiers or output stages in class: **Class A**, **Class B**, and **Class AB**.

Which type has the worst distortion? \_\_\_\_\_

Which type has the highest power efficiency? \_\_\_\_\_

Which type has the lowest power efficiency? \_\_\_\_\_

(b) If we put a square wave into a feedback amplifier, and the output shows too much ringing for our application, is the phase margin too high or too low? \_\_\_\_\_

(c) Name a clever circuit structure used to generate binary-weighted currents that does not require binary-weighted resistors: \_\_\_\_\_

(d) All else being equal, which ADC consumes more power: a flash ADC or a successive-approximation ADC? \_\_\_\_\_

(e) All else being equal, which ADC is *fastest*: a flash ADC, a successive-approximation ADC, or a dual-slope ADC? \_\_\_\_\_

(f) All else being equal, which ADC is *slowest*: a flash ADC, a successive-approximation ADC, or a dual-slope ADC? \_\_\_\_\_