

UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

EL EN 3110
Electronics II

Midterm 2

November 19, 2001



NAME: KEY

(Please print)

- Do not open the exam until instructed.
- Draw a circle or box around your final answers.
- All answers should include units (e.g., V, mA, k Ω) where appropriate. **For frequencies, use Hz (or kHz, or MHz), not radians/second.**
- If you want partial credit on incorrect answers, *show your work on the pages you turn in!* If you choose to turn in any sheets of scratch paper, *write your name on those sheets!*
- Don't spend all of your time on one difficult problem. Don't be afraid to skip ahead if you get stuck. You don't have to work the problems in order.
- Good luck!

1. (18 points) (a) Based on the magnitude Bode plot of an amplifier shown below, reconstruct the phase Bode plot in the space provided.

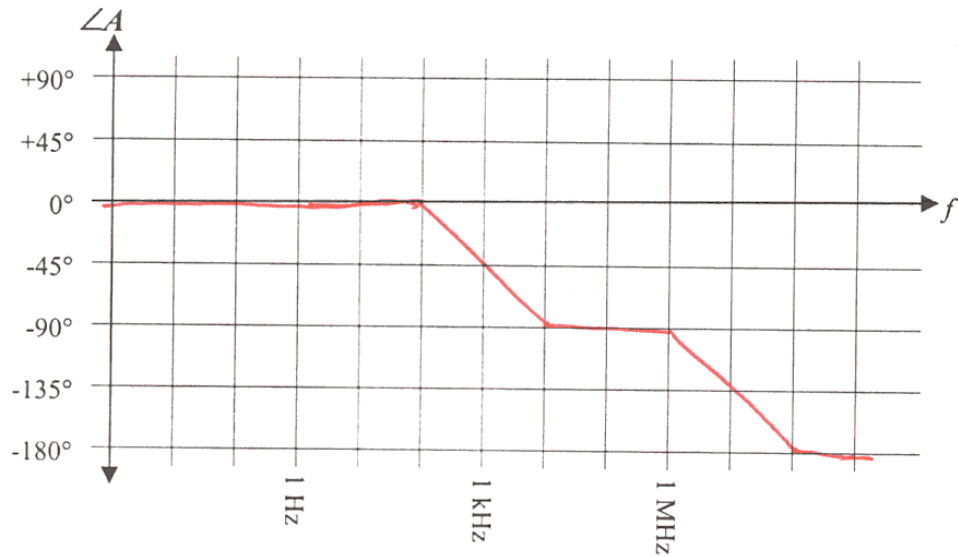
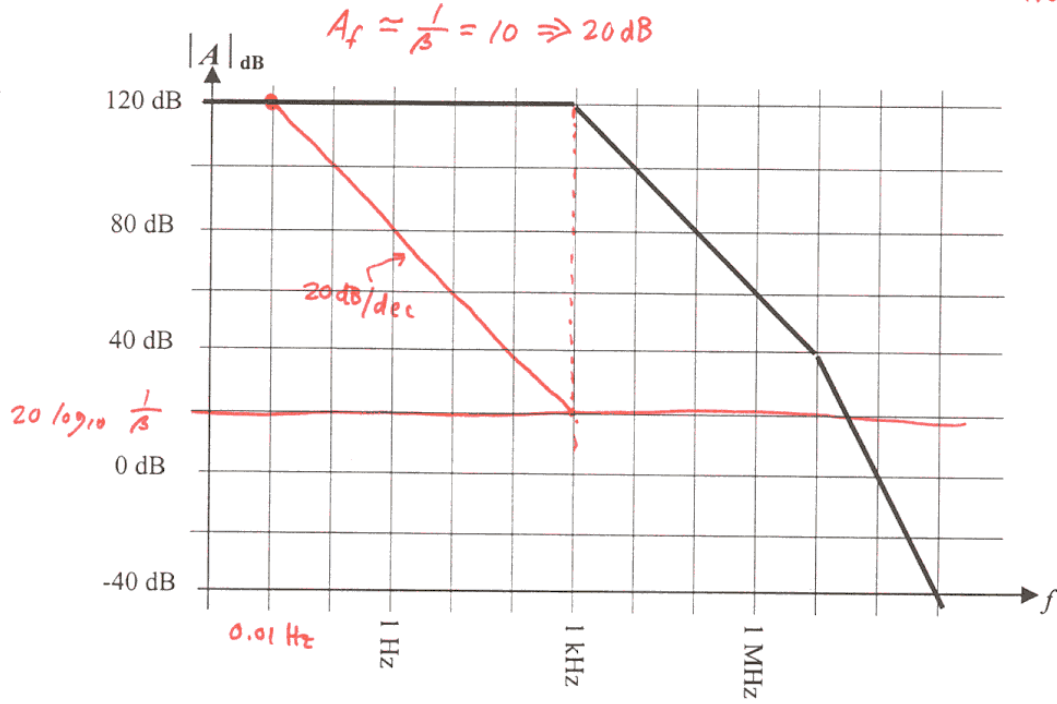
(b) At what frequency f_c should we add a pole to compensate this amplifier (for a phase margin of 45°) in a feedback network with a closed-loop dc gain of 10? $f_c = \underline{0.01 \text{ Hz}}$



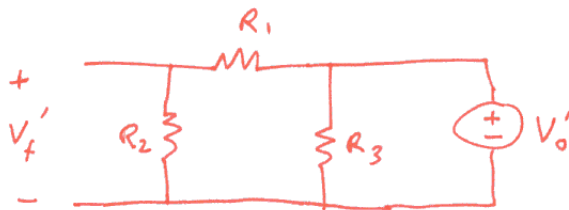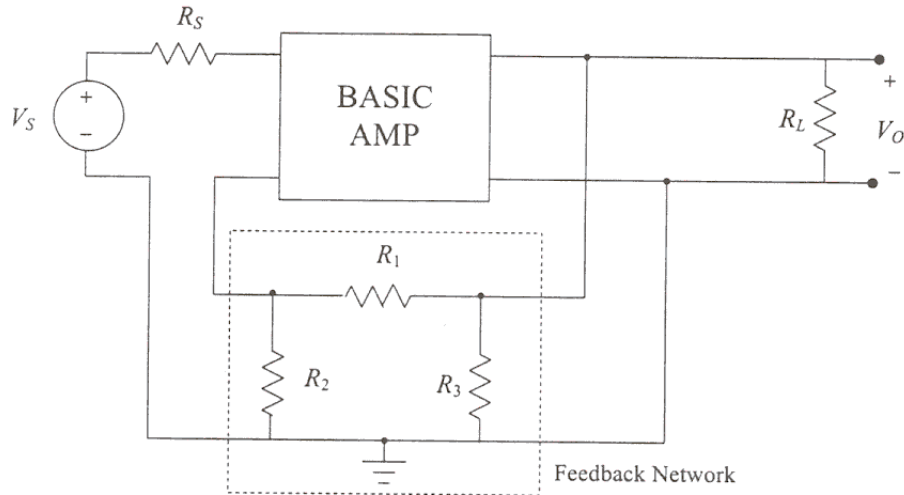
2. (18 points) What type of feedback topology is shown below (e.g., series-series, shunt-series,...)?

series-shunt


Draw three pictures showing the circuit configurations used for measuring β , R_{11} , and R_{22} for the feedback network shown, and derive expressions for β , R_{11} , and R_{22} as a function of circuit parameters.


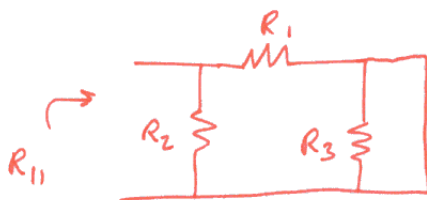
$$\beta = \frac{V'_f}{V'_0} = \frac{R_2}{R_1 + R_2}$$




$$R_{11} = R_1 \parallel R_2$$

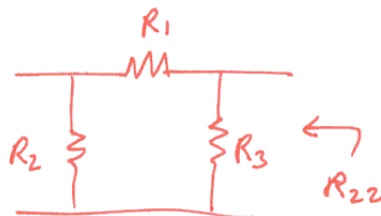

$$R_{22} = R_3 \parallel (R_1 + R_2)$$

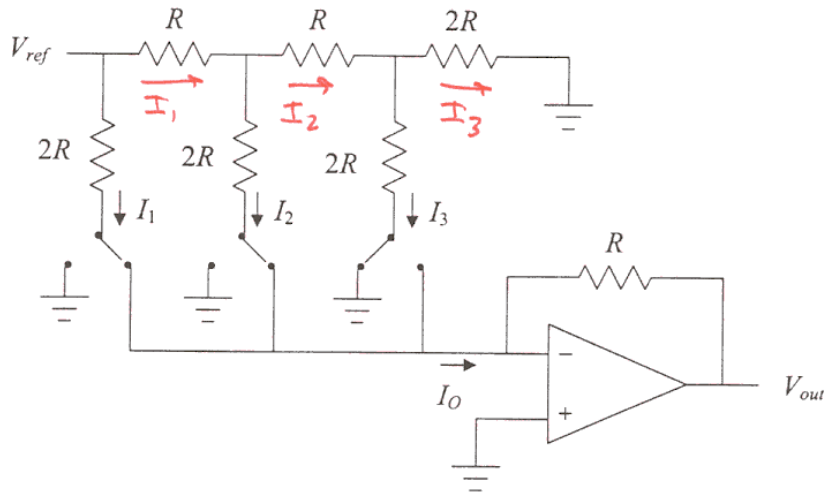3. (22 points) For the digital-to-analog converter shown below, $V_{ref} = 4\text{ V}$ and $R = 500\ \Omega$.



- Find I_1 , I_2 , I_3 , I_0 , and V_{out} . (Note the position of the switches.)

$$I_1 = \frac{V_{ref}}{2R} = \frac{4\text{ V}}{1\text{ k}\Omega} = 4\text{ mA}$$

$$I_2 = \frac{I_1}{2} = 2\text{ mA}$$

$$I_3 = \frac{I_2}{2} = 1\text{ mA}$$


$$I_0 = I_1 + I_2 = 6\text{ mA}$$

$$V_{out} = -I_0 R = -6\text{ mA}(500\ \Omega) = -3\text{ V}$$

- To what binary input does this correspond? (This D/A converter produces an output of zero volts for the binary input 000.)

110

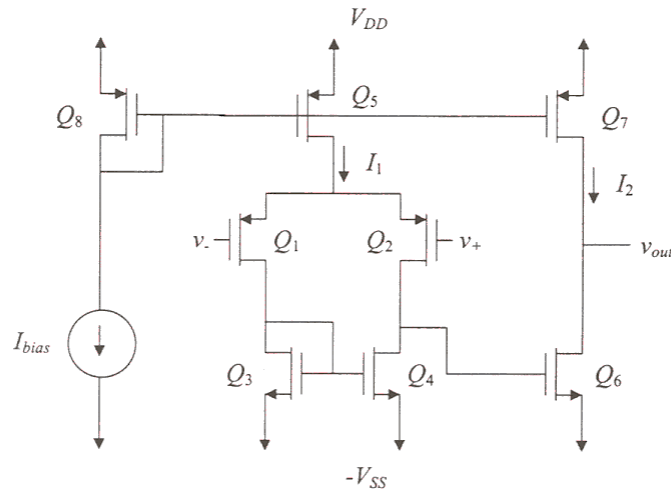4. (20 points) A simple CMOS op-amp is shown below.



$$\begin{aligned}
 V_{DD} = V_{SS} &= 5 \text{ V} & I_{bias} &= 20 \mu\text{A} \\
 \mu_p C_{ox} &= 25 \mu\text{A/V}^2 & \mu_n C_{ox} &= 75 \mu\text{A/V}^2 \\
 |V_t| &= 0.8 \text{ V} & |V_A| &= 40 \text{ V} \\
 (W/L)_1 = (W/L)_2 = (W/L)_3 = (W/L)_4 &= (W/L)_5 = (W/L)_6 = 100 & & \\
 (W/L)_7 &= 400 & (W/L)_8 &= 50
 \end{aligned}$$

- Find I_1 , I_2 , g_{m6} , and r_{o4} . (Provide numerical values for each, with units.)


$$I_1 = \frac{(W/L)_5}{(W/L)_8} I_{bias} = \frac{100}{50} \cdot 20 \mu\text{A} = 40 \mu\text{A}$$

$$I_2 = \frac{(W/L)_7}{(W/L)_8} I_{bias} = \frac{400}{50} \cdot 20 \mu\text{A} = 160 \mu\text{A}$$

$$\begin{aligned}
 g_{m6} &= \sqrt{2k_n' \left(\frac{W}{L}\right)_6 I_{D6}} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_6 I_2} = \sqrt{2 \cdot (75 \mu\text{A/V}^2) \cdot 100 \cdot 160 \mu\text{A}} \\
 &= 1.55 \text{ mA/V}
 \end{aligned}$$

$$r_{o4} = \frac{V_A}{I_{D4}} = \frac{V_A}{I_1/2} = \frac{40 \text{ V}}{20 \mu\text{A}} = 2 \text{ M}\Omega$$

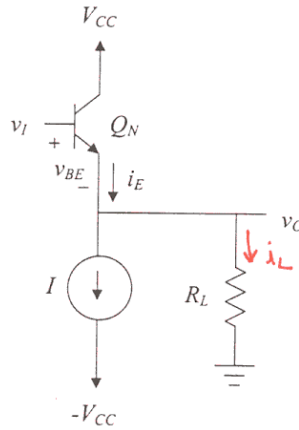5. (22 points) In the output stage below, $V_{CC} = 15\text{ V}$, $I = 6\text{ mA}$, and $R_L = 1\text{ k}\Omega$. For transistor Q_N , $I_S = 10^{-13}\text{ A}$ and β is very large.




(a) Find i_E and v_{BE} (to at least 3 significant figures) in each of three cases: $v_o = -5\text{ V}$, 0 V , and $+5\text{ V}$.

$$v_o = -5\text{ V} \quad i_L = \frac{v_o}{R_L} = -5\text{ mA} \quad i_E = I + i_L = 1\text{ mA}$$

$$v_{BE} = V_T \ln \frac{i_E}{I_S} = 0.576\text{ V}$$

$$v_o = 0\text{ V} \quad i_L = 0 \quad i_E = 6\text{ mA} \quad v_{BE} = 0.620\text{ V}$$
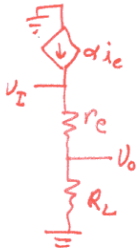
$$v_o = +5\text{ V} \quad i_L = 5\text{ mA} \quad i_E = 11\text{ mA} \quad v_{BE} = 0.636\text{ V}$$



(b) Use small-signal analysis to find the voltage gain v_o/v_i when $v_o = +5\text{ V}$.

$$\frac{v_o}{v_i} = \frac{R_L}{r_e + R_L} = \frac{R_L}{\frac{V_T}{I_E} + R_L} = \frac{1\text{ k}\Omega}{\frac{25\text{ mV}}{11\text{ mA}} + 1\text{ k}\Omega} = 0.9977$$

(c) What is v_{Omin} ?

$$\frac{v_{Omin}}{R_L} + I = 0 \quad \Rightarrow \quad v_{Omin} = -6\text{ V}$$