

# Fundamentals of Digital Logic Design

## ECE 3700

### Practise Exam for the Mid-term 2

### Spring 2009

**Note: Time yourself for 1 hr 20 min. Closed book, closed notes, open minds. Do not panic. Good luck.**

1. (4 points) Consider two 4-bit numbers  $A = \{a_3, a_2, a_1, a_0\}$  and  $B = \{b_3, b_2, b_1, b_0\}$ , given in **two's complement form**. You are asked to design a circuit that takes these two numbers and produces an output  $s$ , such that  $s = 1$  if and only if  $A > B$ . Otherwise  $s = 0$  when  $A \leq B$ . For example:

- If  $A = -2$  and  $B = -3$ ,  $A > B$ .
- If  $A = -2$  and  $B = 0$ ,  $A < B$ .
- If  $A = 5$  and  $B = -1$ ,  $A > B$ .
- If  $A = 5$  and  $B = 7$ ,  $A < B$ .

Clearly, a truth table-based approach ( $2^8$  minterms) is out of the question. Design the above circuit assuming that you have access to pre-designed 4-bit ADD/SUB unit, MUXes, Decoders, AND/OR/NOT/XOR/XNOR gates but *unfortunately, you don't have access to any magnitude comparators*.

2. (2 points) Design a circuit that takes as input *four*  $n$ -bit vectors,  $A[n-1:0]$ ,  $B[n-1:0]$ ,  $C[n-1:0]$ ,  $D[n-1:0]$  given as *unsigned* integers. The circuit selects the minimum, or the smallest amongst them, and outputs the vector. Design the circuit efficiently, using a minimum number of comparators and MUXes.

3. (3 points) Let  $f$  be a Boolean function and  $x$  be one of the variables in its support. We know that  $f$  can be decomposed using the Shannon's expansion w.r.t. variable  $x$  as  $f = x \cdot f(x=1) + \bar{x} \cdot f(x=0)$ . Note that it is customary to use the notation  $f_x = f(x=1)$  and  $f_{\bar{x}} = f(x=0)$ . So, the Shannon's expansion reads  $f = x \cdot f_x + \bar{x} \cdot f_{\bar{x}}$ . This is in fact a sum-of-product representation of the Shannon's expansion of  $f$  w.r.t.  $x$ .

(a) (1 point) Let  $f(x, y, z) = xy + yz + xz$ . Compute  $f_x = f(x=1)$ , then compute  $f_{\bar{x}} = f(x=0)$ . Now compute  $f_x \cdot f_{\bar{x}}$ ; i.e. compute the product (or Boolean AND) of  $f_x$  and  $f_{\bar{x}}$ .

(b) (2 points) Now you are asked to prove that the **product of sum** representation of the Shannon's expansion is  $f = (x + f_{\bar{x}}) \cdot (\bar{x} + f_x)$ . In other words, prove that  $(x + f_{\bar{x}}) \cdot (\bar{x} + f_x) = x \cdot f_x + \bar{x} \cdot f_{\bar{x}}$ . (There's a hint in the exercise above).

4. (3 points) Design a modulo-6 synchronous down counter using TFFs. Assume that each TFF has a  $T$ ,  $Clk$  and  $Reset$

input and  $Q$  output. You can use any logic gates that you need. (Note: Modulo 6 counter counts from 0 to 5 and goes back to 0 and repeats).

5. (3 points) Solve problem 7.22 from the textbook.