

Fundamentals of Digital System Design

ECE/CS 3700

Spring 2015, Homework # 1

Due Date: Friday, Jan 30, 2015

Please deposit the HW in the ECE/CS 3700 HW locker # 28 in MEB 2nd-floor. HW lockers are located near MEB 2325.

Note: The following set of questions correspond to chapter 2 in the textbook. I would advise you to go through chapter 2 (omit the Verilog related section 2.10 and the K-map related sections 2.11) before solving these problems. The homework is due by Jan 30. Show all your work. Should you have difficulty in understanding any of the questions, feel free to ask the TAs or the instructor. Good luck!

1) **(Simplification using Boolean Algebra - 20 points)** Using the laws of Boolean algebra, prove (or disprove) the following:

a) $(X + Y) \cdot (X + \bar{Y}) = X$

b) $(X) \cdot (X + Y) = X$

c) $(X) \cdot (X + \bar{Y}) = X$

d) $(X + Y) \cdot (\bar{X} + Z) = XZ + \bar{X}Y$. By the way, we have studied this function in class. What is it?

e) $X \cdot Y \cdot Z + X \cdot \bar{Y} = X \cdot \bar{Y} + X \cdot Z$

2) **(20 points)** Simplify the following expressions as much as possible:

a) $(x + y)(\bar{x} + y)(x + \bar{y})(\bar{x} + \bar{y})$

b) $\bar{x}(\bar{y} + \bar{z})(x + y + \bar{z})$

c) $\bar{A} \cdot B \cdot (\bar{D} + \bar{C}D) + B(A + \bar{A}CD)$

d) $x \cdot y + y \cdot z + \bar{x} \cdot z$.

3) **(3-var XOR/XNOR - 20 points)** In class, we have analyzed the Exclusive-OR (XOR) function of two variables: $f(a, b)$, which is represented as $f = a \oplus b = ab' + a'b$. Similarly, the XNOR function of two variables, $g(a, b) = a \oplus b = a'b' + ab$. Three variable XOR and XNOR functions can become somewhat tricky. Let us analyze the 3-variable XOR/XNOR functions again:

- Take the 3-variable function $f(a, b, c) = a \oplus b \oplus c$. This function is really the XOR(a, b, c). Write down the truth-table, get the ON-set minterms and obtain a simplified sum-of-product (SOP) form expression for the function. [Does there exist any simplification?]
- Now consider the 3-variable function $f(a, b, c) = \overline{a \oplus b \oplus c}$. Think about it as a NOT of XOR(a, b, c). Obtain its minimized SOP form. [Again, does there exist any SOP form simplification?]
- Now consider the function $f(a, b, c) = a \oplus b \oplus c$, which is *curiously* called the 3-variable XNOR function.

Think of f as $f = a\bar{\oplus}b\bar{\oplus}c = (a\bar{\oplus}b)\bar{\oplus}c = a\bar{\oplus}(b\bar{\oplus}c)$. Construct the truth-table for this function, and derive the minimal SOP form for the function. Do you notice how $f = a\bar{\oplus}b\bar{\oplus}c = a \oplus b \oplus c$?

- By the way, XOR/XNOR functions have many interesting properties; one of which you are kindly requested to prove (or disprove): $f(a, b) = \bar{a} \oplus b = a \oplus \bar{b} = a\bar{\oplus}b$.

4) **(A Digital Design Example - 20 points)** You are asked to design the following warning circuit for your car. The warning signal W should be set to high voltage (logical 1) if: (i) the engine is running and the door is open; OR (ii) with the engine running, somebody is sitting in the driver's seat and the belt is not fastened. Otherwise the output of the circuit is 0. The circuit should rely on the following sensors:

- Sensor from the engine ($C=1$ if engine is running, otherwise it is 0);
- Seat sensor ($S=1$ if somebody is sitting on the seat, otherwise 0);
- Door sensor ($D=1$ if the door is closed, otherwise 0);
- Belt sensor ($B=1$ if it the belt is fastened, otherwise 0).

Derive the truth table corresponding to the above specifications. Subsequently, derive a simplified Boolean expression and draw the logic circuit using AND, OR and NOT gates.

5) **(Minterms and Maxterms - 20 points)** Consider the Boolean function represented by the truth table shown in Table I.

TABLE I
TRUTH TABLE

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- Derive the Minterm Canonical form (also called the Canonical Sum-of-Product form) expression of the Boolean function from the truth table.
- Simplify the derived minterm canonical form as much as possible.
- Derive the Maxterm Canonical form (also called the Canonical Product-of-Sum form) expression of the Boolean function from the truth table.
- Is the minterm canonical form of the function logically equivalent to its maxterm canonical form? If yes, prove the equivalence of the expressions. If not, prove otherwise.

In addition to the above questions, I'm giving you a list of some exercise problems from the book that you can try to solve to gain some more practise with Logic Design and Simplification. These are not part of the HW, and they will not be graded. This is just a suggested exercise for you: Problems: 2.7, 2.12, 2.35, 2.40, 2.42.