

Fundamentals of Digital System Design

ECE/CS 3700

Spring 2018, Homework # 2

Assigned, Tuesday Feb 6, Due Date: Tuesday, Feb 13, 2018, by midnight in the HW locker.

- 1) **(FPGA Placement and Routing - 10 points)** Refer to Fig. B.39, in the textbook, given on page 768 Appendix B. The figure shows how Look-up Tables (LUTs) are interconnected by two layers of wiring: horizontal and vertical. The *blue coloured* cross-mark (\times) indicates that a connection *has been made* between the horizontally and vertically drawn wires. Convince yourselves that $f = f_1 + f_2 = x_1x_2 + x'_2x_3$.

Based on the above concepts, you are asked to *program* an FPGA, whose LUTs and inter-connection wires are shown in Fig. 1. The function to be implemented is $f = f_1 \cdot f_2$, where $f_1 = a + \bar{b}$ and $f_2 = \bar{a} + \bar{c}$. LUT 1 should implement f_1 . LUT 2 should implement f_2 and LUT 3 should implement $f_1 \cdot f_2$. The horizontally and vertically placed interconnection wires are fabricated in different planes. In order to depict a connection between these wires at a cross-point, place a cross-mark (\times). The inputs a, b, c and the output f have already been connected to the “input-output pads” for your (in)convenience. Have fun!

 


Fig. 1. Fill-up the truth-table entries in the look-up tables. Label the inputs and outputs of each LUT properly. Put a \times mark to show an electrical connection between the vertical and horizontal metal wires.

- 2) **(MUX-based design - 10 points)** Given a Boolean function $F(a, b, c) = a \oplus b \oplus c$, implement a circuit using *only* multiplexor (MUX) gates and 0, 1 (ground and V_{DD}) inputs. How many MUXes do you need? Draw a circuit schematic.

If, in addition to MUXes, 0 and 1 inputs, NOT gates (inverters) are also allowed, can the number of MUXes be reduced in the implementation of F ? If so, draw a simplified circuit, and provide the gate count of the number of MUXes and NOT gates needed.

- 3) **(Boolean Function Manipulation - 10 points)** Let $F(a, b, c) = a \cdot b + a \cdot c + b \cdot c$, then $F(\bar{a}, \bar{b}, \bar{c}) = \bar{a} \cdot \bar{b} + \bar{a} \cdot \bar{c} + \bar{b} \cdot \bar{c}$, where \bar{a} denotes the complement of a . Now answer the following:

- Is $\overline{F(a, b, c)} = F(\bar{a}, \bar{b}, \bar{c})$?
- Now consider an *arbitrary* Boolean function $F(a, b, c)$. Is inverting the inputs of F equivalent to inverting the function itself? In other words, for an arbitrary Boolean function $F(a, b, c)$, is $\overline{F(a, b, c)} = F(\bar{a}, \bar{b}, \bar{c})$? If yes, prove it. Otherwise, give a counter-example.

- 4) **(K-Map minimization - 25 points)** For the following functions, whose on-set minterms are shown using the $\text{sigma}(\Sigma)$ notation, derive a minimum Sum-of-Product (SOP) form expression using Karnaugh maps (K-maps). Note that your final answer should be a sum-of-product form Boolean expression, derived using cube-covering on the K-maps.

- $F(A, B, C, D) = \Sigma m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15)$
- $F(A, B, C, D) = \Sigma m(1, 2, 3, 6, 7, 11)$
- $F(A, B, C, D) = \Sigma m(2, 3, 5, 7, 10, 11, 13, 14, 15)$
- $F(A, B, C, D, E) = \Sigma m(2, 5, 7, 8, 10, 13, 15, 17, 19, 21, 23, 24, 29, 31)$
- $F(A, B, C, D, E) = \Sigma m(0, 4, 18, 19, 22, 23, 25, 29)$

- 5) **(K-maps with don't cares - 10 points)**. Derive minimum cost SOP forms for these functions.

- $F(A, B, C, D) = \Sigma m(1, 3, 5, 7, 9) + \Sigma d(6, 8, 12, 13)$
- $F(A, B, C, D) = \Sigma m(0, 2, 8, 9, 10, 15) + \Sigma d(1, 3, 6, 7)$

- 6) **(Another Min cost SOP - 15 points)** Consider the function $f(x_1, \dots, x_4) = \Sigma m(0, 3, 4, 5, 7, 9, 11) + D(8, 12, 13, 14)$. Working on a K-map, first generate and list all the *prime implicants* of the function. Subsequently, from among these primes, identify the essential primes, and then derive a *minimum (literal) cost* SOP form Boolean expression. How many product-terms does the min-cost SOP form have? What is the total literal cost of the min-cost SOP?

7) **(Synthesis of a decomposed Boolean function by exploiting don't care conditions - 20 points)** Consider the Boolean function $F(a, b, c, d, e)$ whose K-map is shown below in Fig. 2 (i). Now suppose that a logic synthesis algorithm decomposes F as $F(a, b, c, d, e) = h(g_0(a, b, c), g_1(a, b, c), d, e)$, shown in Fig. 2, where the SOP representations are:

- Functions $g_0 = a'bc + ab'c + abc'$ and $g_1 = a'b'c + abc$
- Function $h = g_0'g_1'e' + g_0g_1'd' + g_0'g_1e$

You are asked to solve the following:

- a) From the K-map of $F(a, b, c, d, e)$, identify a minimum SOP form representation of F in its *undecomposed* form in terms of the primary inputs $\{a, b, c, d, e\}$. What is the SOP literal cost of F ?
- b) Now assume the a decomposition is applied as shown in Fig. 2. Minimize the SOP form of g_0, g_1, h . Are they already given in minimal form?
- c) This decomposition creates don't care conditions at the input of the $h(g_0, g_1, d, e)$ block. Identify the don't care conditions at the input of h .
- d) Using the don't care conditions, minimize the SOP form of h . What is the total SOP literal cost of g_0, g_1 and h . Do the don't care conditions result in further logic simplification with literal cost savings?

a	0	0	0	0	1	1	1	1
b	0	0	1	1	1	1	0	0
c	0	1	1	0	0	1	1	0
de	00	1	0	1	1	1	0	1
	01	0	1	1	0	1	1	0
	11	0	1	0	0	1	0	0
	10	1	0	0	1	0	0	1

 
(i) $F(a, b, c, d, e)$ (ii) A decomposed implementation of $F(a,b,c,d,e)$

Fig. 2. Decomposition of $F(a, b, c, d, e) = h(g_0(a, b, c), g_1(a, b, c), d, e)$. Compute the don't cares at the input of the $h(g_0, g_1, d, e)$ block and simplify the SOP form of h .