

Q1

Break the problem into two cases:-

① When A & B have diff sign

② " " " " " same "

When A & B have diff. sign ($A_3 \oplus B_3$)

$A > B$ if A +ve (& B is -ve)

When A & B have same sign

$A - B \geq 0 \Rightarrow A \geq B$
Compute $A - B = S$.


or $S[3:0] = A[3:0] - B[3:0]$

if $S[3] == 0, S \geq 0$.


We have to account for $A = B (\Rightarrow A - B = 0)$

$\therefore \underline{S_2 + S_1 + S_0 = 1 \Rightarrow A - B \neq 0}$

$\bar{S}_3 (S_2 + S_1 + S_0)$

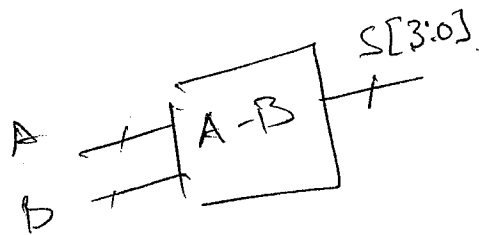

$\bar{S}_3 \cdot (S_2 + S_1 + S_0)$

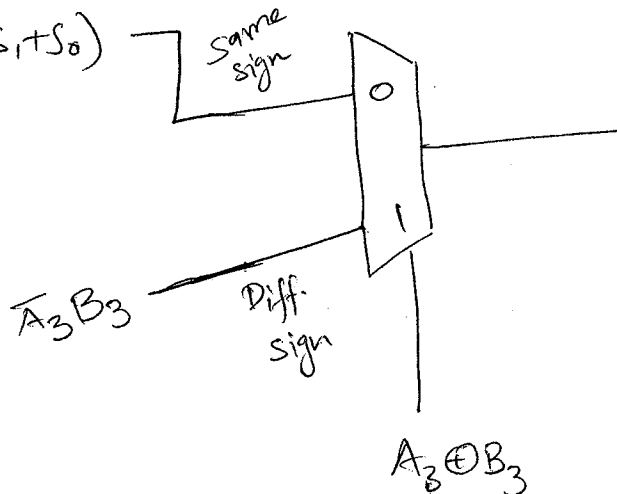

Q2.

If $A < B$, $F_1 = A$.

else $F_1 = B$.

If $C < D$

$F_2 = C$



else $F_2 = D$.

if $F_1 < F_2$

$F = F_1$

else F_2 .

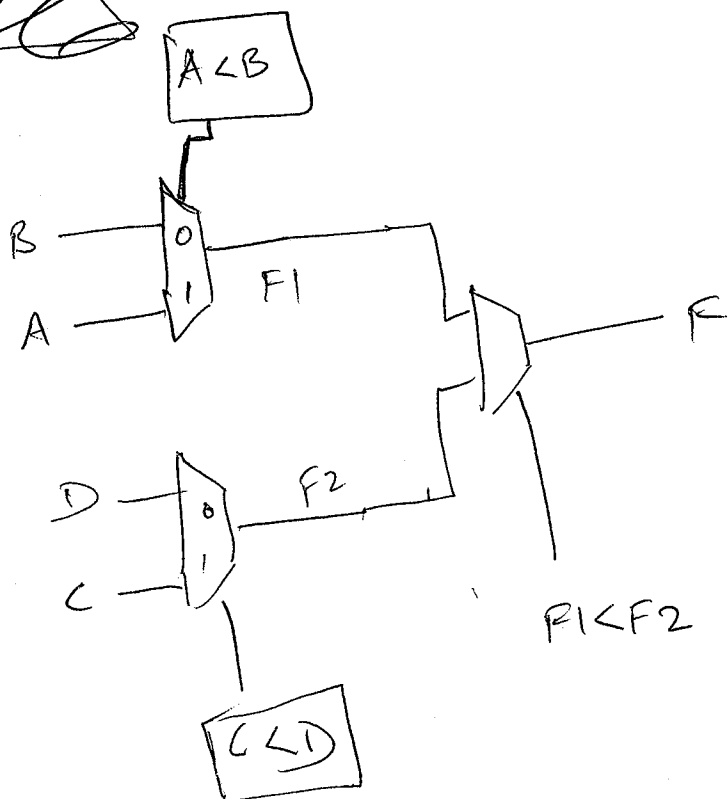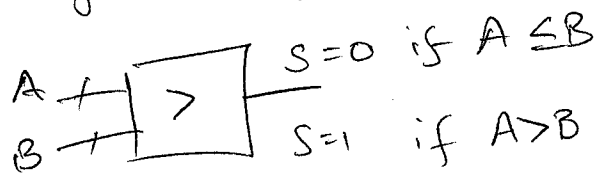Assume predesigned magnitude comparators & Muxes.



Q3. $f = xy + xz + yz.$

(a) ~~f_x~~ $f_x = f(x=1) = y + z + yz = y + z.$

$f_{\bar{x}} = f(x=0) = 0 + 0 + yz = yz.$

$f_x \cdot f_{\bar{x}} = (y+z)(yz) = yz.$

(b) Prove. $f = (x + f_{\bar{x}})(\bar{x} + f_x)$

$= \underbrace{x \cdot \bar{x}}_0 + x f_{\bar{x}} + \bar{x} f_x + f_x \cdot f_{\bar{x}}$

$= x f_{\bar{x}} + \bar{x} f_x + f_x \cdot f_{\bar{x}}$

↳ we know this if f' , by Shannon's expansion

So $f = f + f_x \cdot f_{\bar{x}}$

Note $f_x \cdot f_{\bar{x}} \neq 0$ (as shown in (a))

∴ $f = f + f_x \cdot f_{\bar{x}}$ is possible only if

~~f~~ $f_x \cdot f_{\bar{x}}$ is contained in f

∴ $f = x f_{\bar{x}} + \bar{x} f_x + f_x \cdot f_{\bar{x}}$

$= x f_{\bar{x}} + \bar{x} f_x + \underbrace{1 \cdot f_x \cdot f_{\bar{x}}}_{(x + \bar{x})}$

$$\begin{aligned}
 f &= x f_x + \bar{x} f_{\bar{x}} + (x + \bar{x}) f_x \cdot f_{\bar{x}} \\
 &= x f_x + \bar{x} f_{\bar{x}} + x f_x f_{\bar{x}} + \bar{x} f_x f_{\bar{x}} \\
 &= x f_x (1 + f_{\bar{x}}) + \bar{x} f_{\bar{x}} (1 + f_x) \\
 &= x f_x - 1 + \bar{x} f_{\bar{x}} \cdot 1 \\
 &= x f_x + \bar{x} f_{\bar{x}} = \underline{\underline{f}}.
 \end{aligned}$$

Note $f_x \cdot f_{\bar{x}} =$ contained in f .

\downarrow $y z$
 \downarrow $x y + y z + x z$

$f_x \cdot f_{\bar{x}}$ = that component of f which is independent of x .

$$f = x y + y z + x z$$

$$\underline{\underline{f_x \cdot f_{\bar{x}} = y z}} = \text{independent of } x$$

&


contained in f .

Q4 Note: \rightarrow There is a "typo" in the question.

I wanted you to design an up counter, that counts

modulo-6. ["Down" counting %6 really doesn't mean anything. While such a "down" counter can be designed, it is better done using DFFs rather than TFFs]


\rightarrow you count as:-

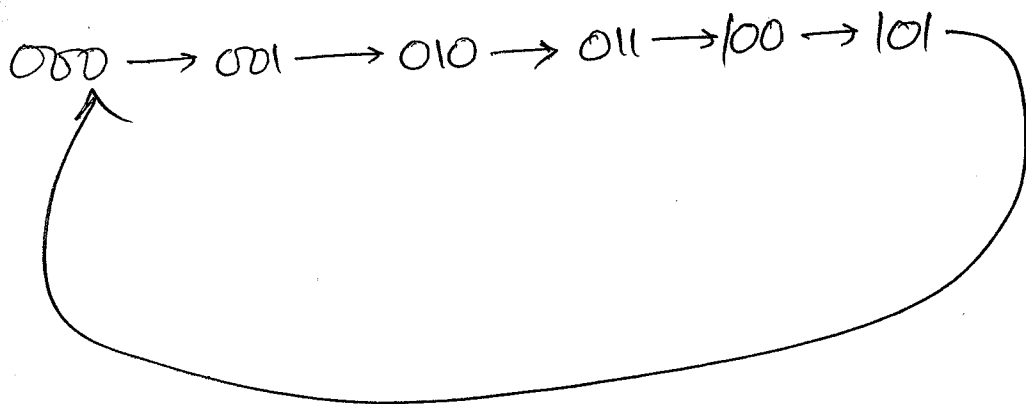

Think of this design as a regular up counter, with a specific reset logic. When $q_2 q_1 q_0 = 101$, then in the next cycle, you reset the TFFs.

\nearrow
this works when reset is synchronous.

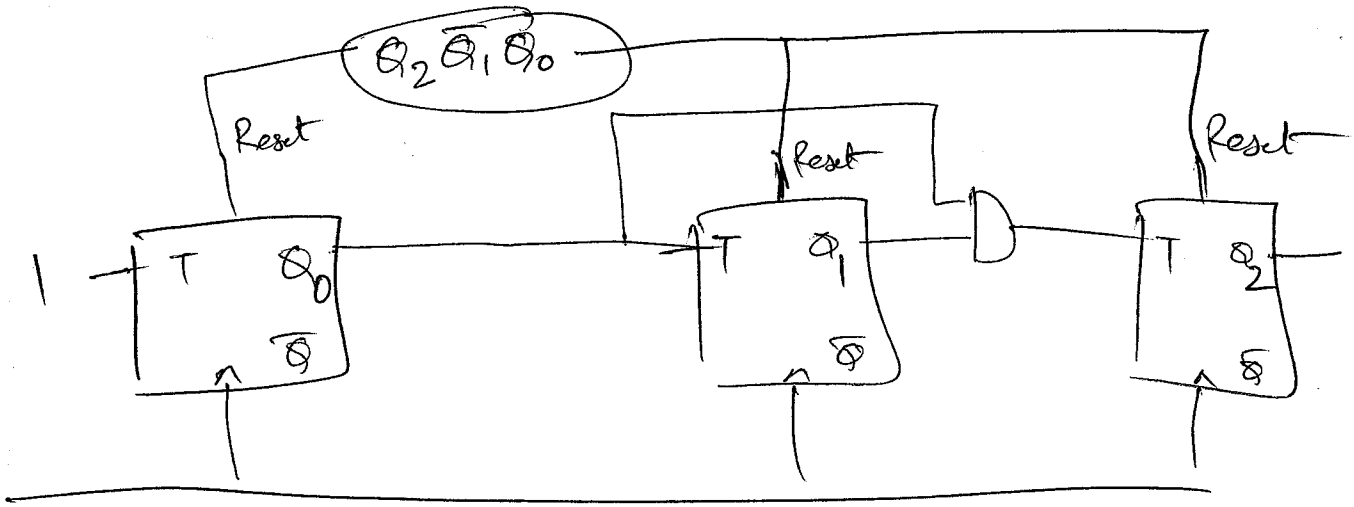When reset is asynchronous, you would rather that the counter count to 110 (6), and as soon as $q_2 q_1 q_0 = 110$, reset logic resets the TFFs immediately to '000' & repeat



OK

Q5

$$T_{su} = 3$$

$$T_h = 1 \text{ ns}$$

$$T_{prop} = 1 \text{ ns}$$

Since $T_{prop} = T_h$, we won't really see hold time violations.

$$\text{So } T_{\text{delay}} = \underbrace{T_{\text{combinational logic}}}_{\text{longest path}} + T_{prop} + T_{su}$$

↓
longest path

↓
 $Q_0 \rightarrow 3 \text{ And gates} \rightarrow \text{XOR} \rightarrow \text{Mux} \rightarrow$

the D-input of last DFF.

$$= \underline{\underline{5 \text{ ns}}}$$

$$T_{\text{delay}} = 5 + 3 + 1 = \underline{\underline{9 \text{ ns}}}$$