

Sequential Circuit Testing

Sequential Circuits and Finite State Machines

Priyank Kalla




Professor
Electrical and Computer Engineering, University of Utah
kalla@ece.utah.edu
<http://www.ece.utah.edu/~kalla>

Slides updated Dec 1, 2021


- Review of Sequential Circuits and Mealy Finite State Machines (FSM)
- The concept of FSM equivalence
- Fault excitation and propagation conditions in FSM
- Reset states, synchronizing sequences and redundant states
- Untestable faults in sequential circuits

Sequential Circuits

 
- We consider sequential circuits with edge-triggered D-flip-flops
- Underlying a sequential circuit is a finite state machine (FSM)
- We will consider only FSMs of the Mealy-type (Moore machine ATPG is similar)
- An example of sequential circuit:



FSM and Circuit example

 

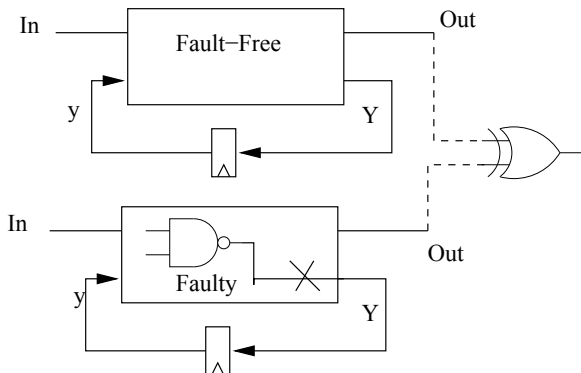Sequential Circuit Testing: Sequential Miter



- Find a **sequence of inputs** (or input vectors) that produces an output 1 at the miter output, sometime in the future clock cycles

Two Machines, \mathcal{M}_1 and \mathcal{M}_2 , are equivalent if

- They are identical; or
- They have identical states but different encoding; or
- $\mathcal{M}_1 \subseteq \mathcal{M}_2$ or vice-versa; or
- They have different reachable states but same distinguishable states (same condition as above); or
- Different unreachable states, and unreachable states are a *don't care* condition

Prove that two machines (sequential circuits) produce the same output response on application of all possible input **sequences**

Sequential ATPG is Harder than Combinational

- Given: A sequential circuit, generate ATPG. Sometimes reset (starting) state available, sometimes not!
- Procedure: Activate a fault, and propagate it to PO
- Bottlenecks: Fault activation requires an “activation state”. How to get to the activation state? Fault can be propagated to the next-state line, but not to PO? Unroll the machine, or in other words, traverse to other states.
- How to distinguish between Faulty and Fault-free machines? The concept of state distinguishing sequences.
- In absence of resets, how to synchronize both faulty and fault-free machines to the same states. Concept of synchronizing sequences.

Untestable Faults in Sequential Circuits


A fault in a sequential circuit can be untestable due to **four reasons**:

- Redundancy in a combinational logic
- Lack of a common synchronizing sequence that can drive both faulty and fault-free machines to a common (starting) state
- Sequential Redundancy: a fault causes a transition to a (faulty) state which may be equivalent to a fault-free state
- Fault excitation or propagation requires getting to an unreachable state

We will look at all these cases!

First example: When reset state exists

 
- Start the machine in a reset state (00), traverse FSM
- At some point in the future, faulty and fault-free machines will diverge



Test: $\underline{x_0 = 1}, x_1 = 1, x_2 = 0, x_3 = 1$

First example: When reset state exists

 
- Start the machine in a reset state (00), traverse FSM
- At some point in the future, faulty and fault-free machines will diverge



Test: $x_0 = 1, \underline{x_1 = 1}, x_2 = 0, x_3 = 1$

First example: When reset state exists

 
- Start the machine in a reset state (00), traverse FSM
- At some point in the future, faulty and fault-free machines will diverge



Test: $x_0 = 1, x_1 = 1, \underline{x_2 = 0}, x_3 = 1$

First example: When reset state exists

 - Start the machine in a reset state (00), traverse FSM
- At some point in the future, faulty and fault-free machines will diverge



Test: $x_0 = 1, x_1 = 1, x_2 = 0, \underline{x_3 = 1}$

Meaning of the above Test

- Fault D or \overline{D} gets into next state line.
- Faulty and Fault-free machines go to different states.
- Machine operation diverges....
- Sometime in the future, you can catch that effect.
- You can distinguish between faulty and faulty-free states of the machine.
- How? Using state distinguishing experiments.

When there is no reset state?


- Power up the machine, it can be in any (unknown) state
- Does there exist a sequence of inputs that can drive the machine to some – singleton – state?
- Some machines have a synchronizing sequence, others do not
- Given an FSM, how to find a synchronizing sequence?
- For ATPG: we are not given the FSM, only the circuit
- For ATPG: We need to find a synchronizing sequence for both the faulty and fault-free machines that can drive both to a common state. This can be hard.

Synchronizing Sequence on an FSM


Table: State Transition Table

P.S.	Next State, Z	
	$x = 0$	$x = 1$
A	B, 0	D, 0
B	A, 0	B, 0
C	D, 1	A, 0
D	D, 1	C, 0

 This machine has no Synchronizing Sequence



ATPG without Reset State

 

No Reset State Example: Test Exists

- No reset state. Start w/ Fault excitation state: $y_1 = 0, y_2 = 1$.
- $x = 1$ propagates the fault effect!
- Problem: How to get to the fault excitation state?
- Answer: Sequential backtrack! Unroll the m/c backwards until you can get unknown values in FFs. This implies there exists a state (backward in time from F.E. state) where you can “control” the FFs (control the state).
- Called Self-Initializing tests! This test implies that both faulty and fault-free machines can be initialized to a “common initial state”; i.e., you can get a common starting point.


ATPG without Reset State

Y = Next state FF inputs, y = present state FF output

Generate a self initializing test: **Start in Time Frame (TF) 1:**


$$Y_2 = 1, Y_1 = 1, Z = D$$

This requires: $y_1 = 0, y_2 = 1, x = 1$

 


ATPG without Reset State

 If in TF 1, present states are $y_1 = 0, y_2 = 1$, then in the **previous state TF 0**: $Y_1 = 0, Y_2 = 1$. Make $x = 1, y_1 = 0, y_2 = 0$





ATPG without Reset State

 In TF 0 : $y_1 = 0, y_2 = 0$, then go back in time again **TF -1**:
 $Y_1 = 0, Y_2 = 0$ is needed, so apply $x = 0$





Test: TF -1 $x = 0$, TF 0 $x = 1$, TF 1 $x = 1$.



No Self Initializing Test without Reset

  


No Self Initializing Test without Reset

  

No Self Initializing Test without Reset

  


No Self Initializing Test without Reset

 


Therefore, no test exists, deduced after 4 clock cycles of sequential backtrace!

Untestable Faults: Unreachable State

 


$$Y1 = y1 y2 + y1' y2' x'$$

$$Y2 = y1' x + y1 y2'$$

 


Untestable Fault: Sequential Redundancy

 

States (110) and (010) are equivalent -> cannot be distinguished!

What if fault takes m/c to 110 (faulty state), instead of 010 (fault free)?

Redundant Circuit ATPG

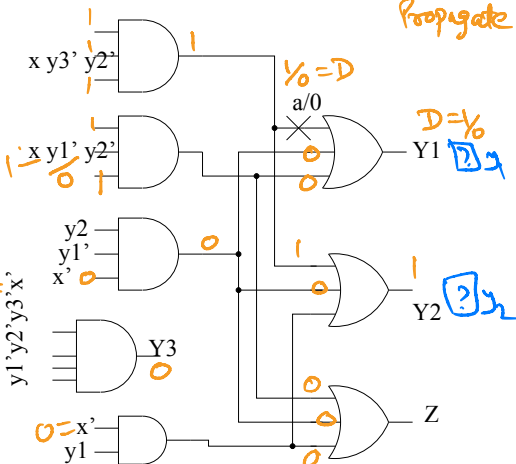

Excite $x=1, y_3=0, y_2=0$

Propagate

$$y_1' = 0 \Rightarrow y_1 = 1$$

Excitation state

$$y_1 y_2 y_3 = 100$$

Next state

$$Y_1 Y_2 Y_3 = D10$$


$$FF = 110$$

$$\text{Faulty} = 010$$

$$Z = 0$$

Redundant Circuit ATPG

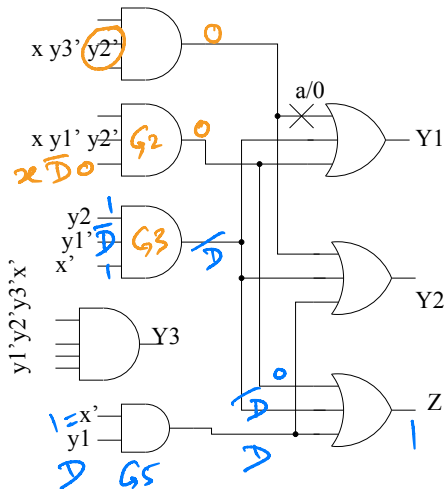Next clk cycle $y_1 y_2 y_3 = PS = \underline{D10}$



Propagate from $G_2 \rightarrow Z$

$$J_2 = 1 \Rightarrow y_2' = 0$$

$$S_2 = 0.$$

$G_3 \rightarrow Z$

$$x' = 1 \Rightarrow x = 0 \text{ reqd.}$$

But $x' = 1$

$$D + D = 1 @ Z$$

Fault masked!

Simplify Sequential ATPG using Scan Design


DFT = Design for Test

- Primary inputs = controllable, Primary outputs = observable
- Lack of controllability and observability of Flip-Flops
- For testing purposes, make the flip-flops both controllable and observable
- Approach: Introduce Scan-registers
- Make a sequential circuit combinational for Testing

LSSD


Scan Flip-Flop Design

normal mode $T_I = T_O = 0$

 


TI/TO: Test input/output
SI/SO: Scan value in/Scan value out

$T_I = 1$
 $T_O = 1$

 

Scan Based ATPG: Use Shift-register Scan Chain


T.I=1 01 Test T.O=1

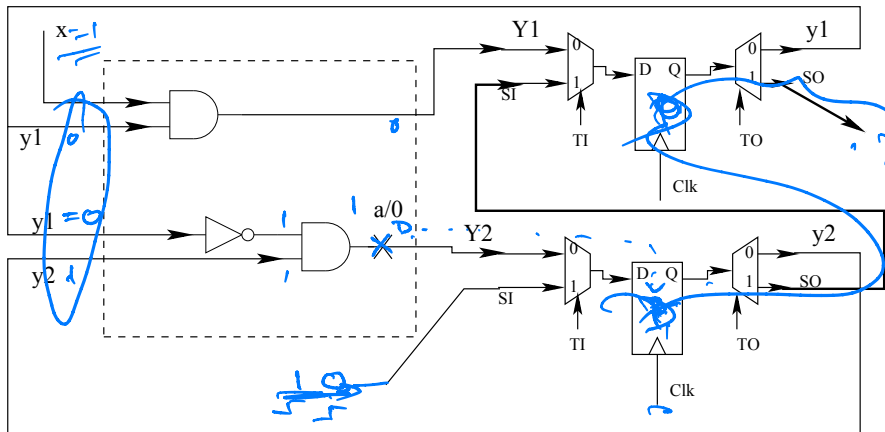

Partial scan

TETRAMAX

Other Test Problems: False Paths

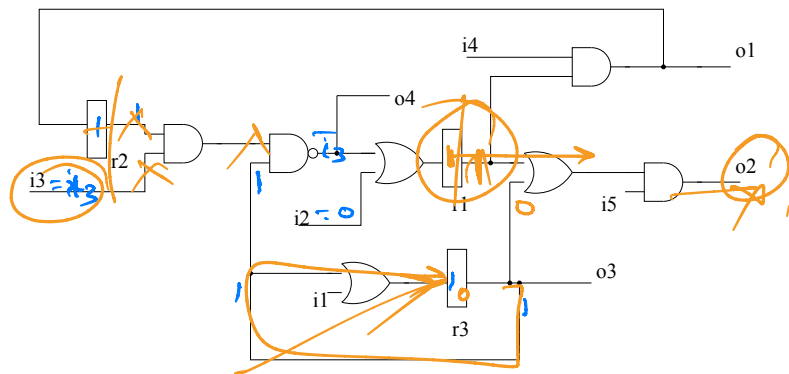


- Input $i_3 \rightarrow r_1 \rightarrow o_2$ is a multi-cycle False Path
- Cannot be sensitized: Need $o_3 = 1$ in clock cycle 1, and $o_3 = 0$ in clock cycle 2. Not possible

IDDQ Testing: Measure Leakage Current

- Fault Location in Transistors: Test I_{DDQ}
- Transistor can be stuck-ON or stuck-open. CMOS gates consume NO static power.
- Test for N_c stuck-open: $\langle V_1, V_3 \rangle$ Two vector test


$$F = \overline{ab + c}$$

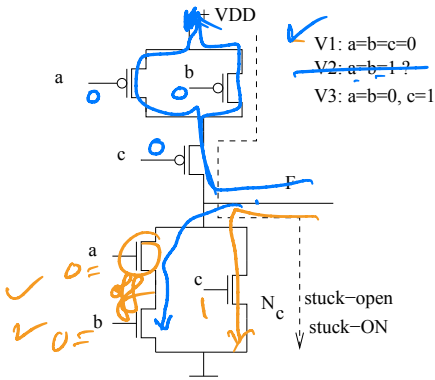

$$F = \overline{ab + c}$$

BIST = built-in self-Test

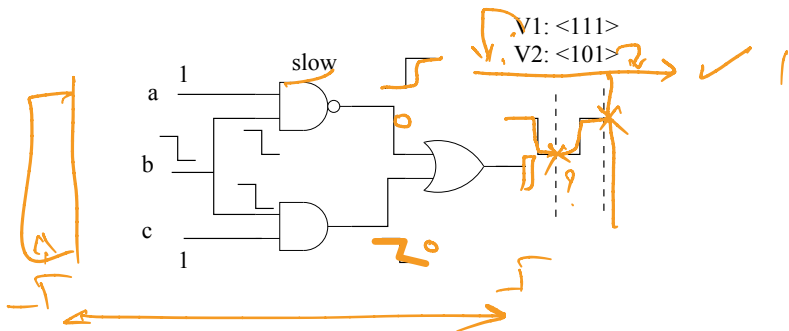- Gates do not switch at desired speed
- Find vectors that detect delay faults!
- Big challenge in Test Application: How to apply 2-vector tests using scan flip-flops at speed?



Delay Fault Testing

- Gates do not switch at desired speed
- Find vectors that detect delay faults!
- Big challenge in Test Application: How to apply 2-vector tests using scan flip-flops at speed?

