

Sequential Circuit Testing

Sequential Circuits and Finite State Machines

Priyank Kalla




Professor
Electrical and Computer Engineering, University of Utah
kalla@ece.utah.edu
<http://www.ece.utah.edu/~kalla>

Slides updated Dec 1, 2021

- Review of Sequential Circuits and Mealy Finite State Machines (FSM)
- The concept of FSM equivalence
- Fault excitation and propagation conditions in FSM
- Reset states, synchronizing sequences and redundant states
- Untestable faults in sequential circuits



Sequential Circuits

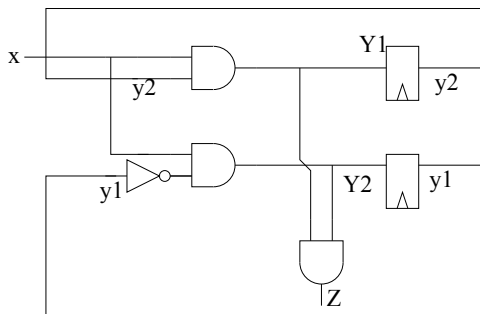- We consider sequential circuits with edge-triggered D-flip-flops
- Underlying a sequential circuit is a finite state machine (FSM)
- We will consider only FSMs of the Mealy-type (Moore machine ATPG is similar)
- An example of sequential circuit:




FSM and Circuit example

  For ATPG, we are not given the FSM.
Given \rightarrow only the circuit



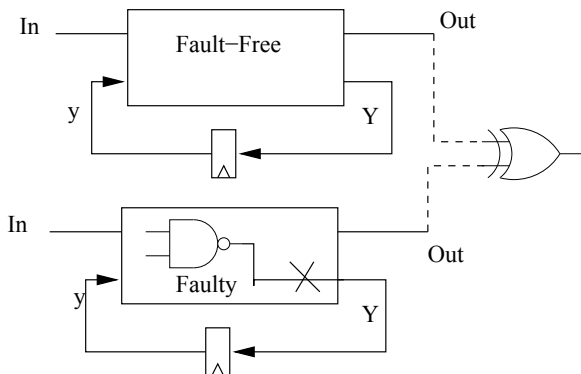Sequential Circuit Testing: Sequential Miter



- Find a **sequence of inputs** (or input vectors) that produces an output 1 at the miter output, sometime in the future clock cycles

Two Machines, \mathcal{M}_1 and \mathcal{M}_2 , are equivalent if

- They are identical; or
- They have identical states but different encoding; or
- $\mathcal{M}_1 \subseteq \mathcal{M}_2$ or vice-versa; or
- They have different reachable states but same distinguishable states (same condition as above); or
- Different unreachable states, and unreachable states are a *don't care* condition

Prove that two machines (sequential circuits) produce the same output response on application of all possible input **sequences**

Sequential ATPG is Harder than Combinational

- Given: A sequential circuit, generate ATPG. Sometimes reset (starting) state available, sometimes not!
- Procedure: Activate a fault, and propagate it to PO
- Bottlenecks: Fault activation requires an “activation state”. How to get to the activation state? Fault can be propagated to the next-state line, but not to PO? Unroll the machine, or in other words, traverse to other states.
- How to distinguish between Faulty and Fault-free machines? The concept of state distinguishing sequences.
- In absence of resets, how to synchronize both faulty and fault-free machines to the same states. Concept of synchronizing sequences.

Untestable Faults in Sequential Circuits


A fault in a sequential circuit can be untestable due to **four reasons**:

- Redundancy in a combinational logic
- Lack of a common synchronizing sequence that can drive both faulty and fault-free machines to a common (starting) state
- Sequential Redundancy: a fault causes a transition to a (faulty) state which may be equivalent to a fault-free state
- Fault excitation or propagation requires getting to an unreachable state

We will look at all these cases!

First example: When reset state exists

 - Start the machine in a reset state (00), traverse FSM
- At some point in the future, faulty and fault-free machines will diverge




Test: $x_0 = 1, x_1 = 1, x_2 = 0, x_3 = 1$

$x_0 = 0$ takes me back to (00) \rightarrow Can't get out

First example: When reset state exists

$x_0=1, Y_1=0, Y_2=1, Z=0$. T.F.I: $y_1=0, y_2=1$

 - Start the machine in a reset state (00), traverse FSM
- At some point in the future, faulty and fault-free machines will diverge





Test: $x_0 = 1, \underline{x_1 = 1}, x_2 = 0, x_3 = 1$

$\hookrightarrow Y_1=1, Y_2=1, Z=0$

First example: When reset state exists

TF1: $x_1=1, y_1=1, y_2=1, z=0$ TF2: $y_1=1, y_2=1$

  - Start the machine in a reset state (00), traverse FSM
- At some point in the future, faulty and fault-free machines will diverge





Test: $x_0 = 1, x_1 = 1, \underline{x_2 = 0}, x_3 = 1$

$\hookrightarrow Y_1 = D, Y_2 = 1$

First example: When reset state exists

TF3: $y_1 = D, y_2 = 1$

  - Start the machine in a reset state (00), traverse FSM
- At some point in the future, faulty and fault-free machines will diverge



Test: $x_0 = 1, x_1 = 1, x_2 = 0, \underline{x_3 = 1}$

Meaning of the above Test

- Fault D or \overline{D} gets into next state line.
- Faulty and Fault-free machines go to different states.
- Machine operation diverges....
- Sometime in the future, you can catch that effect.
- You can distinguish between faulty and faulty-free states of the machine.
- How? Using state distinguishing experiments.


When there is no reset state?

- Power up the machine, it can be in any (unknown) state
- Does there exist a sequence of inputs that can drive the machine to some – singleton – state?
- Some machines have a synchronizing sequence, others do not
- Given an FSM, how to find a synchronizing sequence?
- For ATPG: we are not given the FSM, only the circuit
- For ATPG: We need to find a synchronizing sequence for both the faulty and fault-free machines that can drive both to a common state. This can be hard.



Synchronizing Sequence on an FSM

Table: State Transition Table


P.S.	Next State, Z	
	x = 0	x = 1
A	B, 0	D, 0
B	A, 0	B, 0
C	D, 1	A, 0
D	D, 1	C, 0

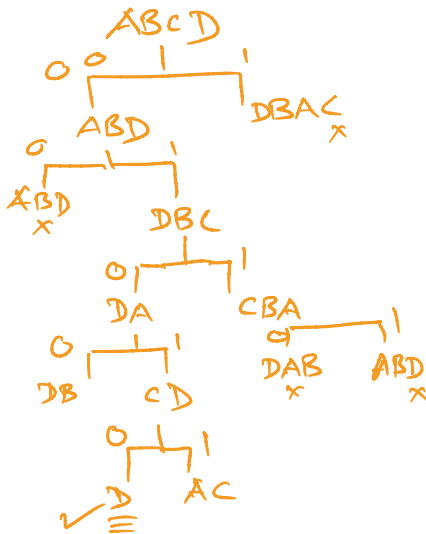

  This machine has no Synchronizing Sequence



ATPG without Reset State

 


TFO: $(y_1=0, y_2=1)$

No Reset State Example: Test Exists

- No reset state. Start w/ Fault excitation state: $y_1 = 0, y_2 = 1$.
- $x = 1$ propagates the fault effect!
- Problem: How to get to the fault excitation state?
- Answer: Sequential backtrack! Unroll the m/c backwards until you can get unknown values in FFs. This implies there exists a state (backward in time from F.E. state) where you can “control” the FFs (control the state).
- Called Self-Initializing tests! This test implies that both faulty and fault-free machines can be initialized to a “common initial state”; i.e., you can get a common starting point.

ATPG without Reset State

Go back.

 

ATPG without Reset State

