

Final Exam.
with Solutions

Name _____
Please Print

UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

MICROWAVE ENGINEERING I

ECE 5320/6322

FINAL EXAMINATION

December 15, 2014

1. (30 points)

Calculate the unloaded Q of a short-circuited microstripline resonator of length $\ell = \lambda_g / 4$ and characteristic impedance $Z'_0 = 30$ ohms at 5000 MHz. For this circuit:

Pts

- 10 a. Calculate the physical length ℓ assuming a substrate of dielectric constant $\epsilon_r = 2.5$ and thickness $1/16"$.
- 15 b. Calculate the unloaded Q at the resonant frequency of 5000 MHz assuming copper as the material for the microstrip and the loss tangent for the dielectric substrate $\tan \delta = 0.001$.
- 5 c. Without calculating individual R, L, and C values, draw the equivalent circuit of this resonator.

1. b. The equations for RLC eqt. of this short-circuited $l = \lambda_g/4$ resonator are given as Eqs. 6.30a, 6.30b and 6.30c, respectively

$$R = \frac{Z_0}{\alpha l} \quad (6.30a) ; \quad C = \frac{\pi}{4w_0 Z_0} \quad (6.30b) \quad \text{and}$$

$$L = \frac{1}{w_0^2 C} \quad (6.30c)$$

$$\text{Furthermore } Q_0 = \frac{\beta}{2\alpha} \quad (6.31)$$

From Eqs. 3.195 - 3.199 of the Text, we need to calculate the parameters for a $Z_0 = 30$ ohm microstrip line printed on a $\epsilon_r = 2.5$ substrate of thickness $d = 1/16$

For this line $\alpha = 0.6614$

$$A = \frac{Z_0}{60} \sqrt{\frac{3.5}{2}} + \frac{1.5}{3.5} \left(\frac{0.23 + 0.11}{2.5} \right) = 0.779$$

Since A is less than 1.52, the second part of Eq. 3.197 should be used. Hence we should also calculate B

$$B = \frac{377\pi}{2Z_0\sqrt{\epsilon_r}} = \frac{377\pi}{2 \times 30 \sqrt{2.5}} = 12.484$$

$$\frac{W}{d} = \frac{2}{\pi} \left[11.484 - \underbrace{\ln \left(\frac{23.968}{3.177} \right)}_{5.727} + \frac{1.5}{5} \underbrace{\left\{ \frac{\ln(11.484)}{2.441} + \frac{0.39 - 0.61}{2.5} \right\}}_{0.6885} \right]^{0.146}$$

From Eq. 3.195

$$\epsilon_e = \frac{3.5}{2} + \frac{1.5}{2} \frac{1}{\sqrt{1 + \frac{12}{5.727}}} = \boxed{2.176}$$

$$\beta = \frac{2\pi}{\lambda_g} = \frac{2\pi\sqrt{\epsilon_e}}{\lambda_0} = \frac{2\pi}{6} \sqrt{\epsilon_e} = \frac{2\pi}{4.067 \times 10^{-2}} = 154.49 \text{ m}^{-1}$$

$$\lambda_g = \frac{\lambda_0}{\sqrt{\epsilon_e}} = \frac{6}{\sqrt{2.176}} = 4.067 \times 10^{-2} \text{ m} = 4.067 \text{ cm}$$

Converting 1.6 dB/m into nepers/m, we can write

$$\alpha = \frac{1.6}{8.686} = 0.1842 \text{ nepers/m}$$

From Eq. 6.31

$$Q_0 = \frac{\beta}{2\alpha} = \frac{154.49}{2 \times 0.1842} = \boxed{419.34}$$

(C) EQVT Ckt.



2. (30 points)

The S-matrix of a three-port circuit measured with a $Z_o = 50$ ohm measurement system is given as follows:


$$S = \begin{bmatrix} 0.2 & 0.2 & 0.5 \\ 0.6 & 0.3 & 0.5 \\ 0.4 & 0.5 & -0.4 \end{bmatrix}$$

Pts

- 10 a. Draw the flow graph for the above circuit.
- 15 b. Calculate the reflection coefficient at port 2 if port 3 is connected to a mismatched load with a reflection coefficient of 0.5 and port 1 is terminated (connected to a matched load).
- 5 c. Calculate the input impedance (magnitude and phase) of the circuit at port 2 when ports 1 and 2 are connected as given in part b.

Hint: Do not draw any branches with value zero.

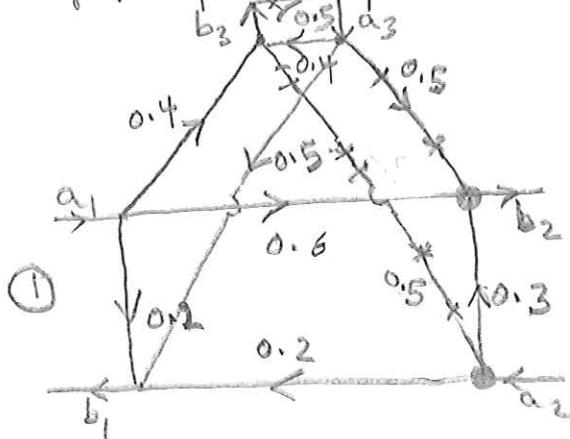2. a. The flow graph of the 3-port circuit is sketched below



b. Paths between a_2 and b_2

Note that the only loop in this circuit is at port ③

<u>P₁</u>	<u>Value</u>	First order non-touching loops L(1)	Second order non-touching loops L(2)
----------------------	--------------	-------------------------------------	--------------------------------------

$$P_1 = 0.3 \quad (0.5)(-0.4) = -0.20$$

$$P_2^{(1)} = 0.5 \times 0.5 \times 0.5$$

$$P_2 = \frac{b_2}{a_2} = \frac{0.3 [1 + 0.2] + 0.5 \times 0.5 \times 0.5 [1 - 0]}{[1 + 0.2]}$$

$$= 0.3 + \frac{0.125}{1.2} = 0.4042$$

$$c. P_2 = \frac{Z_2 - 50}{Z_2 + 50} = 0.4042$$

$$\frac{1+|P_2|}{1-|P_2|} \rightarrow Z_2 = Z_0 \frac{1+0.4042}{1-0.4042} = 50 \times 2.3576 = 117.84 \Omega$$

zero phase

3. (25 points)

Pts

- 10 a. Design a full π -section m-derived low-pass filter with the following specifications:
 $R_o = 60 \Omega$, $f_c = 5.0$ GHz, $f_\infty = 6.0$ GHz.
- 8 b. Calculate the values of series inductance and shunt elements to use for this full π -section m-derived low-pass filter.
- 7 c. Calculate the image impedance Z_π of the filter at 3.0 and 4.0 GHz, respectively.

4. a. From Chapter 3 Notes (also Eq. 3.86 of the Text)

$$Z_{TE} = \frac{\omega \mu}{\beta} = \frac{377}{\sqrt{1 - \left(\frac{f_c^2}{f^2}\right)}} = 480$$

$$1 - \left(\frac{f_c}{f}\right)^2 = \left(\frac{377}{480}\right)^2 = 0.6169$$

$$\frac{f_c}{f} = \sqrt{1 - 0.6169} = 0.619$$

$$f_c = (15 \times 0.619) = 9.284 \text{ GHz}$$

$$b. f_c = \frac{C}{2a} = 9.284 \times 10^9$$

$$TE_{10} \quad a = \frac{30}{2 \times 9.284} = 1.6156 \text{ cm} \Rightarrow 0.636''$$

$$c. f_c|_{TE_{11}} = \frac{c}{2} \sqrt{\frac{1}{a^2} + \frac{1}{b^2}} = \frac{c}{2a} \sqrt{7.25} = \frac{15 \times 10^9}{2 \times 1.6156} \sqrt{7.25} \\ = 25 \text{ GHz}$$

$$f_c|_{TE_{12}} = \frac{c}{2a} \sqrt{1 + (2 \times 2.5)^2} = f_c|_{TE_{10}} \times \sqrt{26} = 47.34 \text{ GHz}$$

$$d. \gamma = \frac{Z_L - Z_{TE}}{Z_L + Z_{TE}} = \frac{480 - 480}{880} = -\frac{80}{880} = 0.091 \angle 180^\circ$$

e. For the dielectric filled waveguide

$$f'_c = \frac{c_e}{2a} = \frac{9.284}{\sqrt{2.5}} = 5.872 \text{ GHz}$$

$$Z_{TE}|_{\substack{\text{dielectric} \\ \text{filled WG}}} = \frac{n_e}{\sqrt{1 - \left(\frac{f'_c}{f}\right)^2}} = \frac{377/\sqrt{2.5} \cdot 238 \cdot 4375}{\sqrt{1 - \left(\frac{5.872}{15}\right)^2} \sqrt{0.84675}} = 259.1 \text{ Ohms}$$

4. (30 points)

The wave impedance of the TE_{10} mode of an air-filled rectangular waveguide at a frequency of 15 GHz is given to be 480 ohms.

Pts


- 5 a. Calculate the cutoff frequency for the TE_{10} mode of this waveguide.
- 4 b. Calculate the “a” dimension for the waveguide.
- 8 c. Calculate the cutoff frequencies for the TE_{11} and TE_{12} modes for this waveguide given that $b = 0.4 a$.
- 5 d. **Without using the Smith chart**, calculate the reflection coefficient Γ (**magnitude and phase**) in the air-filled waveguide if it is connected to a load of effective impedance $Z_L = 400$ ohms.
- 8 e. Calculate the wave impedance at the signal frequency of 15 GHz for the TE_{10} mode if the above waveguide is filled with a dielectric with $\epsilon_r = 2.5$. Note that the cutoff frequency for the TE_{10} mode of a dielectric-filled waveguide is lower than that for an air-filled waveguide.

3. From Eq. 8.44 of the Text

$$f_{\text{oo}} = \frac{f_c}{\sqrt{1-m^2}}$$

For this filter $1-m^2 = \left(\frac{f_c}{f_{\text{oo}}}\right)^2 \Rightarrow m = \sqrt{1-\left(\frac{5}{6}\right)^2} = \sqrt{\frac{11}{36}} = 0.553$

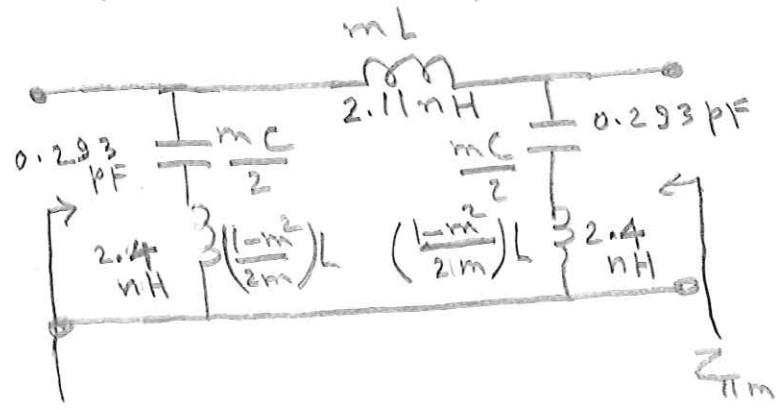The sketch of a full π -section from Table 8.2 of the Text



the derived filter can be written

From Ex. 8.2 of the Text

$$L = \frac{2R_o}{w_c} = \frac{60}{\pi \times 5 \times 18} = 3.82 \text{ nH}$$

$$C = \frac{2}{R_o w_c} = \frac{2}{60 \times 2\pi \times 5 \times 18} = \frac{1000}{360\pi} = 1.061 \text{ pF}$$

$$\frac{mC}{2} = 0.293 \text{ pF}$$

$$\frac{(1-m^2)}{2m} L = \frac{0.594}{2 \times 0.553} \times 3.82 = 2.398 \approx 2.4 \text{ nH}$$

From Eq. (8.46) of the Text

$$Z_{i\pi} = R_o \frac{1 - \left(\frac{f}{f_c}\right)^2}{\sqrt{1 - \left(\frac{f^2}{f_c^2}\right)}}$$

@ 3 GHz $Z_{i\pi} = 60 \frac{1 - \left(\frac{3}{6}\right)^2}{\sqrt{1 - \left(\frac{3}{6}\right)^2}} = 60 \frac{0.75}{0.8} = 56.25 \text{ Ohms}$

@ 4 GHz $Z_{i\pi} = 60 \frac{1 - \left(\frac{4}{6}\right)^2}{\sqrt{1 - \left(\frac{4}{6}\right)^2}} = 60 \frac{0.36}{0.6} = 55.56 \text{ Ohms}$

ECE 5320/6322
Final Examination
December 15, 2014

Name _____

Score:

Problem 1 _____ of a possible 30 points

Problem 2 _____ of a possible 30 points

Problem 3 _____ of a possible 25 points

Problem 4 _____ of a possible 30 points

Total _____ of a possible 115 points