

Additional Pages of Notes for Chapter 7


T-Junction Unequal Power Dividers

See also Ex. 7.1 of the Text

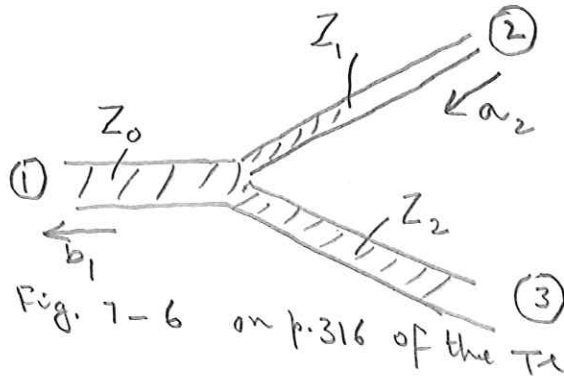Question:

Can we show that the reciprocity of S-parameters ($S_{ij} = S_{ji}$) holds even though the circuit of Fig. 7.6 for a lossless, but not symmetric, power divider T-junction is not symmetric with respect to parts 1, 2, 3.

Proof: The T-junction of Fig. 7.6 of the Text p. 316 is shown below.



For this circuit let us mark parts ①, ②, ③ as shown here. For Example 7.1 we can match only port ① with $Z_0 = 50 \Omega$ provided we use $Z_1 = 3Z_0 = 150 \Omega$ and $Z_2 = \frac{3Z_0}{2} = 75 \Omega$ and this circuit results in a lossless 2:1 ratio power divider with power input P_{in} at port ① resulting in $\frac{1}{3} P_{in}$ power output from port ② and $\frac{2}{3} P_{in}$ power output from port ③. We can write the S-matrix for this circuit as follows:

$$[S] = \begin{bmatrix} 0 & \frac{1}{\sqrt{3}} & \sqrt{\frac{2}{3}} \\ \frac{1}{\sqrt{3}} & -2/3 & \sqrt{2/3} \\ \sqrt{\frac{2}{3}} & \sqrt{2/3} & -1/3 \end{bmatrix} \quad (1)$$

In writing Eq. (1) I have used the power divisions $|S_{21}|^2 = 1/3$; $|S_{31}|^2 = 2/3$, $\Gamma_2 = S_{22} = -2/3$; $\Gamma_3 = S_{33} = -1/3$ derived on p. 317 of the Text.

I have also used $S_{21} = S_{12} = \frac{1}{\sqrt{3}}$, $S_{31} = S_{13} = \sqrt{2/3}$ and the lossless circuit properties

1. Sum of the squares of S-parameters in any column = 1
2. Sum of the S-parameters in any column multiplied by the conjugate of the

Corresponding S-parameters in any other column = 0

7-1-2

In the following I would show as an example that $S_{21} = S_{12} = \frac{1}{\sqrt{3}}$ even though parts ① and ② use different characteristic impedances $Z_0 = 50 \Omega$, $Z_1 = 150 \Omega$ and are not symmetrical.

Note that from Eq. (1) we can write

$$(2) \quad b_1 = \frac{1}{\sqrt{3}} a_2 \quad \text{when power is input to part ② and all port ③ is terminated i.e. } a_3 = 0$$

$$\text{From Eq. (2) we can write } S_{12} = \left. \frac{b_1}{a_2} \right|_{a_3=0} = \frac{1}{\sqrt{3}}$$

Is this true?

For signal a_2 into port ②, the load is presented by a parallel combination of Z_0 and Z_2 i.e. $50 \Omega \parallel 75 \Omega$ which is a load impedance of 37.5Ω . This gives a reflective coefficient $S_{22} = -2/3$ as derived in the text.

Power delivered to the effective load of 37.5Ω i.e. $50 \Omega \parallel 75 \Omega$ is $a_2 a_2^* - b_2 b_2^* = a_2 a_2^* (1 - |S_{22}|^2) = \frac{5}{9} a_2 a_2^*$

This power delivered to the junction is split two ways

$$\text{out of port ①} \quad b_1 b_1^* = \left(\frac{75}{50+75} \right) \times \left(\frac{5}{9} a_2 a_2^* \right) = \frac{a_2 a_2^*}{3}$$

$$\text{This gives } |S_{12}| = \left| \frac{b_1}{a_2} \right| = \frac{1}{\sqrt{3}}$$

$$\text{out of port ③} \quad b_3 b_3^* = \left(\frac{50}{50+75} \right) \times \left(\frac{5}{9} a_2 a_2^* \right) = \frac{2}{9} a_2 a_2^*$$

$$\text{This gives } |S_{32}| = \left| \frac{b_3}{a_2} \right| = \frac{\sqrt{2}}{3}$$

Both of these terms were used in writing Eq. (1) for the S-matrix.