


2 additional pages of
Notes on Chapter 4

Ex.1 For a two-part circuit, calculate (See also Ex. 4.5 Text p.179)

a. the reflection coefficient Γ_1 at port ① if port ② is connected to a mismatched load of reflection Γ_L

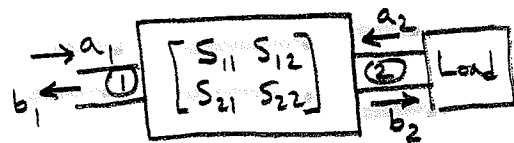b. the power delivered to this mismatched load in terms of input power a_1, a_1^*

Solution a. The circuit diagram is given in Fig.1



$$b_1 = S_{11} a_1 + S_{12} a_2 \quad (1)$$

$$b_2 = S_{21} a_1 + S_{22} a_2 \quad (2)$$

For the mismatched load of reflection Γ_L , note that $a_2 = \Gamma_L b_2$ (3)

Eq. (3) can be rewritten as $b_2 = \frac{a_2}{\Gamma_L}$ (4)

Substituting Eq. (4) into Eq. (2) and rearranging terms

$$S_{21} a_1 = \left(\frac{1}{\Gamma_L} - S_{22} \right) a_2 = \left(\frac{1 - S_{22} \Gamma_L}{\Gamma_L} \right) a_2 \quad (5)$$

Substitute Eq. (5) into Eq. (1), we can write

$$\Gamma_1 = \frac{b_1}{a_1} = \left[S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right] \quad (6)$$

b. Power delivered to the mismatched load = $b_2 b_2^* - a_2 a_2^* = b_2 b_2^* (1 - |\Gamma_L|^2)$ (7)

Expressing Eq. (2) in terms of a_1 , we can write (by using Eq. (5))

$$b_2 = \left[S_{21} + \frac{S_{22} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right] a_1 = \left[\frac{S_{21}}{1 - S_{22} \Gamma_L} \right] a_1 \quad (8)$$

Combining Eqs. (7) and (8), we can write

$$\frac{\text{Power delivered to the mismatched load}}{\text{Power input } a_1, a_1^*} = \left| \frac{S_{21}}{1 - S_{22} \Gamma_L} \right|^2 (1 - |\Gamma_L|^2) \quad (9)$$

Ex.2 Calculate the quantities a. and b. in Ex.1 for a circuit for which the S-parameters are $\begin{bmatrix} 0.1 & 0.8j \\ 0.8j & 0.2 \end{bmatrix}$ and $\Gamma_L = 0.333$

Solution a. From Eq. (6), $\frac{b_1}{a_1} = \Gamma_1 = \left[S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right] = -0.1285$


Return loss $RL = 20 \log \left| \frac{b_1}{a_1} \right| = 17.82 \text{ dB}$

b. From Eq. (9), $\frac{\text{power delivered to the load}}{\text{input power } a_1, a_1^*} = 0.654$

i.e. 65.4% of the input power can be delivered to this mismatched load

c. For a perfectly matched load connected to the output port ②, $\Gamma_L = 0$ and $\frac{\text{power delivered to this perfectly matched load}}{\text{input power}} = |S_{21}|^2 = (0.8)^2 = 0.64$

Similar to
Prob. 4.17
p. 218 Text

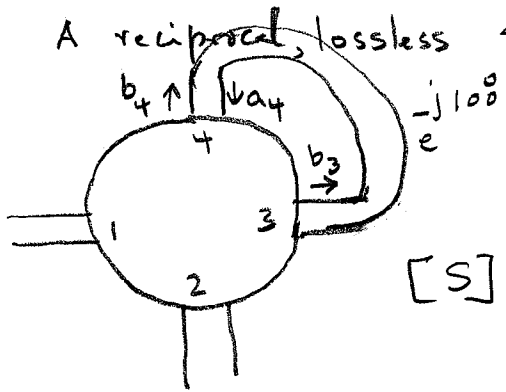


A reciprocal, lossless 4-port network

$$a_4 = b_3 e^{-j100^\circ}$$

$$a_3 = b_4 e^{j100^\circ}$$

$$[S] = \begin{bmatrix} 0.6 \angle 90^\circ & 0 & 0 & 0.8 \angle 0^\circ \\ 0 & 0.7 \angle 45^\circ & 0.7 \angle -45^\circ & 0 \\ 0 & 0.7 \angle -45^\circ & 0.7 \angle 45^\circ & 0 \\ 0.8 \angle 0^\circ & 0 & 0 & 0.6 \angle 90^\circ \end{bmatrix}$$

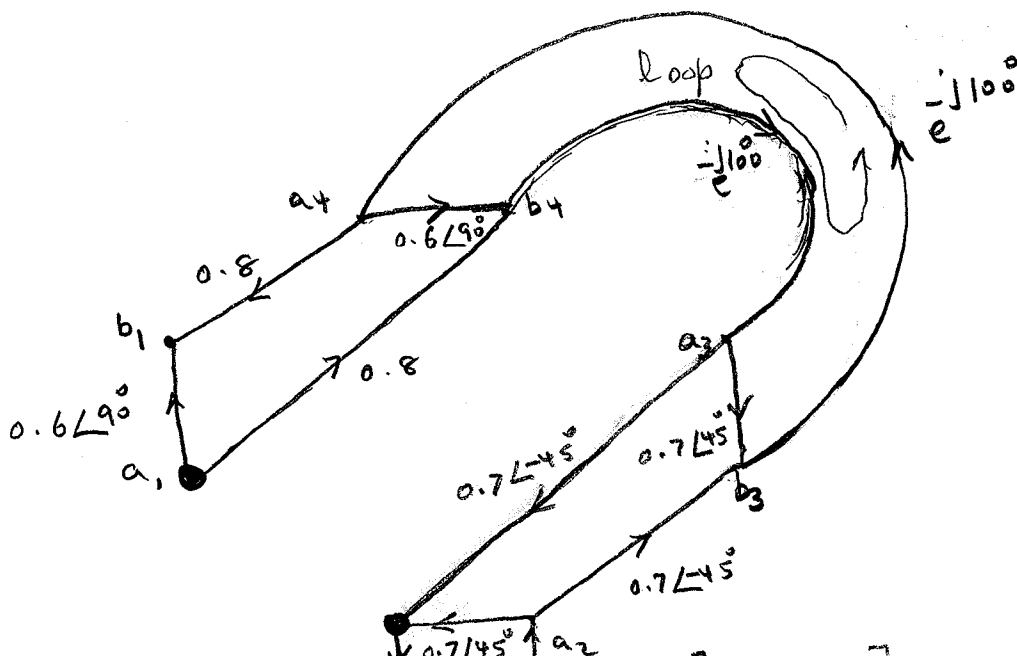Note that parts 3 and 4 are connected with a lossless matched transmission line of electrical length 100



$$\frac{b_2}{a_1} = \frac{\text{path } P_1 = 0.8 \times e^{j100^\circ} \times 0.7 e^{-j45^\circ} [1 - 0]}{1 - \left[(0.6 e^{j90^\circ}) (e^{-j100^\circ}) (0.7 e^{j45^\circ}) (e^{-j100^\circ}) \right]}$$

$$= \frac{0.56 e^{j145^\circ}}{1 - 0.42 e^{-j65^\circ}}$$

$$\frac{b_2 b_2^*}{a_1 a_1^*} = \frac{(0.56)^2}{(1 - 0.42 e^{-j65^\circ})(1 - 0.42 e^{j65^\circ})} = \frac{(0.56)^2}{1 + (0.42)^2 - 2 \times 0.42 \cos 65^\circ}$$

$$= \boxed{0.4648}$$

$$IL = -10 \log(0.4648) = -3.33 \text{ dB}$$