

Chapter 6

Notes

# Chapter 6

## A series resonant circuit

## A parallel resonant ckt (6-1)

$f_0 = 3 \text{ GHz}$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$LC = \frac{1}{4\pi^2 f_0^2} = \frac{1}{4\pi^2 \times 9 \times 10^{18}}$$

say  $C = 1 \text{ pF}$

$$L = 2.81 \text{ nH}$$

$f_0 = \frac{1}{2\pi\sqrt{LC}}$

$= 2.81 \times 10^{-21}$

$Q = 1000$

$Q = 1000$

$$Q = \frac{\omega_0 L}{R_s} \quad (6.8)$$

$$R_s = \frac{(2\pi \times 10^9 \times 3) \times 2.81 \times 10^{-9}}{1000}$$





$$= 0.053 \Omega$$

$R_p = Q \quad (6.18)$

$$R_p = \frac{R_s}{\omega_0^2 L^2} = 2\pi \times 3 \times 10^9 \times 2.81 \times 10^{-9} \times 10^3$$

$$= 52.97 \text{ k}\Omega$$

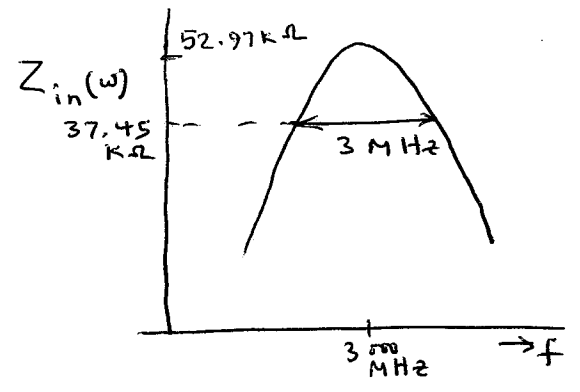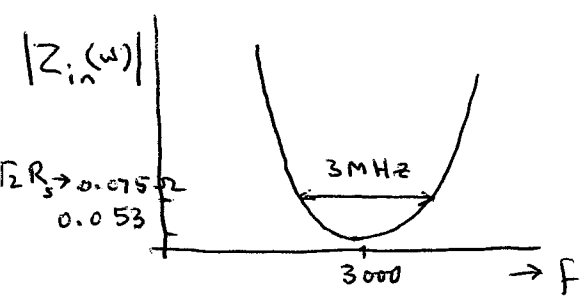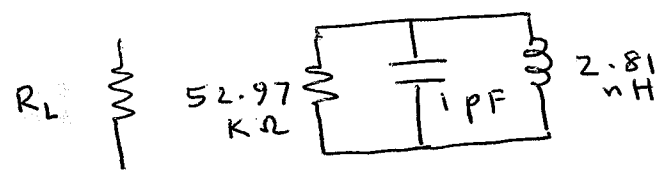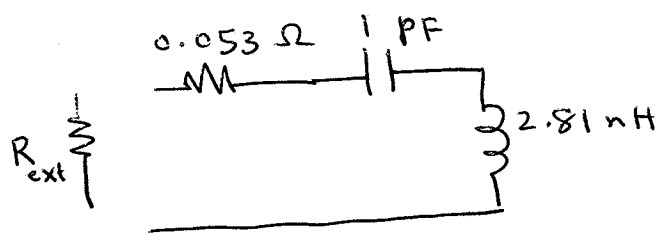$BW = \frac{f_0}{Q} = \frac{3000}{1000} = 3 \text{ MHz}$



$$Q_L = \frac{\omega L}{R_{int} + R_{ext}}$$

For  $R_L = 100 \text{ k}\Omega$

$$\frac{R_L}{\omega_0 L} = Q_e = 1888$$

$$Q_L = \frac{Q_e Q}{Q + Q_e} = \frac{1888 \times 1000}{2888} = 653.74$$

$$\frac{1}{Q_L} = \frac{1}{Q_e} + \frac{1}{Q_{un}} \quad (6.23)$$

p. 275 Ex. A Quarter Wave Microstrip Resonator made of a short circuited line (6-2)  
(6-2)

$$R = \frac{Z_0}{\alpha l} \quad (6.30a) \quad L = \frac{1}{\omega_0^2 C}$$

$$C = \frac{\pi}{4 \omega_0 Z_0} \quad (6.30b)$$



A parallel resonator

$$Q = \frac{\pi}{4 \alpha l} \quad (6.31)$$

parallel type resonator

$$l = \lambda_g / 4$$

from pp. 144, 145

For  $Z_0' = 100 \Omega$

$$A = 2.123 > 1.52$$

$$\frac{W}{d} = 0.896$$

$$\epsilon_r = 2.3$$

$$f = 3 \text{ GHz}$$

$$\tan \delta = 10^{-3}$$

$$d = \frac{1}{32} = 0.793 \text{ mm}$$

$$W = 0.711 \text{ mm}$$

$$(3.195) \quad \epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \frac{1}{\sqrt{1 + 12 \frac{d}{W}}} = 1.82$$

$$\lambda_g = \frac{\lambda_0}{\sqrt{\epsilon_e}} = \frac{10}{\sqrt{1.82}} = 7.41 \text{ cm}$$

$$l = \lambda_g / 4 = 1.852 \text{ cm}$$

$$(3.198) \quad \alpha_d = \frac{k_0 \epsilon_r (\epsilon_e - 1) \tan \delta}{2 \sqrt{\epsilon_e} (\epsilon_r - 1)} = \frac{2\pi \times 2.3 \times 0.82 \times 10^{-3}}{10^{-2} \times 2 \sqrt{1.82} \times 1.3} = 3.38 \times 10^{-2} \text{ Np/m}$$

$$(3.199) \quad \alpha_c = \frac{R_s}{Z_0 W} = \frac{1.988 \sqrt{\frac{f \text{ MHz}}{5.817 \times 10^9}} \times \frac{1}{100 \times 0.711 \times 10^{-3}}}{\sigma_{Cu}} = 20.08 \times 10^{-2} \text{ Np/m}$$

$$\alpha_T = \alpha_c + \alpha_d = 23.46 \times 10^{-2} = 0.2346 \text{ Np/m}$$


$$R = \frac{Z_0}{\alpha l} = \frac{100}{0.2346 \times 1.852 \times 10^{-2}} = 2.3 \times 10^4 = 23 \text{ k}\Omega$$

$$C = \frac{\pi}{4 \omega_0 Z_0} = \frac{\pi}{4 \times 3 \times 10^9 \times 100} = 2.62 \text{ pF}$$


$$L = \frac{1}{\omega_0^2 C} = \frac{1}{4\pi^2 \times 10^{18} \times 2.62 \times 10^{-12}} = 1.074 \text{ nH}$$

$$Q_{\text{unloaded}} = \frac{\pi}{4 \times \alpha l} = \frac{\pi}{4 \times 0.2346 \times 1.852 \times 10^{-2}} = 180.8$$

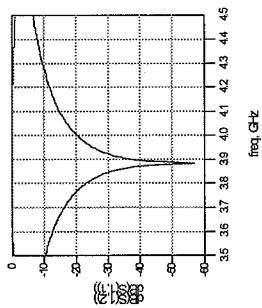
Compare this to a Q of 526 calculated for a  $Z_0 = 50 \Omega$  on p. 1/2 microstrip resonator



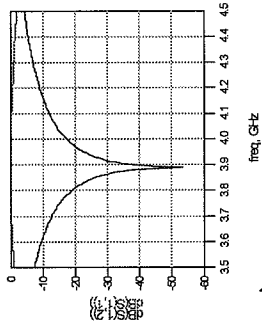
Zo\_stub = 50 ohm  
 W = 91.048 mil  
 L = 525.039 mil



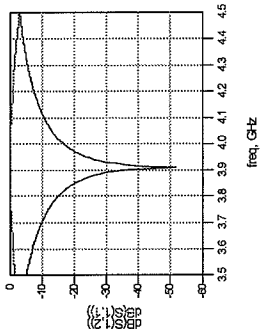
Zo\_stub = 75 ohm  
 W = 46.084 mil  
 L = 536.606 mil



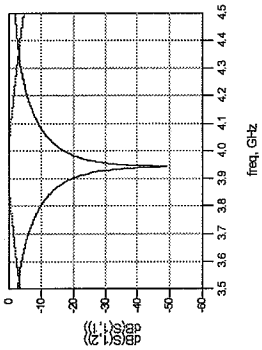Zo\_stub = 100 ohm  
 W = 25.260 mil  
 L = 545.283 mil



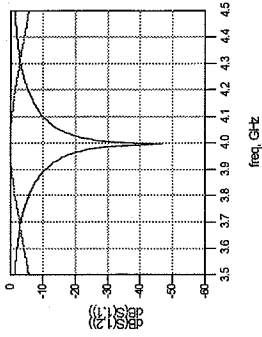Zo\_stub = 150 ohm  
 W = 7.771 mil  
 L = 557.087 mil



Zo\_stub = 200 ohm  
 W = 2.101 mil  
 L = 566.783 mil

Broader scan from 3.5 - 4.5 GHz

Zoom scan from 3.80 to 4.00 GHz

$\lambda_g/4$

Note that the resonance frequency is lower as broader (lower impedance) stubs are used.


S PARAMETERS

S\_Param  
 SP1  
 Start=3.5 GHz  
 Stop=4.5 GHz  
 Step=0.005 GHz

MSub

MSub  
 MSUB  
 MSub1  
 H=31 mil  
 E1=2.33  
 Mu\_r=1  
 Cond=1.0E+50  
 Hu=3.9e+034 mil  
 T=.7 mil  
 TanD=0.001  
 Rough=0 mil

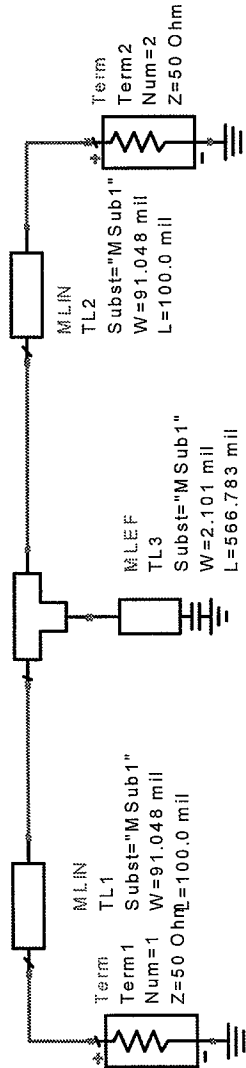MTEE  
 Tee1  
 Subst="MSub1"  
 W1=91.048 mil  
 W2=91.048 mil  
 W3=2.101 mil



p. 292 Excitation of Resonators

For  $R_{L \rightarrow ext} = R_{int}$

$Q_{ext} = Q_{unloaded}$

Critically coupled

We can define (6.76)

$g = \frac{Q_u}{Q_e} = \frac{R_{int}}{R_{ext}}$

for a parallel resonator

$= \frac{R_{ext}}{R_{int}}$  for a series resonator

for a parallel resonator

$g < 1$

under coupled

$Q_u < Q_{ext}$

$R_{int} < R_{ext}$

$g = 1$

critically coupled

$Q_u = Q_{ext}$

$R_{int} = R_{ext}$

$g > 1$

over coupled

$Q_u > Q_{ext}$


$R_{int} > R_{ext}$

p. 292

For a gap coupled microstrip resonator

$$\zeta = \frac{Z}{Z_0} = -j \frac{\left[ \frac{1}{\omega C} + Z_0 \cot \beta l \right]}{Z_0}$$
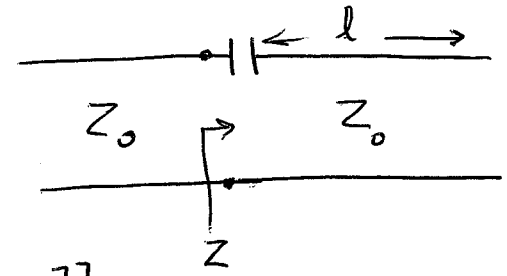
$$= -j \left( \frac{\tan \beta l + b_c}{b_c \tan \beta l} \right) \quad (6.77)$$



$b_c = Z_0 \omega C$  is the normalized susceptance of the coupling capacitor C

Resonance occurs for  $\zeta = 0$  or when


$\tan \beta l + \omega C Z_0 = \tan \beta l + b_c = 0 \quad (6.78)$


At resonance

$$R = \frac{Z_0 \pi}{2Q b_c^2}$$

For critical coupling  $R_{se} = Z_0$

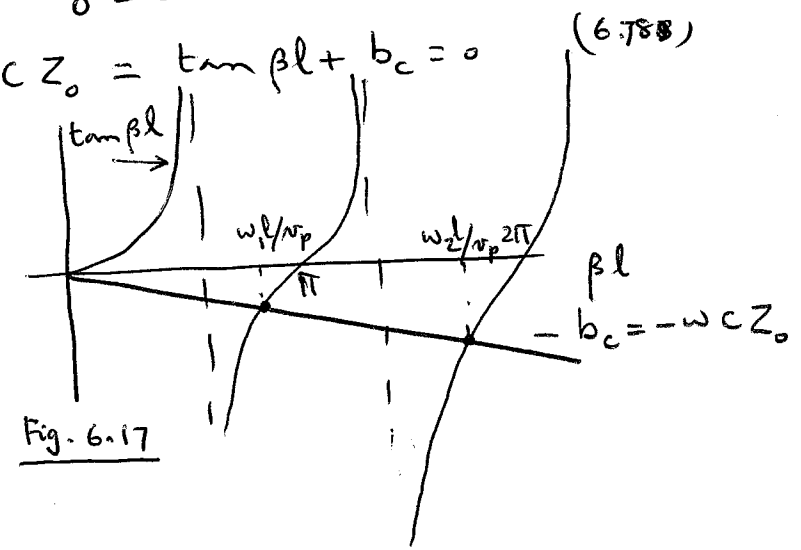or  $b_c = \omega C Z_0 = \sqrt{\frac{\pi}{2Q}}$



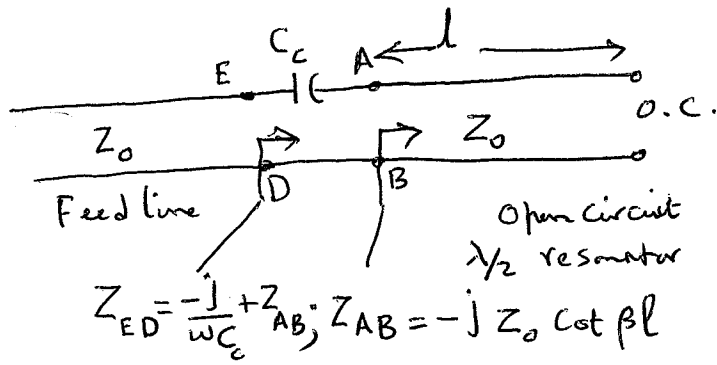


$$Z_{ED} = -j \frac{1}{\omega C_c} + Z_{AB}; \quad Z_{AB} = -j Z_0 \cot \beta l$$

$$\beta = \frac{Z_{ED}}{Z_0} = -\frac{j}{\omega C_c Z_0} - j \cot \beta l = -j \left( \frac{\tan \beta l + b_c}{b_c \tan \beta l} \right) \quad (6.77)$$

where  $b_c = \omega C_c Z_0$  is the normalized susceptance of the coupling capacitor  $C_c$

The coupling capacitor acts as an impedance inverter and converts the <sup>equivalent</sup> parallel resonant circuit between terminals A B to a series resonant circuit as sketched below

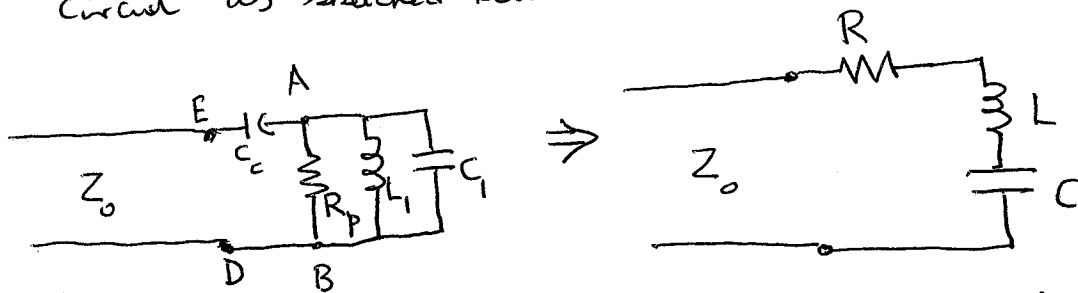

Eq. 6.81 is similar to the expression (6.9) for a series resonant circuit.

From Eq. 6.81

$$\beta(\omega) = \frac{\pi}{2Q b_c^2} + j \frac{\pi \Delta \omega}{\omega_1 b_c^2} \text{ of the form } \frac{R}{Z_0} + j \frac{2L \Delta \omega}{Z_0} \quad (6.9)$$

For ~~critically coupled~~ <sup>critically coupled</sup> resonator

$$g = \frac{R}{Z_0} = 1 = \frac{\pi}{2Q b_c^2}$$

This gives  $b_c = \omega C_c Z_0 = \sqrt{\frac{\pi}{2Q}} \quad (6.82)$

$$g = \frac{R_{ext}}{R_{int}} = \frac{Z_0}{R} = \frac{2Q b_c^2}{\pi} \quad (6.83)$$

For the new Eqn cut

$$\frac{R}{Z_0} = \frac{\pi}{2Q b_c^2} \Rightarrow R = \frac{\pi Z_0}{2Q b_c^2}$$

$$\frac{2L}{Z_0} = \frac{\pi}{\omega_1 b_c^2} \Rightarrow L = \frac{\pi Z_0}{2 \omega_1 b_c^2}$$

$$\omega_1 = \sqrt{\frac{1}{LC}} \Rightarrow C = \frac{1}{\omega_1^2 L}$$

The new resonant frequency  $\omega_1$  is obtained from the transcendental Eq.

$$\tan \left( \frac{\omega l}{v_p} \right) + b_c = \tan \left( \frac{\omega l}{v_p} \right) + \omega C_c Z_0 = 0 \quad (6.78)$$