

Notes on chapter 7

Chapter 7


A 3-port, lossless, reciprocal network such as a T-junction (7-1)

Cannot be matched at all ports

Say it can be matched at port 1; $S_{11} = 0$

Note that ports 2 and 3 are symmetrical
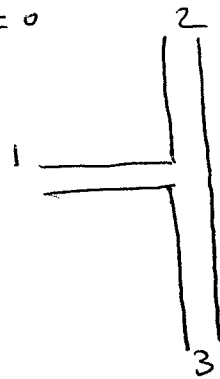
$$[S] = \begin{bmatrix} 0 & 1/\sqrt{2} & 1/\sqrt{2} \\ 1/\sqrt{2} & S_{22} & S_{23} \\ 1/\sqrt{2} & S_{23} & S_{22} \end{bmatrix} \quad (1)$$



From columns 2 or 3

$$\frac{1}{2} + |S_{22}|^2 + |S_{23}|^2 = 1 \quad (2)$$

$$\text{Therefore, } |S_{22}|^2 + |S_{23}|^2 = \frac{1}{2} \quad (3)$$

Also from columns 1, 2 or 1, 3

$$\frac{1}{\sqrt{2}} S_{22}^* + \frac{1}{\sqrt{2}} S_{23}^* = 0 \quad (4)$$

$$\text{Thus } S_{22} = -S_{23} \quad (5)$$

From (3) and (5)

$$2|S_{22}|^2 = 2|S_{23}|^2 = \frac{1}{2}$$

$$|S_{22}| = \frac{1}{2} = |S_{23}|$$

$$\text{From Eq. (5) } S_{22} = \frac{1}{2} ; S_{23} = -\frac{1}{2}$$


$$[S] = \begin{bmatrix} 0 & 1/\sqrt{2} & 1/\sqrt{2} \\ 1/\sqrt{2} & 1/2 & -1/2 \\ 1/\sqrt{2} & -1/2 & 1/2 \end{bmatrix}$$

This matrix all of the conditions for a lossless, reciprocal network.

A Four-port Circuit (Lossless, reciprocal ckt.)

(7-2)

p. 312

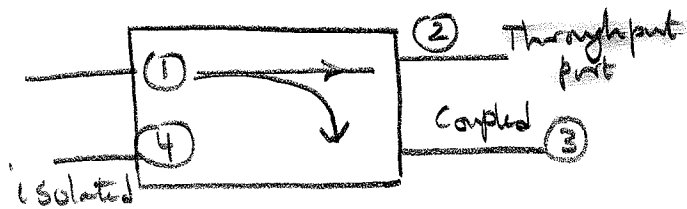

$$[S] = \begin{bmatrix} 0 & \alpha & S_{13} & 0 \\ \alpha & 0 & 0 & S_{24} \\ S_{13} & 0 & 0 & \alpha \\ 0 & S_{24} & \alpha & 0 \end{bmatrix}$$

$$S_{41} = S_{32} = 0$$

$$S_{21} = S_{34} = \alpha$$

Two possibilities

$$1. S_{31} = S_{42} = j\beta$$

$$2. S_{42} = -S_{31} = -\beta$$

$$[S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$

Symmetrical coupler

90° phase shift for outputs at ports 2 and 3

$$\alpha^2 + \beta^2 = 1 \quad (7.19)$$

For a lossless network

$$[S] = \begin{bmatrix} 0 & \alpha & -\beta & 0 \\ \alpha & 0 & 0 & \beta \\ -\beta & 0 & 0 & \alpha \\ 0 & \beta & \alpha & 0 \end{bmatrix}$$

Antisymmetric coupler

180° phase shifts for output ports 2 and 3

$$C = 0.1 \rightarrow 20 \text{ dB coupler}$$

$$0.0316 \rightarrow 30 \text{ dB coupler}$$

$$\text{Coupling } C = 10 \log \left(\frac{P_1}{P_3} \right) = -20 \log \beta \quad \text{dB} \quad (7.20a)$$

$$\text{Directivity } D = 10 \log \left(\frac{P_3}{P_4} \right) = 20 \log \frac{\beta}{|S_{14}|} \quad \text{dB} \quad (7.20b)$$

$$\text{Isolation } I = 10 \log \left(\frac{P_1}{P_4} \right) = -20 \log |S_{14}| = C + D \quad (7.20c)$$

p. 313



For $\beta = \alpha = \frac{1}{\sqrt{2}}$ — 3dB Hybrid (equal power divider)

90° hybrid — branch line coupler p. 333

180° hybrid — ring hybrid p. 353

Four port Directional couplers

(7-3)

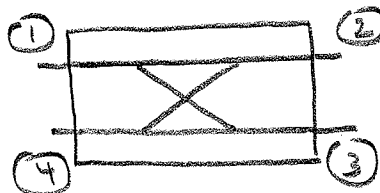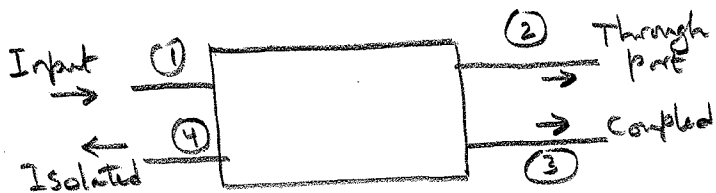

All ports can be matched

Note $S_{21} = S_{12}$ $S_{34} = S_{43}$

$S_{21} = S_{34}$, $S_{14} = S_{23}$

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix}$$

$$|S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2 = 1$$

$$S_{13} S_{23}^* + S_{14} S_{24}^* = 0$$

$$S_{12} S_{13}^* + S_{24} S_{34}^* = S_{13} S_{14}^* + S_{23} S_{24}^*$$

Possible solutions

1. $S_{14} = 0$; $S_{12} = \alpha$; $S_{13} = j\beta = S_{24}$

$$[S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$

Symmetric coupler

$S_{13} = S_{24}$ (both are imaginary)

$\alpha^2 + \beta^2 = 1$

(7.17)

p. 312

2. $S_{14} = 0$; $-S_{13} = S_{24}$

Anti symmetric coupler

$S_{24} = -S_{13}$ (both are real)

$$[S] = \begin{bmatrix} 0 & \alpha & -\beta & 0 \\ \alpha & 0 & 0 & \beta \\ -\beta & 0 & 0 & \alpha \\ 0 & \beta & \alpha & 0 \end{bmatrix}$$

$\alpha^2 + \beta^2 = 1$

(7.18)

p. 312

$IL = -20 \log |S_{12}|$

$RL = -20 \log |P|$

Eq. 2.38 $= -20 \log |S_{11}|$

$\frac{dB}{dB} = C + D$

1. Coupling $C = 10 \log_{10} \frac{P_1}{P_3} = -20 \log \beta$


3. Isolation $I = 10 \log_{10} \frac{P_1}{P_4} = -20 \log |S_{14}|$

2. Directivity $D = 10 \log_{10} \frac{P_3}{P_4} = -20 \log \frac{\beta}{|S_{14}|}$

pp. 562, 563
Text

Use of a branch line coupler for a balanced amplifier

See also p. 562 Text

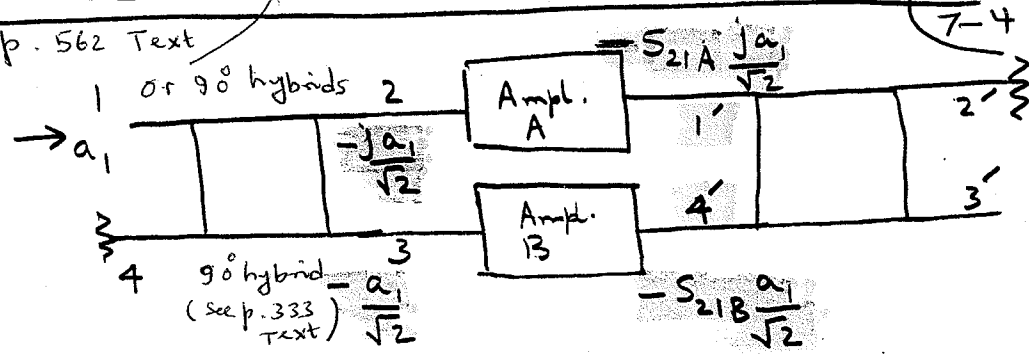

$$\begin{bmatrix} b_1' \\ b_2' \\ b_3' \\ b_4' \end{bmatrix} = -\frac{1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix} \begin{bmatrix} -S_{21A} j \frac{a_1}{\sqrt{2}} \\ 0 \\ 0 \\ -S_{21B} \frac{a_1}{\sqrt{2}} \end{bmatrix}$$

Eq. 7.61 p. 333


$$b_1' = b_4' = 0$$

see eqs. 11.62, 11.63, 11.64


$$b_2' = -\frac{1}{\sqrt{2}} \left\{ S_{21A} - S_{21B} \right\} \frac{a_1}{\sqrt{2}} \approx 0$$

$$b_3' = +\frac{j}{\sqrt{2}} \left\{ S_{21A} + S_{21B} \right\} \frac{a_1}{\sqrt{2}}$$

A chain of serial combiners or dividers

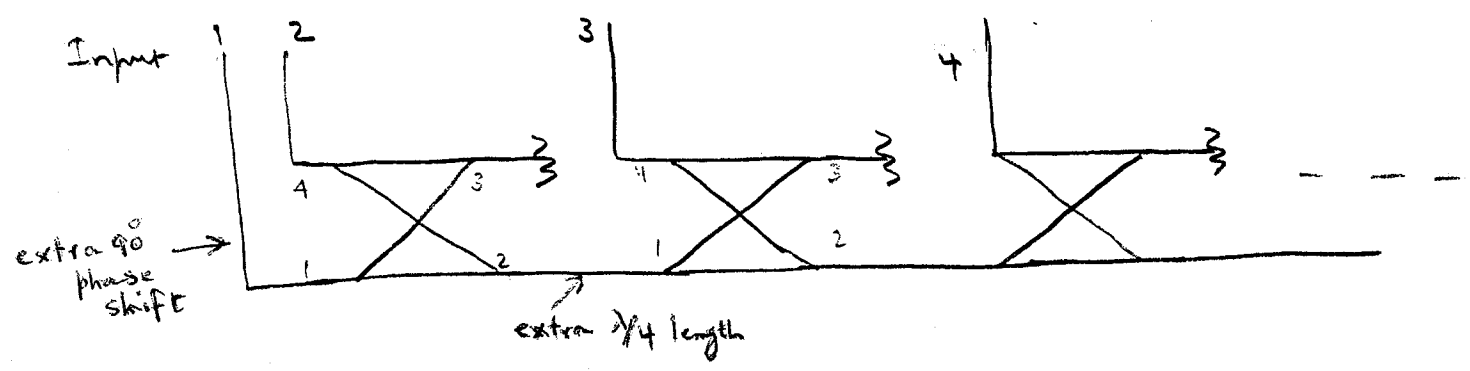

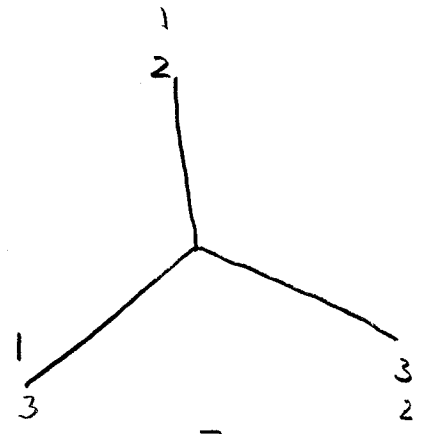S-parameters of a (angularly) Symmetric, Lossless, 3-part reciprocal Network
A Y-junction



$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{12} & S_{11} & S_{23} \\ S_{13} & S_{23} & S_{11} \end{bmatrix}$$

output \rightarrow $S_{12} = S_{31} = S_{13} = S_{23}$
input port \leftarrow

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{12} \\ S_{12} & S_{11} & S_{12} \\ S_{12} & S_{12} & S_{11} \end{bmatrix}$$

$$|S_{11}|^2 + 2|S_{12}|^2 = 1$$

$$S_{11} S_{12}^* + S_{12} S_{11}^* + |S_{12}|^2 = 0$$

$$2 S_{11} S_{12} + S_{12}^2 = 0 \Rightarrow S_{12} = -2 S_{11}$$

$$S_{11}^2 = 1$$

$$S_{11} = \pm \frac{1}{3}, \pm \frac{j}{3}$$

$$S_{12} = \mp \frac{2}{3}, \mp \frac{2j}{3}$$

Assuming that S_{11}, S_{12} are real

$$S = \begin{bmatrix} \frac{1}{3} & -\frac{2}{3} & \frac{2}{3} \\ -\frac{2}{3} & \frac{1}{3} & \frac{2}{3} \\ \frac{2}{3} & \frac{2}{3} & \frac{1}{3} \end{bmatrix}$$

$$e^{j\theta_1} = j^{1/2}, e^{j\theta_2} = j, e^{j\theta_3/2} = 1$$

Also possible

$$S = \begin{bmatrix} \frac{j}{3} & -\frac{2}{3}j & \frac{2}{3}j \\ -\frac{2}{3}j & \frac{1}{3}j & \frac{2}{3}j \\ \frac{2}{3}j & \frac{2}{3}j & \frac{j}{3} \end{bmatrix}$$

$$\theta_1 = \theta_2 = \theta_3 = 45^\circ$$

$$2j e^{j\theta_1} = j = e^{j(\theta_1 + \theta_2)}$$