

SAMPLE FINAL EXAM

Name _____

Please Print

UNIVERSITY OF UTAH

ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

MICROWAVE ENGINEERING I

ECE 5320

FINAL EXAM

December 13, 2004

1. a. $Z_L = \frac{Z_L}{Z_0} = 0.4 - j 0.4$ The normalized value of Z_L is shown as point L in the attached Smith chart.

Shown also in the Smith chart is the transmission line circle T for section A-B of the matching circuit of Fig. 1 of the Exam.

Also from the Smith chart we can determine y_L at point A as the diametrically opposite point on the transmission line circle T.

$$y_L \Big|_{\text{point A}} = 1.25 + j 1.25$$

From point A we can move to point B on the circle T such that for

$$y_B = 2.0 - j 1.3$$

$$\frac{l}{\lambda_g} \rightarrow \frac{\text{length } l \text{ between points A and B}}{\lambda_g} = 0.29 - 0.18j = 0.109$$

b. Add capacitance C

such that

$$j\omega C = +j \frac{1.3}{100}$$


$$C = \frac{1.3}{100 \times 2\pi \times 3 \times 10^9} = 0.69 \text{ pF}$$

$$Y_D = \frac{1}{50} - j \frac{1.3}{100} + j\omega C = \frac{1}{50} + j0$$

Thus the transmission line is matched for all planes left of point D in Fig. 1

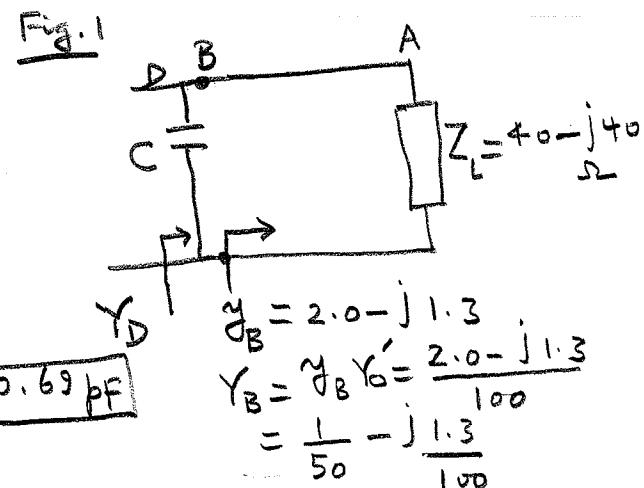
c. From the Smith chart

$$\text{SWR for section AB of the circuit} = 3.02$$



The Complete Smith Chart

Black Magic Design

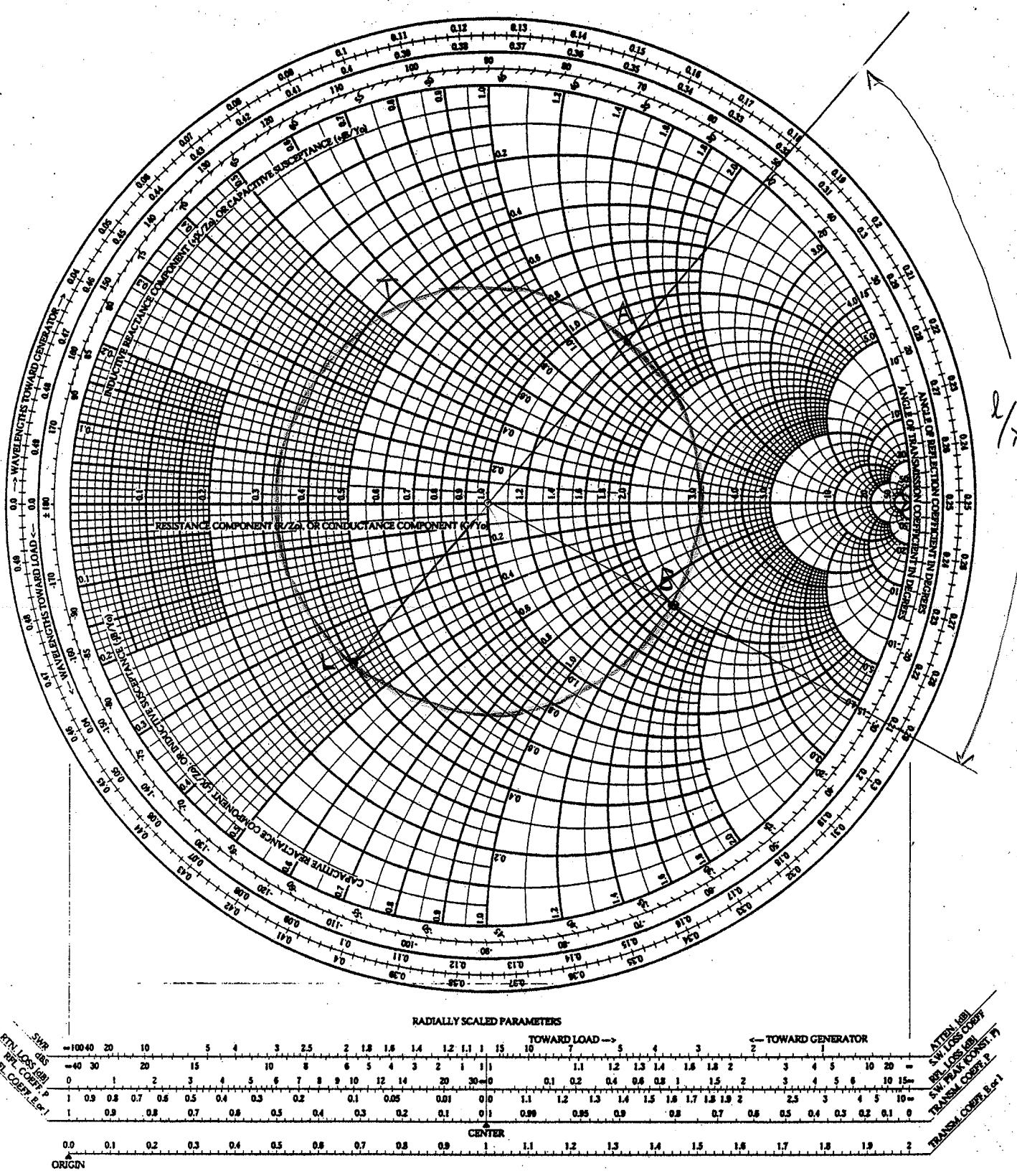

2. (25 points)


The S-matrix of a three-port circuit is given as follows:

$$S = \begin{bmatrix} 0.3 & 0.2 & 0.5j \\ 0.2 & 0.1 & 0.6 \\ 0.5j & 0.6 & 0.3 \end{bmatrix}$$

Pts

- 10 a. Draw the flow graph for the above circuit given that ports 1 and 3 are connected to mismatched loads with reflection coefficients $\Gamma_1 = 0.4$ and $\Gamma_3 = 0.3$, respectively.
- 15 b. Calculate the reflection coefficient b_2/a_2 at port 2.

2. a.

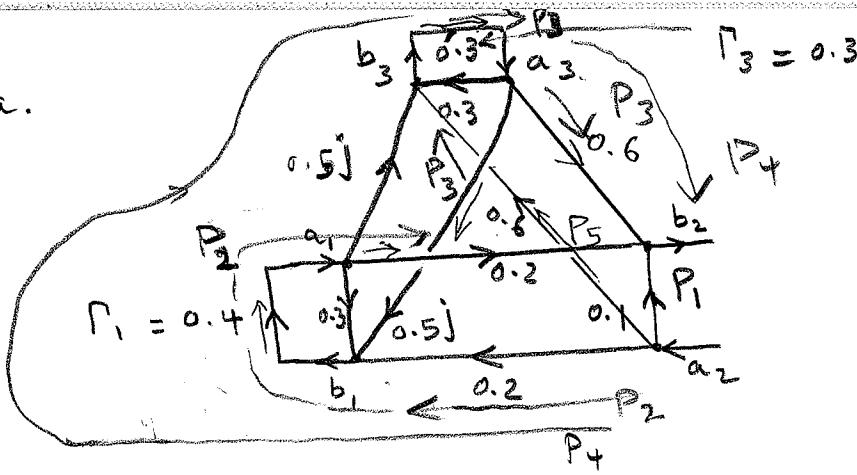

(3)

b. Reflection Coeff. $\frac{b_2}{a_2}$

paths First order
Non-touching Loops
 $L(1)$

$$P_1 \geq 0.1 \quad 0.3 \times 0.4, 0.3 \times 0.3, 0.4 \times 0.5 \downarrow \times 0.3 \times 0.5 \downarrow \\ \downarrow \quad \downarrow \quad \downarrow \\ 0.12 \quad 0.09 \quad -0.03$$

2nd order
Non-touching loops
 $L(2)$

$$(0.4 \times 0.3)(0.3 \times 0.3) \\ = 0.0108$$

$$P_2 = 0.2 \times 0.4 \times 0.2 \quad 0.3 \times 0.3 \geq 0.09$$

0

0

$$P_3 = 0.6 \times 0.3 \times 0.6 \quad 0.4 \times 0.3 \geq 0.12$$

$$P_4 \quad 0.2 \times 0.4 \times 0.5 \downarrow \times 0.3 \times 0.6 \quad 0$$

0

0

$$P_5 \quad 0.6 \times 0.3 \times 0.5 \downarrow \times 0.4 \times 0.2 \quad 0$$

All second order loops
touching or non-touching
 $L(2)$

Touching or non-touching $L(1)$

$$0.4 \times 0.3, 0.3 \times 0.3$$

$$(0.4 \times 0.3)(0.3 \times 0.3) \\ = 0.0108$$

$$0.4 \times 0.5 \downarrow \times 0.3 \times 0.5 \downarrow$$

↓

$$0.12, 0.09$$

$$-0.03$$

$$\frac{b_2}{a_2} = \frac{0.1 \left[1 - \left(\frac{0.18}{0.12 + 0.09 - 0.03} \right) + 0.0108 \right] + 0.016 \left[1 - 0.09 \right] + 0.108 \left[1 - 0.12 \right]}{1 - \left(\frac{0.12 + 0.09 - 0.03}{0.18} \right) + 0.0108}$$

$$0.2326 / 4.273$$

$$= \frac{0.08308 + 0.01456 + 0.09504 + 0.0144}{0.8308} = \frac{0.19268 + 0.0144}{0.8308} = 0.23192 + j0.01733$$

3. (30 points)

Pts

- 11 a. Design a 0.5 dB equal-ripple low-pass filter with a cutoff frequency of 5 GHz and attenuation of 40 dB at twice the cutoff frequency i.e. at 10 GHz. The filter should be matched to a 60Ω microstripline. For this filter, calculate the values of individual inductances and capacitances that are needed **starting with a series element**.
- 4 b. Sketch the LC equivalent circuit of the designed low-pass filter.
- 10 c. Using a stepped impedance filter design, calculate the lengths ($\beta_c \ell$) of the sections to use for high impedance sections of characteristic impedance $Z_h = 120\Omega$ and low impedance sections of characteristic impedance $Z_\ell = 15\Omega$.
- 5 d. Sketch the microstrip layout of the final filter. Find the total length $\beta_c \ell$ of the designed filter.

3. From Fig. 8.27 a for a 0.5 dB ripple filter, an attenuation of 40 dB @ $\frac{\omega}{\omega_c} = 2$ can be obtained for $n = 5$ filter

(4)

From Table 8.4 the element values for an inductance input prototype are:

$$g_1 = \frac{\omega_c L_1}{Z_0} = 1.7058 \quad g_4 = \frac{\omega_c C_4}{Y_0} = 1.2296$$

$$g_2 = \frac{\omega_c C_2}{Y_0} = 1.2296 \quad g_5 = \frac{\omega_c L_5}{Z_0} = 1.7058$$


$$g_3 = \frac{\omega_c L_3}{Z_0} = 2.5408$$

$$L_1 = L_5 = \frac{1.7058 \times 60}{2\pi \times 5 \times 10^9} = 3.26 \text{ nH}$$

$$C_2 = C_4 = \frac{1.2296 \times \frac{1}{60}}{2\pi \times 5 \times 10^9} = 0.652 \text{ pF}$$

$$L_3 = \frac{2.5408 \times 60}{2\pi \times 5 \times 10^9} = 4.85 \text{ nH}$$

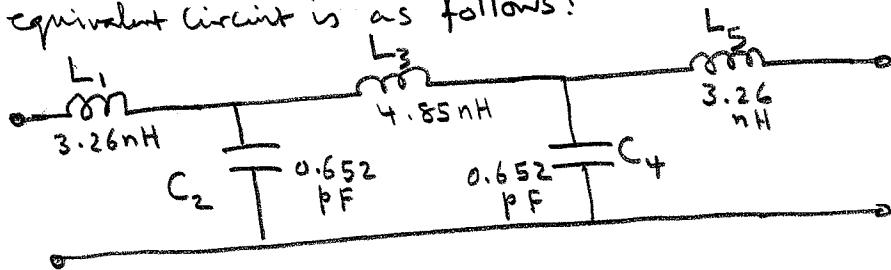- b. The LC equivalent circuit is as follows:



- c. From p. 18-1 of Class Notes, for inductive elements

$$\beta_c l = g \frac{Z_0}{Z_h} = g \frac{60}{120}$$

for inductances L_1, L_5

$$\beta_c l_1 = \beta_c l_5 = 1.7058 \times \frac{60}{120} = 0.8529 \text{ rad} = 48.87^\circ$$


for inductance L_3

$$\beta_c l_3 = 2.5408 \times \frac{60}{120} = 1.2704 \text{ rad} = 72.79^\circ$$

for capacitive elements C_2, C_4

$$\beta_c l_2 = \beta_c l_4 = g_2 \frac{Z_l}{Z_0} = 1.2296 \times \frac{15}{60} = 0.3074 \text{ rad} = 17.61^\circ$$

d.

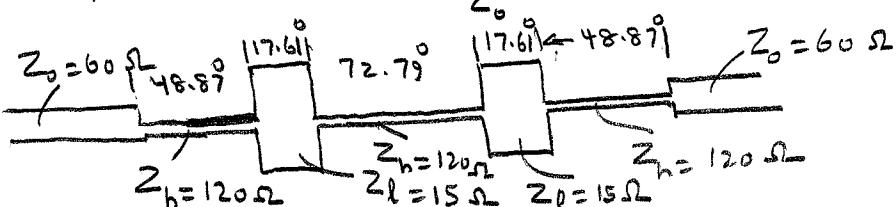

$$\begin{aligned} \text{Total length} &= 205.75^\circ \\ &\rightarrow 0.57 \lambda_g \end{aligned}$$

4. (30 points)

For a WR159 air-filled rectangular waveguide, the distance between two consecutive minima (i.e. $\lambda_g / 2$) for the TE₁₀ mode has been measured to be 3.8 cm and the reflection coefficient of a particular load is 0.4. Calculate the following:

Pts

- 6 a. Frequency of the signal.
- 6 b. Cutoff frequencies of the TE₂₀ and TE₁₁ modes of the waveguide.
- 6 c. SWR in the waveguide.
- 6 d. Maximum electric field E_{max} for the input power of 10 KW.
- 6 d. Actual power delivered to the load given that an input power $P_{inc} = 10$ KW .

$$4. a. \lambda_g = \frac{\lambda_0}{\sqrt{1 - \frac{f_c^2}{f^2}}} = \frac{c}{\sqrt{f^2 - f_c^2}} = 2 \times 3.8 = 7.6 \text{ cm} \quad (1)$$

$$\left| \frac{f_c}{TE_{10}} \right| = \frac{c}{2a} = \frac{30}{2 \times 4.039} = 3.714 \text{ GHz}$$

For WR 159
 $a = 1.59'' = 4.039 \text{ cm}$
 $b = 0.795'' = 2.02 \text{ cm}$

From Eq. (1) $f^2 - f_c^2 = \left(\frac{30}{7.6} \right)^2 = 15.582$

$$f = \sqrt{f_c^2 + 15.582} = \sqrt{(3.714)^2 + 15.582} = 5.42 \text{ GHz}$$

b. $\left| \frac{f_c}{TE_{20}} \right| = \frac{c}{a} = 2 \times 3.714 = 7.428 \text{ GHz}$

$$\left| \frac{f_c}{TE_{11}} \right| = c \sqrt{\left(\frac{1}{2a}\right)^2 + \left(\frac{1}{2b}\right)^2} = c \sqrt{\frac{1}{4a^2} + \frac{1}{a^2}} = \frac{c \sqrt{1.25}}{a} = 8.305 \text{ GHz}$$

c. $SWR = \frac{1 + |P|}{1 - |P|} = \frac{1 + 0.4}{1 - 0.4} = \frac{1.4}{0.6} = 2.33$

e. From Eq. (3.86) $Z_{TE} = \frac{377}{\sqrt{1 - \left(\frac{f_c^2}{f^2}\right)}} = 517.63 \Omega$

From Eq. (3.92)

$$P_{10} = 10 = \frac{a \cdot b}{4Z_{TE}} (E_{max})^2 = \frac{4.039 \times 2.02}{4 \times 517.63} (E_{max})^2$$

$$E_{max} = \sqrt{\frac{10^4 \times 4 \times 517.63}{4.039 \times 2.02}} = 1593 \text{ V/cm} \quad \text{or} \quad 1.593 \times 10^5 \text{ V/m}$$

d. power delivered to the load = $P_{inc} (1 - |P|^2) = 10 \times (1 - 0.16) = 8.4 \text{ kW}$

wj
EE 5320
Final Exam
December 13, 2004

Name _____

Score:

Problem 1 _____ of a possible 25 points

Problem 2 _____ of a possible 30 points

Problem 3 _____ of a possible 30 points

Problem 4 _____ of a possible 30 points

Total _____ of a possible 115 points