

Midterm I with Solutions

Name _____
Please Print

UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

MICROWAVE ENGINEERING I

ECE 5320/6322

MIDTERM EXAMINATION NO. I

October 3, 2014

1. (25 points)

Design a coaxial line of characteristic impedance $Z_0 = 60$ ohms using a dielectric filler medium $\epsilon_r = 1.9$. For this coaxial line,

Pts

- 5 a. Calculate the ratio of the radii b/a of outer and inner conductors.
- 8 b. Assuming $a = 2.5$ mm, calculate the loss α_c in dB/m at a frequency of 6 GHz.
Assume copper as the material for the conductors of the coaxial line.
- 8 c. The dielectric loss α_d in dB/m given that the loss tangent for the filler medium $\tan \delta = 0.001$.
- 4 d. The length of the line needed to get a total attenuation of less than 1 dB.

1. a. For a coaxial line, from Table 2.1 of the Text
- $$Z_0 = \sqrt{\frac{L}{C}} = \frac{60}{\sqrt{\epsilon_r}} \ln\left(\frac{b}{a}\right) = 60 \Omega$$

$$\frac{b}{a} = \frac{\sqrt{\epsilon_r}}{e} = \frac{\sqrt{1.9}}{e} = 3.97$$

Radius b of the outer conductor = $3.97 a = 9.925 \text{ mm}$

- b. From Ex. 2.6 of the Text

$$\begin{aligned} \alpha_{cf} &= \frac{1}{2} \left[\frac{R_s}{\eta_e \ln(b/a)} \left(\frac{1}{a} + \frac{1}{b} \right) \right] \\ &\text{units/m} \\ &= \frac{1}{2} \frac{R_s}{2\pi Z_0} \left(\frac{1}{a} + \frac{1}{b} \right) \\ &= \frac{0.0202}{4\pi \times 60} \left(\frac{1}{2.5} + \frac{1}{9.925} \right) \times 10^3 \\ &= \frac{20.2}{240\pi} \times 0.5 = 0.0134 \text{ nper/m} \times 8.686 \\ &= 0.1165 \text{ dB/m} \end{aligned}$$

$$\begin{aligned} R_s &= 1.988 \frac{\text{FMHz}}{\text{A}} \\ &= 1.988 \frac{6000}{5.813 \times 10^{14}} \\ &= 0.0202 \Omega \end{aligned}$$

$$\begin{aligned} \eta_e \ln\left(\frac{b}{a}\right) &= \frac{120\pi}{\sqrt{\epsilon_{eff}}} \ln \frac{b}{a} \\ &= 2\pi Z_0 \end{aligned}$$

$$\begin{aligned} c. \quad \alpha_d &= \frac{1}{2} \omega \epsilon'' \eta_e \times 8.686 = \frac{1}{2} 2\pi \times 6 \times 10 \times \frac{1}{10} \times 8.85 \times \frac{1}{10} \times \frac{1}{10} \times 8.686 \\ &= 6\pi \times 8.85 \times 0.377 \times \frac{1}{10} \times 8.686 \sqrt{1.9} \\ &= 0.753 \text{ dB/m} \end{aligned}$$

d. $\alpha_c + \alpha_d = 0.8695 \text{ dB/m}$

Length for a total atten of 1 dB = $\frac{1}{0.8695} = 1.15 \text{ m}$

2. (25 points)

Pts

- 8 a. Sketch the equivalent circuit of the microstripline circuit shown in Fig. 1.

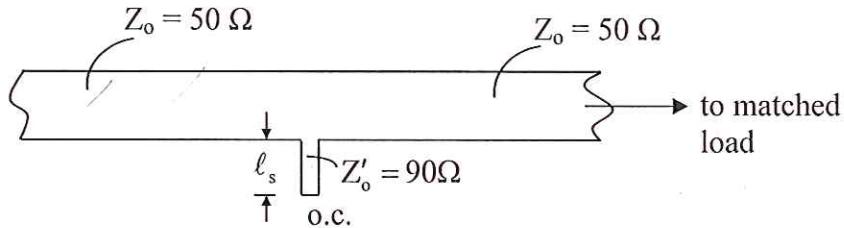


Fig. 1. Shown here is the printed microstrip with an open-circuited shunt stub.

Note that the open-circuited stubline may be represented by an admittance


$$Y_{\text{stub}} = j Y'_o \tan\left(\frac{2\pi\ell_s}{\lambda_g}\right)$$

across the main microstripline of $Z_0 = 50 \Omega$.

- 8 b. Calculate the length of the shunt stub to get $Y_{\text{stub}} = \infty$ [$Z_{\text{stub}} = 0$] at a frequency of 6000 MHz given that $\epsilon_{\text{eff}} = 2.8$ for the shunt stubline. *Shunt cct.*
- 9 c. Using this length of the shunt stub, calculate the admittance that the shunt stub presents across the microstripline at 3000 MHz where $\ell_s = \lambda_g/8$. Is this a capacitance or an inductance, and what is the value of this shunt element across the transmission line?

$$C = 0.59 \text{ pF}$$

2. a. EQVT ckt. is as shown below
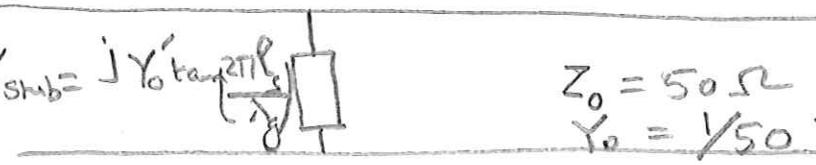
$$Z_0 = 50 \Omega \quad Y_{\text{Stub}} = j Y_0 \tan 2\pi f_s l_s$$

$$Z_0 = 50 \Omega$$
$$Y_0 = 1/50 \text{ mhos}$$

b. To get $Y_{\text{Stub}} = \infty$ or $Z_{\text{Stub}} = 0$ we need a length $l_s = \lambda_g/4$ at 6000 MHz

$$l_s = \frac{\lambda_0}{4} \frac{1}{\sqrt{\epsilon_{\text{eff}}}} = \frac{5}{4} \frac{1}{\sqrt{2.8}} = 0.747 \text{ or } 7.47 \text{ mm}$$

c. once this length l_s has been calculated

$$Y_{\text{Stub}} = j Y_0 \tan 45^\circ \text{ at } 3000 \text{ MHz}$$
$$= j \frac{1}{90}$$

This is a capacitance which can be calculated from

$$j \omega C_{\text{eq}} = j \frac{1}{90}$$

$$C_{\text{eq}} \Big|_{3000 \text{ MHz}} = \frac{1}{90 \times 2\pi \times 3 \times 10^9} = \boxed{0.589 \text{ pF}}$$

3. (25 points)

Pts

5 a. Draw a flow graph for a transistor amplifier with S-parameters given in the following:

$$[S] = \begin{bmatrix} 0.4\angle -45^\circ & 0.4 \\ 3.5 & 0.4\angle 45^\circ \end{bmatrix}$$

8 b. Calculate the power delivered to a fully matched load with $\Gamma_\ell = 0$. It is given that

$$a_1 a_1^* = 0.05 \text{W}$$

8 c. Calculate the power delivered to a conjugate matched load with

$$\Gamma_\ell = S_{22}^* = 0.4\angle -45^\circ$$


4 d. How much higher is the power delivered for condition c as compared to the power for the fully matched load of condition b in this problem?

For 10 extra points:

6 e. Calculate the power input to the amplifier $a_1 a_1^* - b_1 b_1^*$ for conditions b and c, and

4 f. the power gains of the amplifier for conditions b and c above.

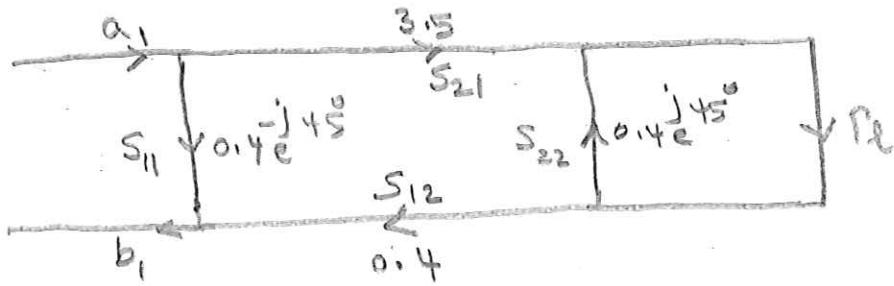3.a. The flow graph for the transistor amplifier is sketched below



b. For a fully matched load $P_L = 0$

$$\frac{b_2}{a_1} = S_{21}$$

Power delivered to this fully matched load $= b_2 b_2^* = |S_{21}|^2 a_1 a_1^*$
 $= (3.5)^2 a_1 a_1^* = (3.5)^2 \times 0.05 = 0.6125 \text{ W}$

c. Power delivered to a conjugate matched load $P_L = S_{22}^* = 0.4e^{-j45}$

$$= b_2 b_2^* (1 - |P_L|^2) = |S_{21}| + \frac{S_{22} S_{21} P_L^2}{1 - S_{22} P_L} [a_1 a_1^* [1 - |P_L|^2]]$$

$$= \left| 3.5 + \frac{3.5 |P_L|^2}{1 - |S_{22}|^2} \right|^2 a_1 a_1^* \times 0.84$$

$$= \left| 3.5 + \frac{3.5 \times 0.16}{0.84} \right|^2 a_1 a_1^* \times 0.84$$

$$= (4.167) \frac{a_1 a_1^*}{0.05} = 0.729 \text{ W}$$

The power delivered to the conjugate matched load is 19.1% higher than that for the fully matched load.

e. $P_{in} \Big|_{\substack{\text{Condition b} \\ P_L = 0}} = a_1 a_1^* [1 - |S_{11}|^2] = 0.05 \times 0.84 = 0.042 \text{ W}$

$P_{in} \Big|_{\substack{\text{Cond. 2}}} = a_1 a_1^* [1 - |P_{in}|^2] = 0.039 \text{ W}$

f. $\text{Power gain} \Big|_{\substack{\text{cond. b}}} = \frac{0.6125}{0.042} = 14.58$

See next page for condition c which can be turned into an oscillator.

$$\begin{aligned} P_{in} &= \frac{S_{11}(1 - |S_{22}|^2) + S_{21} P_L S_{12}}{1 - |S_{22}|^2} \\ &= S_{11} + \frac{3.5 \times 0.4 \times 0.4 e^{-j45}}{1 - 0.16} \\ &= 0.4 e^{-j45} \left[1 + \frac{1.4}{0.84} \right] = 1.067 e^{-j45} \end{aligned}$$

Solution of Prob. 3 — Continued

- c. It is interesting that the reflected power $b_1 b_1^*$ is more than $a_1 a_1^*$. This is because of amplification of S_{21} in the forward path.

Such an amplifier is potentially unstable unless the reflected power $b_1 b_1^*$ is terminated into an absorbing load. Such an amplifier is also capable of being turned into an oscillatore.

ECE 5320/6322

Midterm No. I

October 3, 2014

Name _____

Score:

Problem 1 _____ of a possible 25 points

Problem 2 _____ of a possible 25 points

Problem 3 _____ of a possible 25 points

Total _____ of a possible 75 points