

Sample Midterm I  
with Solutions

Name \_\_\_\_\_  
Please Print

UNIVERSITY OF UTAH  
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

MICROWAVE ENGINEERING I


ECE 5320/6322

MIDTERM EXAMINATION NO. 1

September 28, 2009

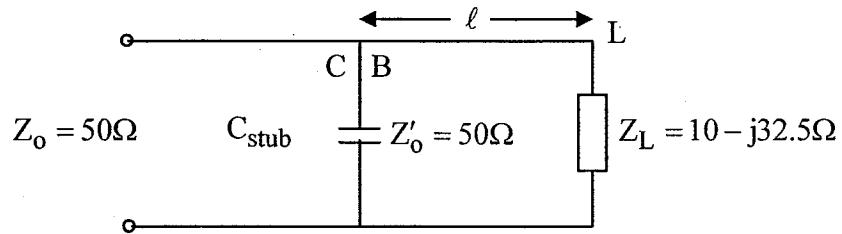1. (25 points)

A load of impedance  $10 - j32.5\Omega$  is to be matched by using an open-circuited stub-created capacitance using a circuit of topology as follows:



Pts

- 12 a. Calculate the distance  $\ell$  between Planes L and B to obtain matching using a capacitance  $C_{\text{stub}}$  created by an open-circuited stub across the transmission line. Use  $\lambda_g = 5$  cm and frequency  $f = 4$  GHz .
- 8 b. Calculate the capacitance  $C_{\text{stub}}$  needed for the matching circuit.
- 5 c. Calculate the length  $\ell_s$  of the open-circuited stub given that

$$Y_{\text{stub}} = j Y'_0 \tan(\beta \ell_s)$$

Take  $Z'_0 = 100\Omega$  for the open-circuited stub.


1.a.  $Z_L = 10 - j32.5$

$$Z_L = \frac{10 - j32.5}{50} = 0.2 - j0.65 \quad (\text{this is represented by point L on the Smith Chart})$$

The transmission line circle for this load is sketched as circle C on the Smith chart

From the Smith chart, the admittance point is diametrically opposite i.e. L' on circle C

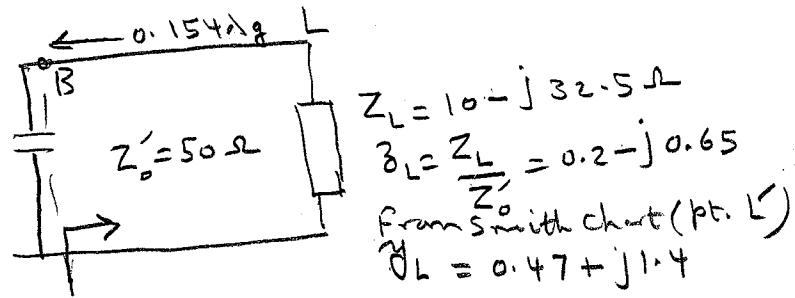The distance  $l$  from the Smith chart to a point with real part 1 is  $(0.31 - 0.156)\lambda_g = 0.154\lambda_g = 0.154 \times 5 = 0.77 \text{ cm}$



$$\gamma_B = 1 - j2.2$$

$$Y_B = (1 - j2.2)Y_0' = \frac{1}{50} - j\frac{2.2}{50}$$

Add  $j\omega C_{\text{smb}} = j\frac{2.2}{50}$


b.  $C_{\text{smb}} = \frac{2.2 \times 10^3 \text{ pF}}{50 \times 2\pi \times 4 \times 10^9} = 1.75 \text{ pF}$

c. It is given that

$$j\omega C_{\text{smb}} = j\frac{2.2}{50} = j\frac{1}{100} \tan(\beta l_s)$$

$$\beta l_s = \frac{2\pi l_s}{\lambda_g} = 77.2^\circ = 0.429\pi = 1.347 \text{ rad}$$
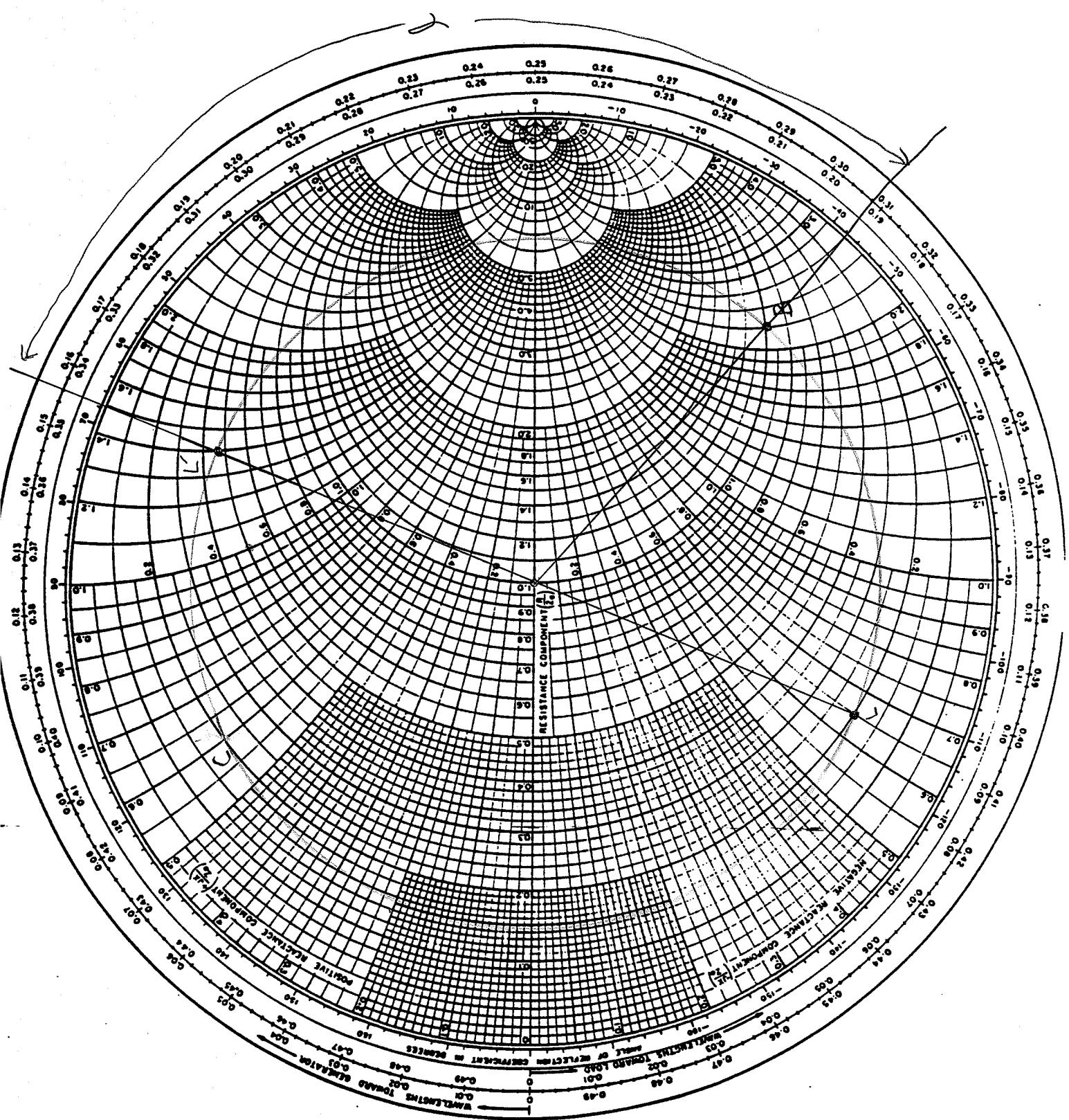
$$\frac{l_s}{\lambda_g} = 0.2145 \rightarrow l_s = 0.2145 \times 5 = 1.073 \text{ cm}$$



2. (25 points)

A microstripline with microstrip width  $w$  to substrate thickness  $d$  ratio  $w/d = 2.3$  is printed on a quartz substrate ( $\epsilon_r = 3.78$ ). For this microstripline, calculate:

Pts

- 5 a. the characteristic impedance.
- 3 b. effective dielectric constant.
- 5 c. the RMS value of the RF voltage between the microstrip and the ground plane for an input power of 1W.
- 6 d. attenuation  $\alpha_d$  in dB/m due to **dielectric** losses for a signal frequency of 20 GHz. The loss tangent for quartz from p. 667 of the Text is given to be  $10^{-4}$ .
- 6 e. for a substrate thickness  $d = 0.1"$ , the maximum frequency to which the microstripline may be used without exciting any of the higher-order modes.

2. From Eq. 3.195 p. 144

b.  $E_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \frac{1}{\sqrt{1 + 12 \frac{d}{W} \frac{1}{2.3}}} = 2.947$

a.  $\frac{w}{d} = 2.3 > 1$

From Eq. 3.196 p. 145

$$Z_0 = \frac{120 \pi}{\sqrt{2.947 \left[ 2.3 + 1.393 + \frac{0.667 \ln(2.3 + 1.444)}{0.8805} \right]}} = 48.02 \Omega$$

c.  $\frac{|V|_{peak}^2}{2Z_0} = 1 \text{ W} ; |V|_{rms} = \sqrt{Z_0} = 6.93 \text{ V rms}$

e.  $f_c = \frac{c}{4d\sqrt{\epsilon_r - 1}} = \frac{30 \times 10^9}{4 \times 0.254 \sqrt{2.78}} = 17.71 \text{ GHz}$

d. From Eq. 3.198  
$$\alpha_d = \frac{2\pi}{0.10} \times \frac{1.89}{3.78 \times 1.947} \times \frac{-4}{\sqrt{2.947}} \times 8.686 = 2210 \times 10^{-4} \text{ dB/m}$$
$$= 0.021 \text{ dB/m}$$

3. (25 points)

Pts

- 8 a. Draw a flow graph for a transistor amplifier with S-parameters given in the following:


$$[S] = \begin{bmatrix} 0.3 & -0.03 \\ 4.1 & 0.5\angle 90^\circ \end{bmatrix}$$

- 8 b. Calculate the reflection coefficient at port ① if port ② is connected to a load of reflection coefficient

$$\Gamma_L = S_{22}^* = 0.5\angle -90^\circ \quad \text{or} \quad -j0.5$$

- 9 b. Calculate the power coupled to the "conjugate-matched" load given in part b if the input power  $a_1 a_1^* = 0.08W$ .

3.

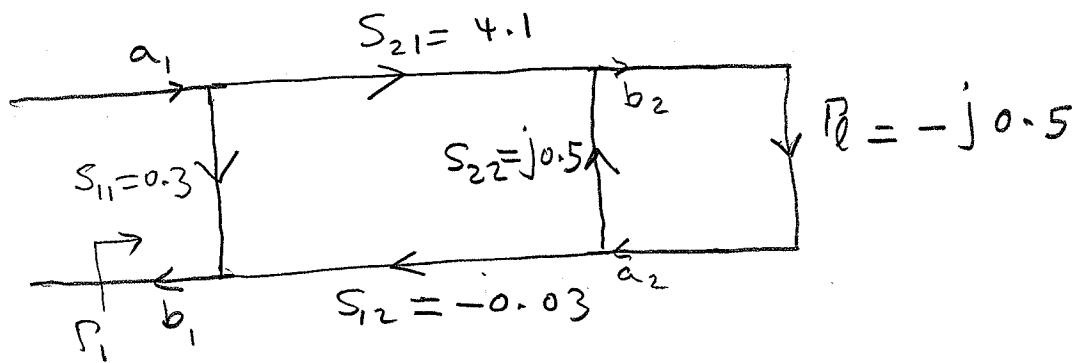

$$\begin{aligned}
 R_1 &= \frac{b_1}{a_1} = S_{11} + \frac{S_{21} P_L S_{12}}{1 - S_{22} P_L} = 0.3 + \frac{(-0.03)(-j0.5)(4.1)}{1 - (j0.5)(-j0.5)} \\
 &= 0.3 + \frac{0.0615j}{1 - 0.25} = 0.3 + j0.082 \\
 &= 0.311 \angle 15.29^\circ
 \end{aligned}$$

$$\frac{b_2}{a_1} = \frac{S_{21}}{1 - S_{22} P_L} \cancel{a_1} = \frac{4.1}{0.75} = 5.467$$

Power coupled to the load

$$\begin{aligned}
 b_2 b_2^* - a_2 a_2^* &= (5.467)^2 a_1 a_1^* [1 - 1 P_L^2] = (5.467)^2 [1 - 0.25] a_1 a_1^* \\
 &= 1.793 \text{ W}
 \end{aligned}$$

ECE 5320/6322  
Midterm No. 1  
September 28, 2009

Name \_\_\_\_\_

Score:

Problem 1 \_\_\_\_\_ of a possible 25 points

Problem 2 \_\_\_\_\_ of a possible 25 points

Problem 3 \_\_\_\_\_ of a possible 25 points

Total \_\_\_\_\_ of a possible 75 points