


Microwave Design Problems  
Using Smith Chart

Prob. 1  $Z_L = 26 + j15$   
 $\Rightarrow 30 \angle 30^\circ$

# The Complete Smith Chart
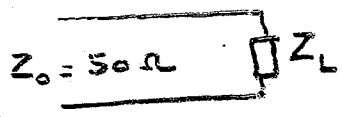
## Black Magic Design


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{26 + j15}{50} = 0.52 + j0.3$$



$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$= 0.366 \angle 136.85^\circ$$


$\rightarrow \frac{0.366}{136.85^\circ}$

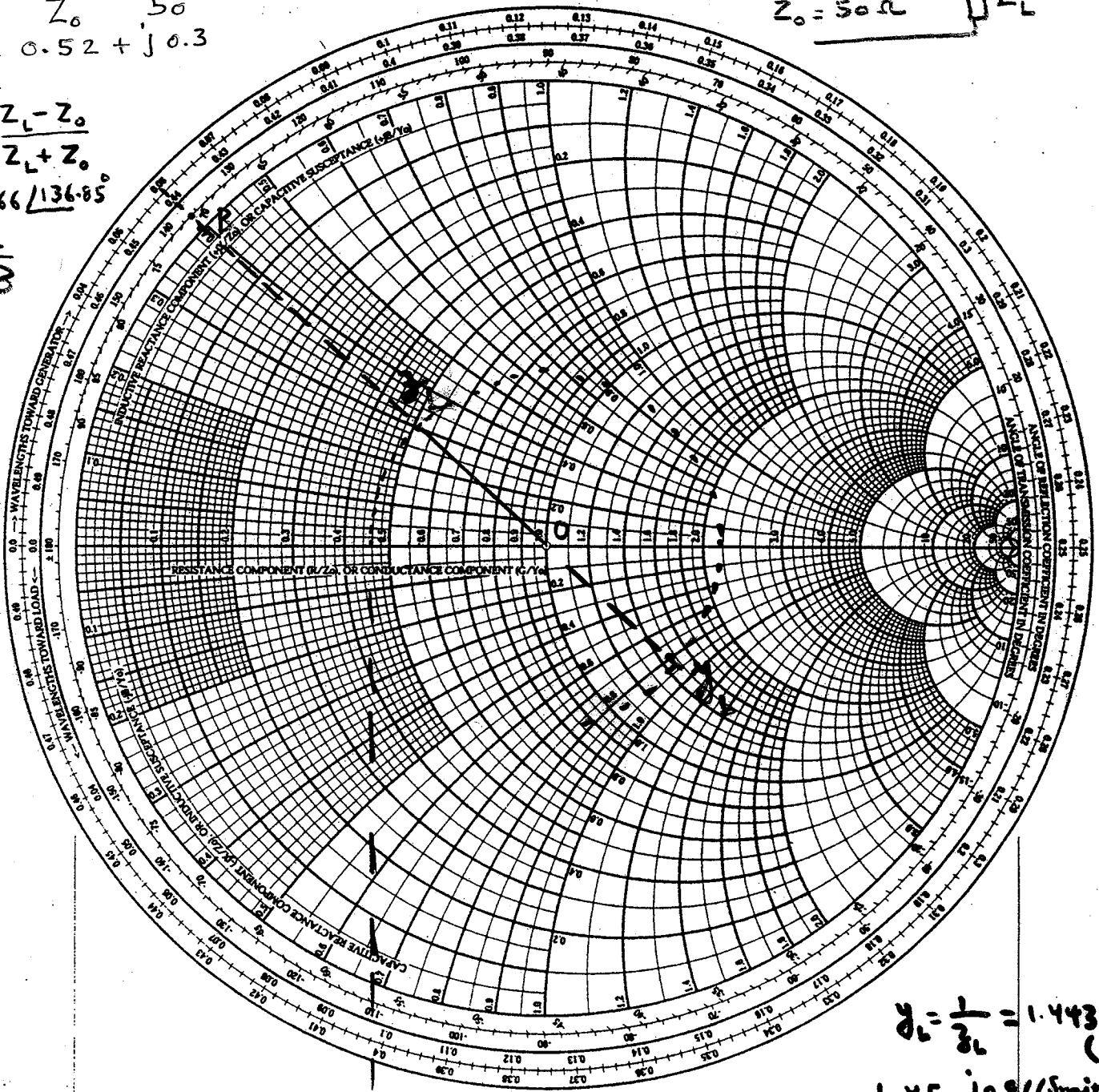

$$\Gamma_L = \frac{1}{\Gamma_L} = 1.443 - j0.81$$

(exact)

1.45 - j0.86 (Smith Chart)

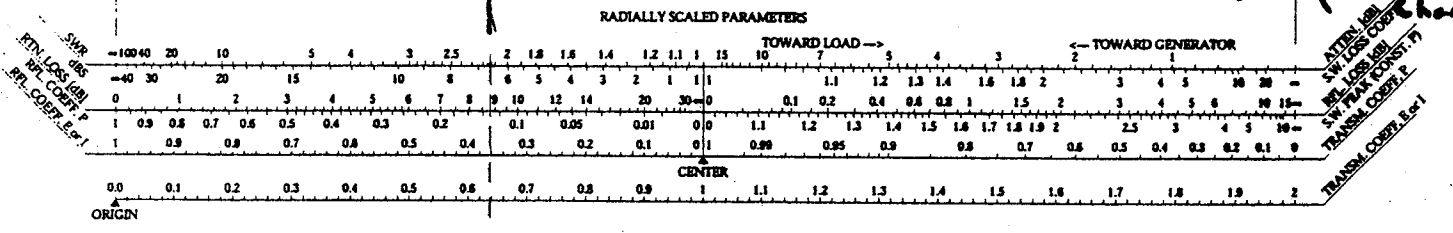

101


THE EMELOID CO., INC.  
HILLSIDE 5, N. J.

$VSWR = 2.14$

$f = 800 \text{ MHz}$   
 $\lambda_0 = 37.5 \text{ cm}$   
 $\gamma_g = \frac{\lambda_0}{\sqrt{\epsilon_{eff}}} = 28.76 \text{ cm}$   
 $\rightarrow 1.7$

$r = \frac{OL}{OB}$   
 $= 0.35 \angle 137.5^\circ$

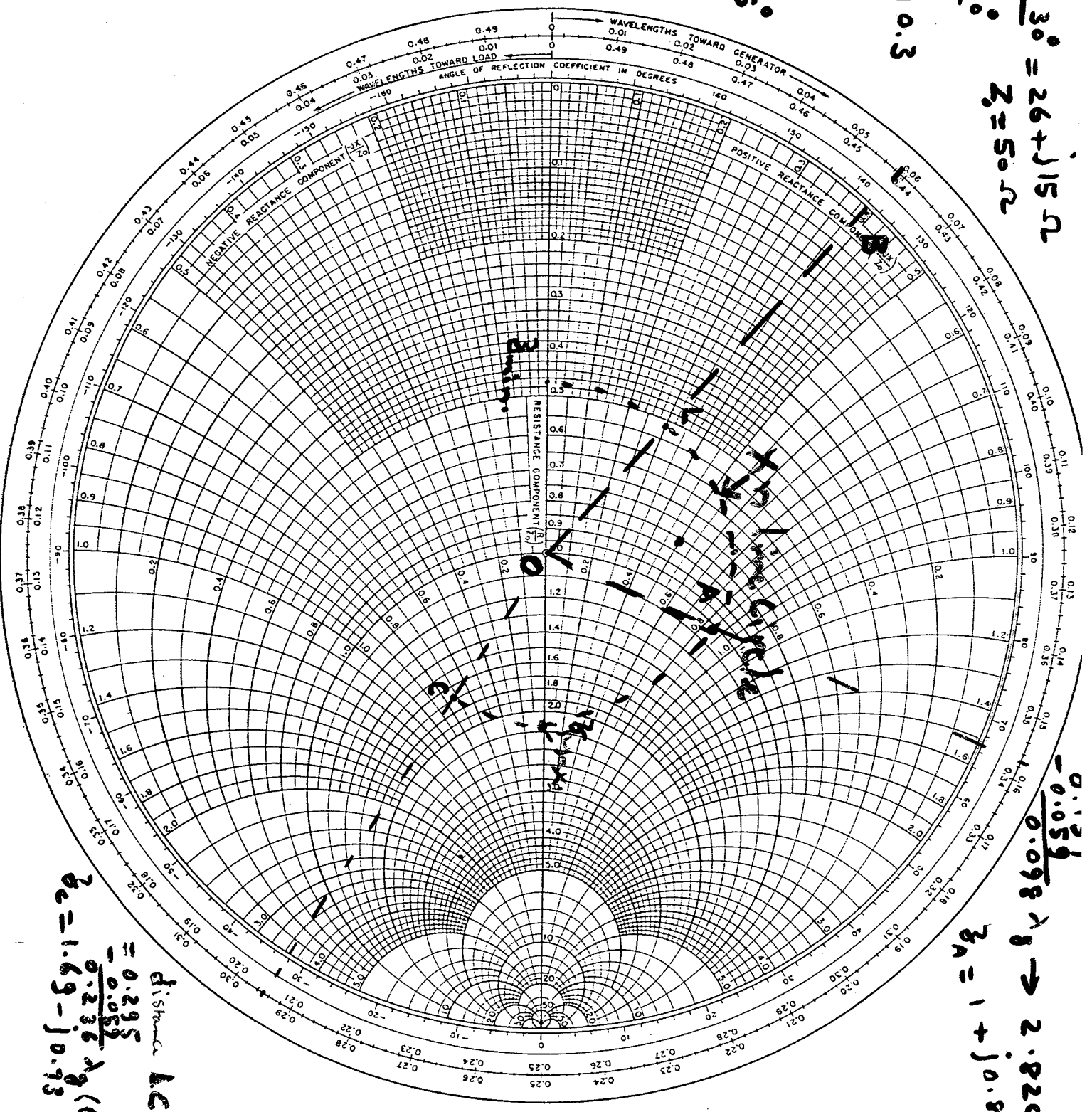$Z_L = 30 \angle 30^\circ = 26 + j15 \Omega$   
 $Z_0 = 50 \Omega$   
 $\Gamma_L = 0.6 \angle 30^\circ$   
 $= 0.52 + j0.3$



$\frac{-0.134}{0.059} \lambda_g \rightarrow 2.82 \text{ cm}$   
 $Z_A = 1 + j0.85$

distance AC  
 $= \frac{0.295}{0.059} \lambda_g (6.79 \text{ cm})$   
 $d_c = 1.69 - j0.93$

Fig 2

Prob. 2

$$Y_L = \frac{1}{30} \angle -30^\circ \quad f = 800 \text{ MHz}$$

$$\lambda_0 = 37.5 \text{ cm}$$

$$Y_L = 1.443 - j0.833$$

$$\lambda_g = \frac{\lambda_0}{\sqrt{\epsilon_{\text{eff}}}} = \frac{37.5}{1.7} = 22.06 \text{ cm}$$

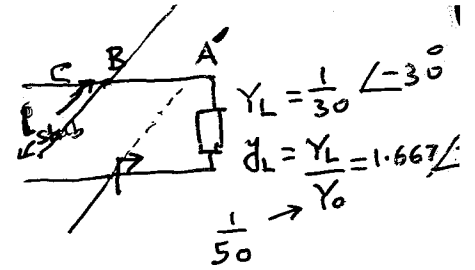


Fig. 2


"SMITH CHART"

For  $d'_{AB} = (0.344 - 0.30)$

$$= \frac{0.035 \lambda_g}{1}$$

$$Y_B = 1 - j0.84$$

$$Y_B = \frac{1}{50} - j0.1$$

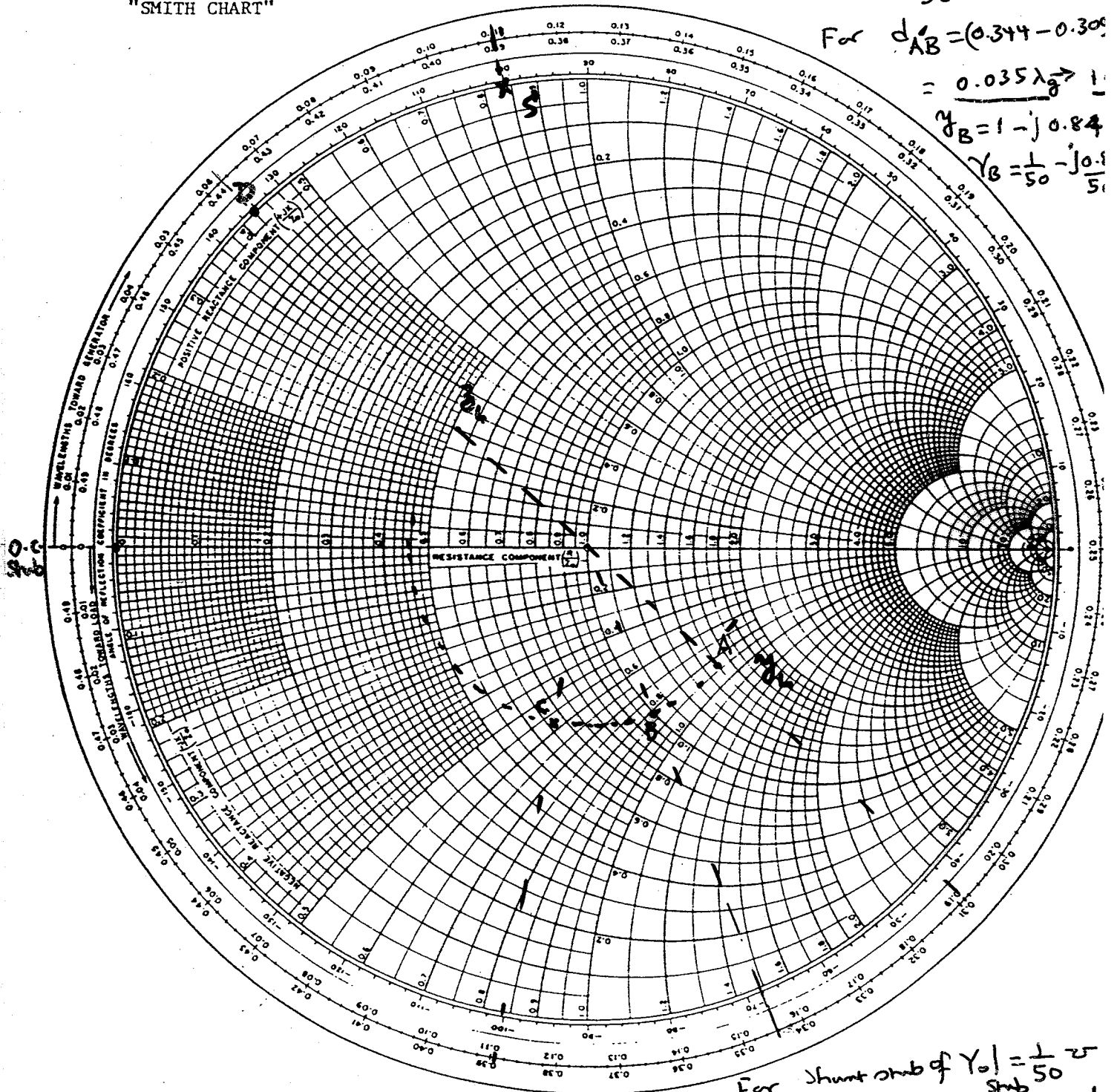

For shunt stub of  $Y_{sh} = \frac{1}{50}$

A.  $L_{sh} = 0.11 \lambda_g$  (Single-sided stub)

$$631.64 \text{ mm} \quad j b_{sh} = +j0.84$$

B. For double-sided stub (D)  $j b'_{sh} = j0.42$

$$L_{sh} = 0.063 \lambda_g \leftarrow 18.1 \text{ mm}$$

2-sided


Example 1

A microwave filter using two shunt capacitors

Take  $f = 10 \text{ GHz}$

The normalized admittance at plane A' is shown on the accompanying Smith chart
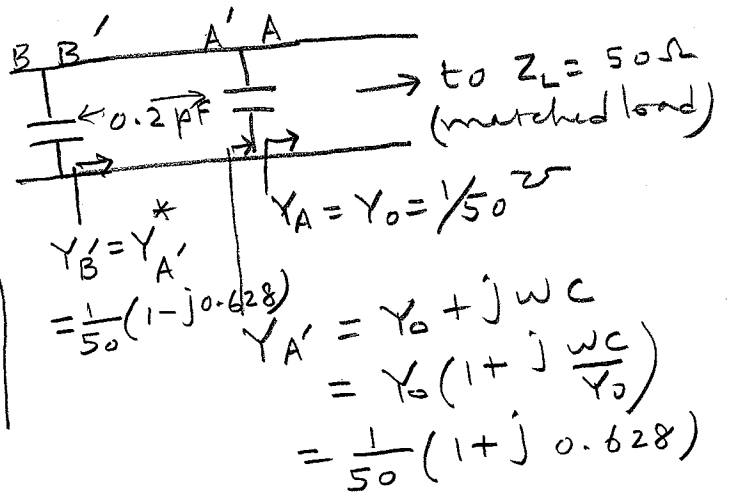
$$Y_{A'} = \frac{Y_A}{Y_0} = 1 + j \frac{\omega C}{Y_0} = 1 + j 0.628$$



Moving from point A' to B' shown in the Smith chart, we get  $Y_{B'} = Y_{A'}^* = Y_0 - j\omega C$

Upon adding an identical capacitor of 0.2 pF, we get the admittance  $Y_B$  at plane B to the left of the second capacitance

$$Y_B = (Y_0 - j\omega C) + j\omega C = Y_0$$


Thus the transmission line to the left of plane B is matched.

distance  $l_{A'B'} = 2(0.25 - 0.149) \lambda_g = 0.202 \lambda_g$  (from Smith chart)

In the following example, we redo this problem using a higher characteristic impedance  $Z_0' = 75 \Omega$  between the two capacitors.

101

$\lambda_L = 1 + j0.628$

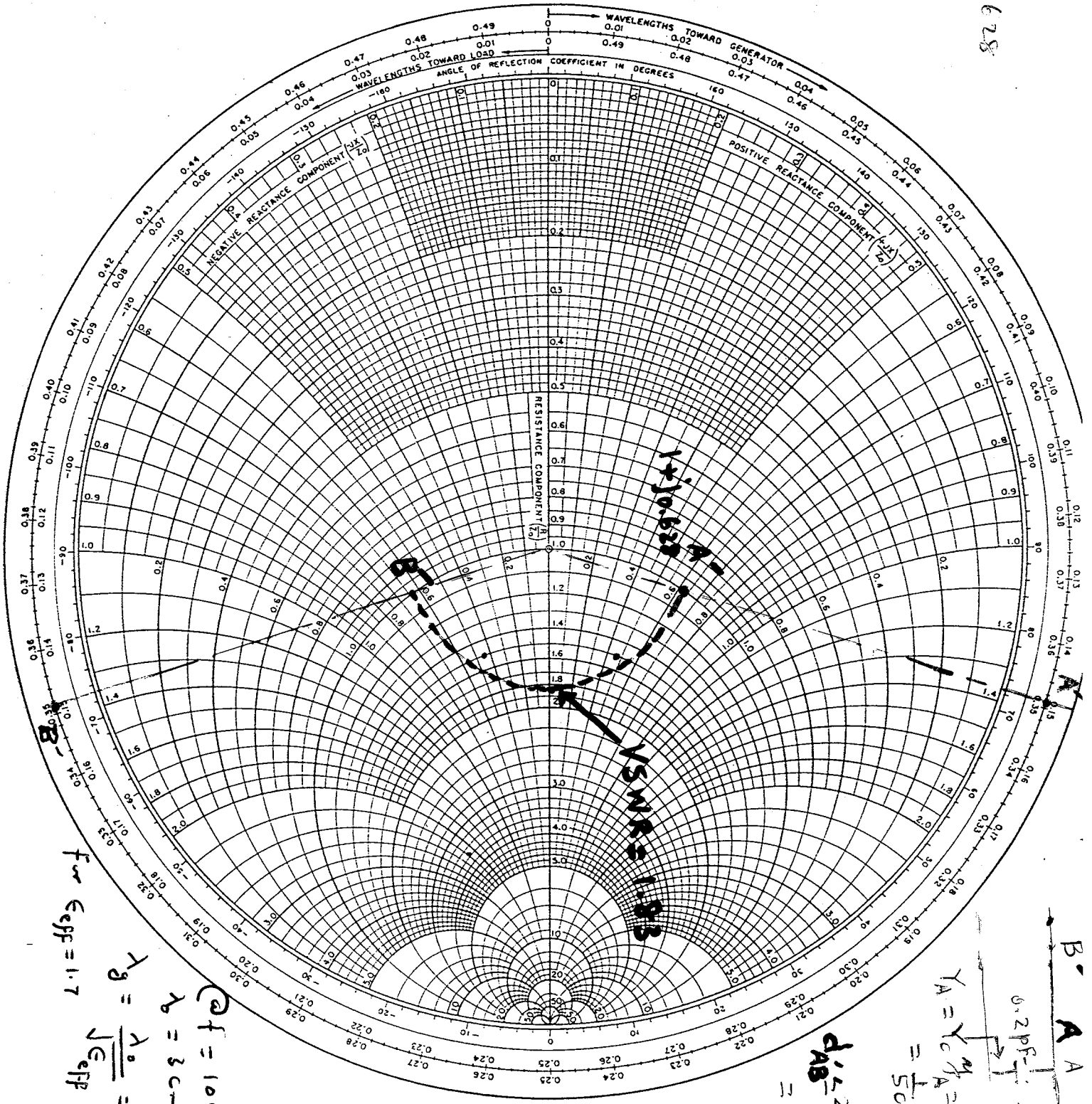

For  $\epsilon_{eff} = 1.7$

$f = 106 \text{ Hz}$   
 $\lambda = 3 \text{ cm}$   
 $\lambda_g = \frac{\lambda_0}{\sqrt{\epsilon_{eff}}} = 2.3 \text{ cm}$

$d_{AB} = 2(0.25 - 0.149)\lambda_g = 0.202\lambda_g$

$Y_A = Y_C = \frac{1}{50} + j0.628$   
 $Z_{eff} = 250 \Omega$   
 $0.2 \text{ PFL}$   
 $Z_{eff} = 250 \Omega$   
 $Y_A = Y_C = \frac{1}{50} + j0.628$   
 $= \frac{1}{50} (1 + j0.628)$

A matching circuit using two appropriately spaced capacitors (Similar to Prob. 4 of Typed HW set) (4)

(this can also be used as a bandpass filter)

Ex.  $f = 10 \text{ GHz}$   
 $C = 0.2 \text{ pF}$

Because of the shunt capacitance  $C$  across the transmission line, it is best to solve this as an admittance problem

Diagram: A transmission line with characteristic impedance  $Z_0 = 50 \Omega$  and length  $l$ . Point E is at the input, and point A is at the output. A shunt capacitor  $C = 0.2 \text{ pF}$  is connected at point A. The load is  $Z_L = 50 \Omega$ . A second shunt capacitor  $C = 0.2 \text{ pF}$  is connected at point D, which is a distance  $l$  from point A. The admittance at point D is  $Y_D$ , and the admittance at point A is  $Y_A$ . The admittance at point A' is  $Y_{A'}$ .

$$Y_A = \frac{1}{Z_0} = \frac{1}{50} \text{ S}$$

$$Y_{A'} = Y_A + Y_{A'} = Y_A + j\omega C = \frac{1}{50} (1 + j0.628)$$

$$Y_{A''} = \frac{Y_{A'}}{Y_0'} = \frac{\frac{1}{50} (1 + j0.628)}{\frac{1}{75}} = 1.5 + j0.942$$

The effective normalized "load" to the  $Z_0' = 75 \Omega$  line is point A'' in Fig. 3.

a. After traversing a distance  $l = 0.2 \lambda_g$  to a plane D of the Xn line

$$Y_D = Y_0' (0.625 - j0.575) = \frac{1}{75} (0.625 - j0.575)$$

For actual admittance

At point D' we connect a second capacitor  $C = 0.2 \text{ pF}$ ;  $Y_{D'} = j\omega C$

$$Y_{D''} = Y_D + Y_{D'} = \frac{1}{75} (0.625 - j0.575 + j0.3\pi) = \frac{1}{75} (0.625 + j0.367)$$

This is the effective "load" to the section D''E of the Xn line with  $Z_0 = 50 \Omega$

$$Y_{D''} = \frac{Y_{D''}}{Y_0} = 50 Y_{D''} = 0.417 + j0.295$$

This is shown as point D'' in Fig. 3. We can draw a transmission line circle with radius OD''. This will intercept the positive x-axis at point E (in Fig. 3). Thus VSWR for the transmission line to the left of point D'' is 2.6.

b. In order to match the transmission line, we move to a point B'' for which  $Y_{B''}$  is complex conjugate of  $Y_{A''}$ . Thus  $Y_{B''} = Y_{A''}^* = 1.5 - j0.942$

Why? Upon adding a second identical capacitance

$$Y_B = Y_{B''} + j\omega C$$

$$= Y_0' Y_{B''} + j\omega C = \frac{1}{75} (1.5 - j0.942) + j\omega C$$

$$= \frac{1}{50} + j0$$

and the line is matched for all points of the transmission line to the left of point B. From Smith chart Fig. 3

length  $l_{A''B''} = (0.307 - 0.193) \lambda_g = \boxed{0.114 \lambda_g} = 0.114 \frac{\lambda_0}{\sqrt{\epsilon_{eff}}} = 2.62 \text{ mm}$


Example 3  $F = 10 \text{ GHz}$

$$\frac{B''}{A''} = \frac{1}{\Gamma_{0.25}} \quad Z_0 = 50 \Omega$$

$$\Gamma_{A'} = \frac{1}{\sqrt{75}} (1 + j0.628)$$

$$= 1.5 + j0.942$$

$$d_{A'B''} = \lambda'$$

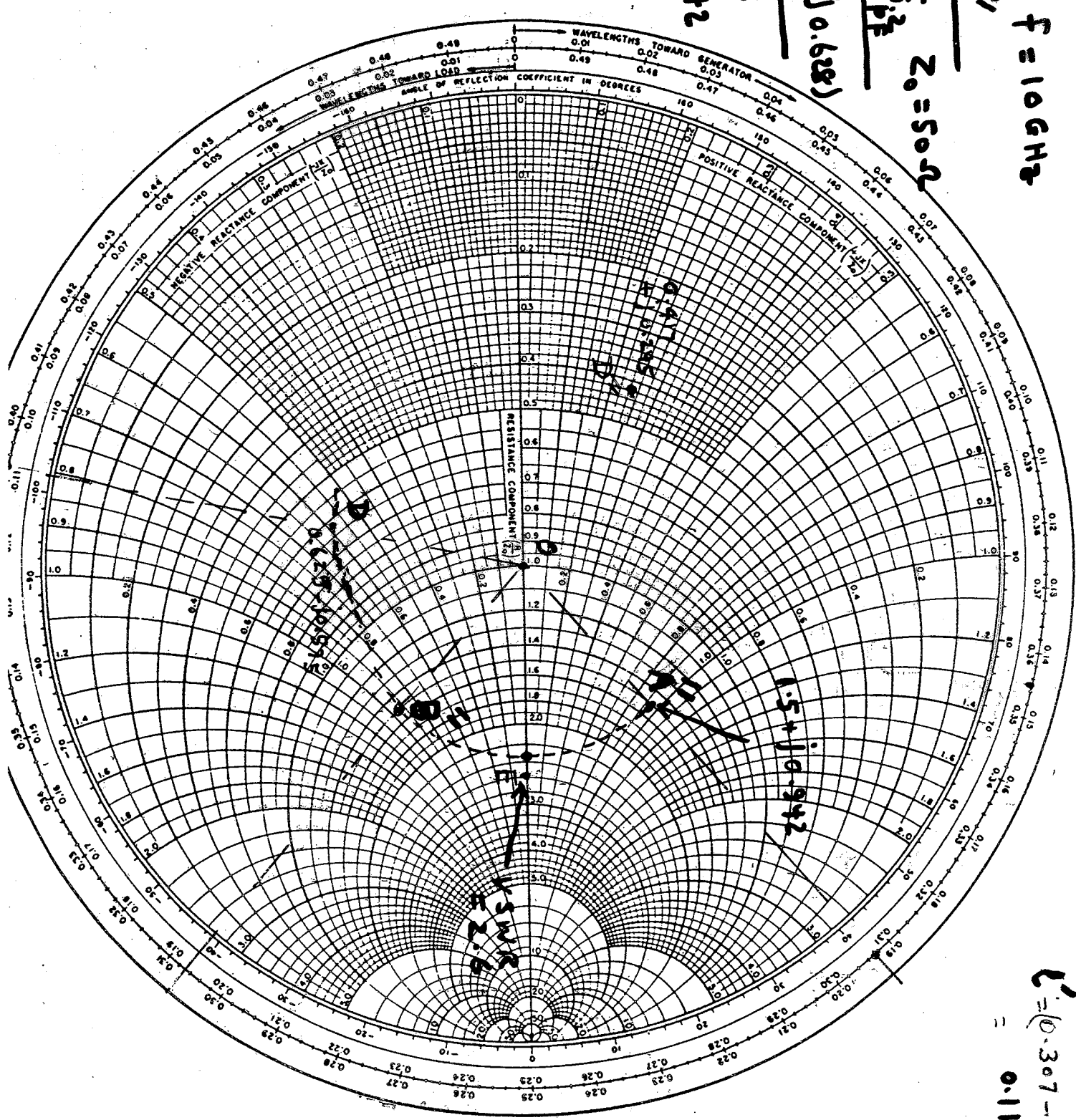

$$L = (0.307 - 0.193) \lambda$$

$$= 0.114 \lambda$$