

## Notes on Chapter 4

General Properties of Lossless Networks (see pp. 177, 178 - Text)

$$\begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_N \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \dots & S_{1N} \\ S_{21} & \dots & \dots & S_{2N} \\ \dots & \dots & \dots & \dots \\ S_{N1} & \dots & \dots & S_{NN} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ \vdots \\ a_i \\ \vdots \\ 0 \end{bmatrix}$$

$$b_1 = S_{1i} a_i$$

$$b_2 = S_{2i} a_i$$

$$b_N = S_{Ni} a_i$$

$$b_1 b_1^* + \dots + b_N b_N^* = (S_{1i} S_{1i}^* + S_{2i} S_{2i}^* + \dots + S_{Ni} S_{Ni}^*) a_i a_i^*$$

$$\sum_{k=1}^N S_{ki} S_{ki}^* = 1 \quad \text{for any } i \quad \begin{matrix} (4.53a) \\ \text{p. 178} \\ i = 1, 2, \dots \end{matrix}$$

Property 1: Sum of the squares of the S-parameters in any column = 1

II. Property 2 Let us feed power to any 2 ports say i, j

$$b_1 = S_{1i} a_i + S_{1j} a_j$$

$$b_N = S_{Ni} a_i + S_{Nj} a_j$$

$$b_1 b_1^* + \dots + b_N b_N^* = S_{1i} S_{1i}^* a_i a_i^* + S_{1j} S_{1j}^* a_j a_j^* + S_{Ni} S_{Ni}^* a_i a_i^* + S_{Nj} S_{Nj}^* a_j a_j^* + S_{1i} S_{1j}^* a_i a_j^* + S_{Ni} S_{Nj}^* a_i a_j^* + \dots = a_i a_i^* + a_j a_j^*$$

$$\left( \sum_{k=1}^N S_{ki} S_{ki}^* \right) a_i a_i^* + \left( \sum_{k=1}^N S_{kj} S_{kj}^* \right) a_j a_j^* + \left( \sum_{k=1}^N S_{ki} S_{kj}^* \right) a_i a_j^* + \left( \sum_{k=1}^N S_{ki}^* S_{kj} \right) a_i^* a_j = a_i a_i^* + a_j a_j^* \quad (1)$$

Since  $a_i$  and  $a_j$  are arbitrary both for magnitude and phase, we can select them in phase

From Eq. (1) we can write  $\sum_{k=1}^N S_{ki} S_{kj}^* + S_{ki}^* S_{kj} = 0$


We can also select  $a_i, a_j$  to be 90° out of phase say  $a_j = j a_i$  in which case we can write

$$\text{so } \sum_{k=1}^N S_{ki} S_{kj}^* = \sum_{k=1}^N S_{ki} S_{kj} - S_{ki}^* S_{kj} = 0 \quad (4.53b) \quad \text{for } i \neq j$$

Ex.1 For a two-port circuit, calculate (see also Ex. 4.5 Text p.179)

- the reflection coefficient  $\Gamma_1$  at port ① if port ② is connected to a mismatched load of reflection  $\Gamma_L$
- the power delivered to this mismatched load in terms of input power  $a_1 a_1^*$

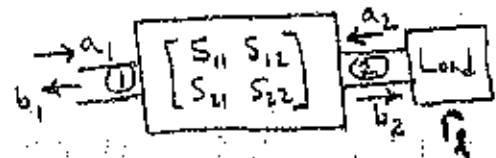Solution a. The circuit diagram is given in Fig.1



$$b_1 = S_{11} a_1 + S_{12} a_2 \quad (1)$$

$$b_2 = S_{21} a_1 + S_{22} a_2 \quad (2)$$

For the mismatched load of reflection  $\Gamma_L$ , note that  $a_2 = \Gamma_L b_2$  (3)

Eq. (3) can be rewritten as  $b_2 = \frac{a_2}{\Gamma_L}$  (4)

Substituting Eq. (4) into Eq. (2) and rearranging terms

$$S_{21} a_1 = \left( \frac{1}{\Gamma_L} - S_{22} \right) a_2 = \left( \frac{1 - S_{22} \Gamma_L}{\Gamma_L} \right) a_2 \quad (5)$$

Substitute Eq. (5) into Eq. (1), we can write

Eq. 11.300 p. 537 2nd Ed.  
13.36 p. 300 4th Ed

$$\Gamma_1 = \frac{b_1}{a_1} = \left[ S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right] \quad (6)$$

b. Power delivered to the mismatched load =  $b_2 b_2^* - a_2 a_2^* = b_2 b_2^* (1 - |\Gamma_L|^2)$  (7)

Expressing Eq. (2) in terms of  $a_1$ , we can write (by using Eq. (5))

$$b_2 = \left[ S_{21} + \frac{S_{22} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right] a_1 = \left[ \frac{S_{21}}{1 - S_{22} \Gamma_L} \right] a_1 \quad (8)$$

Combining Eqs. (7) and (8), we can write

$$\frac{\text{Power delivered to the mismatched load}}{\text{Power input } a_1 a_1^*} = \left| \frac{S_{21}}{1 - S_{22} \Gamma_L} \right|^2 (1 - |\Gamma_L|^2) \quad (9)$$

Ex.2 Calculate the quantities a. and b. in Ex.1 for a circuit for which the S-parameters are  $\begin{bmatrix} 0.1 & 0.8j \\ 0.8j & 0.2 \end{bmatrix}$  and  $\Gamma_L = 0.333$

Solution

a. From Eq. (6),  $\Gamma_1 = \left[ S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right] = -0.1285$

Return loss RL =  $-20 \log \left| \frac{b_1}{a_1} \right| = 17.82 \text{ dB}$

b. From Eq. (9),  $\frac{\text{power delivered to the load}}{\text{input power } a_1 a_1^*} = 0.654$

i.e. 65.4% of the input power can be delivered to this mismatched load

c. For a perfectly matched load connected to the output port ②,  $\Gamma_L = 0$   
and  $\frac{\text{power delivered to this perfectly matched load}}{\text{input power}} = |S_{21}|^2 = (0.8)^2 = 0.64$

d. Max power delivered to the load if  $\Gamma_L = S_{22}^* \Rightarrow 0.667 a_1 a_1^*$

Stephen F. Adam

Microwave Theory and Applications

Prentice-Hall, Inc. 1969

### 3.2 FLOW GRAPH REPRESENTATION OF MICROWAVE NETWORKS

#### 3.2.1 SCATTERING PARAMETERS

In analyzing microwave transmission line problems, one would like to find some generalized parameters to write for a network in question—parameters which can be measured with reasonable simplicity, even in microwave frequencies. Analysis of the energy flow through a two-port network is one way to do this.

A simple two-port network can be shown as a "black box" (Fig. 3-2-1).



Fig. 3-2-1. Simple two-port network.

We are not interested in knowing what is built into the black box, but only in what it will do to a signal applied to either port. For example, if the black box contains an amplifier and we would like to know the various parameters, we can measure the input impedance while the output is short- and open-circuited and measure the output impedance while the input is short- and open-circuited. This will give us some of the commonly known  $z$ ,  $y$ , and  $h$  parameters. However, this technique has some shortcomings at higher frequencies. Some devices may oscillate (probably at some frequency different from the measurement frequency) or have some unwanted, parasitic effects if they are terminated with a short or open circuit.

The ideal case would be to express a set of parameters when the input and output ports are terminated with their own characteristic impedances at all frequencies. The scattering ( $s$ ) parameters are the set of parameters that are measured under such conditions. An added, inherent advantage of these

parameters is that they describe the signal flow within the network. Kurokawa,<sup>1</sup> Penfield,<sup>2</sup> and Youla<sup>3</sup> studied generalized scattering parameters. Hunton<sup>4</sup> used signal flow to analyze microwave-measurement techniques with 2 parameters and expressed them with flow graphs, since these parameters relate directly to the signal flow. Kuhn<sup>5</sup> used a topographical approach for resolving these flow graphs.

#### 3.2.2 BASIC FLOW GRAPHS

A flow graph can be drawn to analyze the energy flow of a two-port network. (See Fig. 3-2-2.) A flow graph has two nodes for each port, one for

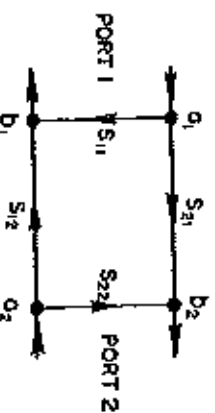


Fig. 3-2-2. Flow graph of a two-port network.

the entering (incident) wave and the other for the leaving (reflected) wave of that port. The incident node is the  $a$  node and the reflected node is the  $b$  node. In our example of the simple two-port network, when the incident wave enters the device at port 1, part of it will be returned through the  $S_{11}$  path and  $b_1$  node. The remaining part of the incident wave goes through the  $S_{12}$  path and leaves the network through the  $a_2$  node. If a device that has some reflections is connected to port 2, and if it will reflect part of the wave leaving  $b_2$ , this reflection will reenter the network through the  $S_{21}$  node. Then, part of that may be reflected, passing along the  $S_{22}$  path and leaving the network

<sup>1</sup> Kurokawa, K., *IEEE Trans-AFAP*, March 1965, p. 194.

<sup>2</sup> Penfield, H., Jr., "Noise in Negative Resistance Amplifiers," *IRE Trans-CT*, Vol.

CT-7, June 1960, pp. 166-70.

<sup>3</sup> Penfield, H., Jr., "A Classification of Lossless Three Ports," *IRE Trans-CT*, Vol. CT-9, September 1962, pp. 215-23.

<sup>4</sup> Youla, D. C., "On Scattering Matrices Normalized to Complex Port Numbers," *Proc. IRE*, Vol. 49, July 1961, p. 122.

<sup>5</sup> Hunton, J. K., "Analysis of Microwave Measurement Techniques by Means of Signal Flow Graphs," *Trans. IRE*, Vol. MTT-8, March 1960, pp. 206-12.

<sup>6</sup> Kuhn, Nicholas, "Simplified Signal Flow Graph Analysis," *The Microwave Journal*, November 1963, pp. 59-66.

through the  $b_2$  node. The other part of the wave passes through the  $s_{11}$  path and leaves the circuit through the  $b_1$  node.

Following the arrows in the flow graph, we can write the following equations.

$$b_1 = a_2 s_{11} + a_2 s_{12} \quad (3.2-1)$$

$$b_2 = a_1 s_{21} + a_2 s_{22} \quad (3.2-2)$$

By analyzing these equations, one can see that these parameters can be easily measured under certain conditions.

Assume that there is no signal entering at  $a_2$  node (this can be achieved by terminating port 2 with its characteristic impedance). Then Eqs. (3.2-1) and (3.2-2) become

$$b_1 = a_1 s_{11} \quad (3.2-3)$$

$$b_2 = a_2 s_{21} \quad (3.2-4)$$

By reversing the network, that is, terminating port 1 with its characteristic impedance and applying the signal to port 2, Eqs. (3.2-1) and (3.2-2) will become

$$b_1 = a_2 s_{12} \quad (3.2-5)$$

$$b_2 = a_1 s_{22} \quad (3.2-6)$$

since  $a_1 = 0$ .

Expressing the scattering parameters from Eqs. (3.2-3), (3.2-4), (3.2-5), and (3.2-6), we can write the following:

$$s_{11} = \frac{b_1}{a_1} \quad \left| \quad a_2 = 0 \quad (3.2-7) \right.$$

$$s_{21} = \frac{b_2}{a_2} \quad \left| \quad a_2 = 0 \quad (3.2-8) \right.$$

$$s_{12} = \frac{b_1}{a_2} \quad \left| \quad a_1 = 0 \quad (3.2-9) \right.$$

$$s_{22} = \frac{b_2}{a_2} \quad \left| \quad a_1 = 0 \quad (3.2-10) \right.$$

Furthermore, these expressions show the means of measuring these parameters:  $s_{11}$  can be measured when port 2 is terminated with its characteristic impedance and only the ratio of reflected wave and incident wave has to be measured at port 1. We saw that in Chap. 2, where reflection coefficients were discussed. This means that  $s_{11}$  is really the input-reflection coefficient of the device.

$s_{22}$  is measured in exactly the same manner as  $s_{11}$ , except that port 1 is terminated with its characteristic impedance and the signal is applied to port 2;  $s_{21}$  is the output-reflection coefficient of the network.

$s_{12}$  is measured when port 2 is terminated with its characteristic imped-

ance and the signal is applied into port 1. The ratio of the signals measured at the  $b_2$  and  $a_1$  nodes (voltage between output and input ports) defines the value of  $s_{21}$ . Simply,  $s_{21}$  is the forward transducer coefficient.

$s_{12}$  is measured by reversing the ports and terminating port 1 in its characteristic impedance and applying the signal to port 2. The ratio of the signals appearing at the  $b_1$  and  $a_2$  nodes will define the value of the  $s_{12}$  parameter.  $s_{12}$  is the reverse transducer coefficient of the network.

These parameters are vector values, and they have both magnitude and phase information.

It is much easier to make swept-frequency, wideband measurements of  $s$  parameters than of  $h$ ,  $y$ , and  $z$  parameters, especially above 100 MHz. To use the many design techniques defined in terms of  $h$ ,  $y$ , and  $z$  parameters, it is quite simple to convert data to any of these parameters from the scattering parameters. Table (3.2-1) shows the conversion equations for each of these parameters and the scattering parameters.

Table 3.2-1. Conversion Equations Between  $h$ ,  $z$ ,  $y$ , and  $s$  Parameters

|                                                                                                            |                                                                                                                |
|------------------------------------------------------------------------------------------------------------|----------------------------------------------------------------------------------------------------------------|
| $s_{11} = \frac{(Z_{11} - Y_{22}^{-1}) + Z_{12} Y_{21}^{-1}}{(Z_{11} + Y_{22}^{-1}) - Z_{12} Y_{21}^{-1}}$ | $z_{11} = \frac{(1 + s_{11} Y_{22}^{-1}) + s_{12} Y_{21}^{-1}}{(1 - s_{11} Y_{22}^{-1}) - s_{12} Y_{21}^{-1}}$ |
| $s_{21} = \frac{2 Z_{12} Y_{21}^{-1}}{(Z_{11} + Y_{22}^{-1}) - Z_{12} Y_{21}^{-1}}$                        | $z_{21} = \frac{2 s_{21} Y_{21}^{-1}}{(1 - s_{11} Y_{22}^{-1}) - s_{12} Y_{21}^{-1}}$                          |
| $s_{12} = \frac{(Y_{11}^{-1} - Z_{22}) + Y_{12} Z_{21}}{(Y_{11}^{-1} + Z_{22}) - Y_{12} Z_{21}}$           | $y_{11} = \frac{(1 + s_{12} Z_{22}) + s_{11} Y_{12}^{-1}}{(1 - s_{12} Z_{22}) - s_{11} Y_{12}^{-1}}$           |
| $s_{22} = \frac{(Y_{11}^{-1} - Z_{22}) + Y_{12} Z_{21}}{(Y_{11}^{-1} + Z_{22}) - Y_{12} Z_{21}}$           | $y_{21} = \frac{(1 + s_{12} Z_{22}) + s_{21} Y_{12}^{-1}}{(1 - s_{12} Z_{22}) - s_{21} Y_{12}^{-1}}$           |
| $s_{11} = \frac{(h_{11} - Y_{22}^{-1}) + h_{12} Y_{21}^{-1}}{(h_{11} + Y_{22}^{-1}) - h_{12} Y_{21}^{-1}}$ | $h_{11} = \frac{(1 + s_{11} Y_{22}^{-1}) + s_{12} Y_{21}^{-1}}{(1 - s_{11} Y_{22}^{-1}) - s_{12} Y_{21}^{-1}}$ |
| $s_{21} = \frac{2 h_{12} Y_{21}^{-1}}{(h_{11} + Y_{22}^{-1}) - h_{12} Y_{21}^{-1}}$                        | $h_{21} = \frac{2 s_{21} Y_{21}^{-1}}{(1 - s_{11} Y_{22}^{-1}) - s_{12} Y_{21}^{-1}}$                          |
| $s_{12} = \frac{(h_{21}^{-1} - Y_{11}) + h_{22} Y_{12}}{(h_{21}^{-1} + Y_{11}) - h_{22} Y_{12}}$           | $h_{12} = \frac{(1 + s_{12} Y_{11}) + s_{11} h_{22}}{(1 - s_{12} Y_{11}) - s_{11} h_{22}}$                     |
| $s_{22} = \frac{(h_{21}^{-1} - Y_{11}) + h_{22} Y_{12}}{(h_{21}^{-1} + Y_{11}) - h_{22} Y_{12}}$           | $h_{22} = \frac{(1 + s_{12} Y_{11}) + s_{21} h_{22}}{(1 - s_{12} Y_{11}) - s_{21} h_{22}}$                     |

### 3.2.3 TOPOGRAPHICAL APPROACH TO RESOLVE FLOW GRAPHS:

It was emphasized in the previous section that the scattering parameters are descriptive of signal flow; consequently, signal flow graphs can easily show the scattering parameters as signal flow elements. A two-port network has been described already. The flow graph of a three-port network can be realized in the same manner. Figure 3.2-3 shows such a flow graph.

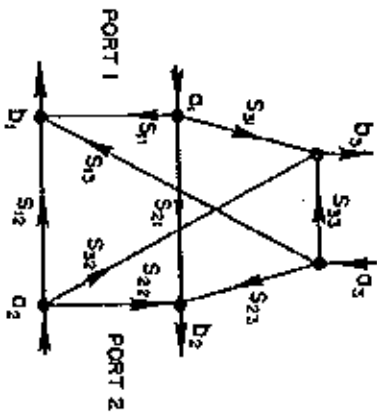


Fig. 3.2-3. Flow graph of a three-port network.

Nodes that represent waves entering and leaving the network are designated  $a_n$  and  $b_n$ , respectively. There is always a connecting line from an  $a_n$  node to a  $b_n$  node within the network flow graph, and these connecting lines always go from  $a$  to  $b$ . They are associated with an  $s$  parameter.

Networks can be cascaded one after the other, and their flow graphs can be cascaded similarly, as in Fig. 3.2-4, which shows two two-port networks cascaded in this way. It is interesting to note that node  $b_2$  and  $a_1$  are synonymous;  $a_1$  and  $b_1$  are also synonymous. In a flow graph, synonymous nodes can be connected with an arrow having a value of "1," meaning that there is no electrical length between them. These two groups of nodes should not be considered identical; the direction of the arrow between  $b_2$  and  $a_1$  is important. Basic transmission line elements can be divided into one-port, two-port, and multiport groups. Every port will have two nodes: one where the wave enters ( $a$ ) and the other where the wave leaves that port ( $b$ ).

Flow graph representation of some one-port networks is shown in Fig.

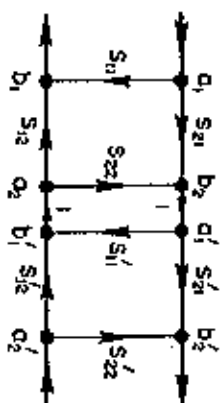


Fig. 3.2-4. Two two-port networks cascaded.

3.2-5.  $M$  is the meter reading of an indicator, as shown;  $K$  represents the law of the detector and does not change with power level so long as the detector law does not change with power level. Furthermore,  $M$  includes the effect of the transmission loss due to the detector's reflection  $\sqrt{1 - \rho_d^2}$ . Flow graphs of some two-port networks are shown in Fig. 3.2-6. These flow graphs are only the most-used elements. Remember that  $T$  stands for

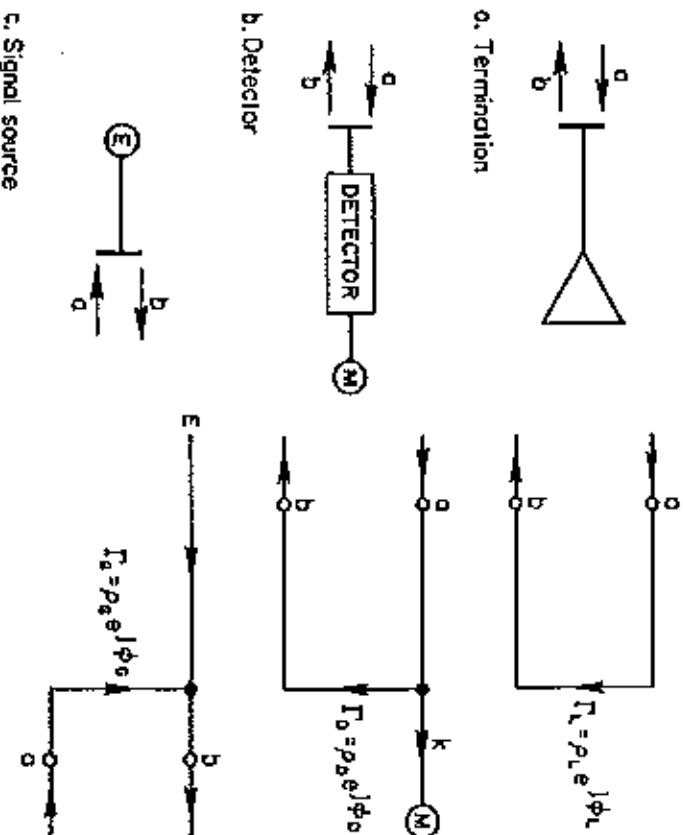


Fig. 3.2-5. Flow graph representation of some one-port networks.

<sup>1</sup> Kuhn, "Simplified Signal Flow Graph Analysis," *Microwave Journal*, November 1963.


Figure 3.2-18 shows the flow graph of a two-port network driven with a signal source and terminated with a load. One path goes from the generator to node  $b_1$ ; its value is  $s_1$ . There are two paths from the generator to node  $b_2$ . The values of these paths are  $s_2$  and  $s_2\Gamma_1s_1$ .

If a path starts and finishes in the same node, it is called a "loop," rather than a path. A "first-order loop" is a path coming to a closure with no node passed more than once. The value of the loop is calculated as the value of the path, or the product of the value of all branches encountered en route.


A "second-order loop" is defined as two first-order loops not touching each other at any node. The value of a second-order loop is the product of



Apply rule No. 4

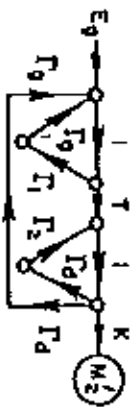

Apply rule No. 1

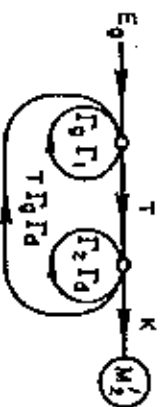

Apply rule No. 3



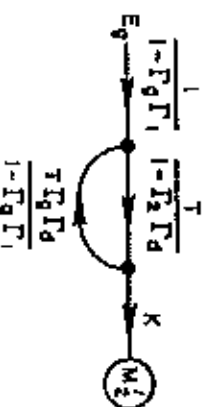



Fig. 3.2-17. Reduction of the measurement flow graph.

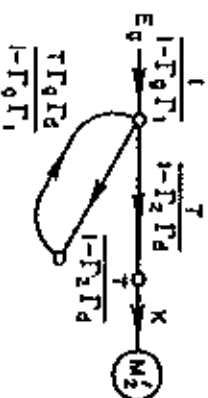

Apply rule No. 4

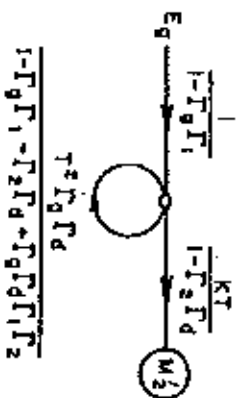

Apply rule No. 1

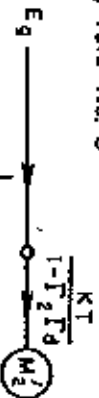

Apply rule No. 3

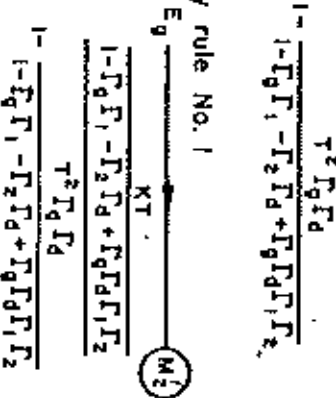


Fig. 3.2-17 (continued)

the values of the two first-order loops. Third- and higher-order loops are three or more first-order loops not touching each other at any point. Their values are calculated in the same manner as described above for the second-order loop, that is, by multiplying the coefficients of branches encountered.

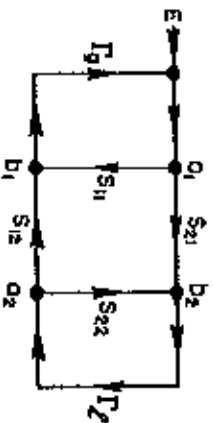


Fig. 3.2-18. Flow graph of a two-port network with a signal source and a load.

For example, in Fig. 3.2-18, there are three first-order loops ( $S_{21}T$ ,  $S_{21}T_L$ , and  $T_S S_{11} T_S S_{21}$ ) and one second-order loop ( $T_S S_{21} S_{11} T_S$ ).

The nontouching-loop rule<sup>4</sup> can be applied to solve any flow graph. The equation in symbolic form is

$$T = \frac{P_1 [1 - \Sigma L(1)^m + \Sigma L(2)^m - \Sigma L(3)^m + \dots] + P_2 [1 - \Sigma L(1)^m + \Sigma L(2)^m - \dots] + P_3 [1 - \Sigma L(1)^m + \dots] + \dots}{1 - \Sigma L(1) + \Sigma L(2) - \Sigma L(3) + \dots}$$

where  $\Sigma L(1)$  stands for the sum of all first-order loops,  $\Sigma L(2)$  is the sum of all second-order loops, and so on;  $P_1$ ,  $P_2$ ,  $P_3$ , etc., stand for the values of all paths that can be followed from the independent variable, in most cases the generator, to the node whose value is desired;  $\Sigma L(1)^m$  denotes the sum of those first-order loops which do not touch the path of  $P_1$  at any node;  $\Sigma L(2)^m$  denotes then the sum of those second-order loops which do not touch the path of  $P_1$  at any point;  $\Sigma L(1)^m$  consequently denotes the sum of those first-order loops which do not touch the path of  $P_2$  at any point. Each path is multiplied by the factor in parentheses which involves all the loops of all orders that the path does not touch.  $T$  represents the ratio of the dependent variable in question and the independent variable.

The example shown in Fig. 3.2-18 can be calculated for two dependent variables. One is the reflection coefficient of the two-port network  $b_1/a_1$ , and the second is the transmission coefficient  $b_2/E$ . In the first case, when  $b_1/a_1$  is to be found, the generator is not involved, so it should be neglected. The solution is

$$\frac{b_1}{a_1} = \frac{\Sigma L(1 - S_{21}^2 T_L) + S_{21} T_S S_{21}}{1 - S_{21}^2 T_L}$$

$S_{21}$  is the first path,  $P_1$ , which has to be multiplied with  $1 - \Sigma L(1)^m$ .  $S_{21} T_L$  is

<sup>4</sup> Lorens, C. S., "A Proof of the Nontouching Loop Rule for the Solution of Linear Equations by Flow Graphs," *Res. Lab. of Electronics, M.I.T., Cambridge, Mass., Quarterly Progress Report, January 1956*, pp. 97-102.

<sup>5</sup> Hopp, W. W., "Lecture Notes on Signal Flow Graphs," from *Analysis of Transistor Circuits*, Extension Course, University of California, Catalog 834AB.

the only first-order loop not touching the  $P_1$  path; higher-order loops not touching the  $P_1$  path do not exist. Path number two,  $P_2$ , will be  $S_{21} T_S S_{21}$ ; since there are no first-order or any higher-order loops not touching this path, it will be multiplied by 1. The denominator shows the only first-order loop,  $S_{21} T_L$ , subtracted from unity.

The entire flow graph, including the generator, is needed to write the solution for the transmission coefficient.

$$\frac{b_2}{E} = \frac{S_{21}}{1 - T_S S_{11} - S_{21}^2 T_L - T_S S_{11} T_S S_{21} + T_S S_{21} S_{11} T_S}$$

Because there is only one possible path from  $E$  to the  $b_2$  node, and there are no loops not touching this path, only  $S_{21}$  will stay in the numerator. It can be seen that there are three first-order loops and a second-order loop in the denominator.

It would be interesting to see the attenuation measurement flow graph discussed in the topographical approach as another example. Figure 3.2-15 shows the flow graphs in question. Equations have to be written for  $M_1/E_1$  and  $M_2/E_2$ ; the values of  $M_1/E_1$  and  $M_2/E_2$  have already been found analytically.

$$\frac{M_1}{E_1} = \frac{k}{1 - T_S T_L}$$

since  $k$  is the only path and  $T_S T_L$  is the only loop.

$$\frac{M_2}{E_2} = \frac{kT}{1 - T_S T_L - T_S T_L T_L + T_S^2 T_L^2 T_L}$$

Again the only path is  $kT$ , and all loops touch this path. Three first-order loops and a second-order loop can be found in the denominator.

It is worth mentioning that third- and higher-order loops can usually be neglected after careful analysis of the values of various coefficients in question. This is because values smaller than unity multiplied with each other become even smaller. This point will be emphasized later in the text.

#### Nontouching-Loop Rule

$$T = \frac{P_1 (1 - \Sigma L(1)^m + \Sigma L(2)^m - \Sigma L(3)^m + \dots) + P_2 (1 - \Sigma L(1)^m + \Sigma L(2)^m - \dots) + P_3 (1 - \Sigma L(1)^m + \dots) + \dots}{1 - \Sigma L(1) + \Sigma L(2) - \Sigma L(3) + \dots}$$

$\Sigma L(1)$  Sum of all first-order loops

$\Sigma L(2)$  Sum of all second-order loops

$P_1, P_2, P_3$  Values of paths corresponding to indices

$\Sigma L(1)^m$  Sum of those first-order loops which do not touch  $P_1$

$\Sigma L(2)^m$  Sum of those second-order loops which do not touch  $P_1$


$T$  Sum of those  $n$ -order loops which do not touch  $P_n$  path

Ratio of dependent variable in question and independent variable



Similar to  
Prob. 4.11  
Text Two  
p. 211

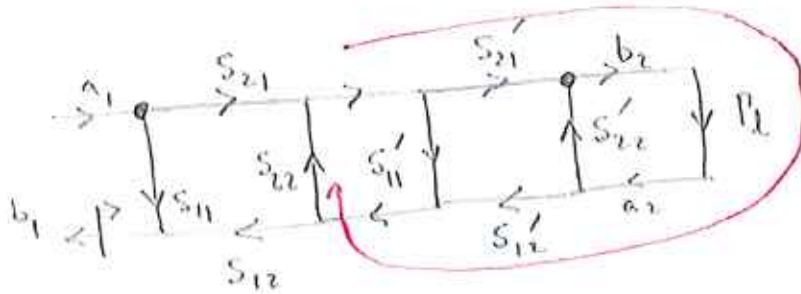2 - ports in cascade (see p. 91 of the handout)  
e.g. a 2-stage amplifier



calculate  $\frac{b_1}{a_1}$

Paths between  $b_1$  and  $a_1$

|       | Value                               | First order Neutralizing Loops $L(1)$                     | 2nd order Neutralizing Loop $L(2)$ |
|-------|-------------------------------------|-----------------------------------------------------------|------------------------------------|
| $P_1$ | $S_{11}$                            | $S'_{11} S_{22}, P_L S'_{22}, S_{22} S'_{21} P_L S'_{12}$ | $(S'_{11} S_{22})(P_L S'_{22})$    |
| $P_2$ | $S_{21} S'_{11} S'_{12}$            | $P_L S'_{22}$                                             | 0                                  |
| $P_3$ | $S_{21} S'_{21} P_L S'_{12} S_{12}$ | —                                                         | —                                  |

$$P_1 = \frac{b_1}{a_1} = S_{11} + \frac{S'_{21} S'_{11} S_{12} [1 - P_L S'_{22}] + S_{21} S'_{21} P_L S'_{12} S_{12}}{1 - \{ S'_{11} S_{22} + P_L S'_{22} + S_{22} S'_{21} P_L S'_{12} \} + (S'_{11} S_{22} \times P_L S'_{22})}$$

Second order loop

$S_{11}$  | load circuit

$$P_1 |_{a_2=0} \Rightarrow P_1 = \frac{S_{21} S'_{11} S_{12}}{1 - S'_{11} S_{22}}$$

$$\frac{b_2}{a_1} = \frac{S_{21} S'_{21} P_L S'_{12} S_{12}}{1 - (S'_{11} S_{22} + P_L S'_{22} + S_{22} S'_{21} P_L S'_{12} + S'_{11} S_{22} \times P_L S'_{22})}$$

$$S_{21T} \rightarrow \frac{b_2}{a_1} \Big|_{\text{if } P_L=0} \Rightarrow \frac{S_{21} S'_{21}}{1 - S'_{11} S_{22}} \Rightarrow \frac{S_{21}^A S_{21}^B}{1 - S_{11}^B S_{22}^A}$$


Power delivered to the load ( $P_L$ ) =  $b_2 b_2^* (1 - |P_L|)$

Fractional power reflected =  $\frac{b_1 b_1^*}{a_1 a_1^*}$

Two 2-ports in cascade

$$S_{12T} = \left. \frac{b_1}{a_2} \right|_{a_1=0} = \frac{S_{12} S_{11}'}{1 - S_{11}' S_{22}}$$

$$S_{22T} = \left. \frac{b_2}{a_2} \right|_{\substack{a_1=0 \\ P_{in}=0}} = S_{22}' + \frac{S_{12}' S_{22} S_{21}'}{1 - S_{11}' S_{22}} \quad \text{when } P_S = 0$$

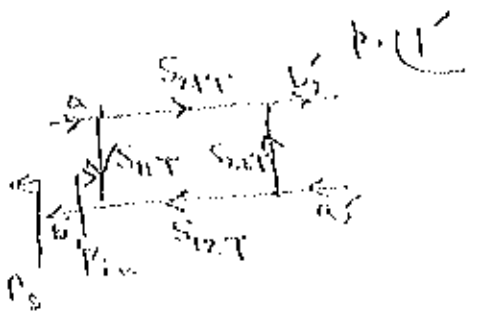


In computing the  $S_{11T}$  and  $S_{21T}$  for the two 2-port circuit in cascade, the equivalent  $S$ -parameters of the combined 2-port circuit can be written as

$$[S] = \begin{bmatrix} S_{11T} & S_{12T} \\ S_{21T} & S_{22T} \end{bmatrix} = \begin{bmatrix} S_{11}' & \frac{S_{21}' S_{11}' S_{12}}{1 - S_{11}' S_{22}} \\ \frac{S_{21} S_{21}'}{1 - S_{11}' S_{22}} & S_{22}' + \frac{S_{12}' S_{22} S_{21}'}{1 - S_{11}' S_{22}} \end{bmatrix}$$

A handicap of the  $S$ -parameters is that for cascaded circuits, there is no easy way to combine the  $S$ -parameters of the individual circuits. This handicap is avoided by introducing  $A, B, C, D$  parameters <sup>in section 4.4 of the text</sup> which are not easy to measure (because of the difficulty of measuring voltages and currents) but do allow multiplication of  $A, B, C, D$  matrices of the circuits in cascade.

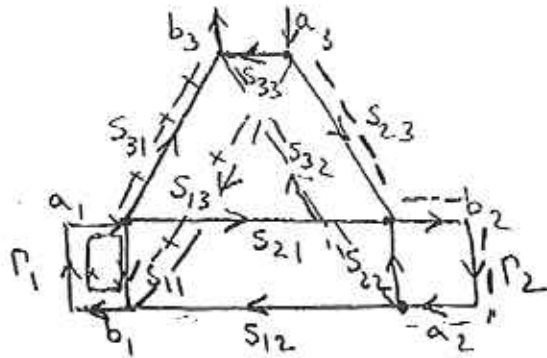Example of a 3 port network (see also p.90 of the handout from Adam's bootc) (2)

Find the reflection coefficient at port 3 if ports 1 and 2 are mismatched with reflection coefficients  $\Gamma_1$  and  $\Gamma_2$ , respectively.



Do not draw any branches for which the value is zero

Paths between  $a_3$  and  $b_3$

|                | Value                                    | First order Non touching loops $L(1)$                                | Second order Non touching loops $L(2)$ |
|----------------|------------------------------------------|----------------------------------------------------------------------|----------------------------------------|
| $\equiv$ $P_1$ | $S_{33}$                                 | $\Gamma_1 S_{11}, \Gamma_2 S_{22}, \Gamma_1 S_{21}, \Gamma_2 S_{12}$ | $(\Gamma_1 S_{11})(\Gamma_2 S_{22})$   |
| $---$ $P_2$    | $S_{23} \Gamma_2 S_{32}$                 | $\Gamma_1 S_{11}$                                                    | $-$                                    |
| $-x-$ $P_3$    | $S_{13} \Gamma_1 S_{31}$                 | $\Gamma_2 S_{22}$                                                    | $-$                                    |
| $P_4$          | $S_{23} \Gamma_2 S_{12} \Gamma_1 S_{31}$ | $-$                                                                  | $-$                                    |
| $P_5$          | $S_{13} \Gamma_1 S_{21} \Gamma_2 S_{32}$ | $-$                                                                  | $-$                                    |

All First order loops touching or nontouching  $L(1)$


$$\Gamma_1 S_{11}, \Gamma_2 S_{22}, \Gamma_1 S_{21}, \Gamma_2 S_{12}$$

All second order loops touching or nontouching  $L(2)$

$$(\Gamma_1 S_{11})(\Gamma_2 S_{22})$$

$$\frac{b_3}{a_3} = S_{33} + \frac{S_{23} \Gamma_2 S_{32} (1 - \Gamma_1 S_{11}) + S_{13} \Gamma_1 S_{31} (1 - \Gamma_2 S_{22}) + S_{23} \Gamma_2 S_{12} \Gamma_1 S_{31} + S_{13} \Gamma_1 S_{21} \Gamma_2 S_{32}}{1 - (\Gamma_1 S_{11} + \Gamma_2 S_{22} + \Gamma_1 S_{21} \Gamma_2 S_{12}) + (\Gamma_1 S_{11})(\Gamma_2 S_{22})}$$

Similar to Prob  
4.17  
B Text

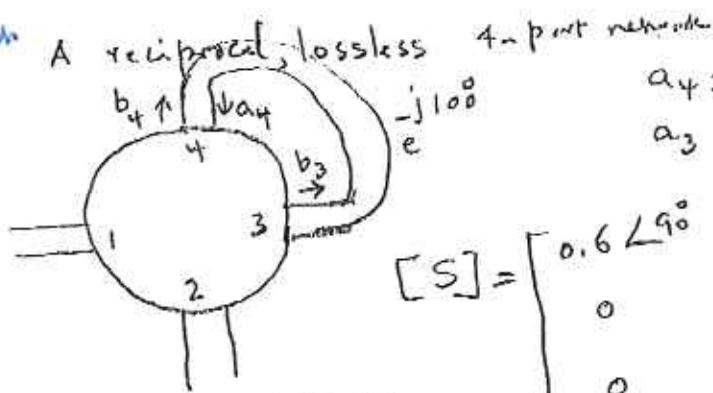


$$a_4 = b_3 e^{-j100^\circ}$$

$$a_3 = b_4 e^{j100^\circ}$$

$$[S] = \begin{bmatrix} 0.6 \angle 90^\circ & 0 & 0 & 0.8 \angle 0^\circ \\ 0 & 0.7 \angle 45^\circ & 0.7 \angle -45^\circ & 0 \\ 0 & 0.7 \angle -45^\circ & 0.7 \angle 45^\circ & 0 \\ 0.8 \angle 0^\circ & 0 & 0 & 0.6 \angle 90^\circ \end{bmatrix}$$

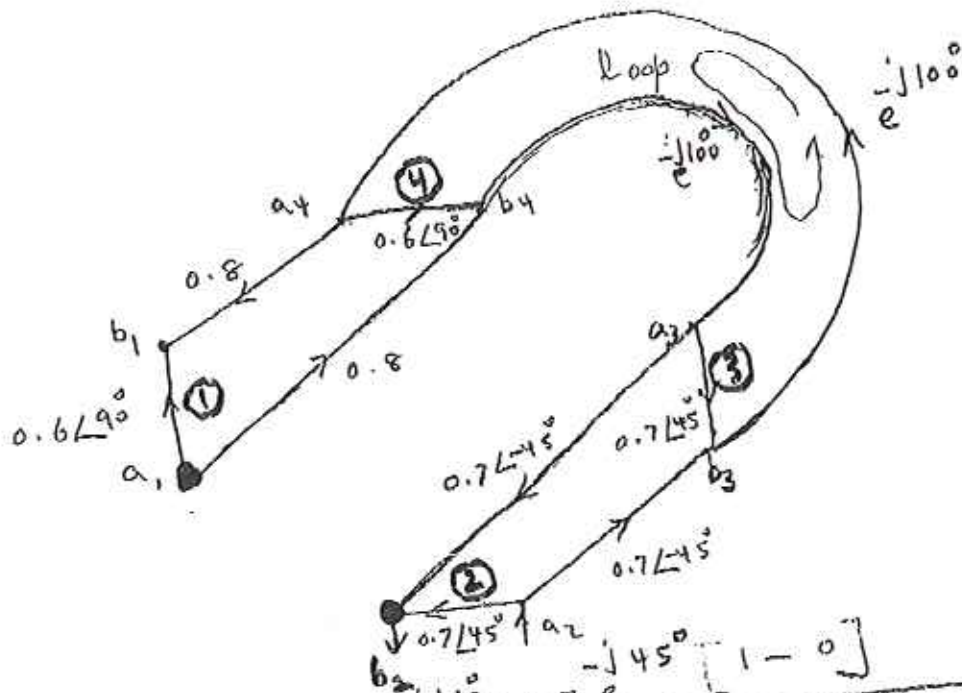Note that ports 3 and 4 are connected with a lossless matched transmission line of electrical length  $100^\circ$



$$\frac{b_2}{a_1} = \frac{\text{path } P_1 = 0.8 \times e^{-j100^\circ} \times 0.7 e^{j45^\circ} \times (-j100)}{1 - [(0.6 e^{j90^\circ})(e^{-j100^\circ})(0.7 e^{j45^\circ})(e^{-j100^\circ})]}$$

$$= \frac{0.56 e^{-j145^\circ}}{1 - 0.42 e^{-j65^\circ}}$$

$$\frac{b_2 b_2^*}{a_1 a_1^*} = \frac{(0.56)^2}{(1 - 0.42 e^{-j65^\circ})(1 - 0.42 e^{j65^\circ})} = \frac{(0.56)^2}{1 + (0.42)^2 - 2 \times 0.42 \cos 65^\circ} = \boxed{0.4648}$$


$$IL = -10 \log(0.4648) = -3.33 \text{ dB}$$

$$P_o = 2.3 \text{ W (Typ.) } @ 10 \text{ GHz}$$

$$G_p = 5 \text{ dB (Typ.) } @ 10 \text{ GHz}$$


**MITSUBISHI GaAs POWER FET**  
**MGF-X34M**  
**INTERNALLY MATCHING, FLIP-CHIP MOUNTING**

$S_{11}, S_{22}$  vs.  $f$

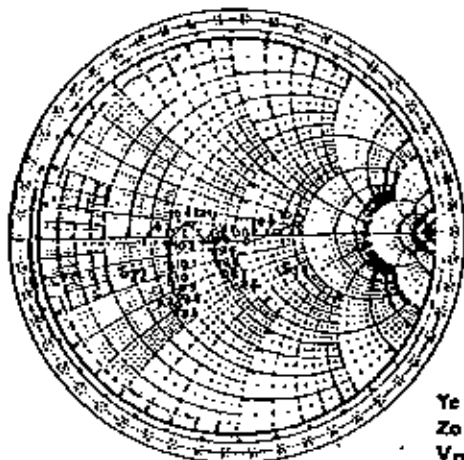

$T_c = 25^\circ\text{C}$   
 $Z_o = 50 \Omega$   
 $V_{DS} = 9 \text{ V}$   
 $I_D = 900 \text{ mA}$

$S_{12}, S_{21}$  vs.  $f$

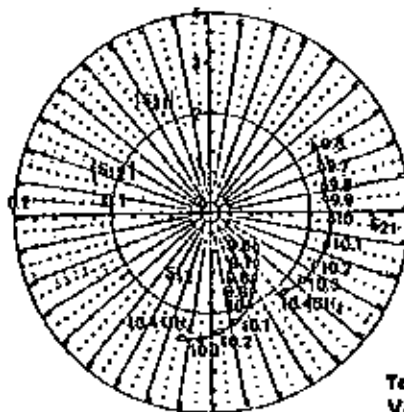

$T_c = 25^\circ\text{C}$   
 $V_{DS} = 9 \text{ V}$   
 $I_D = 900 \text{ mA}$

**S PARAMETERS ( $T_c = 25^\circ\text{C}$ ,  $V_{DS} = 9 \text{ V}$ ,  $I_D = 900 \text{ mA}$ )**

| f<br>(GHz) | S Parameters (TYP.) |              |          |              |          |              |          |              |
|------------|---------------------|--------------|----------|--------------|----------|--------------|----------|--------------|
|            | $S_{11}$            |              | $S_{12}$ |              | $S_{21}$ |              | $S_{22}$ |              |
|            | Magn.               | Angle (deg.) | Magn.    | Angle (deg.) | Magn.    | Angle (deg.) | Magn.    | Angle (deg.) |
| 9.6        | 0.253               | -90.0        | 0.058    | -39.4        | 2.51     | 31.2         | 0.470    | -129.8       |
| 9.7        | 0.193               | -105.5       | 0.068    | -48.2        | 2.44     | 21.9         | 0.447    | -132.8       |
| 9.8        | 0.154               | -124.8       | 0.077    | -55.4        | 2.37     | 13.1         | 0.409    | -132.9       |
| 9.9        | 0.127               | -143.6       | 0.087    | -60.7        | 2.37     | 5.6          | 0.410    | -136.5       |
| 10.0       | 0.097               | -165.9       | 0.100    | -68.4        | 2.43     | -4.5         | 0.402    | -145.4       |
| 10.1       | 0.036               | -156.3       | 0.111    | -78.0        | 2.42     | -15.4        | 0.359    | -155.5       |
| 10.2       | 0.068               | -20.2        | 0.118    | -85.8        | 2.36     | -26.5        | 0.333    | -171.7       |
| 10.3       | 0.203               | 3.5          | 0.126    | -95.2        | 2.30     | -37.5        | 0.301    | 173.3        |
| 10.4       | 0.309               | 10.3         | 0.128    | -103.4       | 2.17     | -48.2        | 0.227    | 164.7        |

self reflection  
coeff.

feedback  
coeff.

forward gain

self refl. coeff.

FHX04FA/LG Fujitsu HEMT (89/90), f=0 extrapolated; Vds=2V, Ids=10mAa

| f    | s11   | s21    | s12          | s22                      |
|------|-------|--------|--------------|--------------------------|
| 0.0  | 1.000 | 0.0    | 4.375 180.0  | 0.000 0.0 0.625 0.0      |
| 1.0  | 0.982 | -20.0  | 4.257 160.4  | 0.018 74.8 0.620 -15.2   |
| 2.0  | 0.952 | -39.0  | 4.113 142.0  | 0.033 62.9 0.604 -28.9   |
| 3.0  | 0.910 | -57.3  | 3.934 124.3  | 0.046 51.5 0.585 -42.4   |
| 4.0  | 0.863 | -75.2  | 3.735 107.0  | 0.057 40.3 0.564 -55.8   |
| 5.0  | 0.809 | -92.3  | 3.487 90.4   | 0.065 30.3 0.541 -69.2   |
| 6.0  | 0.760 | -108.1 | 3.231 75.0   | 0.069 21.0 0.524 -82.0   |
| 7.0  | 0.727 | -122.4 | 3.018 60.9   | 0.072 14.1 0.521 -93.6   |
| 8.0  | 0.701 | -135.5 | 2.817 47.3   | 0.073 7.9 0.524 -104.7   |
| 9.0  | 0.678 | -147.9 | 2.656 33.8   | 0.074 1.6 0.538 -115.4   |
| 10.0 | 0.653 | -159.8 | 2.512 20.2   | 0.076 -4.0 0.552 -125.7  |
| 11.0 | 0.623 | -171.1 | 2.367 7.1    | 0.076 -10.1 0.568 -136.4 |
| 12.0 | 0.601 | 178.5  | 2.245 -5.7   | 0.076 -15.9 0.587 -146.4 |
| 13.0 | 0.582 | 168.8  | 2.153 -18.4  | 0.076 -21.9 0.611 -156.2 |
| 14.0 | 0.564 | 160.2  | 2.065 -31.2  | 0.077 -28.6 0.644 -165.4 |
| 15.0 | 0.533 | 151.6  | 2.001 -44.5  | 0.079 -36.8 0.676 -174.8 |
| 16.0 | 0.500 | 142.8  | 1.938 -58.8  | 0.082 -48.5 0.707 174.2  |
| 17.0 | 0.461 | 134.3  | 1.884 -73.7  | 0.083 -61.7 0.733 163.6  |
| 18.0 | 0.424 | 126.6  | 1.817 -89.7  | 0.085 -77.9 0.758 150.9  |
| 19.0 | 0.385 | 121.7  | 1.708 -106.5 | 0.087 -97.2 0.783 139.1  |
| 20.0 | 0.347 | 119.9  | 1.613 -123.7 | 0.098 -119.9 0.793 126.6 |

**ATF-21186 Typical Scattering Parameters,**

Common Source,  $Z_0 = 50 \Omega$ ,  $V_{GS} = 2 \text{ V}$ ,  $I_{DS} = 15 \text{ mA}$

| Frequency<br>MHz | $S_{11}$ |      | $S_{21}$ |      | $S_{12}$ |      | $S_{22}$ |      |
|------------------|----------|------|----------|------|----------|------|----------|------|
|                  | Mag.     | Ang. | Mag.     | Ang. | Mag.     | Ang. | Mag.     | Ang. |
| 500              | 0.88     | -49  | 3.77     | -47  | 0.069    | 62   | 0.34     | -83  |
| 1000             | 0.92     | -51  | 3.42     | -54  | 0.092    | 54   | 0.33     | -61  |
| 2000             | 0.91     | -57  | 2.85     | 108  | 0.131    | 39   | 0.32     | -81  |
| 3000             | 0.72     | -114 | 2.41     | 84   | 0.159    | 25   | 0.29     | -105 |
| 4000             | 0.64     | -143 | 2.11     | 61   | 0.178    | 12   | 0.26     | -135 |
| 5000             | 0.62     | -172 | 1.83     | 39   | 0.188    | 1    | 0.25     | -170 |
| 6000             | 0.61     | 162  | 1.59     | 19   | 0.189    | -9   | 0.28     | 162  |
| 7000             | 0.62     | 140  | 1.39     | 2    | 0.192    | -15  | 0.33     | 144  |
| 8000             | 0.65     | 123  | 1.25     | -14  | 0.200    | -20  | 0.37     | 129  |

**ATF-21186 Typical Scattering Parameters,**

Common Source,  $Z_0 = 50 \Omega$ ,  $V_{GS} = 2 \text{ V}$ ,  $I_{DS} = 20 \text{ mA}$

| Frequency<br>MHz | $S_{11}$ |      | $S_{21}$ |      | $S_{12}$ |      | $S_{22}$ |      |
|------------------|----------|------|----------|------|----------|------|----------|------|
|                  | Mag.     | Ang. | Mag.     | Ang. | Mag.     | Ang. | Mag.     | Ang. |
| 500              | 0.98     | -51  | 4.17     | 146  | 0.095    | 61   | 0.31     | -62  |
| 1000             | 0.91     | -64  | 3.79     | 132  | 0.097    | 54   | 0.30     | -69  |
| 2000             | 0.80     | -90  | 3.11     | 107  | 0.133    | 40   | 0.28     | -97  |
| 3000             | 0.70     | -118 | 2.60     | 83   | 0.150    | 27   | 0.26     | -111 |
| 4000             | 0.63     | -147 | 2.25     | 60   | 0.169    | 16   | 0.23     | -142 |
| 5000             | 0.61     | -176 | 1.94     | 39   | 0.180    | 5    | 0.23     | -175 |
| 6000             | 0.61     | 129  | 1.68     | 20   | 0.187    | -4   | 0.28     | 155  |
| 7000             | 0.62     | 137  | 1.47     | 2    | 0.193    | -11  | 0.33     | 138  |
| 8000             | 0.64     | 129  | 1.32     | -13  | 0.205    | -17  | 0.36     | 125  |

**ATF-21186 Typical Scattering Parameters,**

Common Source,  $Z_0 = 50 \Omega$ ,  $V_{GS} = 3 \text{ V}$ ,  $I_{DS} = 70 \text{ mA}$

| Frequency<br>MHz | $S_{11}$ |      | $S_{21}$ |      | $S_{12}$ |      | $S_{22}$ |      |
|------------------|----------|------|----------|------|----------|------|----------|------|
|                  | Mag.     | Ang. | Mag.     | Ang. | Mag.     | Ang. | Mag.     | Ang. |
| 500              | 0.95     | -30  | 6.69     | 156  | 0.04     | 74   | 0.31     | -26  |
| 1000             | 0.87     | -57  | 5.74     | 136  | 0.06     | 63   | 0.29     | -58  |
| 2000             | 0.69     | -105 | 4.30     | 102  | 0.10     | 48   | 0.18     | -109 |
| 3000             | 0.63     | -135 | 3.36     | 80   | 0.12     | 41   | 0.18     | -149 |
| 4000             | 0.62     | -170 | 2.63     | 60   | 0.14     | 33   | 0.22     | -173 |
| 5000             | 0.62     | 165  | 2.12     | 42   | 0.15     | 28   | 0.27     | 161  |
| 6000             | 0.67     | 147  | 1.76     | 25   | 0.17     | 23   | 0.33     | 146  |
| 7000             | 0.71     | 133  | 1.49     | 13   | 0.18     | 18   | 0.39     | 136  |
| 8000             | 0.74     | 126  | 1.29     | 5    | 0.19     | 16   | 0.43     | 121  |

**ATF-21186 Typical Noise Parameters,**

Common Source,  $Z_0 = 50 \Omega$ ,  $V_{GS} = 2 \text{ V}$ ,  $I_{DS} = 10 \text{ mA}$

| Frequency<br>MHz | NF <sub>min</sub><br>dB | $F_{opt}$ |      | RNF50 $\Omega$ |
|------------------|-------------------------|-----------|------|----------------|
|                  |                         | Mag.      | Ang. |                |
| 500              | 0.57                    | 0.63      | 30   | 0.78           |
| 1000             | 0.61                    | 0.60      | 39   | 0.88           |
| 2000             | 0.71                    | 0.76      | 61   | 0.48           |
| 4000             | 0.90                    | 0.72      | 119  | 0.23           |
| 5000             | 1.09                    | 0.71      | 168  | 0.04           |
| 8000             | 1.29                    | 0.73      | -145 | 0.10           |

**ATF-21186 Typical Noise Parameters,**

Common Source,  $Z_0 = 50 \Omega$ ,  $V_{GS} = 2 \text{ V}$ ,  $I_{DS} = 15 \text{ mA}$

| Frequency<br>MHz | NF <sub>min</sub><br>dB | $F_{opt}$ |      | RNF50 $\Omega$ |
|------------------|-------------------------|-----------|------|----------------|
|                  |                         | Mag.      | Ang. |                |
| 500              | 0.50                    | 0.91      | 31   | 0.69           |
| 1000             | 0.55                    | 0.87      | 40   | 0.49           |
| 2000             | 0.65                    | 0.77      | 63   | 0.40           |
| 4000             | 0.84                    | 0.66      | 111  | 0.29           |
| 5000             | 1.13                    | 0.65      | 171  | 0.04           |
| 8000             | 1.25                    | 0.79      | -142 | 0.21           |

**ATF-21186 Typical Noise Parameters,**

Common Source,  $Z_0 = 50 \Omega$ ,  $V_{GS} = 2 \text{ V}$ ,  $I_{DS} = 20 \text{ mA}$

| Frequency<br>MHz | NF <sub>min</sub><br>dB | $F_{opt}$ |      | RNF50 $\Omega$ |
|------------------|-------------------------|-----------|------|----------------|
|                  |                         | Mag.      | Ang. |                |
| 500              | 0.45                    | 0.88      | 31   | 0.56           |
| 1000             | 0.50                    | 0.84      | 41   | 0.43           |
| 2000             | 0.60                    | 0.75      | 64   | 0.35           |
| 4000             | 0.82                    | 0.65      | 113  | 0.16           |
| 5000             | 1.03                    | 0.65      | 174  | 0.03           |
| 8000             | 1.24                    | 0.69      | -139 | 0.11           |

We have previously derived (for an imperfectly matched output)

$$P_1 = P_{in} = \frac{b_1}{a_1} = S_{11} + \frac{S_{12} S_{21} P_L}{1 - S_{22} P_L} \quad (11.3 a)$$

This equation can be used to obtain  $Z_{in}$  since  $P_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$

We can similarly write  $P_2$  (for an imperfectly matched input)

$$P_2 = P_{out} = \frac{b_2}{a_2} = S_{22} + \frac{S_{12} S_{21} P_S}{1 - S_{11} P_S} \quad (11.3 b)$$

By voltage division

$$V_1 = V_{in} = V_S \frac{Z_{in}}{Z_{in} + Z_0} = V_1^+ + \vec{V}_1^- = V_1^+ (1 + P_{in}) \quad (1)$$

$$\text{Using } Z_{in} = Z_0 \frac{1 + P_{in}}{1 - P_{in}} \quad (2)$$

$$\text{and } P_S = \frac{Z_S - Z_0}{Z_S + Z_0} \text{ which gives } Z_S = Z_0 \frac{1 + P_S}{1 - P_S} \quad (3)$$

Combining Eqs. (1), (2), (3) we can write

$$V_1^+ = \frac{V_S}{2} \frac{1 - P_S}{1 - P_S P_{in}} \quad (11.4)$$

If peak values are assumed for all voltages, the average power delivered to the amplifier is

$$P_{in} = |a_1|^2 - |b_1|^2 = \frac{|V_1^+|^2}{2Z_0} (1 - |P_{in}|^2) \\ = \frac{V_S^2}{8Z_0} \frac{|1 - P_S|^2}{|1 - P_S P_{in}|^2} (1 - |P_{in}|^2) \quad (11.5)$$

$$\text{Power delivered to the load} = |b_2|^2 - |a_2|^2 = \frac{|V_2^-|^2}{2Z_0} (1 - |P_L|^2) \quad (4)$$

We have previously derived (on p. 3 of the handout)

$$\frac{b_2}{a_1} = \frac{V_2^-}{V_1^+} = \frac{S_{21}}{1 - S_{22} P_L} \quad (5)$$

Thus power delivered to the load

$$P_L = \frac{|V_1^+|^2 |S_{21}|^2 (1 - |P_L|^2)}{2Z_0 |1 - S_{22} P_L|^2} = \frac{V_S^2}{8Z_0} \frac{|1 - P_S|^2 |S_{21}|^2 (1 - |P_L|^2)}{|1 - S_{22} P_L|^2 |1 - P_S P_{in}|^2} \quad (11.7)$$



The power gain can now be written in terms of S-parameters of the amplifier (4)

$$G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) |1 - S_{11} \Gamma_L|^2} \quad (11.8)$$

Where  $\Gamma_{in}$  is given by Eq. 11.3 a.

Note that the power gain obtained in Eq. (11.8) is quite complex, involving as it does,  $\Gamma_L$ , also for  $\Gamma_{in}$  and the S-parameters also in  $\Gamma_{in}$  from Eq. 11.3

The maximum power available from the source (deliverable to the input) is for the condition  $\Gamma_{in} = \Gamma_s^*$ . Under this input conjugate matching condition, the maximum input power  $P_{avs}$  can be written from Eq. (11.5)

$$P_{avs} = \left. \frac{P_{in}}{\Gamma_{in} = \Gamma_s^*} \right| = \frac{|V_s|^2}{8Z_0} \frac{|1 - \Gamma_s|^2}{|1 - |\Gamma_s|^2|^2} \quad (11.9)$$

Similarly the <sup>output</sup> power available from the amplifier is that delivered to a matched load for which  $\Gamma_L = \Gamma_{out}^*$

From Eq. 11.7

$$P_{avn} = \left. \frac{P_L}{\Gamma_L = \Gamma_{out}^*} \right| = \frac{|V_s|^2}{8Z_0} \frac{|S_{21}|^2 (1 - |\Gamma_{out}|^2) |1 - \Gamma_s|^2}{|1 - S_{22} \Gamma_{out}^*|^2 |1 - \Gamma_s \Gamma_{in}|^2} \quad (11.10)$$

However, in Eq. 11.10,  $\Gamma_{in}$  must be evaluated for the output load  $\Gamma_L = \Gamma_{out}^*$ . For this conjugate matched output condition

$$\left. |1 - \Gamma_s \Gamma_{in}|^2 \right|_{\Gamma_L = \Gamma_{out}^*} = \frac{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{out}|^2)^2}{|1 - S_{22} \Gamma_{out}^*|^2} \quad (6)$$

Substituting (6) into Eq. (11.10) gives maximum available output power

$$P_{avn} = \frac{|V_s|^2}{8Z_0} \frac{|S_{21}|^2 |1 - \Gamma_s|^2}{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{out}|^2)} \quad (11.11)$$

From Eqs. 11.11 and 11.9, the available power gain can be written as

$$G_A = \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{out}|^2)} \quad (11.12)$$

From Eqs. (11.7) and (11.9), the transducer power gain is

$$G_T = \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \Gamma_{in}|^2 |1 - S_{22} \Gamma_L|^2} \quad (11.13)$$

Special case I

For a special case where both input and output are matched for zero reflection i.e.  $\Gamma_L = \Gamma_S = 0$ , Eq. (11.13) reduces to

$$G_T \Big|_{\Gamma_L = \Gamma_S = 0} = |S_{21}|^2 \quad (11.14)$$

Special case II Unilateral transducer power gain  $G_{TU}$  can be obtained if  $S_{12} = 0$

For the case  $S_{12} \approx 0$

From Eq. 11.3a,  $\Gamma_{in} = S_{11}$

From Eq. 11.13

$$G_{TU} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|1 - S_{11} \Gamma_S|^2 |1 - S_{22} \Gamma_L|^2} \quad (11.15)$$

For the example 11.1 on p. 539 text

$$G_{TU} = \frac{(2.05)^2 (1 - (0.429)^2) (1 - (0.25)^2)}{|1 + 0.429 \times 0.45 / 15^2|^2 |1 + 0.25 \times 0.4 / 15^2|^2} = \boxed{4.654}$$

From Masera's procedure

$$\frac{b_2}{a_1} = \frac{S_{21}}{1 - S_{22} \Gamma_L} \quad (1)$$

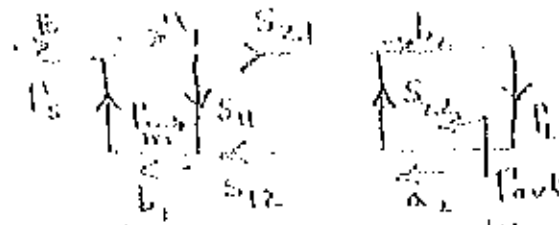


Fig. 1 Flow graph of the amplifier of Fig. 1.1 with source and load mismatch

1. Power Gain: Power delivered to the load  
 $G$  power input to the amplifier

$$G = \frac{b_2 b_2^* (1 - |\Gamma_L|^2)}{a_1 a_1^* - b_1 b_1^*} = \frac{b_2 b_2^* (1 - |\Gamma_L|^2)}{a_1 a_1^* (1 - |\Gamma_{in}|^2)} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22} \Gamma_L|^2 (1 - |\Gamma_{in}|^2)} \quad \text{from eq. (1)}$$

Note that  $b_1 = \Gamma_{in} a_1$  (2) (11.8)

2. Maximum power available from the source is for matching condition

$$P_{in} = P_s^*$$

$$P_{avs} = a_1 a_1^* - b_1 b_1^* = a_1 a_1^* (1 - |\Gamma_{in}|^2) = \frac{E E^* (1 - |\Gamma_{in}|^2)}{|1 - \Gamma_s \Gamma_{in}|^2} \quad (3)$$

$$a_1 = E \Gamma_s \quad b_1 = E + \Gamma_s P_{in} \frac{a_1}{P_{in}(2)} \quad (4)$$

Thus  $a_1 = \frac{E}{1 - \Gamma_s \Gamma_{in}}$  (5)

Max. Power delivered to the load (for conjugate matched condition  $\Gamma_L = \Gamma_{out}^*$ )

$$P_{avn} = b_2 b_2^* (1 - |\Gamma_L|^2) = a_1 a_1^* \frac{|S_{21}|^2}{|1 - S_{22} \Gamma_L|^2} = \frac{E E^* |S_{21}|^2 (1 - |\Gamma_{out}|^2)}{|1 - \Gamma_s \Gamma_{in}|^2 |1 - S_{22} \Gamma_L|^2} \quad \text{from (5)} \quad (11.10)$$

The rest of the steps are the same as on p. 539 of the text

$$\text{Available power gain } G_A = \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_{out}|^2)}{|1 - S_{22} \Gamma_L|^2 (1 - |\Gamma_{out}|^2)} \quad (11.12)$$

$$\text{Transducer power gain } G_T = \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2) (1 - |\Gamma_L|^2)}{|1 - \Gamma_s \Gamma_{in}|^2 |1 - S_{22} \Gamma_L|^2} \quad (11.13)$$

For the condition when both input and output are well matched

$$\Gamma_s = \Gamma_L = 0$$

$$\text{Transducer power gain } G_T = |S_{21}|^2 \quad (11.14)$$

Expressions for power gain of an amplifier (see pp. 536-540 of the text) (5)

We would calculate gain of the amplifier under four different scenarios.

1. Power Gain  $G_P$   

$$G_P = \frac{\text{Power delivered to the load} : b_2 b_2^* (1 - |r_1|^2)}{\text{Power input} : |a_1|^2 |b_1|^2 \leftarrow a_1 a_1^* - b_1 b_1^*} \quad (11.8)$$

2. Available Power Gain  $G_A$   

$$G_A = \frac{\text{max. power delivered to the load} \left| P_L : P_{out} \right.}{\text{max power available from the source / input to the amplifier} \left| P_{avs} : P_{in} \right.}$$

i.e.  $\frac{\text{max. output under output conjugate-matched conditions}}{\text{max. power input under conjugate-matched conditions at input}}$

This is also called available power gain  $G_A$  and is given by Eq. (11.12) of the text


3. Transducer power gain  $G_T$  
$$G_T = \frac{P_L \text{ delivered to the load with } P_L}{P_{avs} \text{ (when input is conjugate matched)}}$$

for the condition that input and output are "well-matched".

4. Unilateral power gain 
$$\rightarrow G_{TU} = G_T \Big|_{S_{12} = 0} = |S_{21}|^2 \quad (11.14)$$

ABCD parameters

p. 183

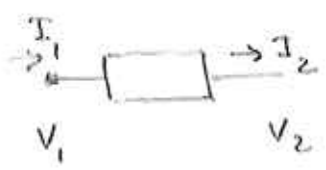

$$V_1 = A V_2 + B I_2$$


$$I_1 = C V_2 + D I_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1$$


$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} = Z$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = 0$$

$$D = 1$$

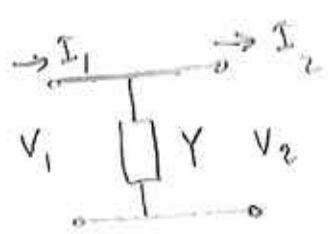
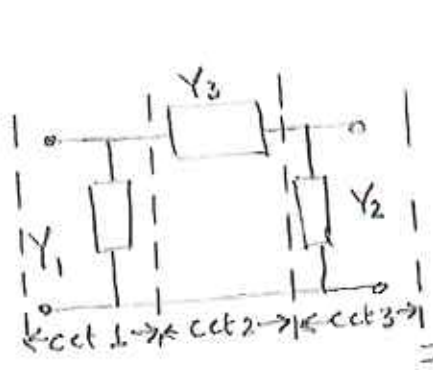
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$



$$\begin{bmatrix} 1 & 0 \\ Y_1 & 1 \end{bmatrix} \begin{bmatrix} 1 & \frac{1}{Y_3} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y_2 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 \\ Y_1 & 1 \end{bmatrix} \begin{bmatrix} 1 + \frac{Y_2}{Y_3} & \frac{1}{Y_3} \\ Y_2 & 1 \end{bmatrix}$$


$$= \begin{bmatrix} 1 + \frac{Y_2}{Y_3} & \frac{1}{Y_3} \\ Y_1 (1 + \frac{Y_2}{Y_3}) + Y_2 & \frac{Y_1}{Y_3} + 1 \end{bmatrix}$$

Note that  $AD - BC = \left( 1 + \frac{Y_1}{Y_3} + \frac{Y_1 Y_2}{Y_3^2} \right) - \left( \frac{Y_1}{Y_3} \left( 1 + \frac{Y_2}{Y_3} \right) + \frac{Y_2}{Y_3} \right)$

$= 1$   
for all reciprocal circuits with bilateral performance

$$Z_{12} = Z_{21}; \quad Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}; \quad Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$
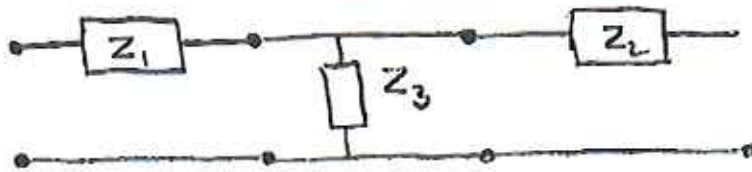
# ABCD Parameters of the circuit in item 6 of Table 4.1



This circuit may be considered to be composed of 3 circuits in cascade, as sketched above.

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{Z_3} & 1 \end{bmatrix} \begin{bmatrix} 1 & Z_2 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & Z_2 \\ \frac{1}{Z_3} & \frac{Z_2}{Z_3} + 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 + \frac{Z_1}{Z_3} & Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3} \\ \frac{1}{Z_3} & \frac{Z_2}{Z_3} + 1 \end{bmatrix}$$

You may also be able to derive the ABCD parameters using the defining relationships given in (4.63)

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}, \quad B = \left. \frac{V_1}{I_2} \right|_{V_2=0} \quad \text{etc.}$$

For homework problem, this basic approach should be followed.