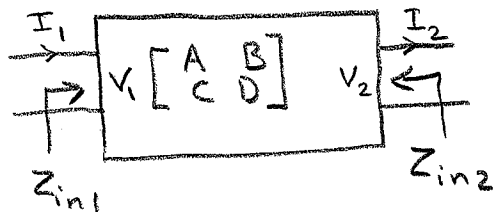


Notes for  
Chapter 8 - 2008

Section 8.2 Text (p.378)



$Z_{i1}$  = input impedance at port ① when port ② is terminated with  $Z_{i2}$

$Z_{i2}$  = input impedance at port 2 when port 1 is terminated with  $Z_{i1}$

From Eq. 4.63 p.183 of the Text, the port voltages and currents are related as follows:

$$V_1 = A V_2 + B I_2 \quad (8.22 a)$$

$$I_1 = C V_2 + D I_2 \quad (8.22 b)$$

$$Z_{i1} = \frac{V_1}{I_1} = \frac{A V_2 + B I_2}{C V_2 + D I_2} = \frac{A Z_{i2} + B}{C Z_{i2} + D} \quad (8.23)$$

Note that  $V_2 = I_2 Z_{i2}$

From Eq. 4.67 p.186 of the Text,  $AD - BC = 1$  for passive networks

From Eqs. 8.22 a, b, we can derive the following:

$$V_2 = D V_1 - B I_1 \quad (8.24 a)$$

$$I_2 = -C V_1 + A I_1 \quad (8.24 b)$$

$$Z_{i2} = -\frac{V_2}{I_2} = -\frac{D V_1 - B I_1}{-C V_1 + A I_1} = \frac{D Z_{i1} + B}{C Z_{i1} + A} \quad (8.25)$$

We desire that  $Z_{i1} = Z_{i1}$  and  $Z_{i2} = Z_{i2}$

From Eqs. (8.23) and (8.25) we can therefore write

$$Z_{i1} (C Z_{i2} + D) = A Z_{i2} + B \quad (8.26 a)$$


$$Z_{i1} D - B = Z_{i2} (A - C Z_{i1}) \quad (8.26 b)$$

Solving for  $Z_{i1}, Z_{i2}$  gives


$$Z_{i1} = \sqrt{\frac{AB}{CD}} \quad (8.27 a); \quad Z_{i2} = \frac{D}{A} Z_{i1} = \sqrt{\frac{BD}{AC}} \quad (8.27 b)$$

If the network is symmetric, then  $A = D$  and  $Z_{i1} = Z_{i2}$

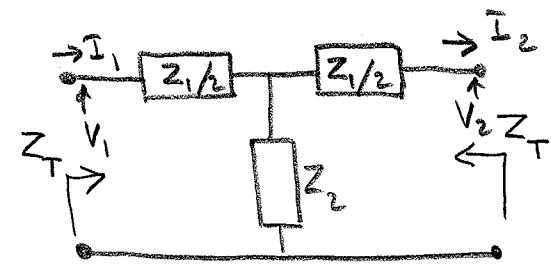See Table 4-1  
A = D for  
Symmetric Networks



Full section T

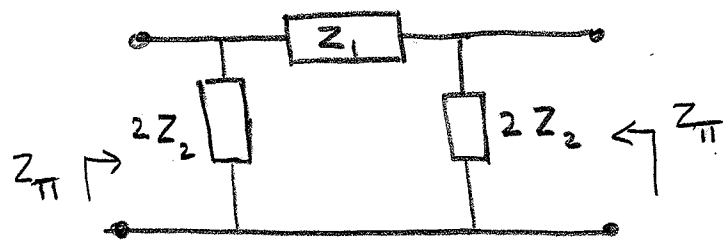

Full section  $\Pi$

From the expressions for elements 5 & 6 in Table 4.1 (p. 185) Text

$$A = 1 + \frac{Z_1}{2Z_2}$$

$$B = Z_1 + \frac{Z_1^2}{4Z_2}$$

$$C = \frac{1}{Z_2}$$

$$D = 1 + \frac{Z_1}{2Z_2}$$

$$A = 1 + \frac{Z_1}{2Z_2}$$

$$B = Z_1$$

$$C = \frac{1}{Z_2} + \frac{Z_1}{4Z_2^2}$$

$$D = 1 + \frac{Z_1}{2Z_2}$$

$$Z_T = \sqrt{\frac{AB}{CD}} \quad (8.27(a))$$

$$= \sqrt{Z_1 Z_2} \sqrt{1 + \frac{Z_1}{4Z_2}}$$

$$Z_{\Pi} = \sqrt{\frac{AB}{CD}} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}}$$

$$\cosh \gamma = \sqrt{AD} = 1 + \frac{Z_1}{2Z_2} \quad (8.31)$$

$$= \frac{e^{\gamma} + e^{-\gamma}}{2}$$

$$\boxed{\gamma = \alpha + j\beta}$$

$$\cosh \gamma = 1 + \frac{Z_1}{2Z_2} \quad (8.31)$$

$$\boxed{\frac{V_2 I_2}{V_1 I_1} = e^{-2\gamma}}$$

For pass band  $\gamma = j\beta$  ;  $\alpha = 0$

$$\cos \beta = 1 + \frac{Z_1}{2Z_2} = \cos^2(\beta/2) - \sin^2(\beta/2) = 1 - 2\sin^2(\beta/2)$$

$$= 1 + \frac{Z_1}{2Z_2}$$


For  $\beta$  to be real  $-1 \leq \cos \beta \leq 1$

$$-2 \leq \frac{Z_1}{2Z_2} \leq 0 \quad \text{or} \quad -1 < \frac{Z_1}{4Z_2} \leq 0$$


For pass band

$$\beta = \cos^{-1} \left( 1 + \frac{Z_1}{2Z_2} \right) = \pm 2 \sin^{-1} \left( \sqrt{-\frac{Z_1}{4Z_2}} \right)$$

Bisected half-section Filters

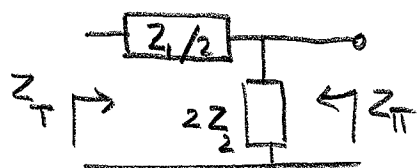


$$\boxed{Z_T Z_{\Pi} = Z_1 Z_2}$$

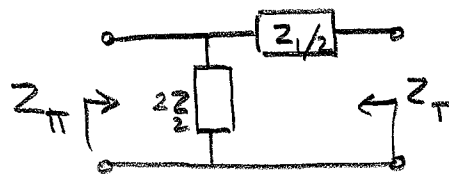

**Some General Relationships for Filter Design by Image Parameter Method**

See Table 8.1 p. 381

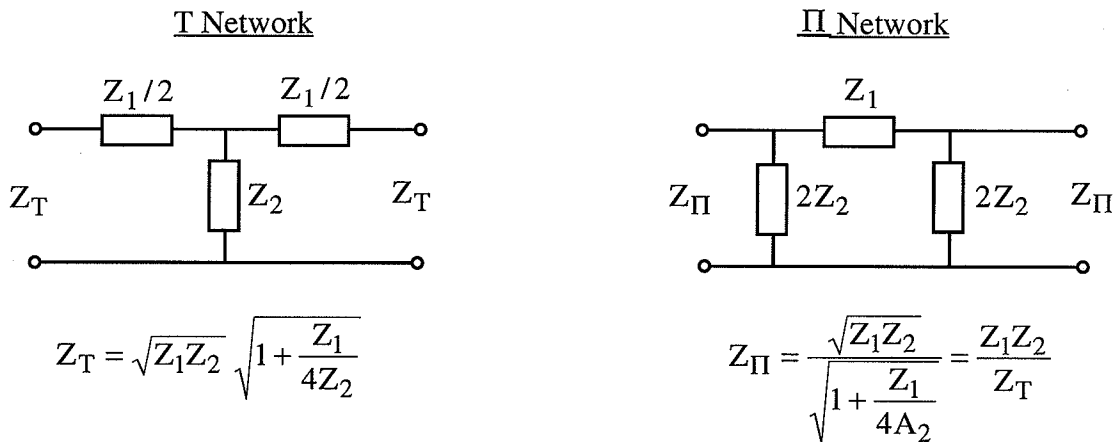

For pass band: Both  $Z_T$  and  $Z_{\Pi}$  are purely resistive.

$$-1 \leq \frac{Z_1}{4Z_2} \leq 0$$

$$\beta = \pm 2 \sin^{-1} \left( -\frac{Z_1}{4Z_2} \right)^{1/2} \text{ radians}$$

For stop band: Both  $Z_T$  and  $Z_{\Pi}$  are purely reactive.

$$\frac{Z_1}{4Z_2} > 0; \quad \alpha = 2 \sinh^{-1} \left( \frac{Z_1}{4Z_2} \right)^{1/2}$$

$$\frac{Z_1}{4Z_2} < -1; \quad \alpha = \cosh^{-1} \left| 1 + \frac{Z_1}{2Z_2} \right|$$

$$= 2 \cosh^{-1} \left( \frac{-Z_1}{4Z_2} \right)^{1/2}$$

**Constant-k Filters**

p. 380, also Table 8.2, p. 387


$$\text{Nominal terminating resistance } R = (Z_1 Z_2)^{1/2} \Rightarrow k$$

Low pass

$$Z_1 = j\omega L \quad R_o = \sqrt{\frac{L}{C}}$$

$$Z_2 = \frac{1}{j\omega C} \quad L = \frac{2R_o}{\omega_c}, \quad C = \frac{2}{\omega_c R_o}$$
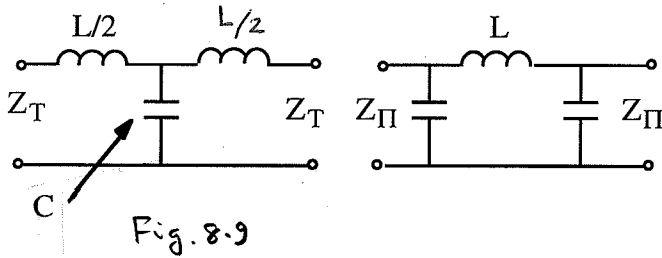
$$\omega_c = \frac{2}{\sqrt{LC}} \quad \beta = 2 \sin^{-1}\left(\frac{\omega}{\omega_c}\right)$$




$$Z_T = R_o \left(1 - \frac{\omega^2}{\omega_c^2}\right)^{1/2}; \quad Z_{\Pi} = \frac{R_o}{\left(1 - \frac{\omega^2}{\omega_c^2}\right)^{1/2}}$$

High pass

$$Z_1 = \frac{1}{j\omega C} \quad R_o = \sqrt{\frac{L}{C}}$$

$$Z_2 = j\omega L \quad L = \frac{R_o}{2\omega_c}, \quad C = \frac{1}{2\omega_c R_o}$$
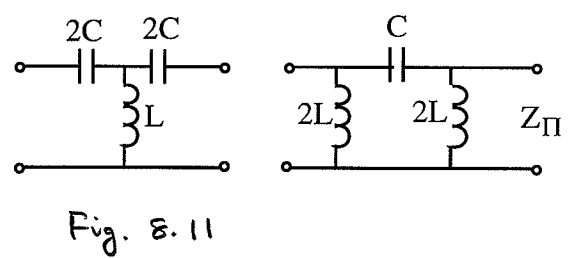
$$\omega_c = \frac{1}{2\sqrt{LC}} \quad \beta = 2 \sin^{-1}\left(\frac{\omega_c}{\omega}\right)$$



$$Z_T = R_o \left(1 - \frac{\omega_c^2}{\omega^2}\right)^{1/2}; \quad Z_{\Pi} = \frac{R_o}{\left(1 - \frac{\omega_c^2}{\omega^2}\right)^{1/2}}$$

Disadvantages of Constant-k Filters

1. Actual termination resistances  $Z_T, Z_{\Pi}$  vary greatly over the pass band.
2. The attenuation constant  $\alpha$  varies undesirably slowly over the stop band.

**m-Derived Filters**

p. 383

The m-derived filters are a considerable improvement for both of the enumerated disadvantages of the constant-k filters.


T Network (series m-derived)

$$Z'_1 = mZ_1 \quad (8.39)$$

Π Network (shunt m-derived)

$$Z'_2 = \frac{Z_2}{m}$$

T-Section Constant-k Filters

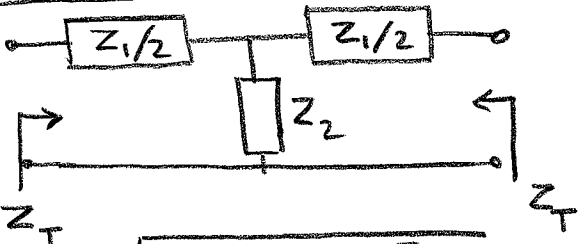

$$Z_T = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}$$


For pass band

$$0 \leq -\frac{Z_1}{4Z_2} \leq 1 ; \beta = \pm 2 \sin^{-1} \sqrt{-\frac{Z_1}{4Z_2}}$$

For stop band



$$\left| \frac{Z_1}{4Z_2} \right| > 1 ; \alpha = 2 \sinh^{-1} \left( -\frac{Z_1}{4Z_2} \right)^{1/2}$$

Π-Section

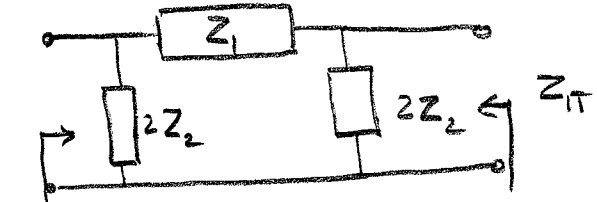

$$Z_{\pi} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}} = \frac{Z_1 Z_2}{Z_T}$$

Case I: Low Pass FILTERS


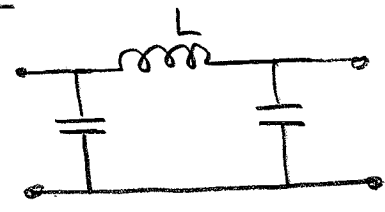
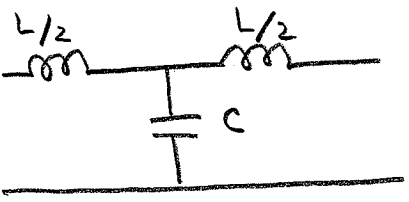


$$L = \frac{2 R_0}{\omega_c} ; C = \frac{2}{\omega_c R_0} ; \omega_c = \sqrt{\frac{2}{LC}}$$

$$\beta = 2 \sin^{-1} (\omega/\omega_c)$$

$$Z_T = R_0 \left(1 - \frac{\omega^2}{\omega_c^2}\right)^{1/2}$$
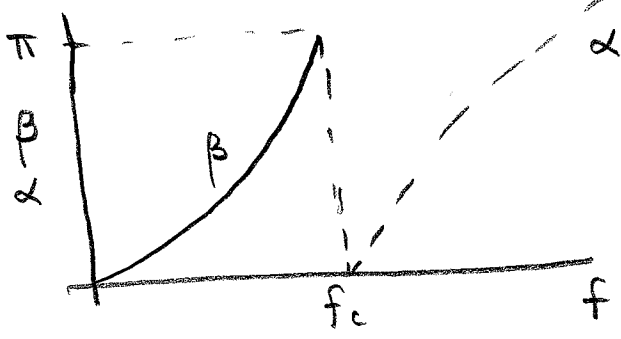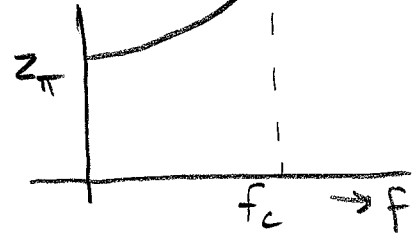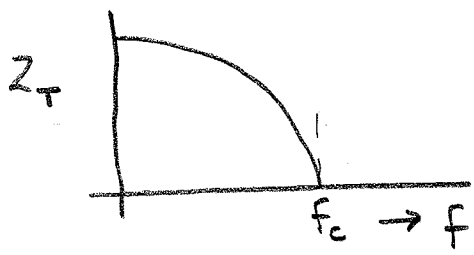
$$Z_{\pi} = \frac{R_0}{\left(1 - \frac{\omega^2}{\omega_c^2}\right)^{1/2}}$$



$$Z'_2 = \frac{Z_2}{m} + \frac{1-m^2}{4m} Z_1 \quad (8.41)$$


$$\left. \frac{1}{Z_\Pi} \right|_{m\text{-derived}} = \left. \frac{1}{Z'_\Pi} \right|_{k\text{-section}}$$

$$\left. \frac{1}{Z_T} \right|_{m\text{-derived}} = \left. \frac{1}{Z_T} \right|_{k\text{-section}}$$


$$\frac{1}{Z'_1} = \frac{1}{mZ_1} + \frac{(1-m^2)/m}{4Z_2}$$

$Z'_2 \equiv$  Series combination of  $\frac{Z_2}{m}$  and  $\frac{1-m^2}{4m} Z_1$


$$Z_{\Pi}|_{m\text{-derived}} = \frac{Z'_1 Z'_2}{Z_T} = \frac{Z_1 Z_2 + \frac{1-m^2}{4} Z_1^2}{Z_T} \quad \left. Z'_1 = \right. \text{Parallel combination of } mZ_1 \text{ and } \frac{4Z_2}{(1-m^2)/m}$$

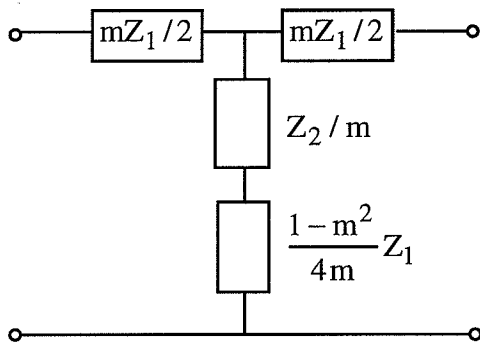


Full section T (Fig. 8-12, p. 383)

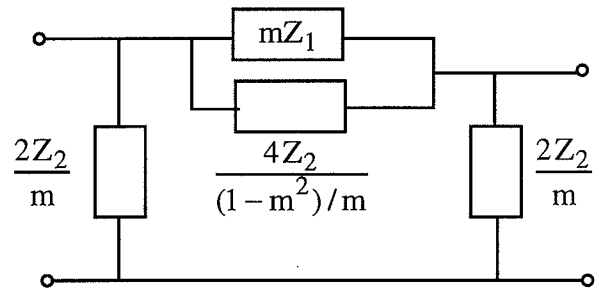

Full section  $\Pi$

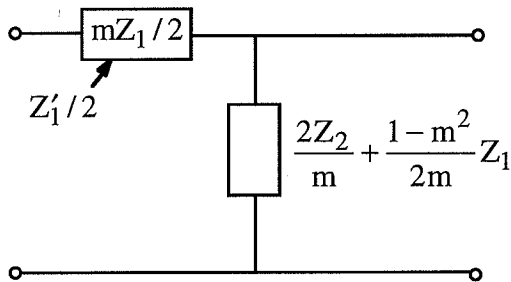

Half section T

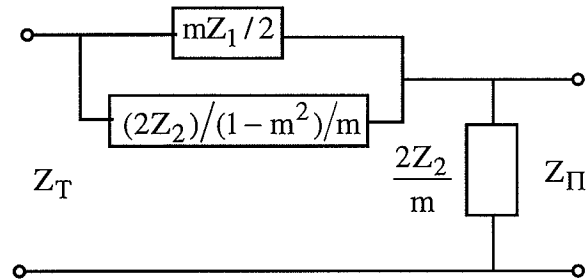





### For Low Pass Filters

$$Z'_1 = j\omega Lm$$

$$Z'_2 = \frac{1}{j\omega(mC)}$$

$$Z'_2 = \frac{1}{j\omega(mC)} + \left( \frac{1-m^2}{4m} \right) j\omega L$$
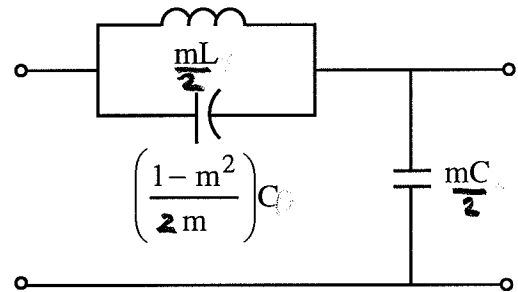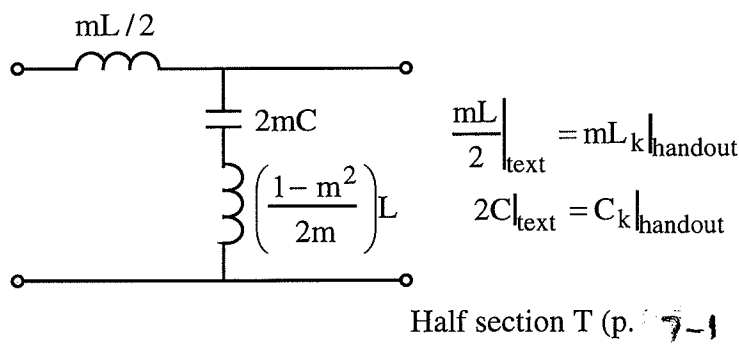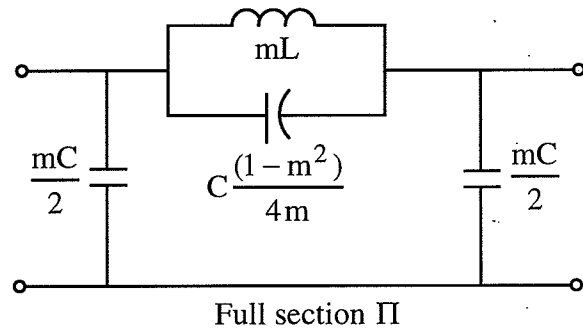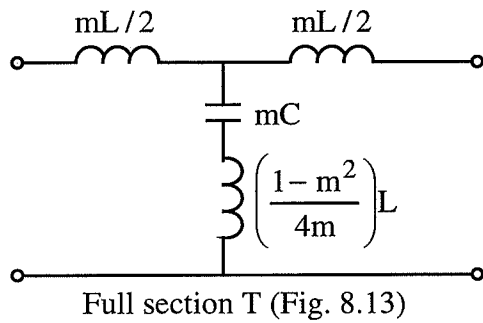
$$\frac{1}{Z'_1} = \frac{1}{j\omega(mL)} + j\omega C \frac{(1-m^2)}{4m}$$



### Design of Constant-k and m-Derived Low Pass Filters

Example: Select  $R_o$ ,  $f_c$ ,  $f_\infty$  (for m-derived sections)

$$R_o = 50\Omega; \quad f_c = 2.0 \text{ GHz}; \quad f_\infty = 2.5 \text{ GHz}$$


$$m = 0.6$$

From Eqs. 8.33, 8.34 (p. 380 text)


$$L = \frac{2R_o}{\omega_c} = \frac{100}{2\pi \times 2 \times 10^9} = 7.96 \text{ nH}$$

$$C = \frac{2}{\omega_c R_o} = \frac{2}{2\pi \times 2 \times 10^9 \times 50} = 3.18 \text{ pF}$$

### Constant k-Section Filters

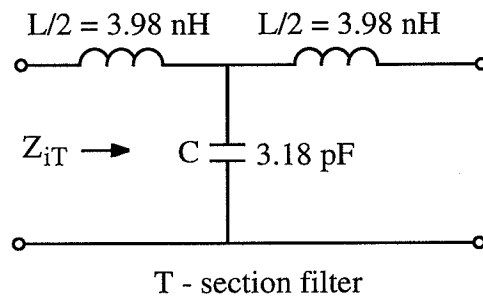
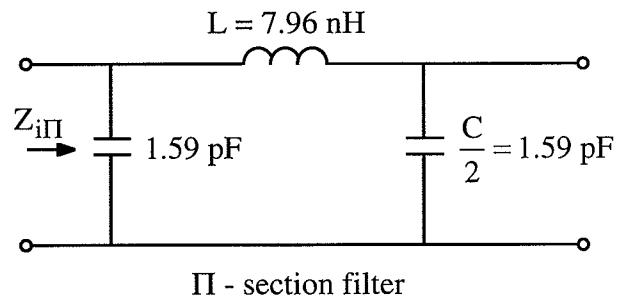
$$Z_{iT} = R_o \sqrt{\left(1 - \frac{f^2}{f_c^2}\right)}$$



$$Z_{i\Pi} = \frac{R_o}{\sqrt{1 - \frac{f^2}{f_c^2}}}$$





### m-Derived Filters

From Eq. 8.44,

$$f_{\infty} = \frac{f_c}{\sqrt{1-m^2}}$$
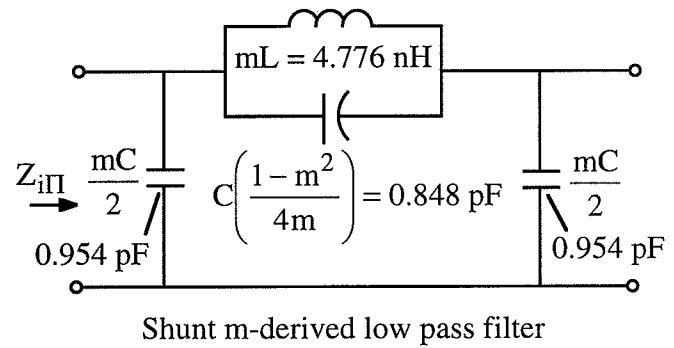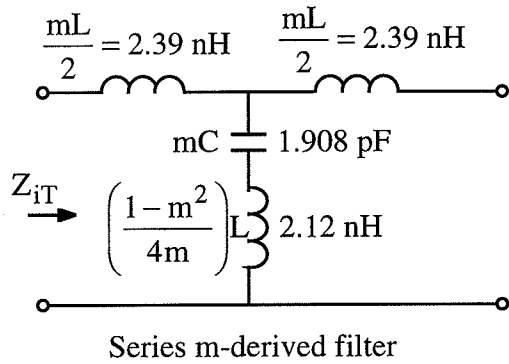
$$m = \sqrt{1 - \frac{f_c^2}{f_{\infty}^2}} = \sqrt{1 - \left(\frac{2}{2.5}\right)^2} = 0.6$$




$$Z_{iT} = R_o \sqrt{1 - \frac{f^2}{f_c^2}}$$


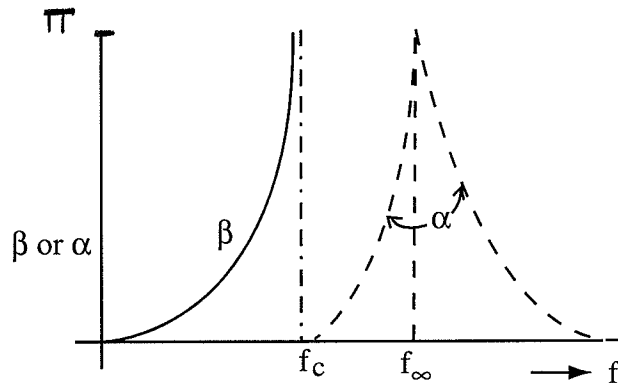
### For Stop Band

$$\alpha = 2 \cosh^{-1} \left( -\frac{Z'_1}{4Z'_2} \right) \text{ for } \frac{Z'_1}{4Z'_2} < -1$$

$$= 2 \sinh^{-1} \left( \frac{Z'_1}{4Z'_2} \right) \text{ for } \frac{Z'_1}{4Z'_2} > 0$$




### Half Section Filters (k-Section)

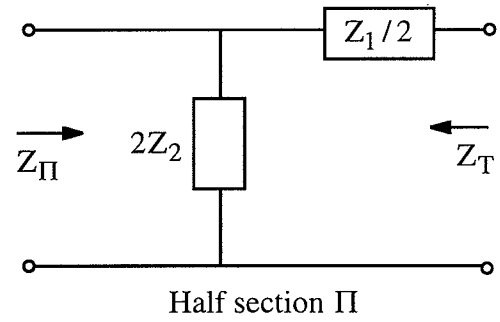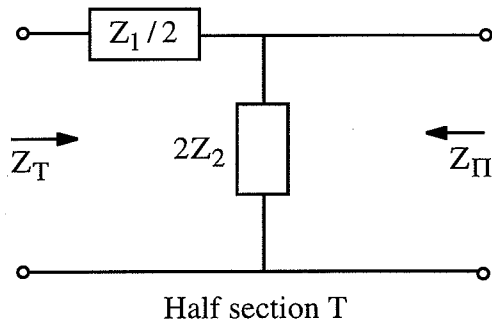


$$Z_T Z_\Pi = Z_1 Z_2$$

### m-Derived Half Section Filters

#### Series m-derived

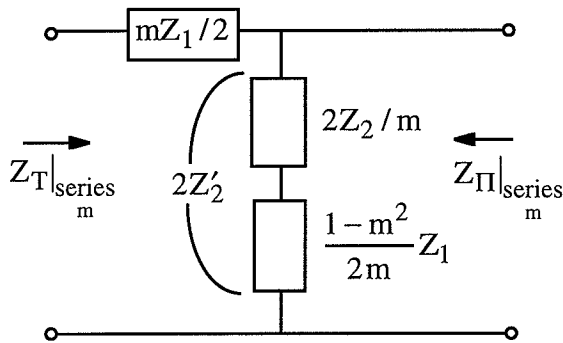

#### Shunt m-derived

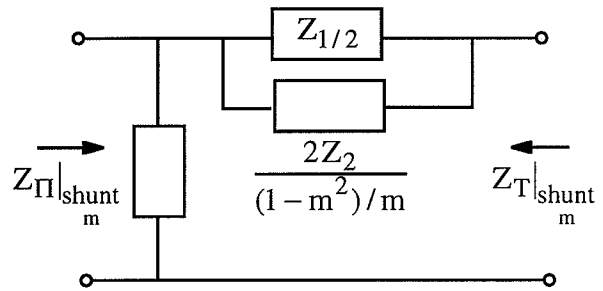

$$Z_T|_{\text{series } m\text{-derived}} = Z_T|_{\text{k-section}} = R_o \sqrt{1 - \frac{f_c^2}{f^2}}$$

$$Z_\Pi|_{\text{shunt } m} = Z_\Pi|_{\text{k-section}} = \frac{R_o}{\sqrt{1 - \frac{f_c^2}{f^2}}}$$


$$Z_\Pi|_{\text{series } m\text{-derived}} = \frac{Z_1' Z_2'}{Z_T} = \frac{Z_1 Z_2 + \left(\frac{1-m^2}{4}\right) Z_1^2}{Z_T}$$

$$Z_T|_{\text{shunt } m} = \frac{Z_1' Z_2'}{Z_\Pi|_{\text{shunt } m}}$$

# m-derived filters

purpose: to get  $\alpha \rightarrow \infty$  at a frequency  $f_{\infty}$  close to  $f_c$


## Series m-derived $Z'_1 = mZ_1$

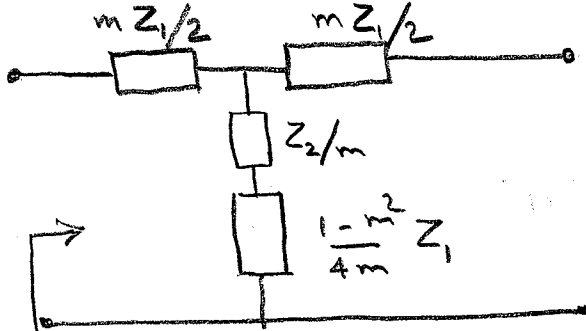

$$Z_T |_{\text{Series m-derived}} = Z_{\pi} |_{\text{k-section}} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}$$

$$Z_{\pi} |_{\text{Series m-derived}} = \frac{Z'_1 Z'_2}{Z_T}$$

## Case I Low pass-filters

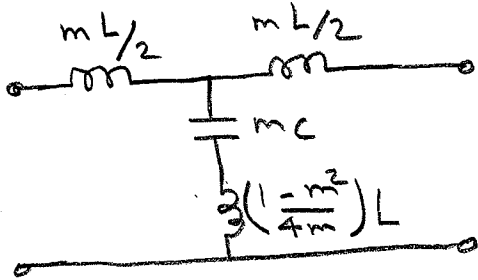



$$L = \frac{2R_0}{\omega_c}, \quad C = \frac{2}{\omega_c R_0}, \quad \omega_c = \frac{2}{\sqrt{LC}}$$

$$f_{\infty} = \frac{f_c}{\sqrt{1-m^2}}$$


$$Z_T |_{\text{Series m-derived}} = Z_T |_{\text{k-section}} = R_0 \left(1 - \frac{\omega^2}{\omega_c^2}\right)^{1/2}$$

$$Z_{\pi} |_{\text{Series m-derived}} = \frac{Z'_1 Z'_2}{Z_T} = \frac{R_0 \left(1 - \frac{\omega^2}{\omega_{\infty}^2}\right)}{\sqrt{1 - \frac{\omega^2}{\omega_c^2}}}$$

### Series m-derived

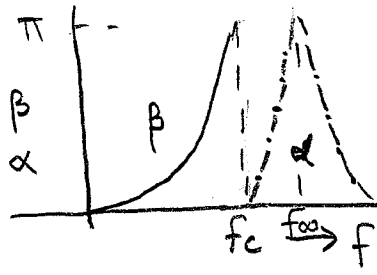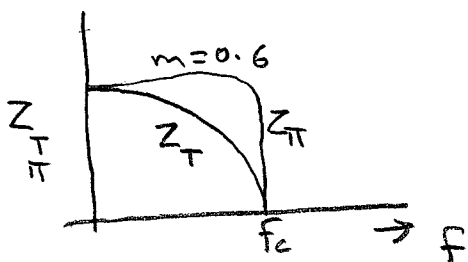

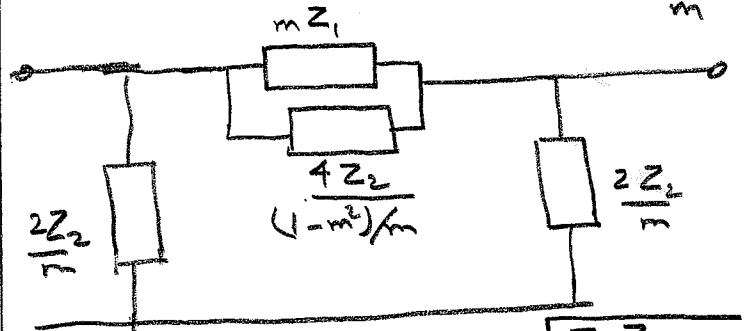
## Shunt m-derived $Z'_2 = \frac{Z_2}{m}$




$$Z_{\pi} |_{\text{Shunt m-derived}} = Z_{\pi} |_{\text{k-section}} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}}$$

$$Z_T |_{\text{Shunt m-derived}} = \frac{Z'_1 Z'_2}{Z_{\pi} |_{\text{k-section}}}$$

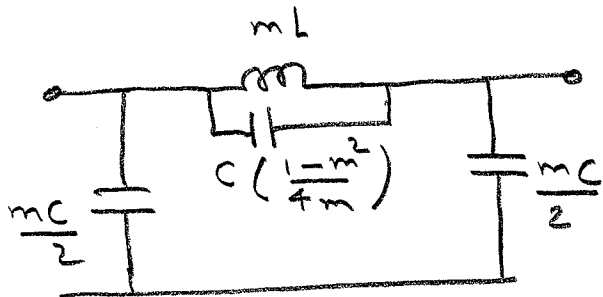

$$Z_{\pi} |_{\text{Shunt m-derived}} = Z_{\pi} |_{\text{k-section}} = \frac{R_0}{\sqrt{1 - \frac{\omega^2}{\omega_c^2}}}$$

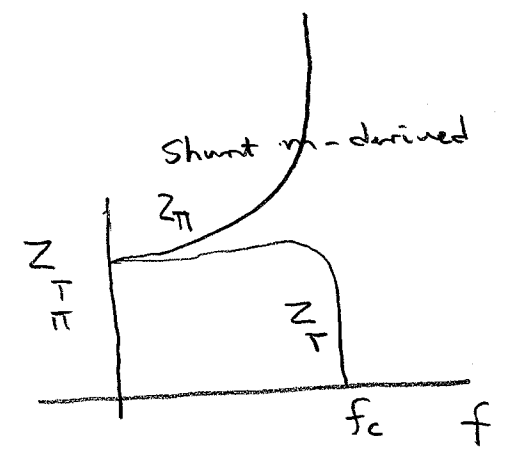

For a high pass filter

$$Z_1 = \frac{1}{j\omega C} ; Z_2 = j\omega L$$

pass band:  $-1 \leq \frac{Z_1}{4Z_2} (= -\frac{\omega_c^2}{\omega^2}) \leq 0$

@  $\omega = \omega_c ; \frac{Z_1}{4Z_2} = -1$   
 for  $\omega > \omega_c ; \frac{Z_1}{4Z_2} = -\frac{\omega_c^2}{\omega^2}$   
 is between -1 & 0


$$\beta = \cos^{-1} \left( 1 + \frac{Z_1}{4Z_2} \right) = \cos^{-1} \left( 1 - 2 \frac{\omega_c^2}{\omega^2} \right)$$

$$= \pm 2 \sin^{-1} \sqrt{-\frac{Z_1}{4Z_2}} = \pm 2 \sin^{-1} \left( \frac{\omega_c}{\omega} \right)$$

Stop band


$$\alpha = 2 \cosh^{-1} \left( -\frac{Z_1}{4Z_2} \right)^{1/2}$$

$$= 2 \cosh^{-1} (\omega_c/\omega)$$


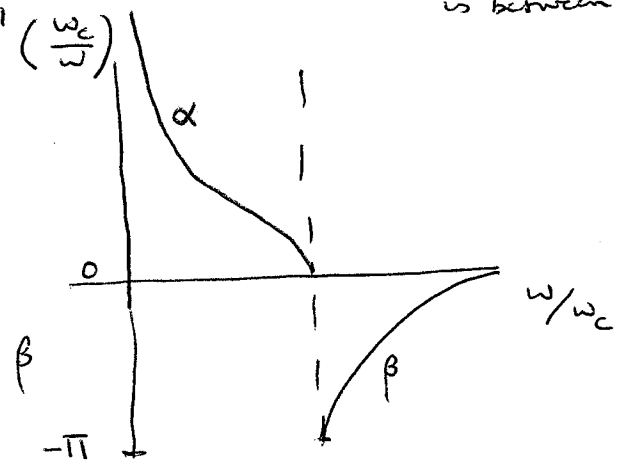


$$Z_{iT} = R_0 \sqrt{1 - \frac{\omega_c^2}{\omega^2}}$$
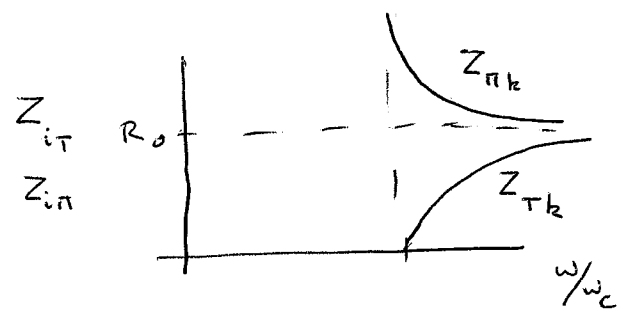
$$Z_{i\pi} = R_0 / \sqrt{1 - \frac{\omega_c^2}{\omega^2}}$$




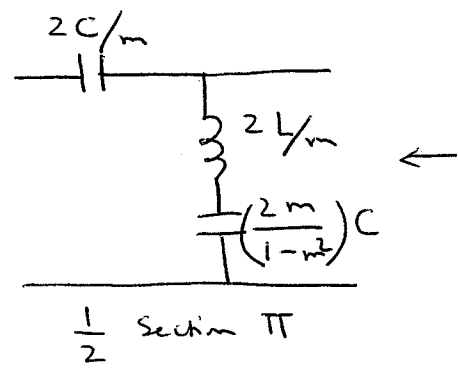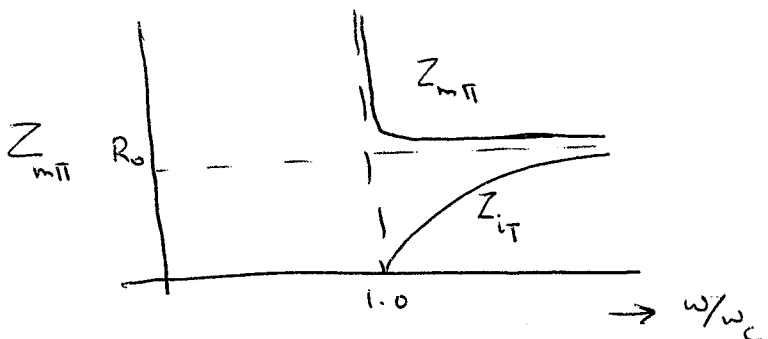For series m-derived (see also p.442 Table 8.2)



$$Z_{m\pi} = R_0 \frac{1 - f_{\infty}^2/f^2}{\sqrt{1 - f_c^2/f^2}}$$

# A Composite Low-Pass Filter

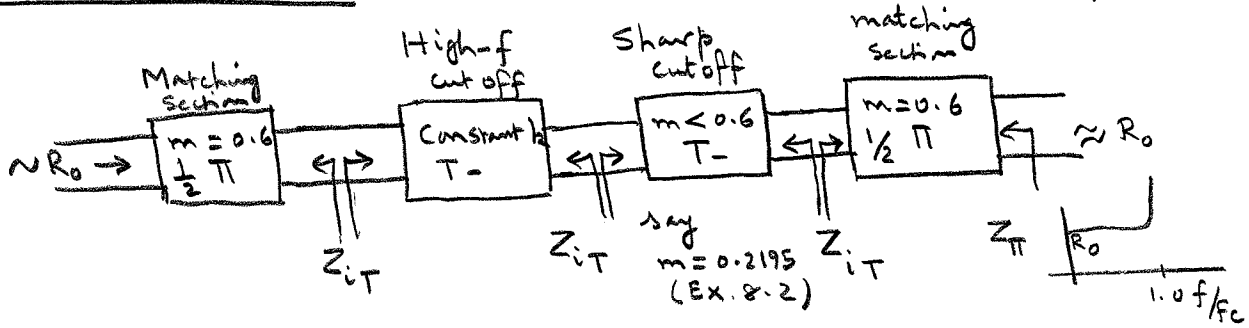


EX. 8.2 p. 388

$f_c = 2.0 \text{ MHz}$   
 $f_{\infty} = 2.05 \text{ MHz}$

$f'_c = 3000 \text{ MHz}$   
 $f'_{\infty} = 3075 \text{ MHz}$


$f_{\infty} = \frac{f_c}{\sqrt{1-m^2}}$   
 $m' = 0.2195$

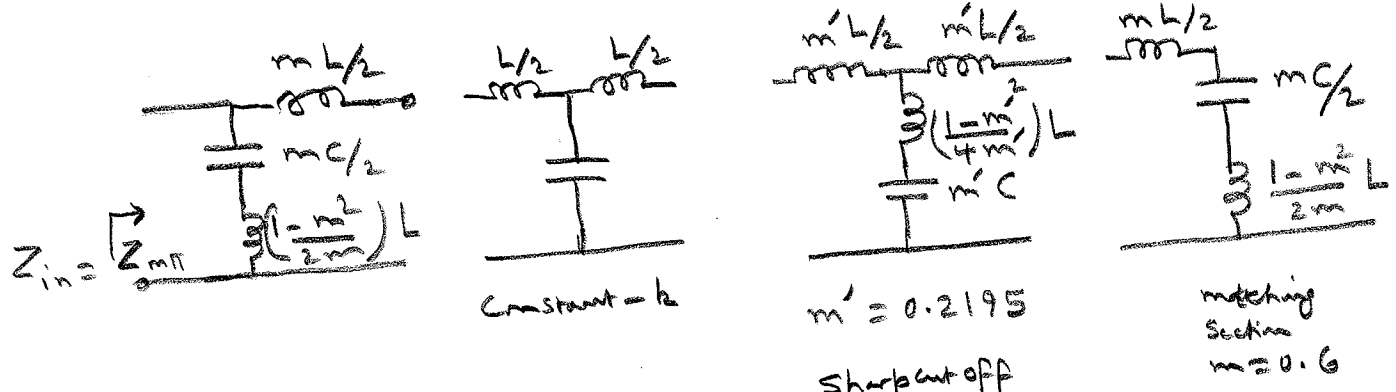$Z_{m\pi} = R_0 \frac{1 - \frac{\omega L}{\omega_c L}}{\sqrt{1 - \frac{\omega L}{\omega_c L}}}$   
 $\frac{Z_1 Z_2}{Z_{m\pi}}$



From p. 2 of handout notes

$$L = \frac{2 R_0}{\omega_c} ; C = \frac{2}{\omega_c R_0} ; \omega_c = \frac{2}{\sqrt{LC}}$$

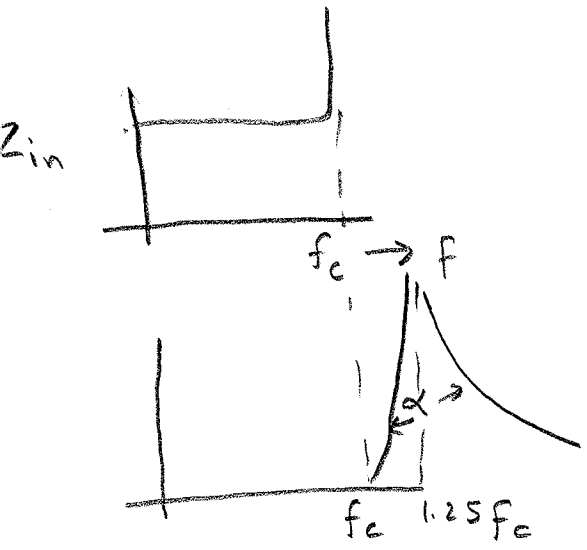

Ex 8.2 p. 388 Text

$$f_c = 2 \text{ MHz}$$

$$f_{\infty} = 2.05 \text{ MHz}$$

$$m = \sqrt{1 - \frac{f_c^2}{f_{\infty}^2}} = 0.2195$$

$$R_o = \sqrt{\frac{L}{C}} = 75 \Omega \quad (8.34) \quad \text{p. 433 Text}$$

$$f_c = \frac{1}{2\pi} \sqrt{\frac{2}{LC}} \quad (8.33)$$

$$L = \frac{2R_o}{\omega_c} = 11.94 \mu\text{H}$$

$$C = \frac{2}{R_o \omega_c} = 2.122 \text{ nF}$$

$$f'_c = 3000 \text{ MHz}$$

$$f'_{\infty} = 3075 \text{ MHz}$$

$$m = \sqrt{1 - \frac{f'_c{}^2}{f'_{\infty}{}^2}} = 0.2195$$

$$R'_o = \sqrt{\frac{L'}{C'}} = 50 \Omega$$

$$f'_c = \frac{1}{2\pi} \sqrt{\frac{2}{L'C'}}$$

$$L' = \frac{2R'_o}{\omega'_c} = \left(\frac{50}{75 \times 1500}\right) \times 11.94 \times 10^3 \text{ nH} = 5.31 \text{ nH}$$

$$C' = \frac{2}{R'_o \omega'_c} = \left(\frac{75}{50}\right) \frac{1}{1500} \times 2122 \text{ pF} = 2.122 \text{ pF}$$

Redrawn ckt. of Fig. 8.19 p. 388 (divide L's by 2250 and C's by 1000)

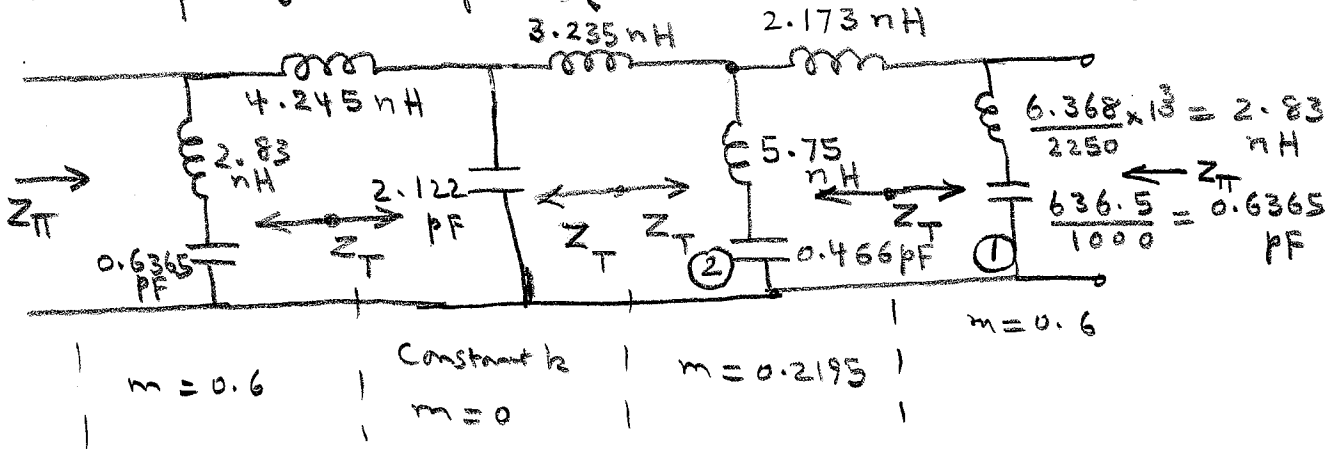



Fig. 8.19 A Composite filter with  $f'_c = 3000 \text{ MHz}$ ;  $f'_{\infty} = 3075 \text{ MHz}$   
(redrawn)  $m = 0.2195$

For the above circuit note the following resonant frequencies for the shunt arms:


For arm ① 
$$f_{r,1} = \frac{1}{2\pi \sqrt{(2.83 \times 10^{-9})(0.6365 \times 10^{-12})}} = 3.75 \text{ GHz} \quad (m = 0.6)$$

for arm ② 
$$f_{r,2} = \frac{1}{2\pi \sqrt{(5.75 \times 10^{-9})(0.466 \times 10^{-12})}} = 3.075 \text{ GHz} \quad (m = 0.2195)$$

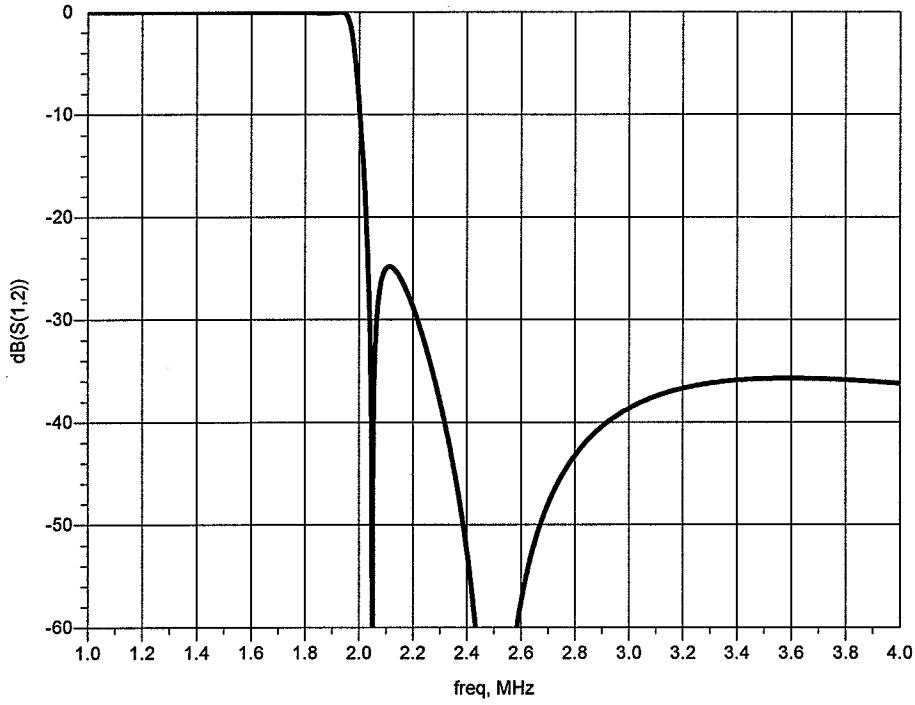Frequency response for the low-pass filter of Example 8.2 with cut-off frequency of 2 MHz.  $R_0 = 75 \text{ ohm}$ .



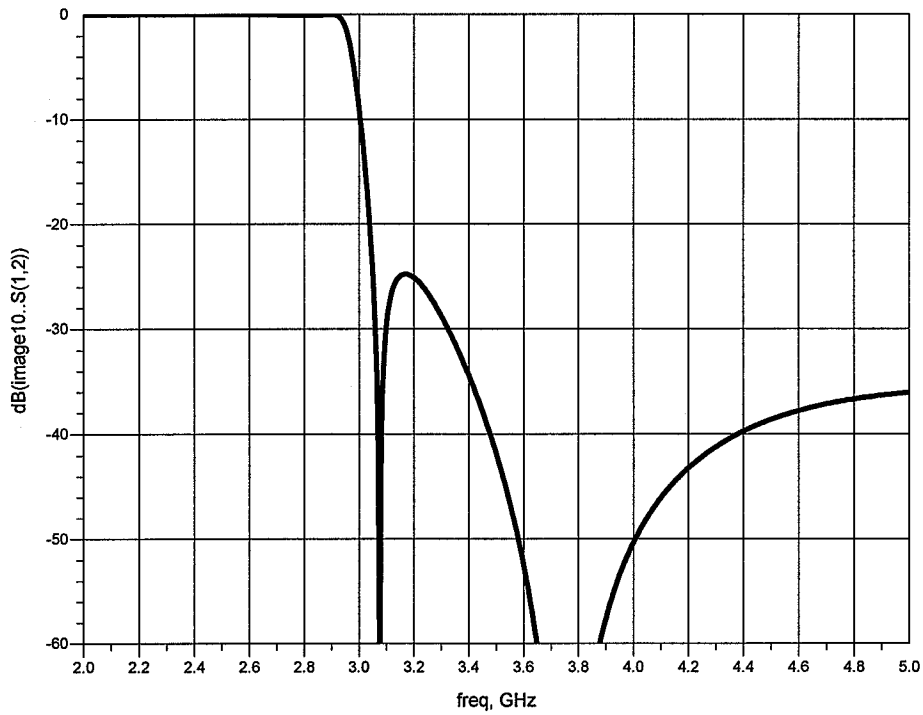Frequency response for the scaled microwave filter with cut-off frequency of 3 GHz, designed on pg. 10 of classnotes.  $R_0 = 50 \text{ ohm}$




Lab. #4 Filter #2 See Section 8.3 Insertion Loss Method

(See also Example 8.3 p. 400 Text)

$N = 5$ ,  $0.5$  dB, Low Pass Filter (Equal-ripple filter)

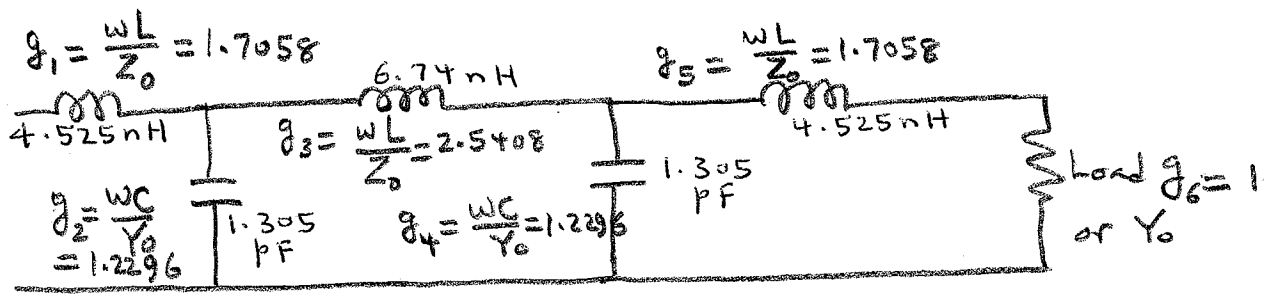For a filter starting and ending with a series inductor (see the suggested configuration for filter #2 for Lab. 4, use the circuit of Fig. 8.25(b) p. 393 Text (see parameters  $g_1$  to  $g_6$  in Table 8.4)



See p. 394  $g_k =$  inductance for series inductors ( $\omega L/Z_0$ )  
 ( $k=1$  to  $N$ )  
 $=$  Capacitance for shunt capacitors ( $\frac{\omega C}{Y_0}$ )

For cutoff frequency  $f_c = 3.0$  GHz,  $Z_0 = 50 \Omega$

for  $\frac{\omega L}{Z_0} = 1.7058$        $L = 4.525$  nH  
 $\frac{\omega C}{Y_0} = 1.2296$        $C = 1.305$  pF  
 $\frac{\omega L}{Z_0} = 2.5408$        $L = 6.740$  nH

As discussed on the following page 12, the inductances can be obtained by using high  $Z_0$  microstriplines (for  $Z_0 = 120 \Omega$ ;  $L_c = 0.521$  nH/mm) and capacitances may be obtained by using low  $Z_0$  microstriplines (for  $Z_0 = 20 \Omega$ ,  $C_l = \frac{1}{v_p Z_0} = 0.283$  pF/mm). Alternatively the capacitances may be obtained by using open circuited stublines.

$$Y = j\omega C = jY_{0,s} \tan\left(\frac{\omega l}{v_p}\right)$$

As given in the writeup for Lab. 4 for filter #2,  $N=7$  filter may also be used. From Table 8.4 (p. 396) for  $N=7$  filter ( $0.5$  dB ripple)

$g_1 = g_7 = \frac{\omega L}{Z_0} = 1.7372$ ;  $g_2 = g_6 = \frac{\omega C}{Y_0} = 1.2583$ ;  $g_3 = g_5 = \frac{\omega L}{Z_0} = 2.6381$   
 $g_4 = \frac{\omega C}{Y_0} = 1.3444$



## Design of the filter circuit using Microstrip Lines

8-16

For any transmission line, from Eqns. 2.13, 2.16 p. 52

$$\text{Inductance per unit length } L_l = \frac{Z_0}{v_p}$$

$$\text{Capacitance per unit length } C_l = \frac{1}{v_p Z_0}$$

For inductances use a high  $Z_0$  line, say  $Z'_0 = 120 \Omega$

$$v_p = \frac{c}{\sqrt{\epsilon_{\text{eff}}}} \quad \text{say } \epsilon_{\text{eff}} = 1.7$$

$$L_l = \frac{Z'_0 \sqrt{\epsilon_{\text{eff}}}}{c} = \frac{120 \sqrt{1.7}}{3 \times 10^8} = 521.5 \frac{\text{nH}}{\text{m}} \Rightarrow 0.521 \frac{\text{nH}}{\text{mm}} \\ \left( 0.651 \frac{\text{nH}}{\text{mm}} \text{ for } Z_{0h} = 150 \frac{\Omega}{h} \right)$$

For capacitance use either a low  $Z_0$  line or better an open circuited stub.  $C_l = \frac{\sqrt{\epsilon_{\text{eff}}}}{c Z_0} = 0.283 \text{ pF/mm}$  for  $Z_0 = 20 \Omega$  line

For an open circuited stub, the equivalent capacitance  $C_{\text{eq}}$  is given by:

$$Y = j Y_{0s} \tan(\beta l) \Rightarrow j \omega C_{\text{eq}}$$

For the shunt arms ①, ② use open circuited stubs of lengths  $\lambda_g/4$  at 3.75 GHz and 3.075 GHz, respectively.

$$Y_{\text{stub}} = j Y_{0s} \tan \pi/2 = \infty$$

$$Z_{\text{stub}} = 0$$

The shunt arms ① and ② amount to an impedance of 0 or short circuit at 3.75 and 3.075 GHz.

A high pass filter with  $f_c = 4.0 \text{ GHz}$

From Table 8.2 p. 387

$$R_0 = \sqrt{L/C} = 50 \Omega$$

$$\omega_c = \frac{1}{2\sqrt{LC}}$$

$$L = \frac{R_0}{2\omega_c} = \frac{50}{2 \times 2\pi \times 4 \times 10^9} = 0.995 \text{ nH}$$

$$C = \frac{1}{2\omega_c R_0} = \frac{1}{2 \times 2\pi \times 4 \times 10^9 \times 50} = 0.398 \text{ pF}$$

$m = 0.6$  filter for matching


$$f_{\infty} = f_c \sqrt{1-m^2} = 4 \times 0.8 = 3.2 \text{ GHz}$$

Note that the resonant frequency of the shunt arm is


$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi \times \sqrt{3.317 \times 10^{-9} \times 0.746 \times 10^{-12}}} = 3.2 \times 10^9 \rightarrow 3.2 \text{ GHz}$$

The shunt arm can be realized as an open-circuited shunt stub of length  $\lambda_g/4$  at 3.2 GHz

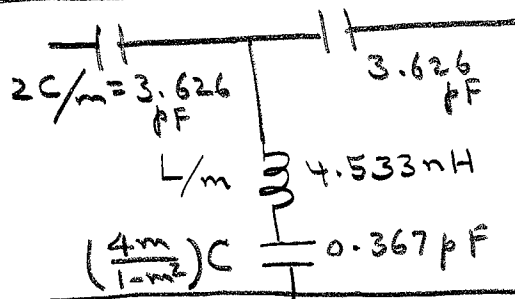
$m = 0.2195$  sharp cut off filter, full section T



Constant-k T section

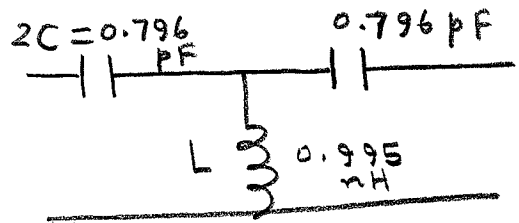


1/2 pi m-derived filter

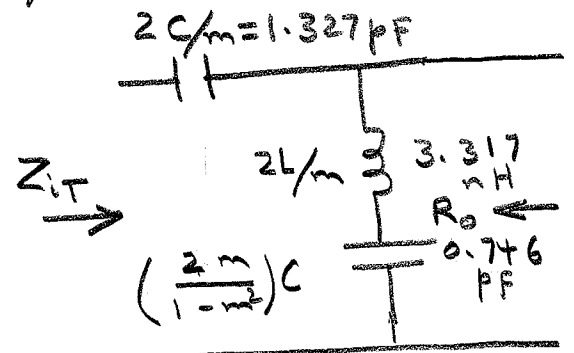

We can combine the various stages to create a four-stage composite filter of configuration similar to Fig. 8.18 p. 387

All C's in pF; All L's in nH

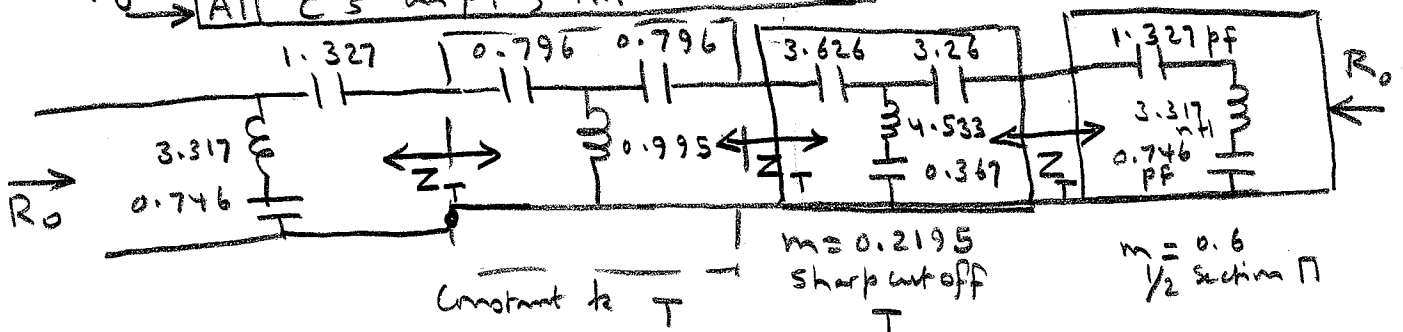

# 8.4 Transformation of Low-Pass to High-Pass Filters

For maximally Flat or Equal-ripple filters

See also Table 8.6

Low-Pass



High-Pass

$$g_k = \frac{\omega_c L}{Z_0}$$




$$\frac{\omega'_c C}{Y_0} = \frac{1}{g_k}$$

$$g_k = \frac{\omega_c C}{Y_0}$$

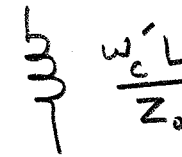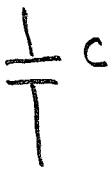

$$\frac{\omega'_c L}{Z_0} = \frac{1}{g_k}$$

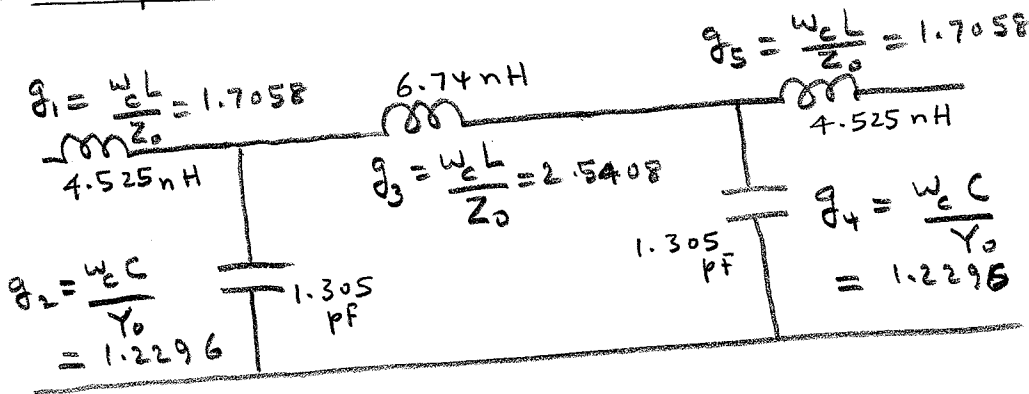For the low-pass filter on p. 111 ( 0.5 dB N=5 Equal-ripple filter )



Transformed High-Pass Filter

