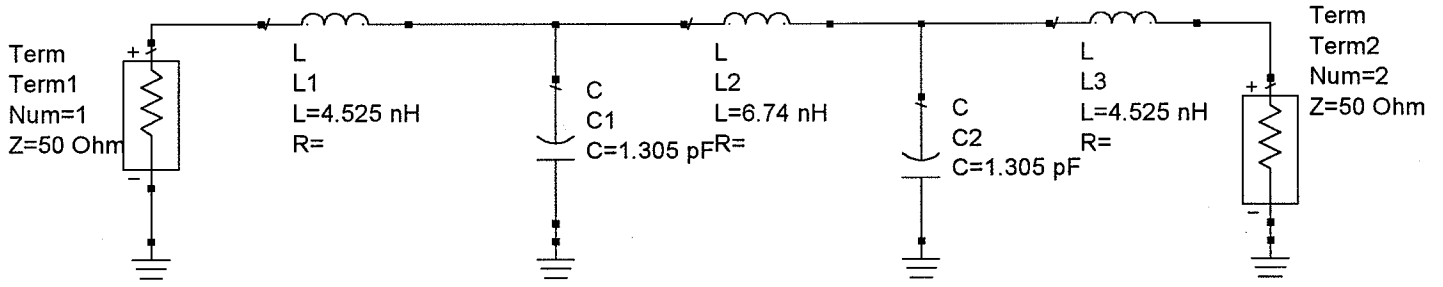



low-pass Filter



S PARAMETERS


S_Param
SP1
Start=1.0 GHz
Stop=8.0 GHz
Step=

← Transformed high-pass Filter

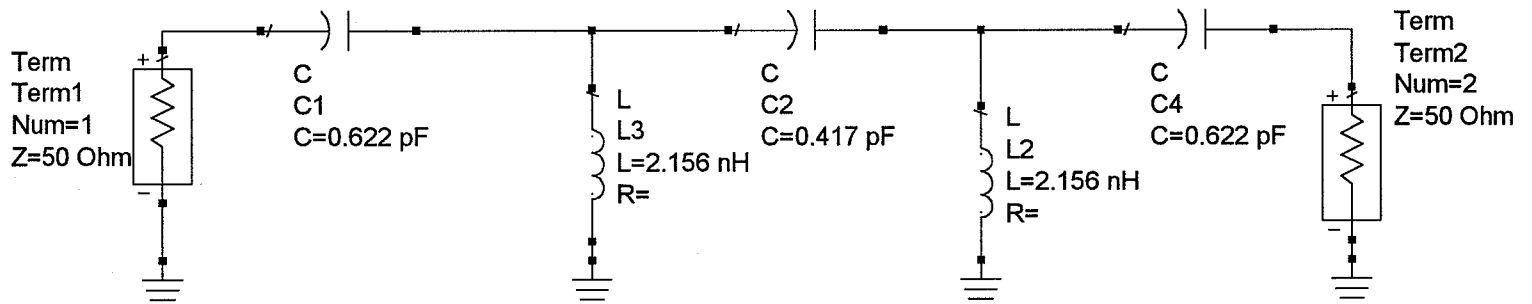


S PARAMETERS

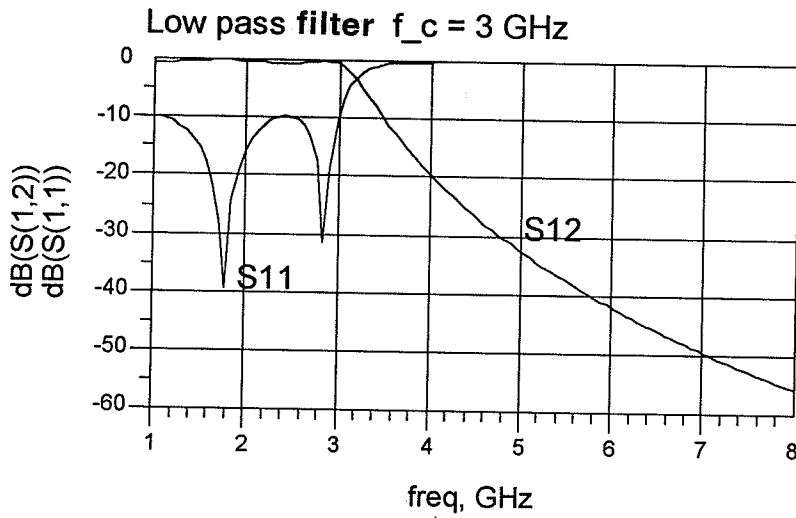S_Param
SP1
Start=1.0 GHz
Stop=8.0 GHz
Step=



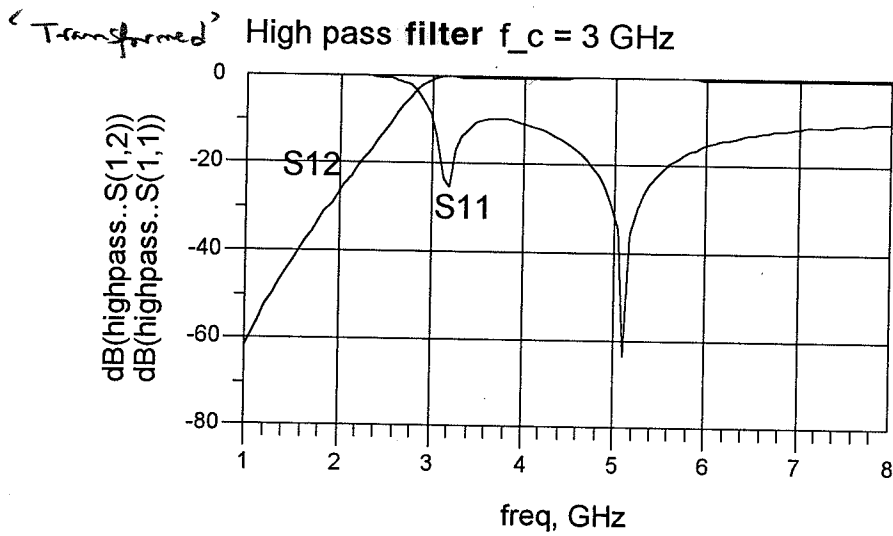Calculated S-parameters for Low-Pass Filter of p. 14




For transformed high-pass filter of p. 14

Alternative Design for the $N=5$, 0.5 dB Low-pass Filter on p. 8-15

8-22


Prototype beginning with a shunt element (Fig. 8.25 a) rather than with a series element (Fig. 8.25 b) used previously on p. 17

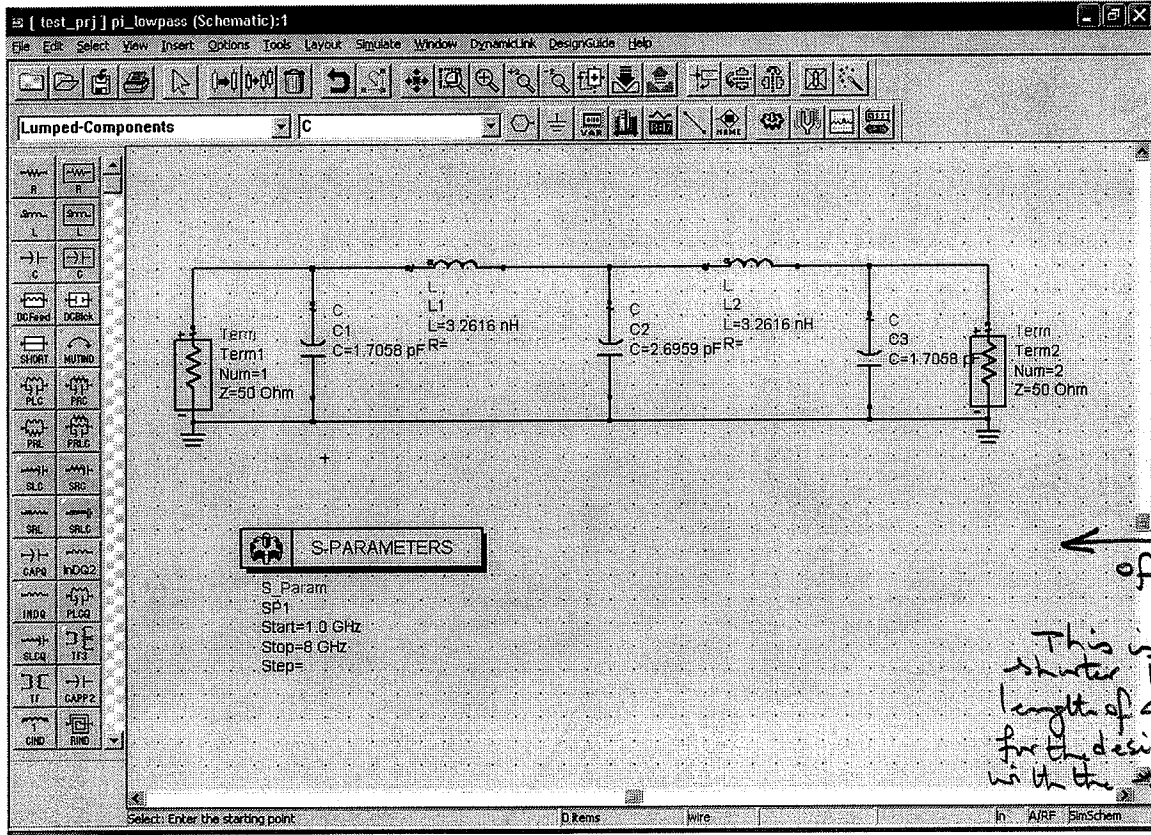Low-pass π -section filter, $f_c = 3$ GHz





Assume
 $L_e = 0.5 \frac{\text{nH}}{\text{mm}}$
 $C_e = 0.3 \frac{\text{pF}}{\text{mm}}$
 Total length of the filter ≈ 33.4 mm

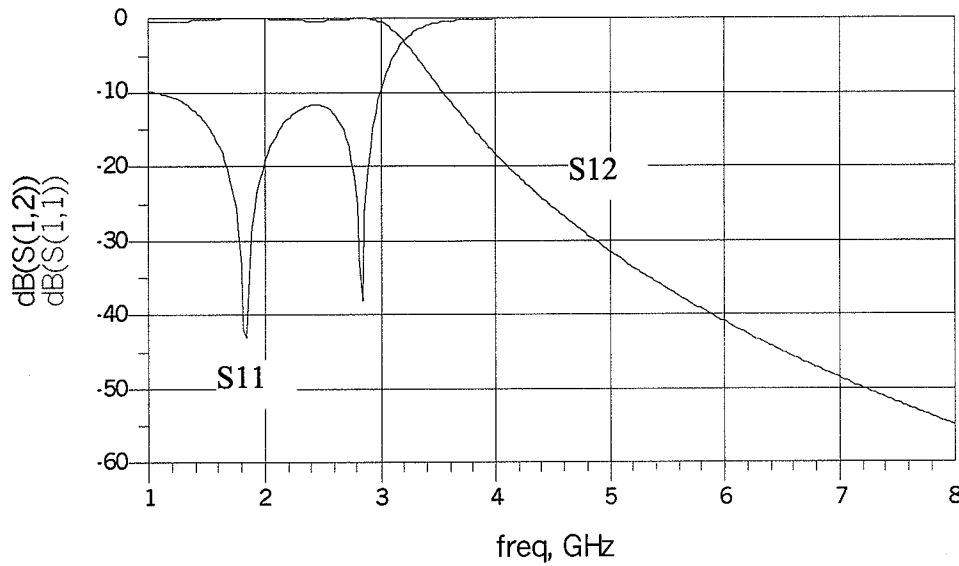This is somewhat shorter than the required length of 40.3 mm for the design beginning with the series element on p. 17 of the Notes.




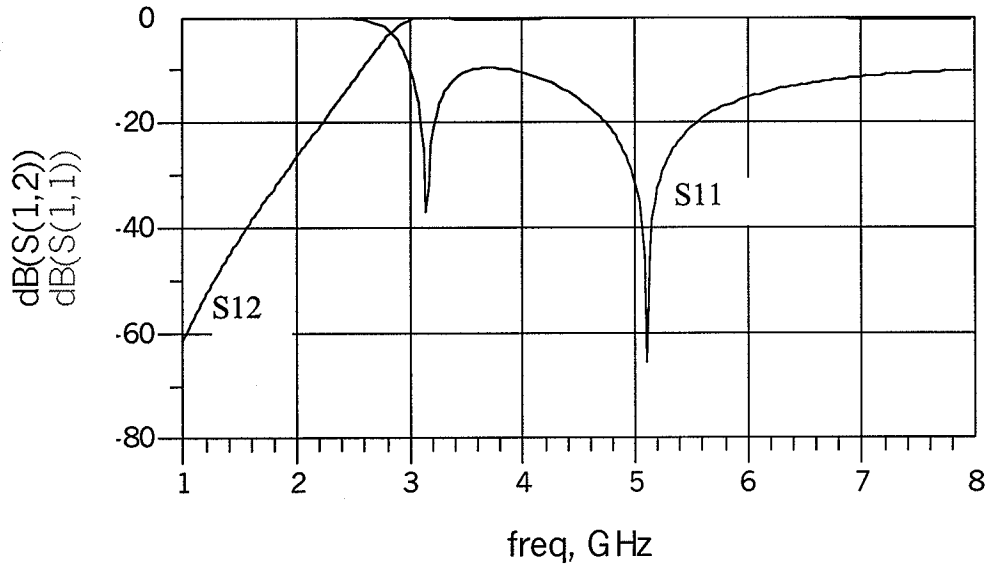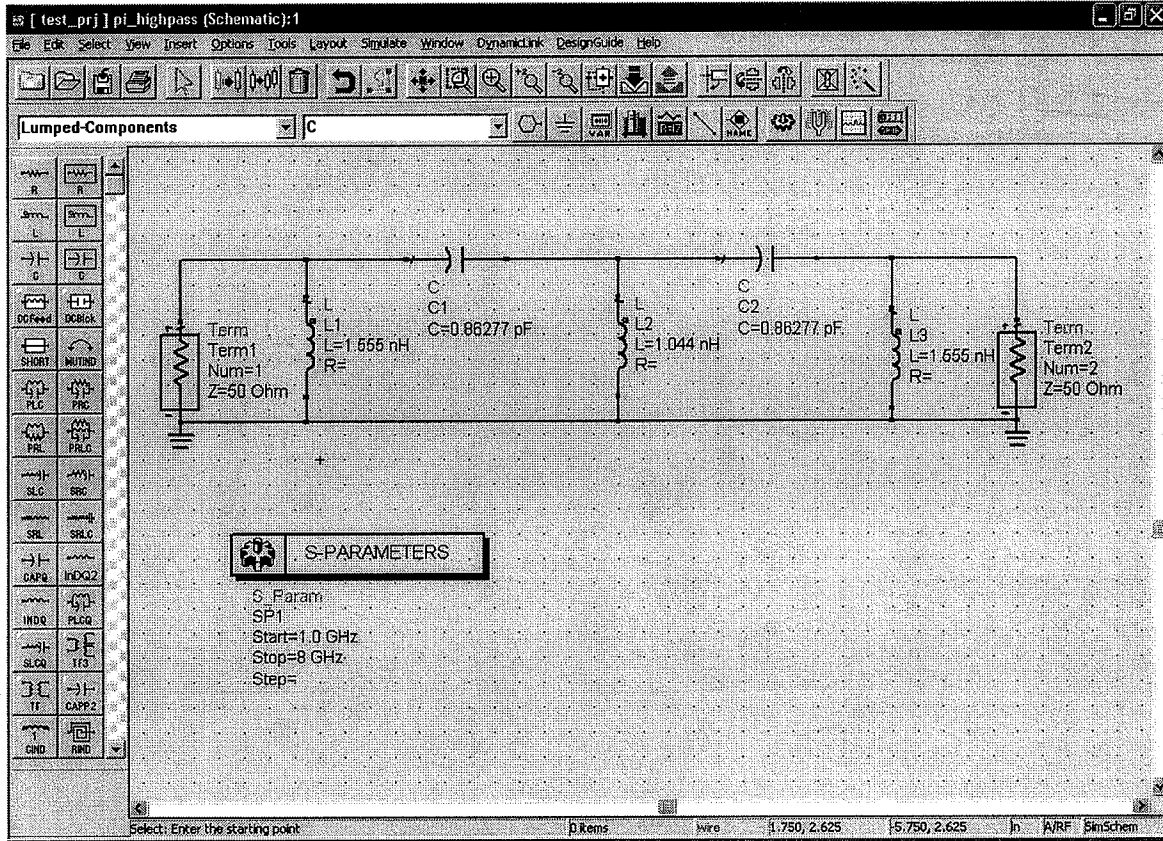High-pass π -section filter, $f_c = 3$ GHz






Define $\Delta = \frac{\omega_2 - \omega_1}{\omega_0}$ (8.72)

See Table 8.6 p. 404

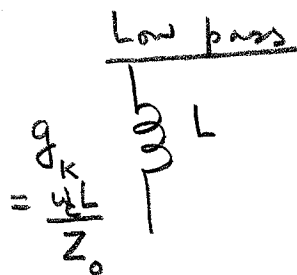

Bandpass

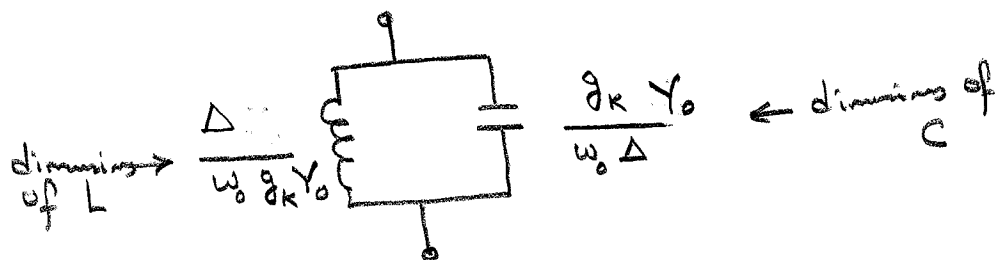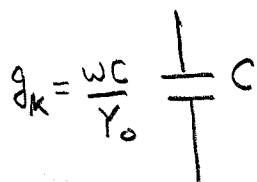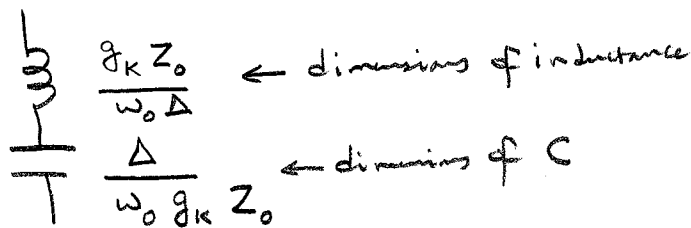

Ex. 8.4 Bandpass Filter Design

p. 404 Text

0.5 dB equal-ripple filter ; $N=3$; $f_0 = 1.6 \text{ kHz}$; $\Delta = 0.1$
 $Z_0 = 50 \Omega$

From Table 8.4 for $N=3$

- $g_1 = 1.5963$ (inductance)
- $g_2 = 1.0967$ (capacitance)
- $g_3 = 1.5963$ (inductance)

for bandpass filter, the inductance g_1 can be replaced by ($g_1 = 1.5963$)

$L = \frac{1.5963 \times 50}{2\pi \times 10^3 \times 0.1} = 127.0 \text{ nH}$


$C = \frac{\Delta / (\omega_0 g_k Z_0)}{2\pi \times 10^3 \times 1.5963 \times 50} = 0.199 \text{ pF}$

The capacitance C of the low pass Filter ($g_k = 1.0967$) can be replaced by

$L = \frac{\Delta}{\omega_0 g_k \frac{1}{50}} = \frac{0.1}{2\pi \times 10^3 \times 1.0967 \times \frac{1}{50}} = 0.726 \text{ nH}$

$C = \frac{g_k Y_0}{\omega_0 \Delta} = \frac{1.0967 \times \frac{1}{50}}{2\pi \times 10^3 \times 0.1} = 34.91 \text{ pF}$

From Fig. 8.32

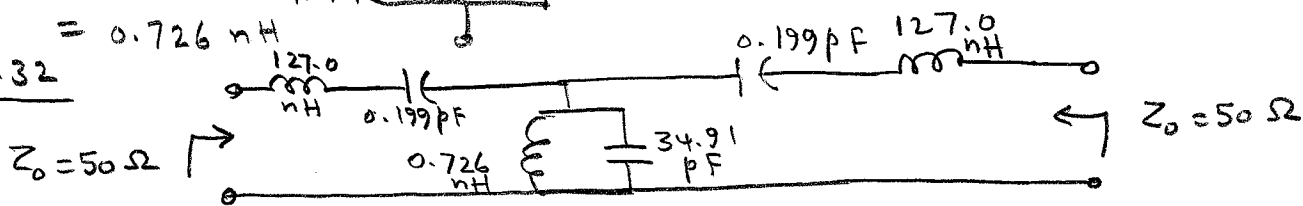

Ex. 8.6 Stepped-Impedance Filter Design
p. 414

From Table 8.3, for $N=6$ maximally flat response lowpass filter, the elements required are:

$$\begin{aligned} g_1 &= 0.517, & g_2 &= 1.414, & g_3 &= 1.932 \\ g_4 &= 1.932, & g_5 &= 1.414, & g_6 &= 0.517 \\ g_7 &= 1.0 \end{aligned} \quad (1)$$

From p. 12 of these notes

$$C_l = \frac{1}{v_p Z_l} \quad (2a) \quad L_l = \frac{Z_h}{v_p} \quad (2b)$$

Thus if a capacitor element is used for the filter, say g_1 ,

$$g_1 = \frac{\omega_c C}{Y_0} = \omega_c C Z_0 \quad (3)$$

length of the microstripline needed to get the needed capacitance (from Eqs. 2a, 3)

$$l = \frac{C}{C_l} = \left(\frac{g_1}{\omega_c Z_0} \right) v_p Z_l = \frac{g_1 Z_l}{\beta_c Z_0} \quad (4)$$

where $\beta_c = \omega_c / v_p$

$$\text{Thus } \beta_c l = g_1 \frac{Z_l}{Z_0} \quad \text{for capacitive sections} \quad (5)$$

Similarly for inductive elements say g_2

$$g_2 = \frac{\omega_c L}{Z_0} \quad (6)$$

$$l = \frac{L}{L_l} = \left(\frac{g_2 Z_0}{\omega_c} \right) \left(\frac{v_p}{Z_h} \right) \quad (7)$$

$$\beta_c l = g_2 \frac{Z_0}{Z_h}$$

For Ex. 8.6 the text selects $Z_0 = 50 \Omega$, $Z_l = 20 \Omega$, $Z_h = 120 \Omega$

- $C_1: \beta_c l_1 = g_1 \frac{20}{50} = 0.517 \times \frac{20}{50} = 0.2068 \text{ rad} \Rightarrow 11.8^\circ$
- $L_2: \beta_c l_2 = g_2 \frac{50}{120} = 1.414 \times \frac{50}{120} = 0.589 \text{ rad} \Rightarrow 33.8^\circ$
- $C_3: \beta_c l_3 = g_3 \frac{20}{50} = 1.932 \times \frac{20}{50} = 0.773 \text{ rad} \Rightarrow 44.3^\circ$
- $L_4: \beta_c l_4 = g_4 \frac{50}{120} = 1.932 \times \frac{50}{120} = 0.805 \text{ rad} \Rightarrow 46.1^\circ$
- $C_5: \beta_c l_5 = g_5 \times \frac{20}{50} = 1.414 \times \frac{20}{50} = 0.5656 \text{ rad} \Rightarrow 32.4^\circ$
- $L_6: \beta_c l_6 = g_6 \frac{50}{120} = 0.517 \times \frac{50}{120} = 0.2154 \text{ rad} \Rightarrow 12.3^\circ$

Total length of filter = 180.7°
 $\approx \lambda_g / 2$

8.7 Design of a Coupled Line Bandpass filter (pp. 416 - 426)

8-26

Step 1

see Ex. 8.7 pp. 425, 426

Determine J_n for the prototype low pass filter
from Table 8.3 for a maximally flat LP filter

from Table 8.4 for an equal-ripple or Chebyshev LP filter (a faster attenuation for stop band)

Step 2

Eqs 8.121 a-c p. 425

determine admittance inverter constants J_1, J_2, \dots, J_{N+1}

This helps in determining $Z_0 J_1, Z_0 J_2, \dots, Z_0 J_{N+1}$

Step 3

Determine Z_{oe}, Z_{oo} for various sections (Eqs. 8.108 a, b p. 421)

$$Z_{oe} = Z_0 [1 + JZ_0 + (JZ_0)^2] \quad (8.108 \text{ a})$$

$$Z_{oo} = Z_0 [1 - JZ_0 + (JZ_0)^2] \quad (8.108 \text{ b})$$

Step 4

Determine C_n from Eq. 7.81 and Z_{on} from Eq. 7.77

$$C_n = \frac{Z_{oe} - Z_{oo}}{Z_{oe} + Z_{oo}} \quad (7.81)$$

$$Z_{on} = \sqrt{Z_{oe} Z_{oo}} \quad (7.77)$$

The spacings and widths to use for the various coupled sections are then given from Figs. 7.29 or 7.30, as appropriate.