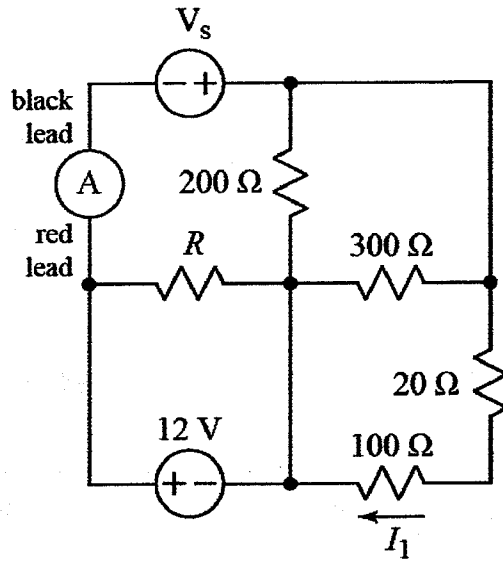


1. (25 points)




The ideal ammeter in the above circuit measures 0.8 A.

15 pts a) Find the value of V_s .

10 pts b) Find the value of I_1 .

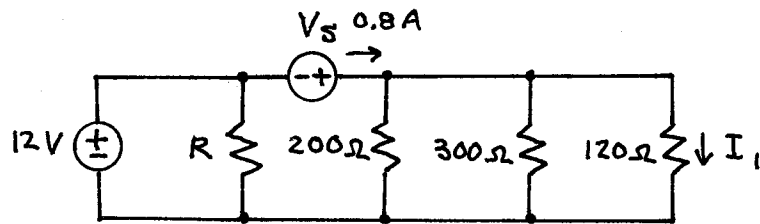Sol'n: a), b) The above circuit is equivalent to the following:



We have two circuits in parallel across the 12V source. One circuit is unknown R . The other circuit is V_s and all other R 's.

We are interested in the second circuit, and since we may solve the circuits separately we ignore R .

We have a current divider for I_1 .

$$I_1 = 0.8 \text{ A} \cdot \frac{200 \parallel 300}{200 \parallel 300 + 120} \frac{\cancel{\Omega}}{\cancel{\Omega}}$$

where $200 \parallel 300 = 100 \cdot 2 \parallel 3 = 100 \left(\frac{6}{5} \right)$

" $= 120 \Omega$


$$I_1 = 0.8 \text{ A} \frac{120}{240} = \boxed{0.4 \text{ A} = I_1}$$

We have $200 \parallel 300 \parallel 120 \Omega = 120 \parallel 120 \Omega = 60 \Omega$

The voltage drop across $200 \parallel 300 \parallel 120 \Omega$ is

$$V_{R's} = 60 \Omega \cdot 0.8 \text{ A} = 48 \text{ V}$$

So we have a V-loop:

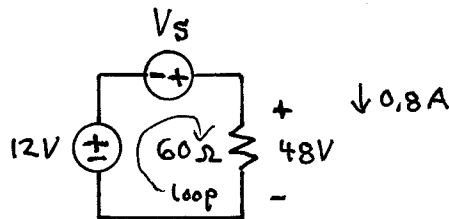

$$12 \text{ V} + V_s - 48 \text{ V} = 0 \text{ V}$$

We have $\boxed{V_s = 36 \text{ V}}$