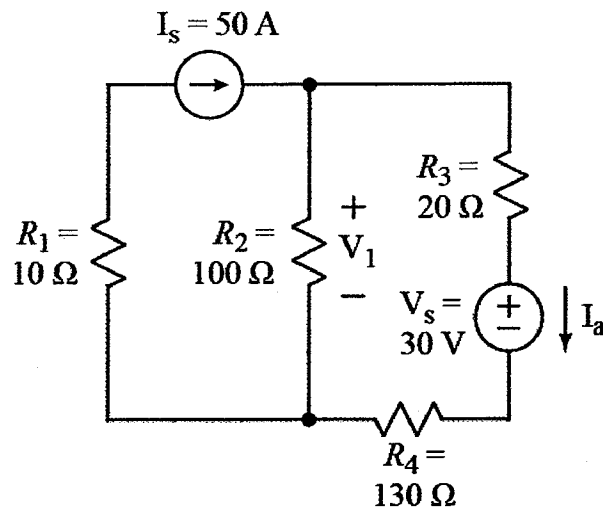


2. (20 points)




Use the method of superposition to find the values of the following:

10 pts a)  $V_1$

10 pts b)  $I_a$

sol'n: a), b) case I:  $I_s$  on,  $V_s$  off = wire

$$I_s = 50A$$

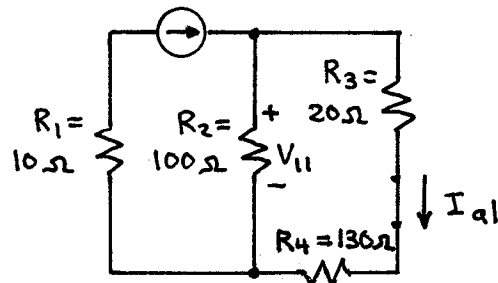

We have current divider.


$$I_{a1} = 50A \cdot \frac{R_2}{R_2 + R_3 + R_4} = 50A \frac{100}{100 + 20 + 130} = 50A \cdot \left(\frac{2}{5}\right)$$

$$I_{a1} = \frac{100}{5} A = 20A$$

$$V_{11} = 50A \cdot \frac{(R_3 + R_4)R_2}{R_2 + R_3 + R_4} = 50A \cdot 150 \parallel 100$$

$$V_{11} = 50A \cdot 50 \cdot 3 \parallel 2 \Omega = \frac{15K}{5} V = 3kV$$

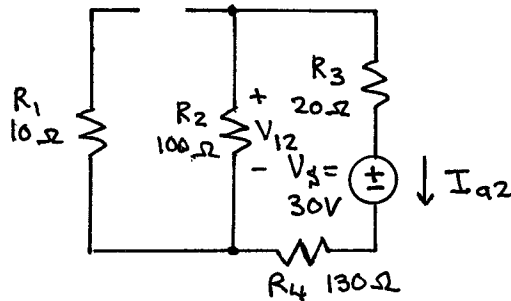case II:  $I_s$  off = open,  $V_s = 30V$



We have a V-divider for  $V_{12}$ .

$$V_{12} = V_s \cdot \frac{R_2}{R_2 + R_3 + R_4} = 30V \cdot \frac{100\Omega}{250\Omega}$$

$$V_{12} = 12V$$

We use Ohm's law to find  $I_{a2}$ .

$$I_{a2} = \frac{-V_s}{R_2 + R_3 + R_4} = \frac{-30V}{250\Omega} = -0.12A$$

Now we'll sum results for final answer.

$$V_1 = V_{11} + V_{12} = 3000V + 12V = 3012V$$

$$I_a = I_{a1} + I_{a2} = 20A + -0.12A = 19.88A$$

$$V_1 = 3012V$$

$$I_a = 19.88A$$