
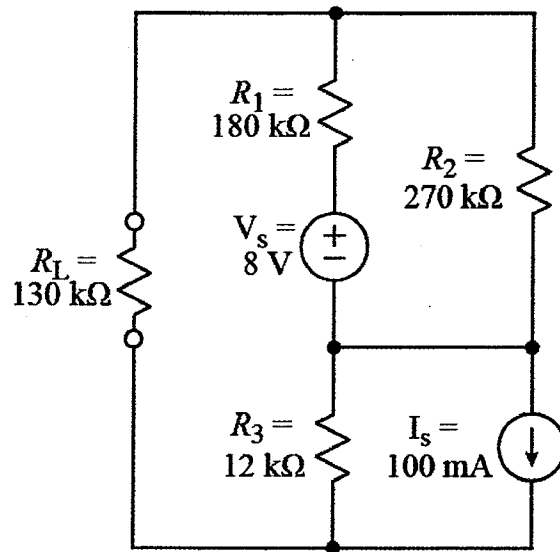


3. (25 points)

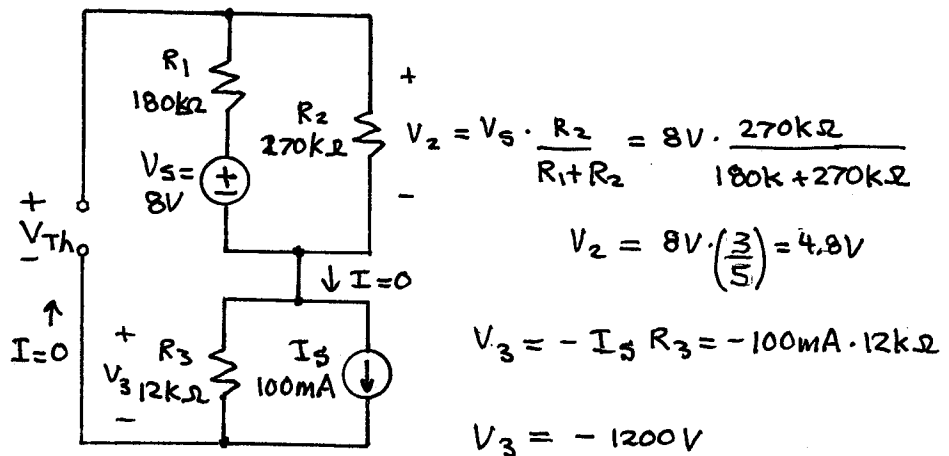


- 15 pts a) Find and draw the Thevenin equivalent of the circuit shown. The load resistor is  $R_L$ .
- 4 pts b) Find the voltage across  $R_L$  using your Thevenin equivalent circuit.
- 6 pts c) Choose a different value of  $R_L$  so as to maximize the power dissipated in  $R_L$ . Find that maximum power.

sol'n: a)  $V_{Th} = V$  across terminals for  $R_L$  with  $R_L$  removed from the circuit.



$$V_{Th} = \frac{16}{3}V - 1200V = -1195.2V$$



We turn off sources to find  $R_{Th}$ .

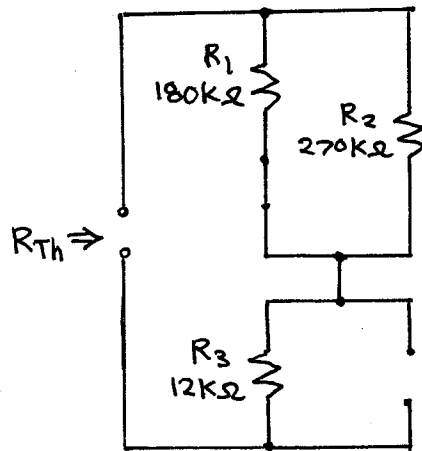

$$R_{Th} = 180k \parallel 270k \Omega + 12k \Omega$$

$$= 90k \cdot 2 \parallel 3 \Omega + 12k \Omega$$
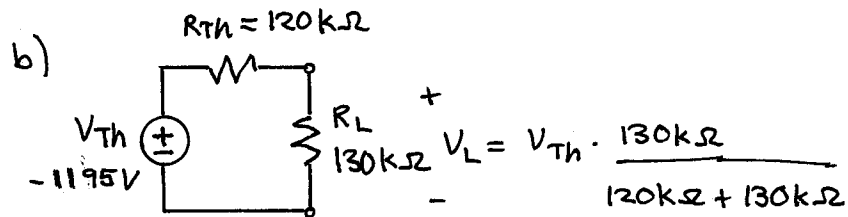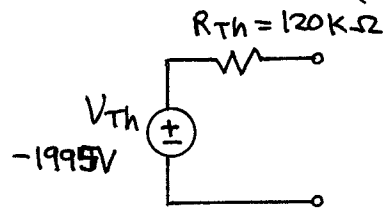
$$R_{Th} = 90k \left( \frac{6}{5} \right) + 12k \Omega = 108k \Omega + 12k \Omega = 120k \Omega$$



$$V_L = -1195V \cdot \frac{13}{25} \approx -1200V \cdot \left( \frac{13}{25} \right)$$

$$V_L \approx -48(13) = -624V$$

c) Use  $R_L = R_{Th} = 120k \Omega$  for max pwr.

$$\text{Max pwr} = \frac{V_{Th}^2}{4R_{Th}} = \frac{1195^2}{4(120k)} = 2.975W$$