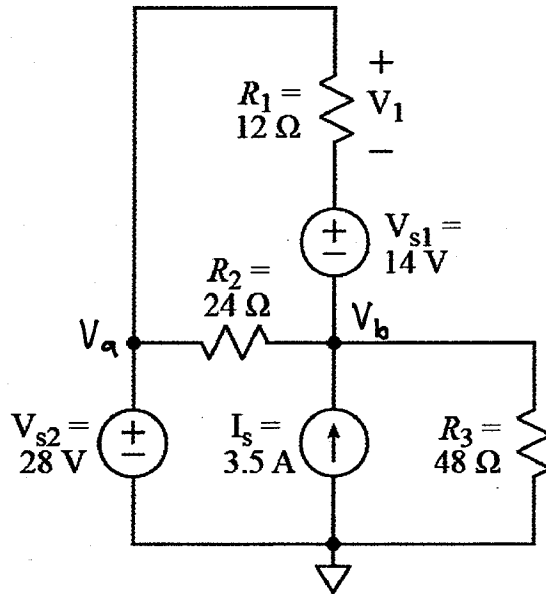


4. (20 points)



Use nodal analysis to find the voltage V_1 . You **must** show all the steps of nodal analysis work to get credit, including drawing appropriate symbols and labels on the circuit shown.

sol'n: V_a node = 28V because of V_{s2}

$$V_b \text{ node: } \frac{V_b - 28V}{24\Omega} + \frac{V_b + 14V - 28V}{12\Omega} + \frac{V_b}{48\Omega} = 3.5A$$

$$\text{or } V_b \left(\frac{1}{24\Omega} + \frac{1}{12\Omega} + \frac{1}{48\Omega} \right) = 3.5A + \frac{28V}{24\Omega}$$

Multiply both sides by 48Ω : $\frac{+14V}{12\Omega}$

$$V_b (2 + 4 + 1) = 3.5A(48\Omega) + 56V + 56V$$

$$V_b (7) = 168V + 56V + 56V = 280V$$

$$V_b = \frac{280}{7} V = 40V$$

$$V_1 = 28V - (V_b + 14V) = -26V$$