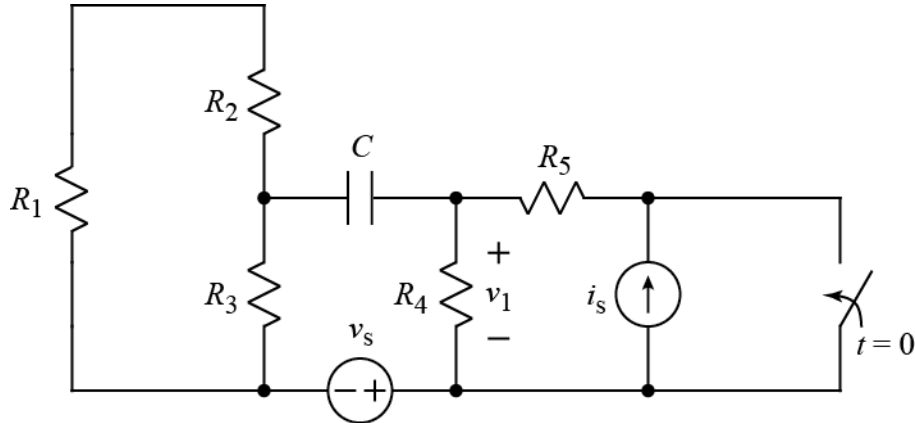


Ex:



After being open for a long time, the switch closes at $t = 0$.

$$v_s = 28 \text{ V} \quad i_s = 112 \text{ mA} \quad C = 2 \text{ nF}$$

$$R_1 = 43 \text{ } \Omega \quad R_2 = 47 \text{ } \Omega \quad R_3 = 120 \text{ } \Omega \quad R_4 = 750 \text{ } \Omega \quad R_5 = 1 \text{ k}\Omega$$

- Calculate the energy stored in the capacitor at $t = 0^+$.
- Write a numerical time-domain expression for $v_1(t > 0)$, the voltage across R_4 .

SOL'N: a) To find the charge on the capacitor at $t = 0^+$, we consider time $t = 0^-$. At $t = 0^-$, we treat the C as an open circuit, and the switch is open. In this case, R_5 is in series with current source i_s and may be ignored. Since C is open, current i_s flows in R_4 , giving rise to a voltage across R_4 . The three resistors on the left collapse into one resistor, and we observe that no current flows in v_s . We conclude that the voltage across C is the voltage drop across R_4 and v_s .

$$v_C(0^-) = v_s + i_s R_4 = 28 \text{ V} + 112 \text{ mA} \cdot 750 \text{ } \Omega = 28 \text{ V} + 84 \text{ V} = 112 \text{ V}$$

The voltage on the capacitor right after the switch moves is the same as the voltage just before the switch moves:

$$v_C(0^+) = v_C(0^-) = 112 \text{ V}$$

Now we can calculate the desired energy:

$$w_C(0^+) = \frac{1}{2} C v_C^2 = \frac{1}{2} 2\text{n}(112)^2 \text{ J} = 12.544 \text{ } \mu\text{J}$$

b) We use the general formula for RC solutions:

$$v_1(t > 0) = v_1(t \rightarrow \infty) + [v_1(0^+) - v_1(t \rightarrow \infty)]e^{-\frac{t}{R_{Th}C}}$$

First we consider time approaching infinity. The capacitor will act like an open circuit, and the switch will be closed, shorting out i_s . All of i_s will flow in the switch, rather than through R_4 and R_5 . No current in R_4 means we have no voltage drop across R_4 .

$$v_1(t \rightarrow \infty) = 0 \text{ V}$$

Second, we consider $t = 0^+$. We replace the three resistors on the left side with one resistor:

$$R_{Eq} = (R_1 + R_2) \parallel R_3 = (43 \Omega + 47 \Omega) \parallel 120 \Omega = 90 \Omega \parallel 120 \Omega$$

or

$$R_{Eq} = 30 \Omega \cdot 3 \parallel 4 = 30 \Omega \cdot \frac{12}{7}$$

We may ignore i_s since it is shorted out by the switch, and we model the C as a voltage source of value $v_C(0^+) = v_C(0^-) = 112 \text{ V}$. We are left with resistors and two voltage sources. Our value of v_1 is given by a voltage divider:

$$v_1(0^+) = (v_C - v_s) \frac{R_4 \parallel R_5}{R_{Eq} + R_4 \parallel R_5} = 84 \text{ V} \frac{250 \Omega \cdot \frac{12}{7}}{280 \Omega \cdot \frac{12}{7}} = 75 \text{ V}$$

Third, we find R_{Th} by turning off the independent sources and looking into the circuit from the terminals where C is attached.

$$R_{Th} = R_{Eq} + R_4 \parallel R_5 = 30 \Omega \cdot \frac{12}{7} + 250 \Omega \cdot 3 \parallel 4 = 30 \Omega \cdot \frac{12}{7} + 250 \Omega \cdot \frac{12}{7}$$

or

$$R_{Th} = 280 \Omega \cdot \frac{12}{7} = 40 \Omega \cdot 12 = 480 \Omega$$

The time constant is $\tau = R_{Th}C$.

$$\tau = 480 \Omega \cdot 2 \text{ nF} = 960 \text{ ns}$$

Fourth and last, we plug values into the general solution:

$$v_1(t > 0) = 0 + [75 - 0]e^{-\frac{t}{960 \text{ ns}}} \text{ V} = 75e^{-\frac{t}{960 \text{ ns}}} \text{ V}$$