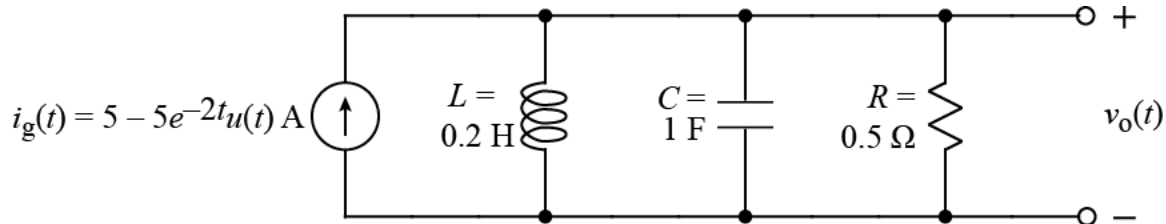


Ex:



Note: The first 5A portion of $i_g(t)$ is always on.


- Write the Laplace transform $I_g(s)$ of $i_g(t)$.
- Draw the s -domain equivalent circuit, including source $I_g(s)$, components, initial conditions for L and C , and terminals for $V_o(s)$.
- Write the Laplace transform $V_o(s)$ of $v_o(t)$. Write your answer as a ratio of polynomials in s with numerical coefficients.
- Write a numerical time-domain expression for $v_o(t)$ where $t \geq 0$.

SOL'N: a) The 5 A portion of the current source acts like $5u(t)$ for $t = 0^-$ to ∞ where the Laplace transform is computed.

$$I_g(s) = \frac{5}{s} - \frac{5}{s+2} \text{ A}$$

- b) To find initial conditions, we use the time-domain circuit at $t = 0^-$ with the C treated as an open circuit and the L treated as a wire. The 5 A portion of the current source will be on, and the second term of the current source will be off.

$t = 0^-$:

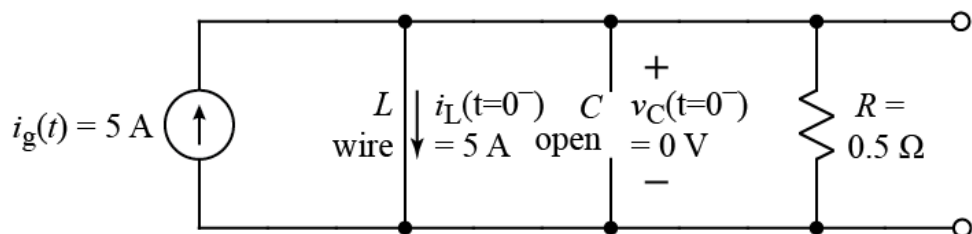

The current will all flow in the wire that models the L .

$$i_L(0^-) = 5 \text{ A}$$


Given the parallel form of the circuit, using a parallel current source for the initial conditions of the L is prudent. The current source corresponds to a step function that turns on a current in parallel with the L at time zero.

$$\frac{i_L(0^-)}{s}$$

The capacitor will have zero initial conditions since it is shorted out by the wire modeling the L .

$$v_C(0^-) = 0 \text{ V}$$

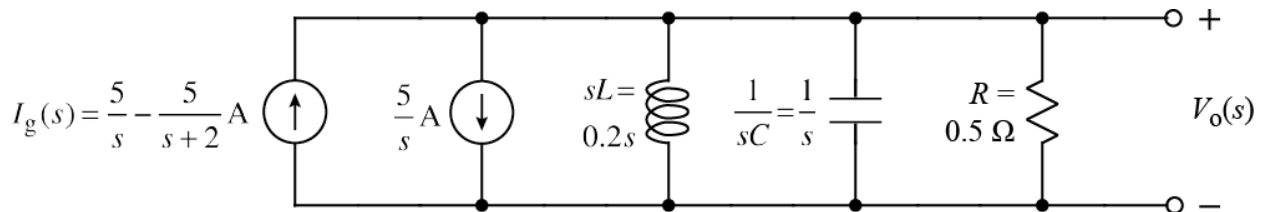The source for initial conditions on the C may be omitted.



- c) We sum the current sources, which results in some convenient cancellation. The output voltage will be the total current times the total parallel impedances.

$$V_o(s) = -\frac{5}{s+2} \text{ A} \left(sL \parallel \frac{1}{sC} \parallel R \right) = -\frac{5}{s+2} \left(\frac{1}{\frac{1}{sL} + sC + \frac{1}{R}} \right)$$

We clear the denominator of the denominator and get a coefficient of unity for the s^2 coefficient.

$$V_o(s) = -\frac{5}{s+2} \left(\frac{1}{\frac{1}{sL} + sC + \frac{1}{R}} \right) \frac{s/C}{s/C}$$

or

$$V_o(s) = -\frac{5}{s+2} \left(\frac{s/C}{\frac{1}{LC} + s^2 + \frac{1}{RC}s} \right) = -\left(\frac{5}{s+2} \right) \left(\frac{s/C}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} \right)$$

or

$$V_o(s) = -\frac{5s}{(s+2)\left(s^2 + \frac{1}{0.5}s + \frac{1}{0.2}\right)} = -\frac{5s}{(s+2)(s^2 + 2s + 5)}$$

d) We factor the quadratic polynomial in the denominator so it matches the form found in the Laplace transforms of decaying cosine and sine.

$$s^2 + 2s + 5 = (s+1)^2 + 2^2 = (s+a)^2 + \omega^2$$

$$\mathcal{L}\{e^{-at} \cos \omega t\} = \frac{s+a}{(s+a)^2 + \omega^2}$$

$$\mathcal{L}\{e^{-at} \sin \omega t\} = \frac{\omega}{(s+a)^2 + \omega^2}$$

We expand the output voltage in a modified partial fraction form.

$$V_o(s) = -\frac{5s}{(s+2)\left[(s+1)^2 + 2^2\right]} = \frac{A}{s+2} + \frac{B(s+1) + C(2)}{(s+1)^2 + 2^2}$$

We use the method of multiplying by the pole and evaluating at the pole to find the value of A.

$$A = V_o(s)(s+2)\Big|_{s=-2} = -\frac{5s}{\left[(s+1)^2 + 2^2\right]}\Big|_{s=-2} = -\frac{5(-2)}{(-2+1)^2 + 2^2}$$

or

$$A = V_o(s)(s+2)\Big|_{s=-2} = -\frac{-10}{5} = 2$$

Having found A, we put terms over a common denominator.

$$\begin{aligned} V_o(s) &= \frac{2(s^2 + 2s + 5) + [B(s+1) + C(2)](s+2)}{(s+2)\left[(s+1)^2 + 2^2\right]} \\ &= -\frac{5s}{(s+2)\left[(s+1)^2 + 2^2\right]} \end{aligned}$$

For the polynomials in the numerator to be equal, the coefficients of each power of s must be equal.

$$2(s^2 + 2s + 5) + [B(s+1) + C(2)](s+2) = -5s$$

We group the coefficients of powers of s .

$$2(s^2 + 2s + 5) + B(s^2 + 3s + 2) + C(2s + 4) = -5s$$

or

$$(2 + B)s^2 + (4 + 3B + 2C)s + (10 + 2B + 4C) = -5s$$

From the s^2 coefficient, which equals zero (on right side of equation), we find the value of B .

$$B = -2$$

From the constant coefficient, which equals zero (on right side of equation), we find the value of C .

$$10 + 2(-2) + 4C = 0$$

or

$$C = -\frac{3}{2}$$

We check our answer by trying some values of s in our original expression for $V_o(s)$ and in our modified partial fraction expression for $V_o(s)$.

$$V_o(s)|_{s=0} = \left[-\frac{5s}{(s+2)[(s+1)^2 + 2^2]} \right]_{s=0} = 0$$
$$\left[\frac{2}{s+2} + \frac{-2(s+1) - \frac{3}{2}(2)}{s^2 + 2s + 5} \right]_{s=0} = \frac{2}{2} + \frac{-2-3}{5} = 0 \text{ works } \checkmark$$

and

$$V_o(s)|_{s=-1} = \left[-\frac{5s}{(s+2)[(s+1)^2 + 2^2]} \right]_{s=-1} = \frac{5}{1(4)} = \frac{5}{4}$$

$$\left[\frac{2}{s+2} + \frac{-2(s+1) - \frac{3}{2}(2)}{s^2 + 2s + 5} \right]_{s=-1} = \frac{2}{1} - \frac{3}{1-2+5} = \frac{5}{4} \text{ works } \checkmark$$

and

$$V_o(s)|_{s=-3} = \left[-\frac{5s}{(s+2)[(s+1)^2 + 2^2]} \right]_{s=-3} = \frac{-15}{-1(4+4)} = \frac{15}{8}$$

$$\left[\frac{2}{s+2} + \frac{-2(s+1) - \frac{3}{2}(2)}{s^2 + 2s + 5} \right]_{s=-3} = \frac{2}{-1} - \frac{4-3}{9-6+5} = -2 - \frac{1}{8} = \frac{15}{8} \text{ works } \checkmark$$

Having verified our expansion, we take the inverse Laplace transform.

$$v_o(t) = \mathcal{L}^{-1} \left\{ \frac{2}{s+2} + \frac{-2(s+1) - \frac{3}{2}(2)}{s^2 + 2s + 5} \right\}$$

or

$$v_o(t) = [2e^{-2t} - 2e^{-t} \cos 2t - \frac{3}{2}e^{-t} \sin 2t]u(t) \text{ V}$$