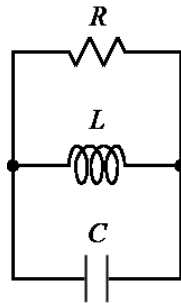





1.



$$R = 0.5 \, \Omega \quad L = 1.5 \, \mu\text{H} \quad C = 1.5 \, \mu\text{F}$$

- Find the characteristic roots, s_1 and s_2 , for the above circuit.
- Is the circuit over-damped, critically-damped, or under-damped? Explain.
- If the L and C values in the circuit are decreased by a factor of two, (and R remains the same), will the circuit be over-damped, critically-damped, or under-damped? Justify your answer with calculations.


2.

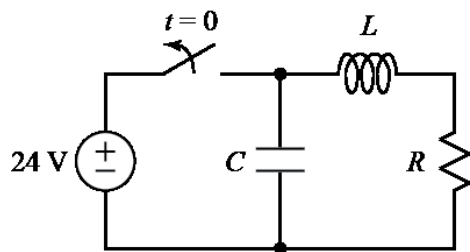

$$C = 1 \, \text{mF} \quad L = 25 \, \text{mH}$$

A relay is driven by a 24 V power supply, as shown above. Power is turned off at $t = 0$. The current, $i(t)$, for $t > 0$ has two terms that decay exponentially without oscillation. One term dies out quickly, and the other term dies out with a time constant of $\tau = 10 \, \text{ms}$, as in $e^{-t/10\text{ms}}$. Given the time constant and the information in the diagram above, find the value of R .


3.

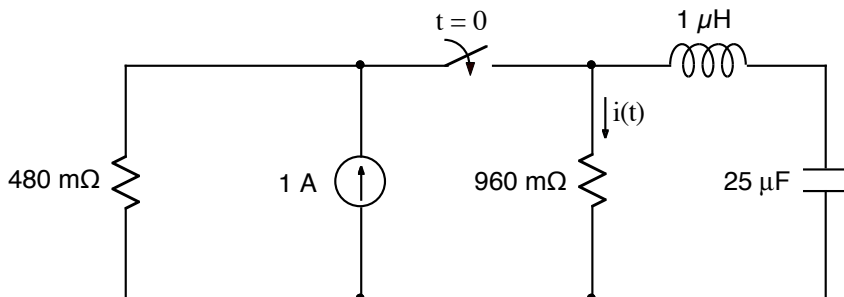

After being open for a long time, the switch closes at $t = 0$.

Find $i(t)$ for $t > 0$.

4.

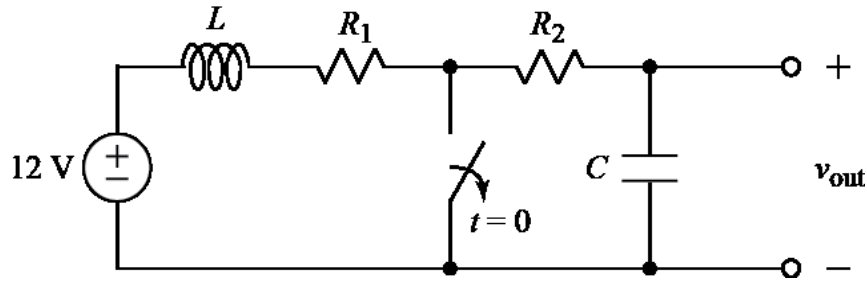


A 12 V power supply drives a long wire, (modeled as L and R_1), followed by a short wire, R_2 , and a smoothing capacitor, C . There is a safety switch, located before the smoothing capacitor, to turn off the output at the remote end. The switch is closed for a long time before opening at $t = 0$.

$$L = 2 \mu\text{H} \quad R_1 = 2.0 \Omega \quad R_2 = 0.1 \Omega \quad C = 200 \mu\text{F}$$

- Find the characteristic roots, s_1 and s_2 , for the above circuit.
- Find v_{out} for $t > 0$.

5.

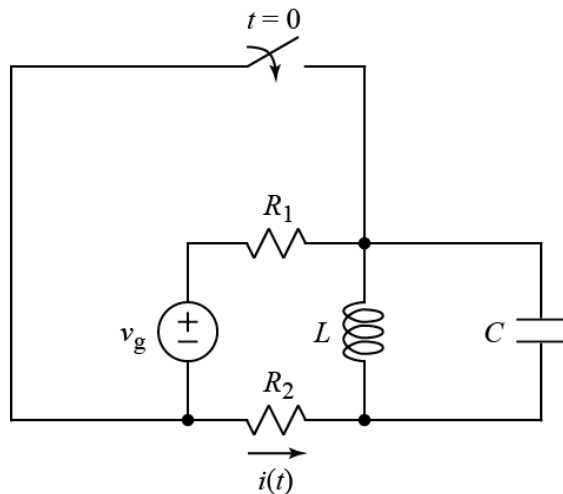

After being open for a long time, the switch closes at $t = 0$.

- Give expressions for the following in terms of no more than v_g , R_1 , R_2 , L , and C :

$$i(t = 0^+) \quad \text{and} \quad \left. \frac{di(t)}{dt} \right|_{t=0^+}$$

- Find the numerical value of R_2 given the following information:

$$R_1 = 150 \Omega \quad L = 40 \text{ mH} \quad C = 3.2 \mu\text{F}$$

$$\alpha = 1250 \text{ r/s} \quad \omega_d = 2500 \text{ r/s}$$

Answers:

1.a) Duplicate roots = $-2/3$ Mr/s. c) critically damped

2. $R = 12.5 \Omega$

3. $i(t) = -\frac{8}{9}e^{-160kt/s} \sin(120kt) + \frac{1}{3} \text{ A}$

4.a) Partial answer: $s_1 \approx -2.4\text{kr/s}$ overdamped.

b) $v_{\text{out}}(t > 0) \approx -12.06e^{-2.4\text{k/s}t} + 0.06e^{-1.05\text{M/s}t} + 12 \text{ V}$ Find a way to handle approximations.

5.a) Partial answer: $\left. \frac{di(t)}{dt} \right|_{t=0^+} = \frac{1}{R_2} \frac{i_C(t=0^+)}{C} = -\frac{v_g}{R_2 C (R_1 + R_2)}$. b) $R_2 = 125 \Omega$.