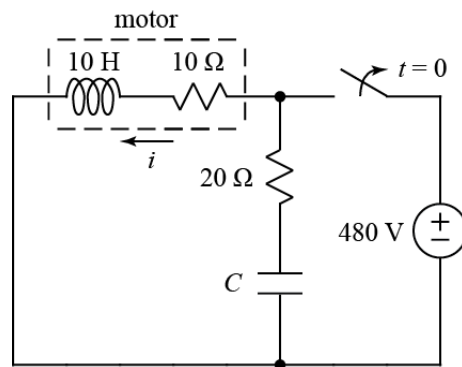


Ex:



After being closed for a long time, the switch opens at $t = 0$.

The above circuit represents a simplified circuit model of a motor and its power supply. The switch opens at time $t = 0$ to turn off the motor, and resistor R_2 and C provide a discharge path for current in the motor.

- Find the smallest **standard value** of C that makes the circuit over-damped after the switch is opened at $t = 0$. For standard values, assume the value of C is of form $1 \cdot 10^n\ \text{F}$ or $2 \cdot 10^n\ \text{F}$ or $5 \cdot 10^n\ \text{F}$ where n is an integer.
- Using the C value from (a), find a numerical expression for the motor current, $i(t)$, for $t > 0$.

sol'n: a) After $t=0$, we have a series RLC circuit.

$$\text{Characteristic roots are } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0^2 = \frac{1}{LC}$$

For over-damped roots we need $\alpha^2 > \omega_0^2$.

$$\alpha^2 = \left(\frac{R}{2L}\right)^2 = \left(\frac{30\ \text{r/s}}{2(10)}\right)^2 = \left(\frac{3}{2}\right)^2 (\text{r/s})^2 = 2.25\ \text{r/s}^2$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{10C}, \quad \text{or} \quad C = \frac{1}{10\omega_0^2}$$

$$\text{To achieve } \alpha^2 > \omega_0^2 \text{ we need } C \geq \frac{1}{10(2.25)}\ \text{F.}$$

$$C \geq \frac{1}{10(2.25)} F = \frac{1}{22.5} F = 44.4 \text{ mF}$$


The smallest $C \geq 44.4 \text{ mF}$ with a standard value is $C = 50 \text{ mF}$.

b) Using $C = 50 \text{ mF}$, we re-calculate characteristic roots.

$$\begin{aligned} s_{1,2} &= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -1.5 \pm \sqrt{2.25 - \frac{1}{10 \cdot 50 \text{m}}} \\ &= -1.5 \pm \sqrt{2.25 - 2} \\ &= -1.5 \pm \sqrt{0.25} \\ &= -1.5 \pm 0.5 \end{aligned}$$

$$s_{1,2} = -1 \text{ and } -2$$

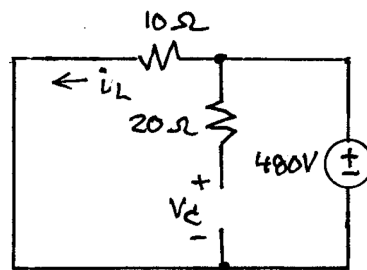We find initial conditions at $t=0^-$.
Switch closed. $L = \text{wire}$, $C = \text{open}$



$$i_L = \frac{480\text{V}}{10\Omega} = 48\text{A}$$

$V_C = 480\text{V}$ since 20Ω
R has no current

The form for the over-damped solution is

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_3$$


We will have $A_3 = 0\text{A}$ since the circuit has no power supply on the left after $t=0$.

Now we find A_1 and A_2 .

$$i(0^+) = A_1 + A_2$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = A_1 s_1 + A_2 s_2 = -A_1 - 2A_2$$

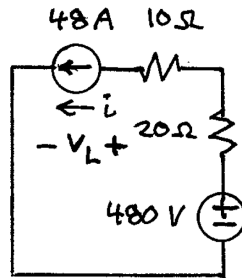Our circuit at $t=0^+$: $L = i_L$ source, $C = v_C$ source



$$i(0^+) = 48 \text{ A}$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = \frac{v_L(0^+)}{L}$$

$$v_L = 480 \text{ V} - 48 \text{ A} (10 \Omega + 20 \Omega) = -960 \text{ V}$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = \frac{-960 \text{ V}}{10 \text{ H}} = -96 \text{ A/s}$$

Matching the circuit values to the symbolic solution, we have the following:

$$\begin{aligned} A_1 + A_2 &= 48 \text{ A} \\ -A_1 - 2A_2 &= -96 \text{ A/s} \end{aligned}$$

If we add the equations, we have

$$-A_2 = -48 \text{ A} \text{ or } A_2 = 48 \text{ A}$$

From the first eq'n, we see that we must have $A_1 = 0 \text{ A}$

$$i(t > 0) = 48 e^{-2t} \text{ A}$$