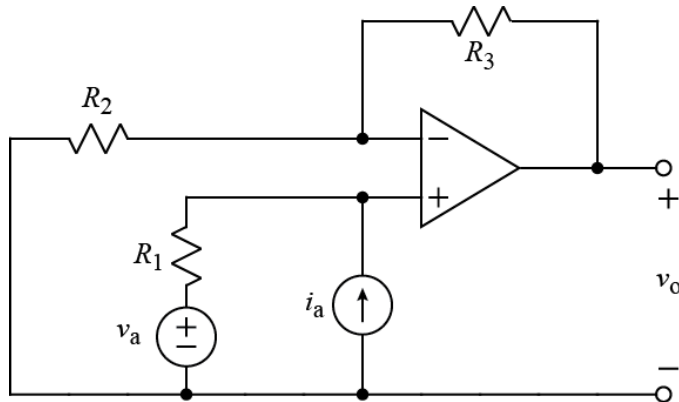





1.




The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for v_o in terms of not more than v_a , i_a , R_1 , R_2 , and R_3 .

2.

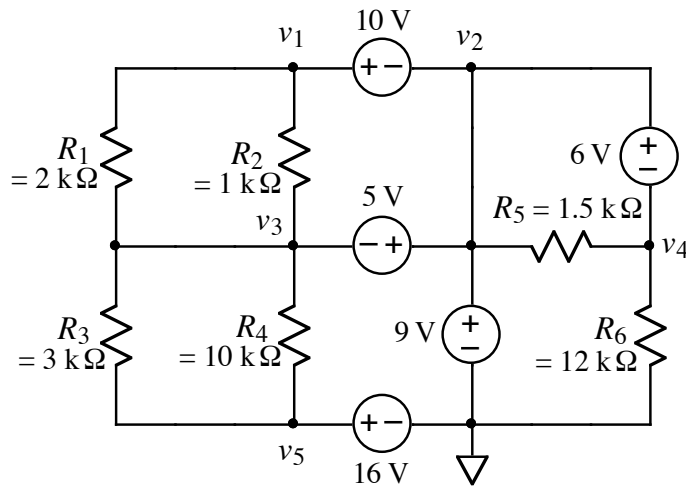


Find the absolute voltages at all the labeled nodes in the above circuit.

3.

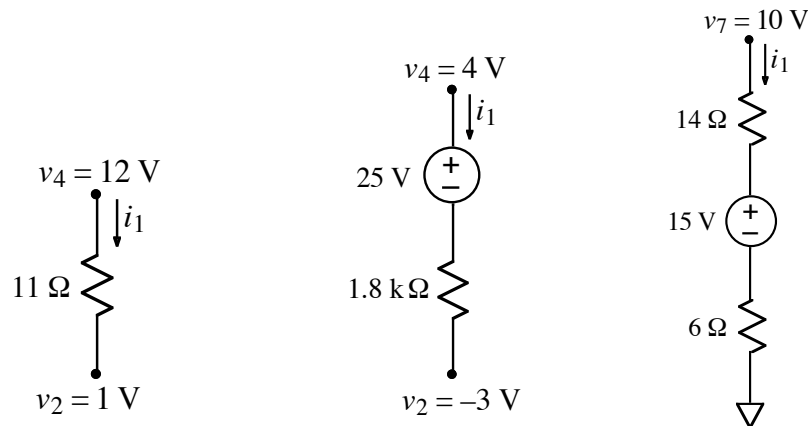


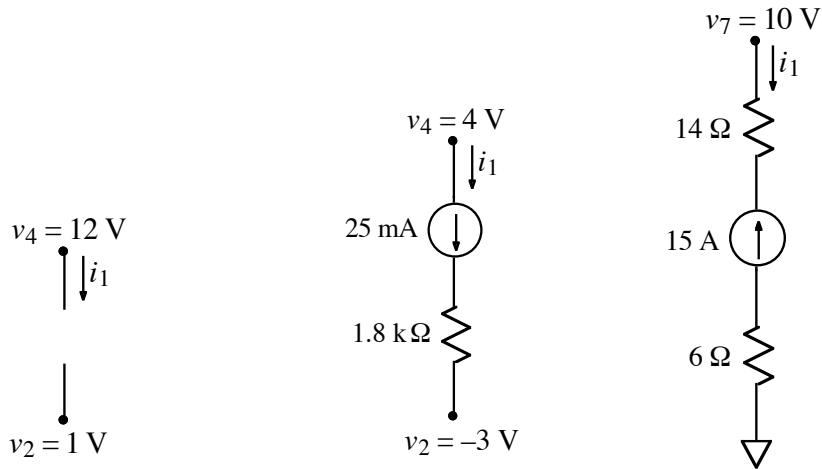a) Find the value of current, i_1 , for each of the above circuits.




b) Find the value of current, i_1 , for each of the above circuits.

4.

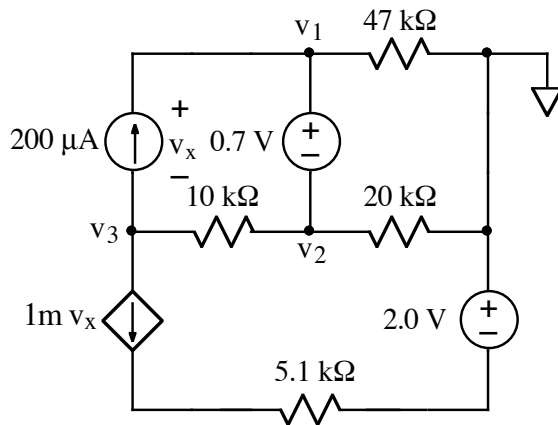

Use the node-voltage method to find v_1 , v_2 , and v_3 .

5.

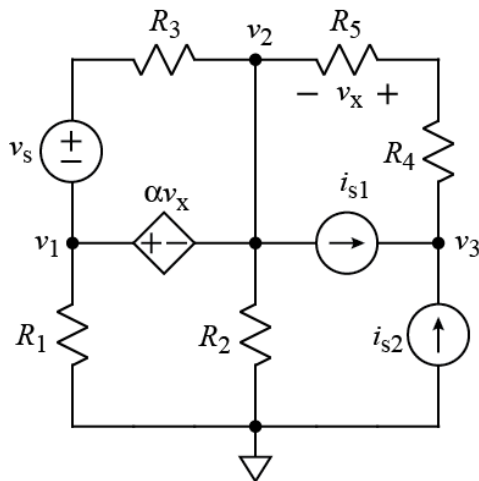

For the circuit shown, write three independent equations for the node-voltages, v_1 , v_2 , and v_3 . The quantity v_x must not appear in the equations. Only component and source names may appear in answer.

Answers:

1. $v_o = (1 + \frac{R_3}{R_2}) \cdot (V \text{ across } i_a \text{ [+ on top]})$

2. $v_2 = 14 \text{ V}$

3.a) $i_1 = -10 \text{ mA}$ for middle circuit, put R's together in 3rd circuit

3.b) How much current flows in an open? What do we do with things in series with current source?

4. Equation for supernode v_2 and v_1 is: $-200 \mu\text{A} + \frac{v_1}{47 \text{ k}\Omega} + \frac{v_2 - v_3}{10 \text{ k}\Omega} + \frac{v_2}{20 \text{ k}\Omega} = 0 \text{ A}$

Also need voltage equation for supernode and current sum for v_3 node. v_x in terms of node V's is just $v_1 - v_3$.

5. First write equation for v_x in terms of node V's: $v_x = (v_3 - v_2) \frac{R_5}{R_4 + R_5}$

Supernode equation for v_1 and v_2 : $\frac{v_1}{R_1} + \frac{v_1 + v_s - v_2}{R_3} + \frac{v_2 - v_3}{R_4 + R_5} + \text{two more terms} = 0 \text{ A}$

Also need to write voltage equation for v_1 and v_2 (they differ by v_x , but use the node voltage version of v_x) and current sum for v_3 node.