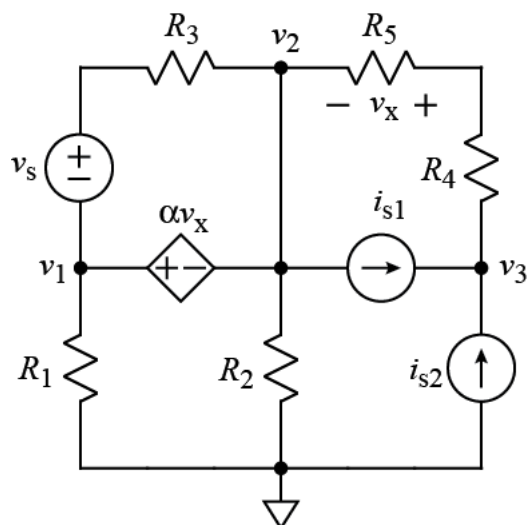


Ex:



For the circuit shown, write three independent equations for the node-voltages, v_1 , v_2 , and v_3 . The quantity v_x must not appear in the equations. Only component and source names may appear in answer.

SOL'N:

Supernode between v_1 and v_2 :

$$\textcircled{1} (v_1 - v_2) = \alpha v_x$$

$$v_x = -\frac{(v_2 - v_3)R_5}{R_4 + R_5}$$

$$\textcircled{1} (v_1 - v_2) = -\alpha \frac{R_5 (v_2 - v_3)}{R_4 + R_5}$$

$$\textcircled{2} \frac{v_1}{R_1} + \frac{(v_1 + v_s - v_2)}{R_3} - \frac{(v_1 + v_s - v_2)}{R_3} + \frac{v_2}{R_2} + I_{s1} + \frac{(v_2 - v_3)}{R_4 + R_5} = 0$$

at node v_3 :

$$\textcircled{3} -I_{s1} - I_{s2} - \frac{(v_2 - v_3)}{R_4 + R_5} = 0$$