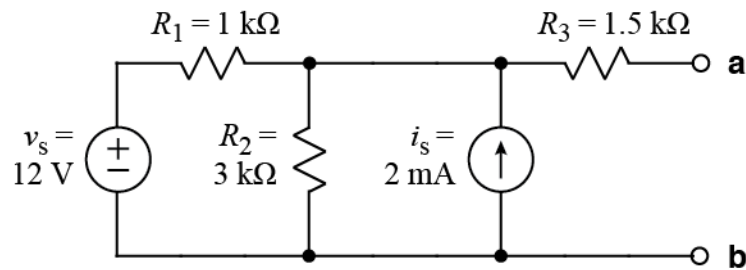





1.



Find the Thevenin equivalent circuit at terminals a-b.


2.

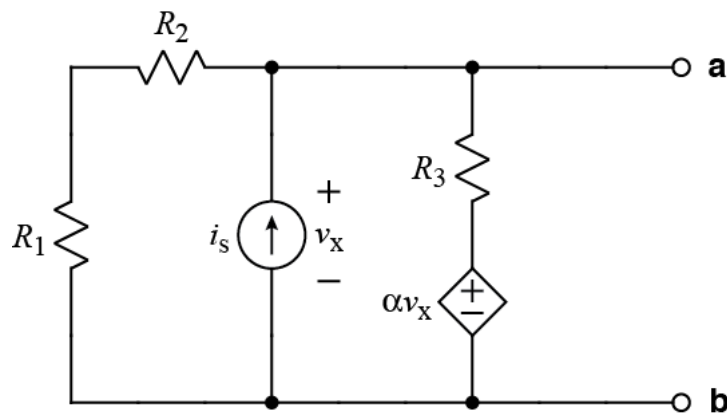

Find the Thevenin equivalent circuit at terminals a-b. v_x must not appear in your solution. The expression must not contain more than circuit parameters α , R_1 , R_2 , R_3 , and i_s . **Note:** $0 < \alpha < 1$.

3. Make at least one consistency check (other than a units check) on your expression for problem 2. In other words, choose component values that make the answer obvious, and verify that your answer to problem 2 gives that obvious answer. State the values of resistors and sources for your consistency check.
4. Find the Norton equivalent of the circuit in problem 2.

5.

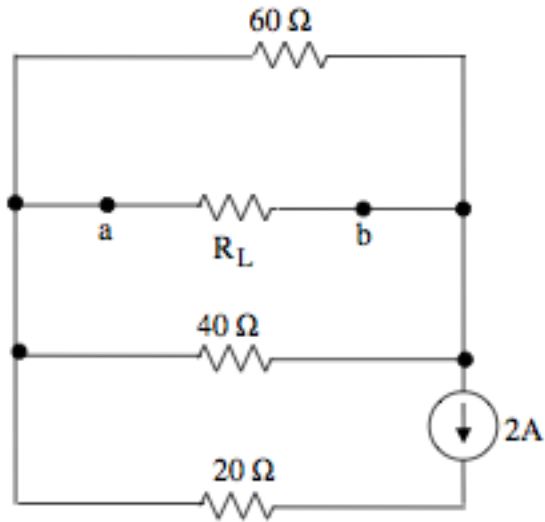

- a) Calculate the value of R_L that would absorb maximum power.
- b) Calculate that value of maximum power R_L could absorb.

Answers:

1. $v_{\text{Th}} = 10.5 \text{ V}$, $R_{\text{Th}} = 2.25 \text{ k}\Omega$

2. $v_{\text{Th}} = i_s \cdot (R_1 + R_2) \parallel R_3 \parallel \frac{-R_3}{\alpha} = i_s \cdot R_{\text{Th}}$

5.a. Hints: Remove R_L when finding the Thevenin equivalent, and $20 \text{ }\Omega$ resistor in series with current source is irrelevant. So if you combine the $40 \text{ }\Omega$ and $60 \text{ }\Omega$, you are starting with a Norton form.

5.b. $p_{\text{max}} = \frac{v_{\text{Th}}^2}{4R_{\text{Th}}} = 24 \text{ W}$