
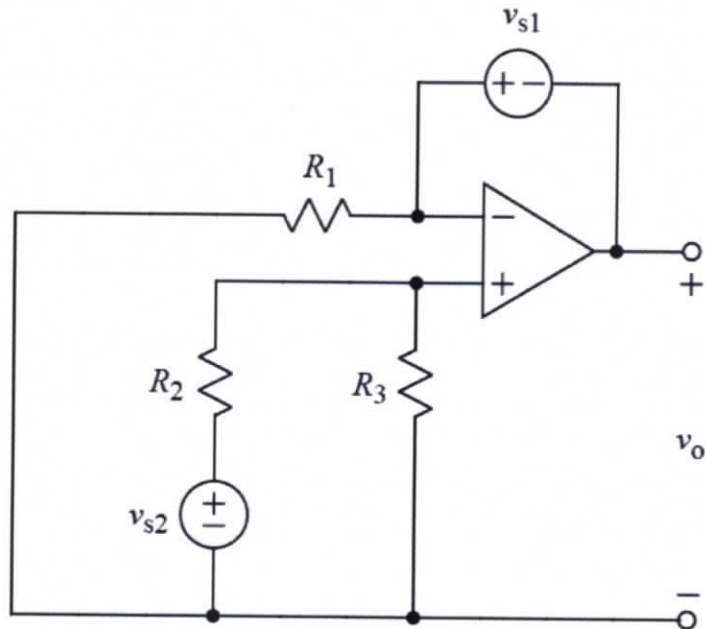


Ex:

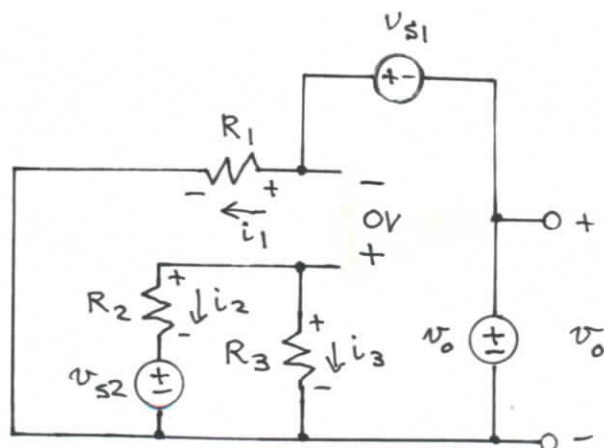

The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for  $v_o$  in terms of not more than  $v_{s1}$ ,  $v_{s2}$ ,  $R_1$ ,  $R_2$ , and  $R_3$ .

sol'n: Using Kirchhoff's and Ohm's laws, we start by labeling the directions of voltage and current measurements. One possibility for the labeling is shown below. We also replace the op-amp with a voltage source  $v_o$ .



Now we write eq'ns for  $v$ -loop and  $i$ -sums, making sure we have a  $v$ -loop that passes through the  $0V$  drop that we assume exists across the inputs of the op-amp.

$$v\text{-loop on left: } +i_1 R_1 + 0V - i_2 R_2 - v_{s2} = 0V$$

$$v\text{-loop lower middle: } +v_{s2} + i_2 R_2 - i_3 R_3 = 0V$$

$$v\text{-loop outside: } +i_1 R_1 - v_{s1} - v_o = 0V$$

The only node not connected to another node by only a  $v$ -source is at the + input of the op-amp.

$$i_2 = -i_3$$

Now we solve the eq'ns to find an expression for  $v_o$ .

Substitute for  $i_3$  in 2nd  $v$ -loop.

$$v_{s2} + i_2 R_2 + i_2 R_3 = 0V$$

We can solve for  $i_2$ .

$$i_2 (R_2 + R_3) = -v_{s2}$$

or

$$i_2 = -\frac{v_{s2}}{R_2 + R_3}$$

Now we can use  $i_2$  to find  $i_1$  from the 1st  $v$ -loop.

$$i_1 R_1 + 0V - -\frac{v_{s2} R_2}{R_2 + R_3} - v_{s2} = 0V$$

or

$$i_1 = \frac{v_{s2}}{R_1} \left( 1 - \frac{R_2}{R_2 + R_3} \right) = \frac{v_{s2}}{R_1} \left( \frac{R_2 + R_3 - R_2}{R_2 + R_3} \right)$$


or

$$i_1 = \frac{v_{s2}}{R_1} \frac{R_3}{R_2 + R_3}$$

Using this value for  $i_1$ , the outer  $v$ -loop yields an expression for  $v_o$ .

$$v_o = i_1 R_1 - v_{s1} = v_{s2} \frac{R_3}{R_2 + R_3} - v_{s1}$$

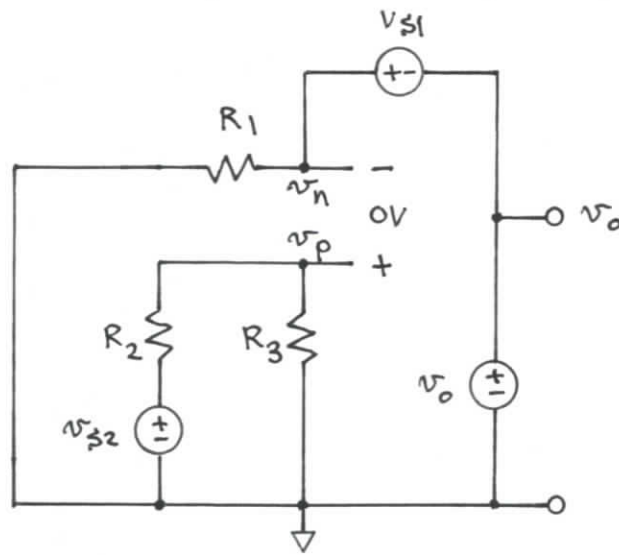An alternative approach is to use the Node- $v$  method. We assume a 0V drop across the op-amp inputs, and we start by finding node voltage  $v_p$ .



We have a  $v$ -divider consisting of  $v_{s2}$ ,  $R_2$ , and  $R_3$ .

$$v_p = v_{s2} \frac{R_3}{R_2 + R_3}$$

The  $v_n$  node has the same voltage as  $v_p$ .

$$v_n = v_p$$

We would normally now use an i-sum at the  $v_n$  node, but we see that  $v_o$  differs from  $v_n$  by  $v_{s1}$ .

$$v_o = v_n - v_{s1}$$

or

$$v_o = v_p - v_{s1}$$

or

$$v_o = v_{s2} \frac{R_3}{R_2 + R_3} - v_{s1}$$