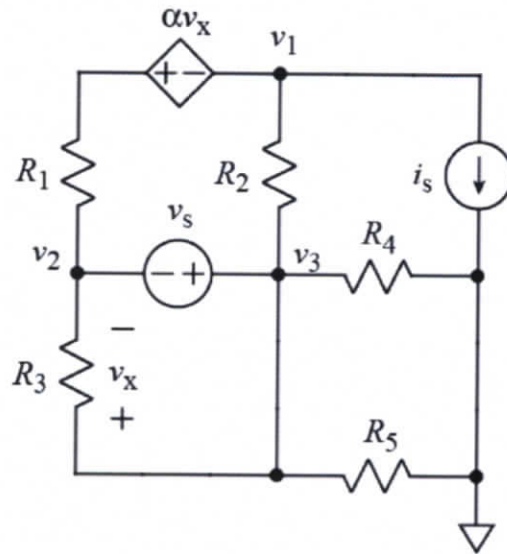


Ex:



For the circuit shown, write (but do not solve) three independent equations for the node voltages v_1 , v_2 , and v_3 . The quantity v_x must not appear in the equations.

sol'n: We use the node- v method. We observe that v_2 and v_3 are connected by only a v -source and so form a super-node. For the dependent source, we define v_x in terms of node voltages. This is a good place to start.

$$v_x = v_3 - v_2 = v_s \quad (\text{This last step is optional but helpful.})$$

Now we can write an eq'n for node v_1 .


$$(1) \quad \frac{v_1 + \alpha \overset{\leftarrow v_x}{(v_3 - v_2)} - v_2}{R_1} + \frac{v_1 - v_3}{R_2} + i_s = 0A$$

Note that we could also replace the $v_3 - v_2$ term with v_s .

The super-node for v_2 and v_3 has a voltage eq'n and a current eq'n. The voltage eq'n is simple.

$$(2) \quad v_3 = v_2 - v_3 \quad \text{or} \quad v_2 + v_3 = v_3$$

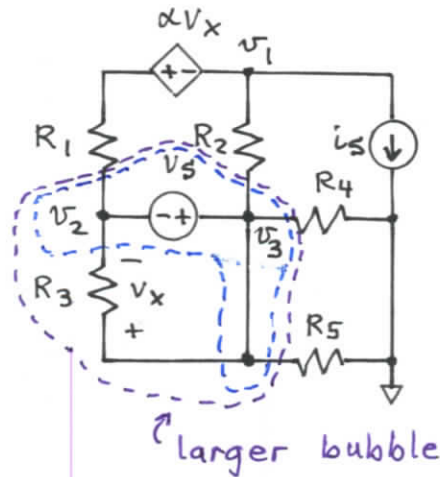For the super-node current summation, we start with a bubble around v_2 , v_3 , and v_3 . Closer inspection, however, reveals that R_3 also connects v_2 to v_3 . Thus, the current in R_3 will be computed in both directions and will cancel out in the i -sum. So we put R_3 in the bubble, too.



The sum out of the bubble is as follows:

$$(3) \quad \frac{v_2 - [v_1 + \alpha(v_3 - v_2)]}{R_1} + \frac{v_3 - v_1}{R_2} + \frac{v_3}{R_4} + \frac{v_3}{R_5} = 0A$$

Eq'ns (1) - (3) are the desired answer.