
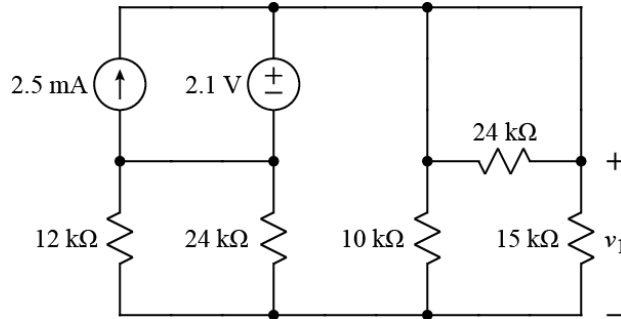


Ex:

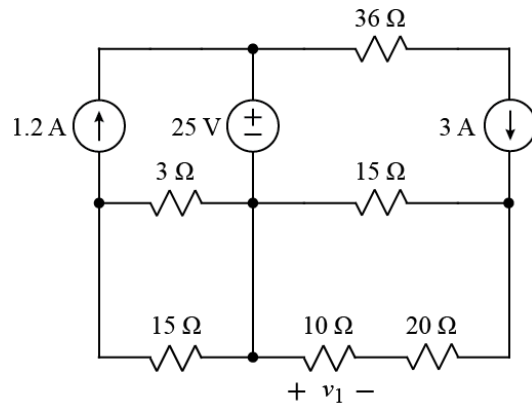

a) Calculate v₁.



b) Calculate v₁.


SOL'N: a)

The lower left 12kΩ and 24kΩ R's are in parallel. The upper right wire and 24 kΩ are in parallel, as well.

$$12\text{k}\Omega \parallel 24\text{k}\Omega = 12\text{k}\Omega \cdot 1 \parallel 2 = 12\text{k}\Omega \cdot \frac{2}{3} = 8\text{k}\Omega$$

$$0\Omega \parallel 24\text{k}\Omega = 0\Omega \text{ (wire)}$$

circuit:

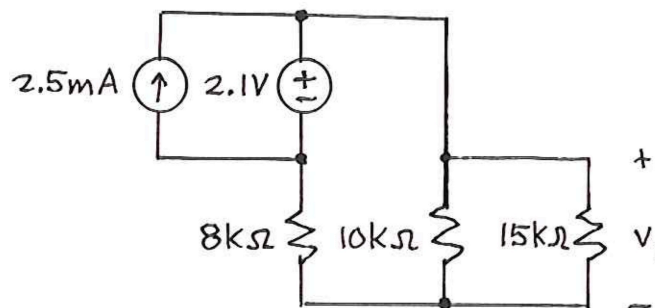


We see that the $10\text{k}\Omega$ is in parallel with the $15\text{k}\Omega$.

$$10\text{k}\Omega \parallel 15\text{k}\Omega = 5\text{k}\Omega \cdot 2 \parallel 3 = 5\text{k}\Omega \cdot \frac{6}{5} = 6\text{k}\Omega$$

We have two separate circuits across the 2.1V source: one circuit is the 2.5mA source, and the other circuit is all the R 's. We may solve these circuits separately, meaning we may ignore the 2.1V source.

circuit for finding V_1 :

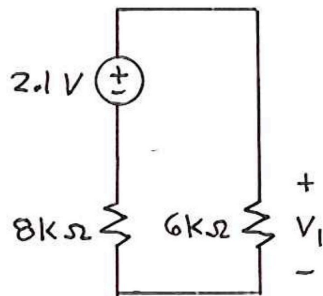

This is a V -divider:


$$V_1 = 2.1\text{V} \cdot \frac{6\text{k}\Omega}{6\text{k}\Omega + 8\text{k}\Omega} = 2.1\text{V} \cdot \frac{6}{14} = 2.1\text{V} \left(\frac{3}{7}\right)$$

or

$$V_1 = 0.9\text{V}$$

b)

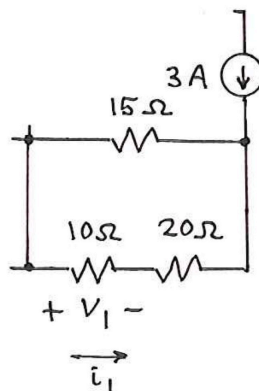We have current divider formed by the 3A source and the 15Ω and $10\Omega + 20\Omega$ on the righthand side:



By the current divider formula

$$i_1 = -3A \cdot \frac{\frac{1}{10\Omega + 20\Omega}}{\frac{1}{10\Omega + 20\Omega} + \frac{1}{15\Omega}} = \frac{-3A \cdot 15\Omega}{15\Omega + 10\Omega + 20\Omega}$$

or

$$i_1 = -3A \cdot \frac{15\Omega}{45\Omega} = -1A$$

By Ohm's law, we find v_1 :

$$v_1 = -1A \cdot 10\Omega = -10V$$