
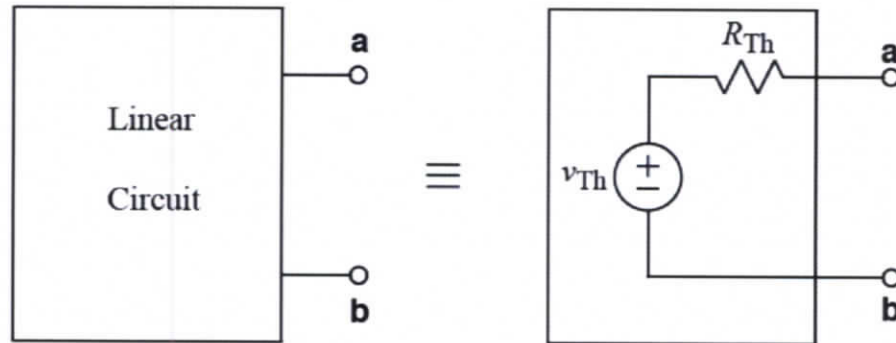


Ex:

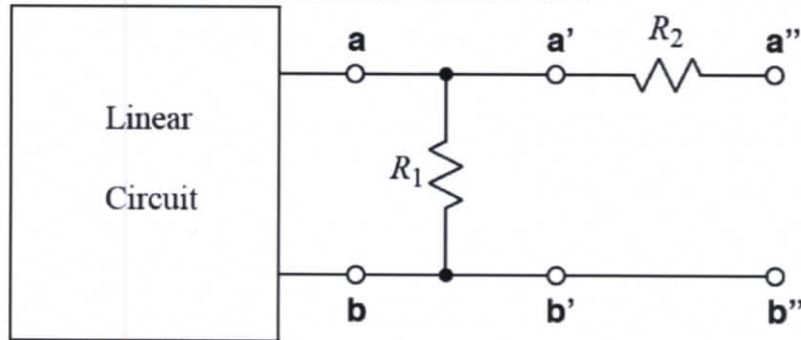


A linear circuit has a Thevenin equivalent, as shown above. Now suppose that components are added to that circuit as shown below.



- Find the Thevenin equivalent circuit at terminals a'-b' in terms of the original v_{Th} and R_{Th} and the added R_1 . (Note that this is the circuit with only R_1 added to it.)
- Find the Thevenin equivalent circuit at terminals a''-b'' in terms of the original v_{Th} and R_{Th} and the added R_1 and R_2 .

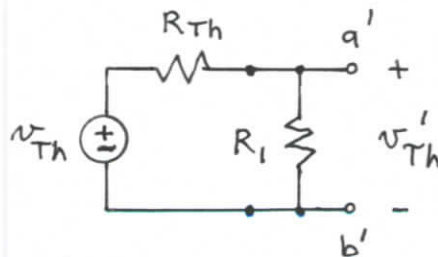
SOL'N: a) The v'_{Th} for a', b' is the voltage across a', b' with nothing connected as a load across a', b'.




This is a voltage divider.

$$v_{Th}' = v_{Th} \frac{R_1}{R_1 + R_{Th}} \quad \text{or} \quad v_{Th}' = v_{Th} \frac{1}{1 + R_{Th}/R_1}$$

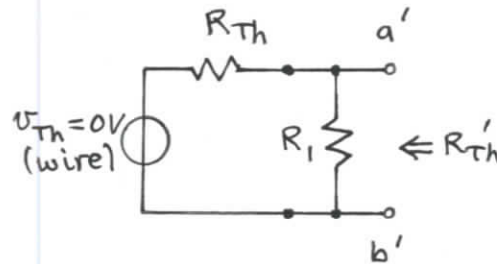To find R_{Th}' , we turn off v_{Th} and look in from a' , b' .



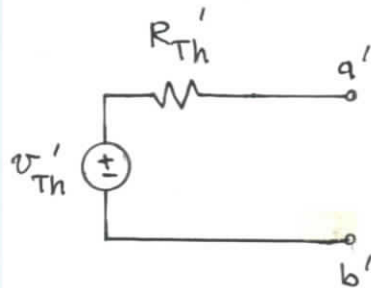
$$R_{Th}' = R_1 \parallel R_{Th} \quad \text{or} \quad R_{Th}' = \frac{R_{Th}}{1 + R_{Th}/R_1}$$



$$v_{Th}' = v_{Th} \frac{R_1}{R_1 + R_{Th}}$$

$$R_{Th}' = R_1 \parallel R_{Th}$$

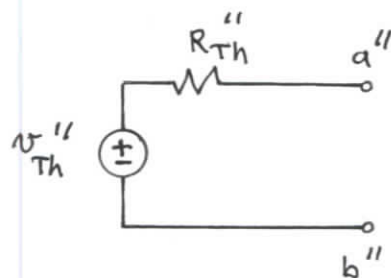b) With R_2 connected to the output of the Thevenin equivalent, the Thevenin equivalent voltage remains v_{Th}' , and the Thevenin equivalent resistance is $R_{Th}' + R_2$, since the R 's are in series.



$$v_{Th}'' = v_{Th}' = v_{Th} \frac{R_1}{R_1 + R_{Th}}$$

$$R_{Th}'' = R_{Th}' + R_2 = R_1 \parallel R_{Th} + R_2$$