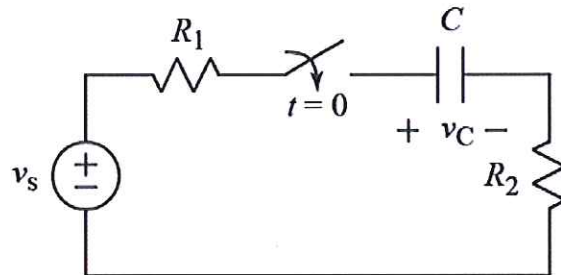


Ex:



$$R_1 = 1.5 \text{ M}\Omega \quad R_2 = 1 \text{ M}\Omega \quad C = 3.3 \text{ nF} \quad v_s = 2.3 \text{ V}$$

After being open for a long time, the switch closes at $t = 0$. The initial voltage on the capacitor is $v_C(t = 0^+) = 1.5 \text{ V}$. Hint: think Thevenin equivalent for the circuit the capacitor is connected to.

- Find an expression for $v_C(t)$ for $t \geq 0$.
- Find the energy stored in the capacitor as t approaches infinity.

sol'n: a) We use the general form of solution:

$$v_c(t \geq 0) = v_c(t \rightarrow \infty) + [v_c(0^+) - v_c(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

Now we find the key quantities, $v_c(0^+)$, R_{Th} (for $t > 0$), and $v_c(t \rightarrow \infty)$.

To find $v_c(0^+)$, we observe that $v_c(0^+) = v_c(0^-)$ since v_c is an energy variable that cannot change instantly. This is helpful because, at $t = 0^-$, the circuit has been sitting for a long time and has settled to constant i's and v's. This in turn implies $dv_c(t)/dt = 0$. This in turn implies $i_c(t) = 0$. This in turn implies that the C acts like an open circuit.


Here, the switch is open and the C acts like an open. Using a v -loop, we find that there

is no current in the R 's and no v -drop across the R 's, meaning the v_s is dropped across the switch and C . There is no way to determine how much of v_s is dropped across the switch and how much is dropped across C . So we need more information.


Fortunately, the problem states that the voltage across C is $1.5V$ at $t=0^+$.

Next, we remove the C from the circuit and find the Thevenin equivalent of the remaining circuit. (The terminals a, b for the Thevenin equivalent are where the C is connected.)

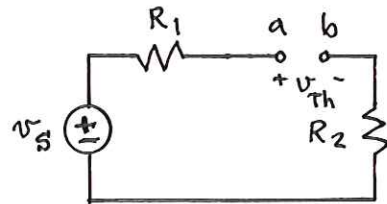Our circuit for the Thevenin equivalent for $t > 0$:



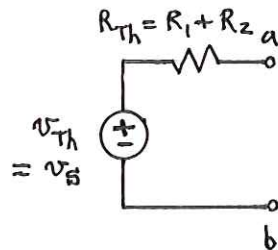Since no current flows, v_{Th} ($= v_{a,b}$ in above circuit) will be v_s . R_{Th} is the R seen looking into a, b with v_s set to zero, which is $R_{Th} = R_1 + R_2$.



Our time constant is $\tau = R_{Th} C = (R_1 + R_2) C$

$$\tau = (1.5 M\Omega + 1 M\Omega) 3.3 nF = 8.25 ms$$

For $t \rightarrow \infty$, our circuit model is the above
Thevenin equivalent with C attached to a, b .
The C , however, acts like an open, so $v_C = v_{Th}$.

$$v_C(t \rightarrow \infty) = v_{Th} = v_S = 2.3V$$

We plug values into the general sol'n:

$$v_C(t \geq 0) = 2.3V + [1.5V - 2.3V] e^{-t/8.25ms}$$

or

$$v_C(t \geq 0) = 2.3V - 0.8V e^{-t/8.25ms}$$

b) Stored energy is $w_C = \frac{1}{2} C v_C^2$.

$$w_C(t \rightarrow \infty) = \frac{1}{2} (3.3nF) (2.3V)^2$$

or

$$w_C(t \rightarrow \infty) \doteq 8.73 \text{ nJ}$$