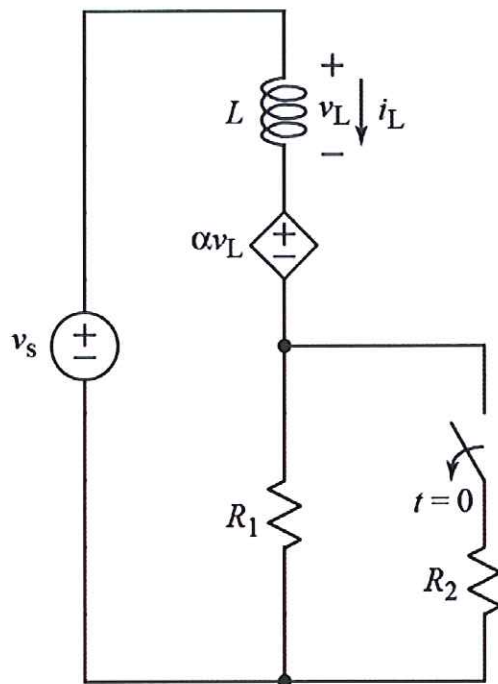


Ex:



After being closed for a long time, the switch opens at $t = 0$.

For the above circuit, determine whether the dependent source acts like an R , an L , or both. Explain your answer by finding the equivalent value of the R , L , or both that give(s) the same solution as the original problem.

sol'n: The sol'n for $i_L(t > 0)$ in the above problem is as follows (see related problem for derivation):

$$i_L(t > 0) = i_L(t \rightarrow \infty) + [i_L(0^+) - i_L(t \rightarrow \infty)] e^{-t/\tau}$$


or

$$i_L(t > 0) = \frac{v_s}{R_1} + \frac{v_s}{R_2} e^{-t/(1+\alpha)L/R_1}$$

This solution is for L connected to the circuit that includes the dependent source.

We may think of the circuit without L as a Thevenin equivalent. From our sol'n above, we have $R_{Th} = R_1 / (1 + \alpha)$.

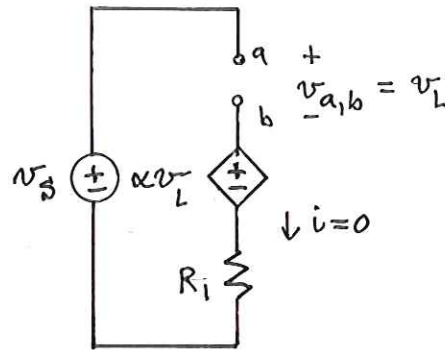To find v_{Th} , we find the $v_{a,b}$ for the following circuit:



Because we have an open circuit $i=0$, and R has no v -drop. For a v -loop, we get

$$v_s - v_{ab} - \alpha v_{ab} - 0V = 0V$$


or

$$v_{ab} (1 + \alpha) = v_s$$

or

$$v_{ab} = \frac{v_s}{1 + \alpha}$$

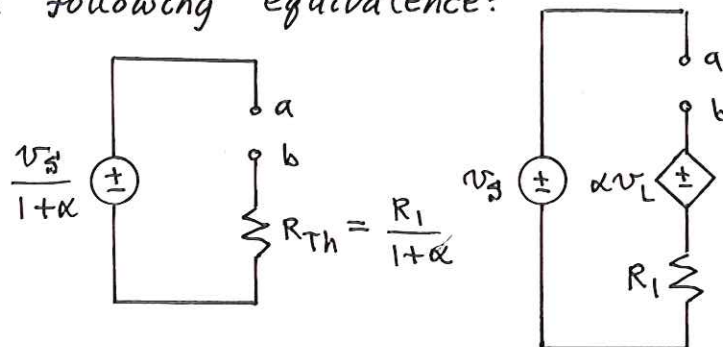If we use a Thevenin equivalent, we have the following equivalence:





We could remove the αv_L source and consider it to be part of the R_{Th} , if we also adjust the independent source. If we accept this change in v_S , then our αv_L source becomes an R_{eq} :

$$R_1 + R_{eq} = \frac{R_1}{1+\alpha}$$

or

$$R_{eq} = \frac{R_1}{1+\alpha} - R_1 = \frac{R_1}{1+\alpha} - R_1 \frac{(1+\alpha)}{1+\alpha} = -\frac{\alpha R_1}{1+\alpha}$$

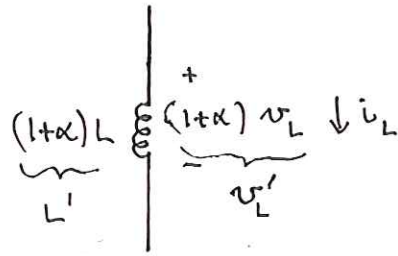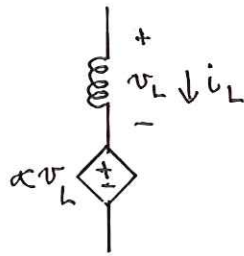On the other hand, we may argue that the L and αv_L source act exactly like $(1+\alpha)L$:



$$v_L = L \frac{di_L}{dt}$$

$$v_L + \alpha v_L = L \frac{di_L}{dt} + \alpha L \frac{di_L}{dt}$$

$$v_L + \alpha v_L = (1+\alpha)L \frac{di_L}{dt}$$

$$(1+\alpha)v_L = (1+\alpha)L \frac{di_L}{dt}$$

$$v_L' = L' \frac{di_L}{dt}$$

$$v_L' = (1+\alpha)L \frac{di_L}{dt}$$

$$v_L' = (1+\alpha)v_L$$

$$(1+\alpha)v_L = (1+\alpha)L \frac{di_L}{dt}$$

We can say that the dependent source looks like an L_{eq} of value αL .