EEE 2240 Laboratory Project 1a: LED Voltage vs Current, Pre-Amps Laboratory Notebook Contents and Grading



10	Communication
1	Work recorded in notebook (rather than pasted in)
4	Student's work Reproducible from notebook
1	Written in Ink
1	Student Signed every page
1	Student Dated every page
2	TA Signature for lab session
Lab 1.a	
2 IV.	CONSTRUCTION OF LED POWER INDICATORS
1	Explanation of task (built power indicators)
1	Diagram of circuit from Fig. 3
8 V.	RESISTOR AND LED CURRENTS
	A. Measurements of Voltages
1	Explanation of task (measured voltages for R and LED)
1	Table II filled in with measured values
	B. Calculation of Current in Resistor and LED
1	Explanation of task (Used Ohm's law to calculate $i_R = i_{\text{LED}}$)
1	Table III filled in with measured values
	C. Plot of Current versus Voltage in LED
1	Explanation of task (Commented on plot of LED current versus voltage)
3	Drew accurate plot of LED current vs voltage with all labels
5 VI.	CONSTRUCTION AND TESTING OF PRE-AMPS
	A. Construction
1	Explanation of task (constructed pre-amps circuits on breadboard)
1	Schematic of pre-amps
1	Explanation of testing (1 V 1 kHz sinusoid in, oscilloscope measure output)
	B. Drawing of Waveforms

2 Careful drawing of oscilloscope screen

/25 Total