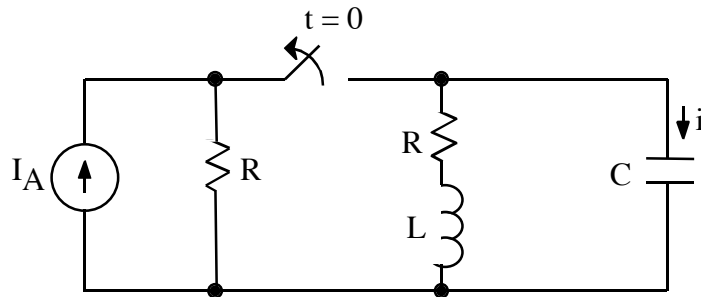



1.



$$\begin{aligned} I_A &= 1 \text{ A} \\ R &= 2400 \ \Omega \\ L &= 200 \ \mu\text{H} \\ C &= 50 \text{ pF} \end{aligned}$$


- After being closed for a long time, the switch is opened at $t = 0$. Give the values of the characteristic roots for the circuit and state whether $i(t)$ is underdamped, overdamped, or critically damped.
- Write a numerical time-domain expression for $i(t)$, the current through the capacitance. This expression must not contain any complex numbers.

2.

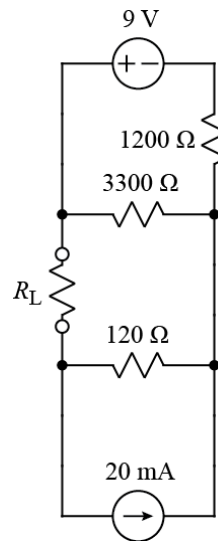


- Calculate the value of R_L that would absorb maximum power.
- Calculate that value of maximum power R_L could absorb.

3.

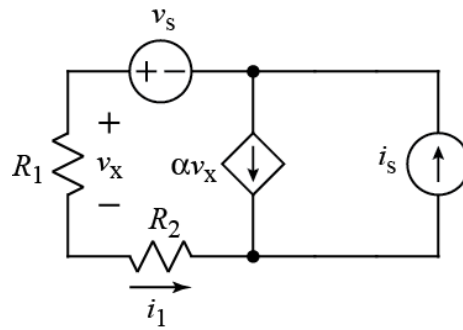

Using superposition, derive an expression for i_1 that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , and α . Note: $\alpha > 0$.

4.

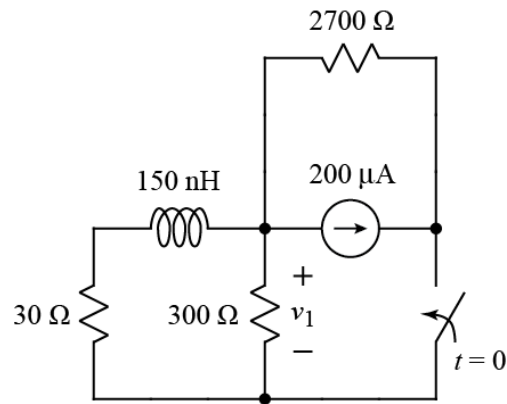

After being open for a long time, the switch closes at $t = 0$.

- Calculate the energy stored on the inductor as $t \rightarrow \infty$.
- Write a numerical expression for $v_1(t)$ for $t > 0$.