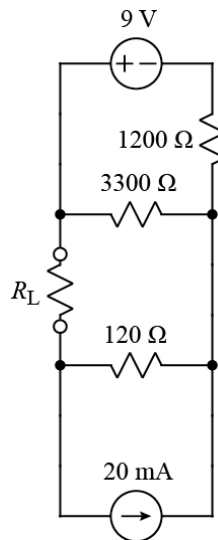



Ex:



- Calculate the value of  $R_L$  that would absorb maximum power.
- Calculate that value of maximum power  $R_L$  could absorb.

sol'n: a)  $R_L = R_{Th}$  for max pwr transfer.

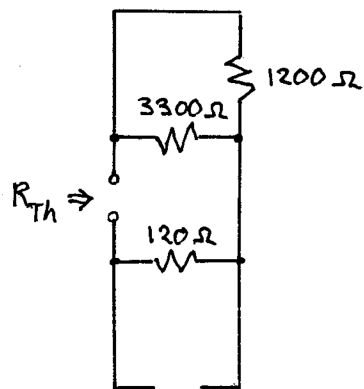We remove  $R_L$ , turn off the independent sources, and look in from the terminals for  $R_L$  to find  $R_{Th}$ .




$$R_{Th} = 120\Omega + 3300\Omega \parallel 1200\Omega$$

$$\begin{aligned}
 \text{We have } 3300 \parallel 1200 \Omega &= 100 \cdot 33 \parallel 12 \Omega \\
 &= 100 \cdot \frac{396}{45} \Omega \\
 &= 880 \Omega
 \end{aligned}$$

$$\text{So } R_L = R_{Th} = 120 \Omega + 880 \Omega = 1 \text{ k}\Omega.$$

$$b) P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

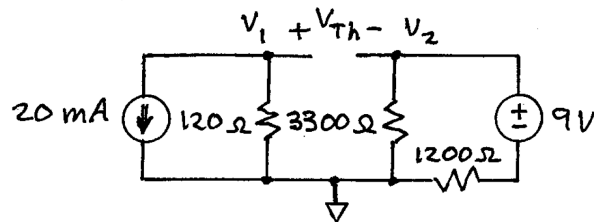We find  $V_{Th}$  at the terminals where  $R_L$  is connected but without  $R_L$ . Since  $V_{Th}$  is squared, we may measure  $V_{Th}$  in either direction.



No current flows in the bottom wire, since otherwise charge would accumulate on one side. So the two sides act as separate circuits.

$$V_1 = -20 \text{ mA} \cdot 120 \Omega = -2.4 \text{ V} \quad (\text{ohm's law})$$

$$V_2 = 9 \text{ V} \cdot \frac{3300 \Omega}{3300 + 1200 \Omega} = 6.6 \text{ V} \quad (\text{v-divider})$$

$$V_{Th} = V_1 - V_2 = -2.4 \text{ V} - 6.6 \text{ V} = -9 \text{ V}$$

$$P_{max} = \frac{(-9 \text{ V})^2}{4 \cdot 1 \text{ k}\Omega} = 20.25 \text{ mW}$$