

100 pts Lab #4 Notebook Grading

THE FOLLOWING ITEMS ARE REQUIRED:

- Student's work reproducible from notebook.
- Title and date for each lab section.
- Written in ink.
- Student signed every page.
- Student dated every page.

50 pts EXPERIMENT 1(DESIGN AND SIMULATION):

10 pts (1) Circuit design shows hand analysis for

- 4 pts $I_D = 0.6mA$
- 2 pts $V_S=3V$
- 2 pts V_D around 9V
- 2 pts $R_{in}>15k$

5 pts (2) PSpice simulation verifying

- 1 pt Circuit schematic from PSpice
- 1 pt $I_D = 0.6mA$
- 1 pt $V_S=3V$
- 1 pt V_D around 9V
- 1 pt $R_{in}>15k$

5 pts (3) Hand analysis that shows the results for gain, R_{in} , and R_{out}

10 pts (4) PSpice AC sweep simulation verifying

- 3 pts Magnitude Bode Plot showing gain
- 3 pts Magnitude Bode Plot showing R_{in}
- 3 pts Magnitude Bode Plot showing R_{out}
- 1 pt low frequency cut-off location marked or noted.

5 pts (5) PSpice AC sweep simulation showing the magnitude Bode Plot for no R_L .

15 pts (6) PSpice transient simulation:

- 4 pts Load resistor connected – V_{in} vs V_{out} graph
- 4 pts Comparison of gain value to #4
- 4 pts No load resistor connected – V_{in} vs V_{out} graph
- 3 pts Comparison of gain value to #5

50 pts EXPERIMENT 2(PROTOTYPE):

10 pts (1) Circuit built and connected correctly.

5 pts (2) DC Measurements

- 1 pt V_D
- 1 pt V_S

1 pt VG

2 pt ID

10 pts (3) Measurements

3 pts Peak to peak value of VD

3 pts Peak to peak value of Vsig

2 pts open circuit amplication

2 pt comparison to hand and simulation values

5 pts (4) Max output voltage before distortion

10 pts (5) AC Amplification with RL

4 pts VD value.

4 pts Amplification value.

2 pts Comments on value and comparison to simulation and hand analysis.

10 pts (6) Frequency response

3 pts low frequency value found.

3 pts high frequency value found.

2 pts Bandwidth stated.

2 pts Comparison of values to simulation.