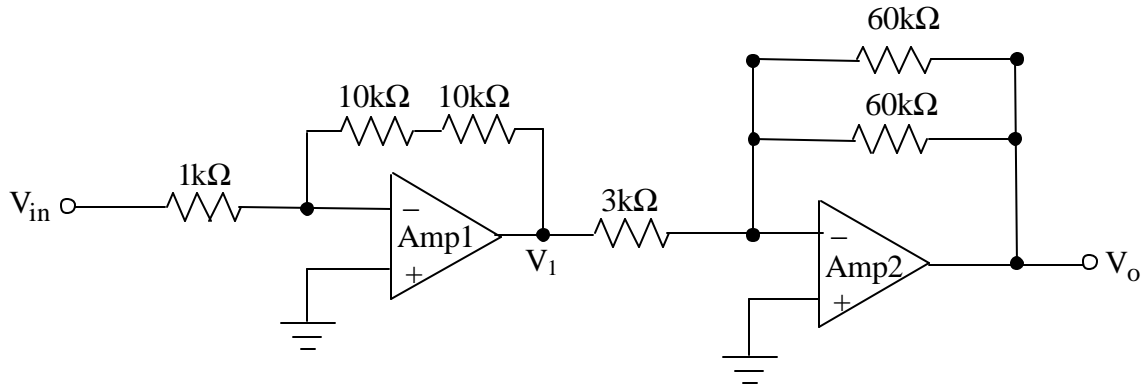



1.
 - (a) Explain how an amplifier works in your own words.
 - (b) Explain in your own words what R_i is.
 - (c) Explain in your own words what R_o is.
 - (d) Describe the ideal characteristics for an amplifier (i.e. ideal value for R_i , R_o , A_{v_o})
 - (e) Describe the characteristics for a buffer amplifier.
 - (f) Describe Gain-Bandwidth Product in your own words.
2. Use the circuit below:



Amp1 is a CA3140 and Amp2 is an LM741. (See attached datasheet information)

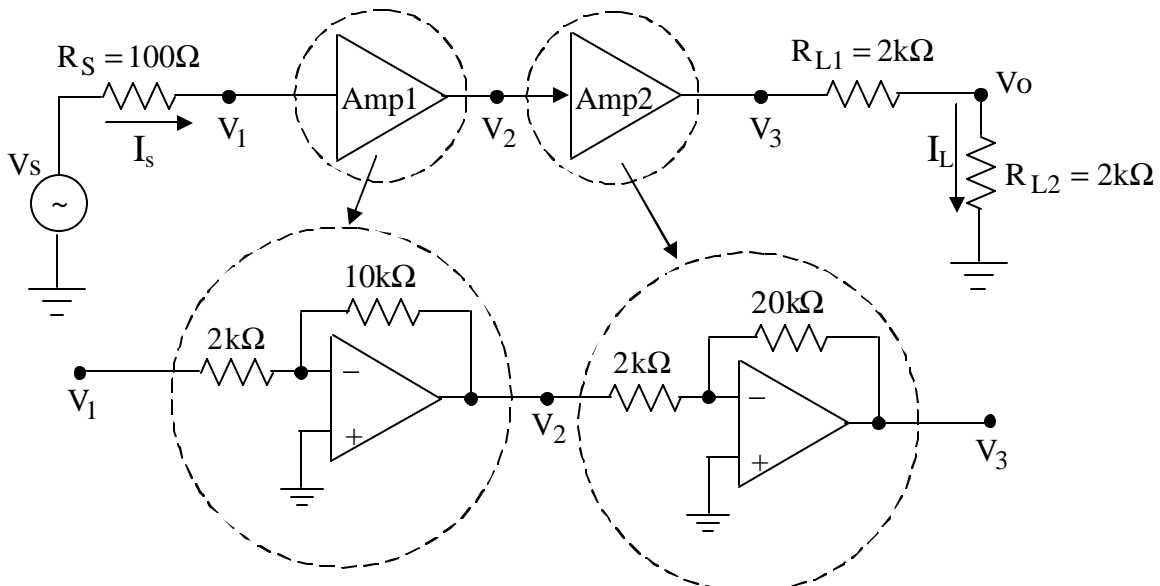
- (a) State each amplifiers frequency response transfer function (V_1/V_{in} and V_o/V_1)
 - (b) State the overall transfer function (V_o/V_{in})
3. Solve for the overall f_{3dB} of the circuit in #2. (You can use Matlab if you like)
4. V_s is an AC signal. Both amplifiers have the following characteristics:

$R_i=100k\Omega$, $R_o=5k\Omega$, Clipping levels: $L=\pm 12V$ (unloaded)




- (a) State the value of A_{v_o} (or gain) for Amp1 (the gain V_2/V_1) and Amp2 (the gain V_3/V_2).
 - (b) Redraw this 2 stage amplifier using the voltage amplifier model. Make sure to label V_s , V_1 , V_2 , V_3 , and V_o on the schematic.

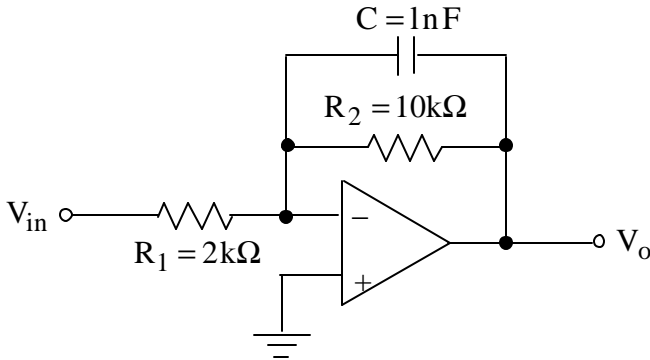5. (a) Find the overall gain of the circuit in #4, $A_v = V_o/V_s$. Express your answer as a ratio(V/V) and in dB. [Round answer to the nearest whole number]
 (b) Find $A_i = I_L/I_s$. Express your answer as a ratio(A/A) and in dB. [Round the answer to the nearest whole number] Hint: Write an equation based on V_o and V_s that have I_L and I_s in them and relate the two.
6. Analyze the circuit below to obtain the transfer function, V_o/V_{in} . Assume an ideal op amp.




7. Sketch the straight line approximation for the Bode Plots for the equation from #6.

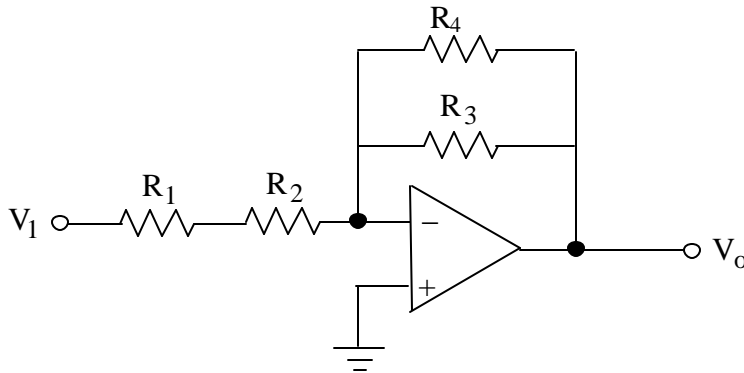8. Redraw or add to the schematic below to show how to reduce the **input bias current**. State the symbolic value(s) of any components added to the schematic.



9. Find I and V_o assuming ideal diodes.

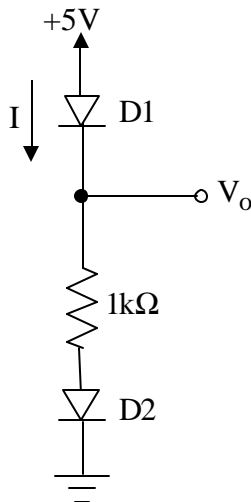

Electrical Specifications $V_{SUPPLY} = \pm 15V, T_A = 25^{\circ}C$

PARAMETER	SYMBOL	TEST CONDITIONS	TYPICAL VALUES		UNITS	
			CA3140	CA3140A		
Input Offset Voltage Adjustment Resistor		Typical Value of Resistor Between Terminals 4 and 5 or 4 and 1 to Adjust Max V_{IO}	4.7	18	$k\Omega$	
Input Resistance	R_I		1.5	1.5	$T\Omega$	
Input Capacitance	C_I		4	4	μF	
Output Resistance	R_O		60	60	Ω	
Equivalent Wideband Input Noise Voltage, (See Figure 27)	e_N	$BW = 140kHz, R_S = 1M\Omega$	48	48	μV	
Equivalent Input Noise Voltage (See Figure 35)	e_N	$R_S = 100\Omega$	f = 1kHz	40	40	nV/\sqrt{Hz}
			f = 10kHz	12	12	nV/\sqrt{Hz}
Short Circuit Current to Opposite Supply	I_{OM+}		Source	40	40	mA
	I_{OM-}		Sink	18	18	mA
Gain-Bandwidth Product, (See Figures 6, 30)	f_T		4.5	4.5	MHz	
Slew Rate, (See Figure 31)	SR		9	9	$V/\mu s$	
Sink Current From Terminal 8 To Terminal 4 to Swing Output Low			220	220	μA	
Transient Response (See Figure 28)	t_r	$R_L = 2k\Omega$ $C_L = 100pF$	Rise Time	0.08	0.08	μs
	OS		Overshoot	10	10	%
Settling Time at 10Vp.p, (See Figure 5)	t_S	$R_L = 2k\Omega$ $C_L = 100pF$ Voltage Follower	To 1mV	4.5	4.5	μs
			To 10mV	1.4	1.4	μs

Electrical Specifications For Equipment Design, at $V_{SUPPLY} = \pm 15V, T_A = 25^{\circ}C$, Unless Otherwise Specified

PARAMETER	SYMBOL	CA3140			CA3140A			UNITS
		MIN	TYP	MAX	MIN	TYP	MAX	
Input Offset Voltage	$ V_{IO} $	-	5	15	-	2	5	mV
Input Offset Current	$ I_{IO} $	-	0.5	30	-	0.5	20	μA
Input Current	I_I	-	10	50	-	10	40	μA
Large Signal Voltage Gain (Note 3) (See Figures 6, 29)	A_{OL}	20	100	-	20	100	-	kV/V
		86	100	-	86	100	-	dB
Common Mode Rejection Ratio (See Figure 34)	CMRR	-	32	320	-	32	320	$\mu V/V$
		70	90	-	70	90	-	dB
Common Mode Input Voltage Range (See Figure 8)	V_{ICR}	-15	-15.5 to +12.5	11	-15	-15.5 to +12.5	12	V

LM741:

