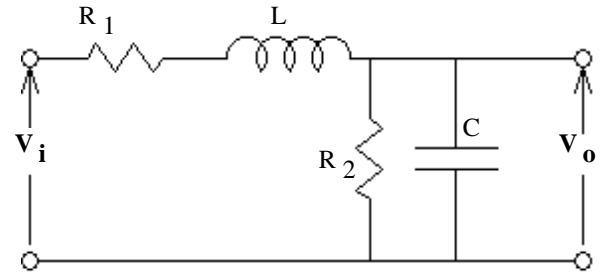


Let's find the transfer function of this circuit.



$$\begin{aligned}
 H(s) &= ? \\
 H(s) &= \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{R_2 + C \cdot s}}{R_1 + L \cdot s + \frac{1}{R_2 + C \cdot s}} \\
 &= \frac{1}{R_1 \cdot \left(\frac{1}{R_2} + C \cdot s\right) + L \cdot s \cdot \left(\frac{1}{R_2} + C \cdot s\right) + 1} \\
 &= \frac{1}{\frac{R_1}{R_2} + R_1 \cdot C \cdot s + \frac{L \cdot s}{R_2} + L \cdot s \cdot C \cdot s + 1} \\
 &= \frac{\frac{1}{L \cdot C}}{s^2 + \left(\frac{R_1}{L} + \frac{1}{R_2 \cdot C}\right) \cdot s + \left(1 + \frac{R_1}{R_2}\right) \cdot \frac{1}{L \cdot C}}
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{\frac{1}{L \cdot C}}{\frac{R_1}{R_2} \cdot \frac{1}{L \cdot C} + \frac{R_1 \cdot C}{L \cdot C} \cdot s + \frac{L \cdot s}{R_2} \cdot \frac{1}{L \cdot C} + s^2 + \frac{1}{L \cdot C}}
 \end{aligned}$$

### Input Impedance

What load does this circuit place on the source of  $V_i$ ?

$$Z_{in}(s) = R_1 + L \cdot s + \frac{1}{\frac{1}{R_2} + C \cdot s} \quad \text{OR, if this circuit is followed by another circuit with } Z_{in2}(s), \text{ then,}$$


$$Z_{in}(s) = R_1 + L \cdot s + \frac{1}{\frac{1}{R_2} + C \cdot s + \frac{1}{Z_{in2}(s)}}$$

Usually, the higher the input impedance, the better.

### Output Impedance

Output Impedance is just like the Thévenin Resistance

#### Thévenin Equivalent Circuit

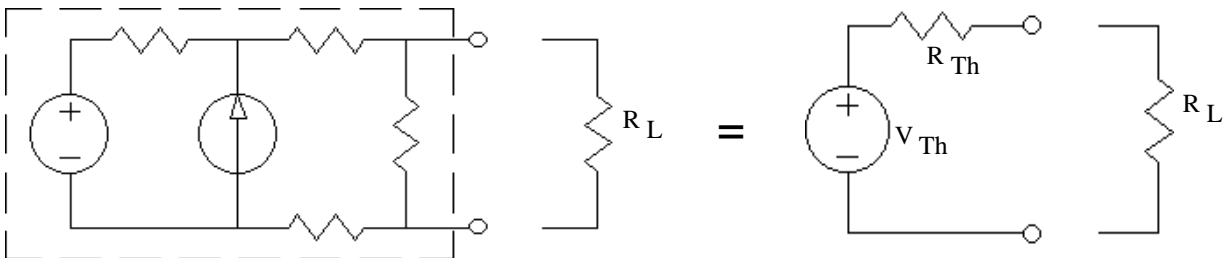

#### Thévenin equivalent



To calculate a circuit's Thévenin equivalent:

- 1) Remove the load and calculate the open-circuit voltage where the load used to be. This is the Thévenin voltage ( $V_{Th}$ ).
- 2) Zero all the sources. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 3) Compute the total resistance between the load terminals. (DO NOT include the load in this resistance.) This is the Thévenin source resistance ( $R_{Th}$ ).
- 4) Draw the Thévenin equivalent circuit and add your values.

**Ex 1** Find the Thévenin equivalent:

To find a circuit's Thévenin equivalent:

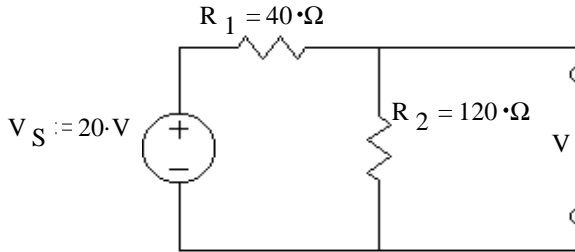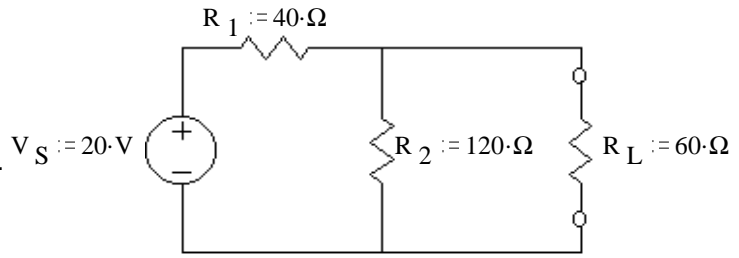- 1) Remove the load and calculate the open-circuit voltage where the load used to be. This is the Thévenin voltage ( $V_{Th}$ ).




Find the open circuit voltage:

$$V_{oc} = V_{Th} := V_S \cdot \frac{R_2}{R_1 + R_2} \quad V_{Th} = 15 \cdot V$$

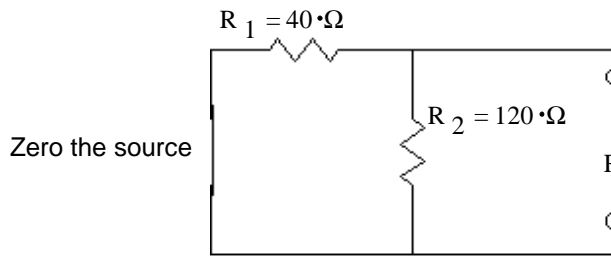- 2) Zero all the sources.

(To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)



Zero the source


- 3) Compute the total resistance between the load terminals. (DO NOT include the load in this resistance.) This is the Thévenin source resistance ( $R_{Th}$ ).

Find the Thevenin resistance:


$$R_{Th} := \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \quad R_{Th} = 30 \cdot \Omega$$

- 4) Draw the Thévenin equivalent circuit and add your values.

Thevenin equivalent circuit:

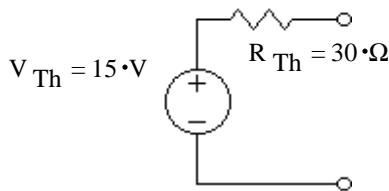


If the load were reconnected:

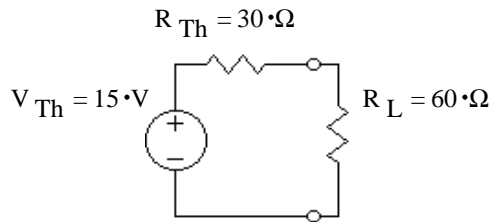

$$V_L = V_{Th} \cdot \frac{R_L}{R_{Th} + R_L} = 10 \cdot V$$

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = 166.7 \cdot mA$$

**Output Impedance**

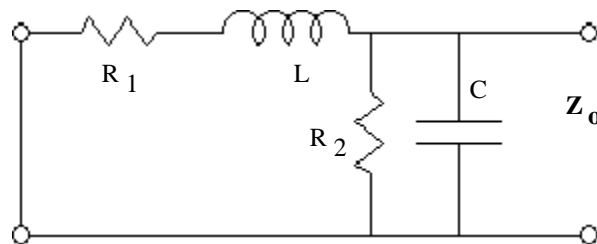

$$Z_{out}(s) = \frac{R_1 + L \cdot s}{1 + \frac{R_1}{R_2} + \frac{L}{R_2} \cdot s + C \cdot s \cdot R_1 + L \cdot C \cdot s^2} \cdot \left( \frac{1}{L \cdot C} \right) = \frac{\frac{1}{L \cdot C} \cdot (R_1 + L \cdot s)}{s^2 + \left( \frac{1}{C \cdot R_2} + \frac{R_1}{L} \right) \cdot s + \frac{1}{L \cdot C} \cdot \left( 1 + \frac{R_1}{R_2} \right)}$$

OR, if this circuit is preceded by another circuit with  $Z_{out0}(s)$ , then,

$$Z_{out}(s) = \frac{1}{\frac{1}{Z_{out0}} + \frac{1}{R_1 + L \cdot s} + \frac{1}{R_2} + C \cdot s}$$

Usually, the lower the output impedance, the better